
 

 
# Fig 2.11 Register Transfers Hardware and Timing for a Single-Bit Register Transfer: $A \leftarrow B$

- Implementing the RTN statement  $A \leftarrow B$




(a) Hardware




(b) Timing
 
# Fig 2.12 Multiple Bit Register Transfer: $A\langle m..1 \rangle \leftarrow B\langle m..1 \rangle$




(a) Individual flip-flops

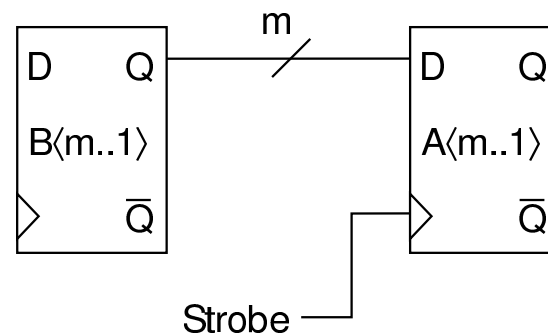


(b) Abbreviated notation
 
## Fig 2.13 Data Transmission View of Logic Gates


- Logic gates can be used to control the transmission of data:



Data gate

 


Controlled complement

 

Data merge

 
## Fig 2.14 Two-Way Gated Merge, or Multiplexer

- Data from multiple sources can be selected for transmission




# Fig 2.15 Basic Multiplexer and Symbol Abbreviation

An n-way gated merge

 

(a) Multiplexer in terms of gates


An n-way multiplexer with decoder

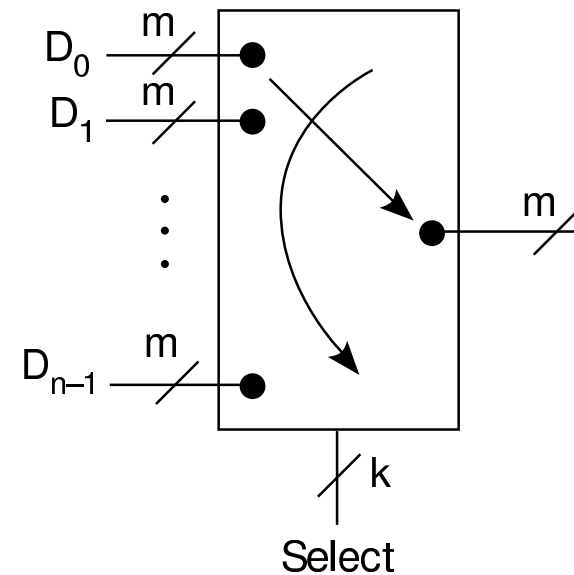

(b) Symbol abbreviation


- Multiplexer gate signals  $G_i$  may be produced by a binary to one-out-of- $n$  decoder

## Fig 2.16 Separating Merged Data

 

- Merged data can be separated by gating at the right time
- It can also be strobed into a flip-flop when valid
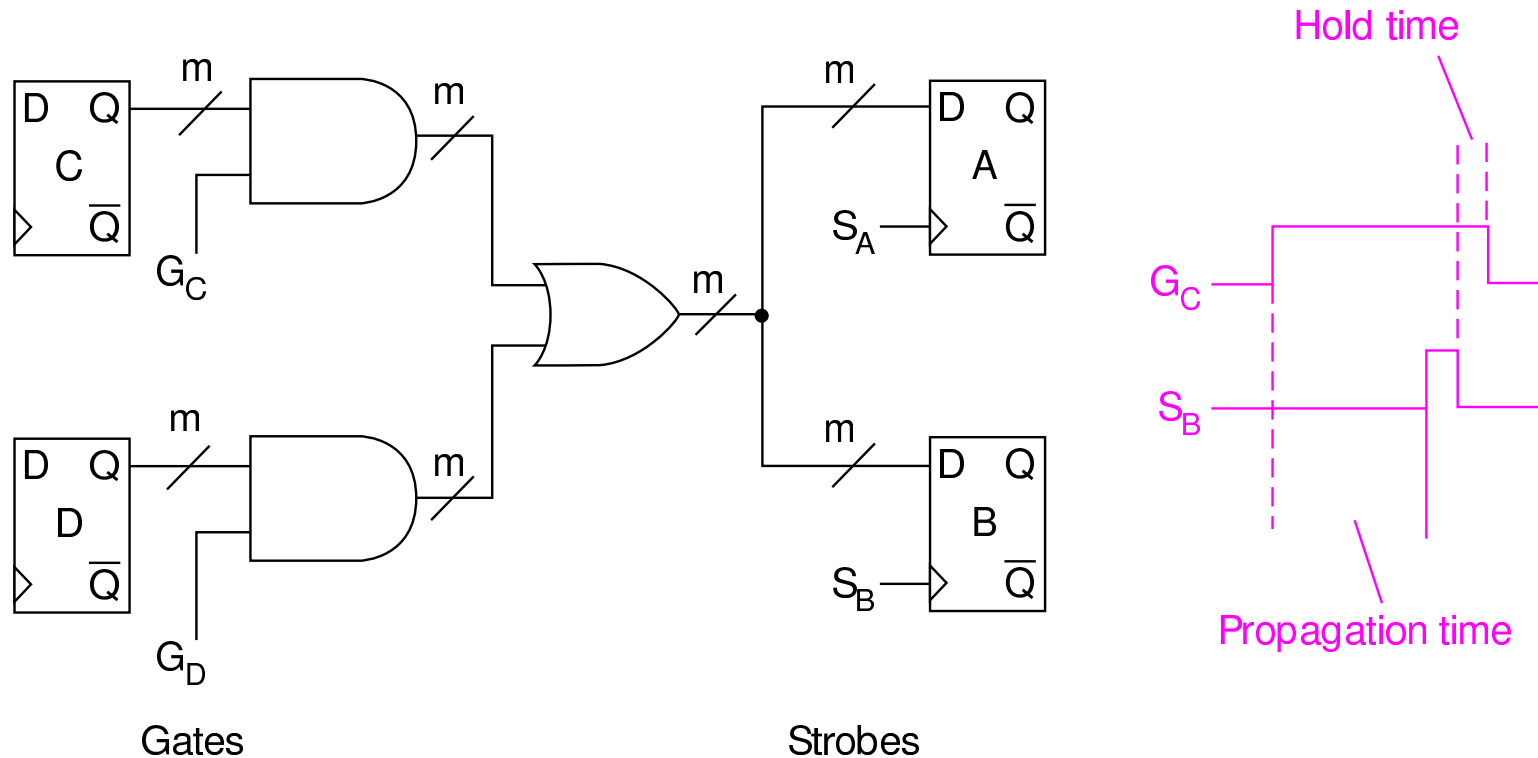
## Fig 2.17 Multiplexed Register Transfers Using Gates and Strobes




- Selected gate and strobe determine which RT
- $A \leftarrow C$  and  $B \leftarrow C$  can occur together, but not  $A \leftarrow C$  and  $B \leftarrow D$


# Fig 2.18 Open-Collector NAND Gate Output Circuit

<u>Inputs</u>		<u>Output</u>	
0v	0v	Open	(Out = +V)
0v	+V	Open	(Out = +V)
+V	0v	Open	(Out = +V)
+V	+V	Closed	(Out = 0v)

(a) Open-collector NAND truth table

 


(b) Open-collector NAND

 

(c) Symbol


 
## Fig 2.19 Wired AND Connection of Open-Collector Gates




Switch		Wired AND output
a	b	
Closed(0)	Closed(0)	0v (0)
Closed(0)	Open (1)	0v (0)
Open (1)	Closed(0)	0v (0)
Open (1)	Open (1)	+V (1)


(c) Truth table
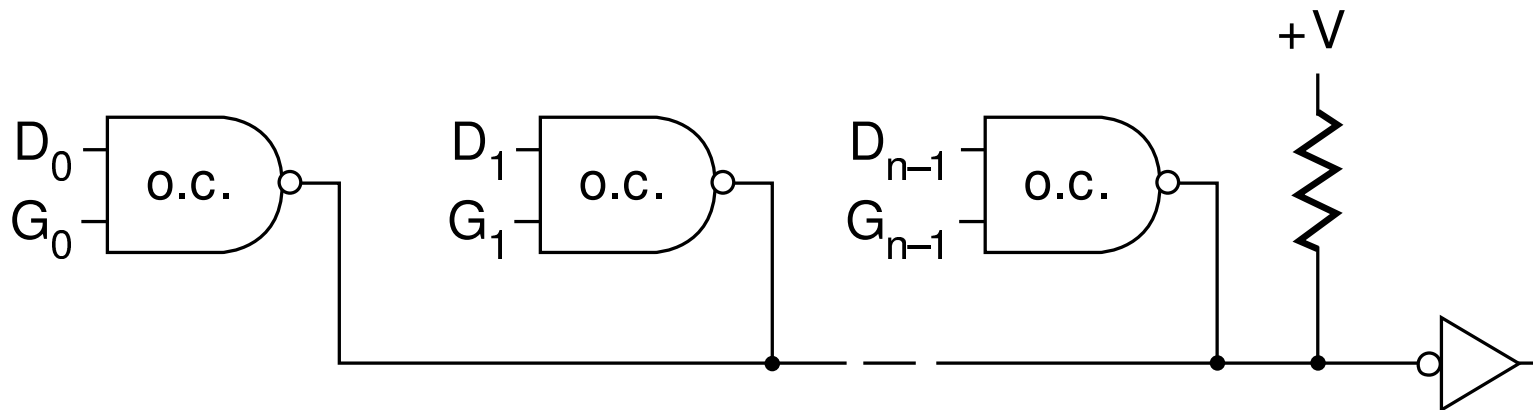
## Fig 2.20 Open-Collector Wired OR Bus


- DeMorgan's OR by not of AND of NOTS
- Pull-up resistor removed from each gate - open collector
- One pull-up resistor for whole bus
- Forms an OR distributed over the connection


 
## Fig 2.21 Tri-State Gate Internal Structure and Symbol



(a) Tri-state gate structure

 


(b) Tri-state gate symbol

Enable	Data	Output
0	0	Hi-Z
0	1	Hi-Z
1	0	0
1	1	1

(c) Tri-state gate truth table
 
## Fig 2.22 Registers Connected by a Tri-State Bus



- Can make any register transfer  $R[i] \leftarrow R[j]$
- Can't have  $G_i = G_j = 1$  for  $i \neq j$
- Violating this constraint gives low resistance path from power supply to ground—with predictable results!

# Fig 2.23 Registers and Arithmetic Units Connected by One Bus

**Example:**

**Abstract RTN**

$R[3] \leftarrow R[1] + R[2];$

**Concrete RTN**

$Y \leftarrow R[2];$

$Z \leftarrow R[1] + Y;$


$R[3] \leftarrow Z;$

**Control Sequence**

$R[2]_{out}, Y_{in};$

$R[1]_{out}, Z_{in};$

$Z_{out}, R[3]_{in};$

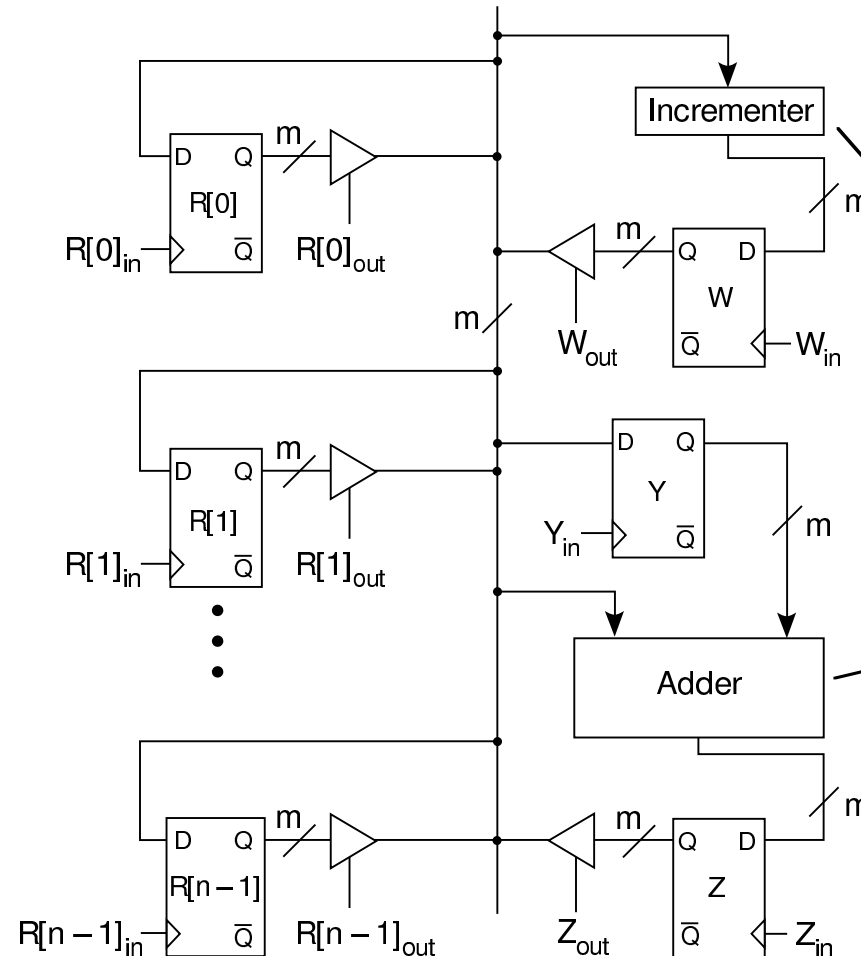

**Combinational  
logic—no  
memory**

Notice that what could be described in one step in the abstract RTN took three steps on this particular hardware

## RTs Possible with the One-Bus Structure

- $R[i]$  or  $Y$  can get the contents of anything but  $Y$
- Since result different from operand, it cannot go on the bus that is carrying the operand
- Arithmetic units thus have result registers
- Only one of two operands can be on the bus at a time, so adder has register for one operand
- $R[i] \leftarrow R[j] + R[k]$  is performed in 3 steps:  $Y \leftarrow R[k]; Z \leftarrow R[j] + Y; R[i] \leftarrow Z;$
- $R[i] \leftarrow R[j] + R[k]$  is high level RTN description
- $Y \leftarrow R[k]; Z \leftarrow R[j] + Y; R[i] \leftarrow Z;$  is concrete RTN
- Map to control sequence is:  $R[2]_{out}, Y_{in}; R[1]_{out}, Z_{in}; Z_{out}, R[3]_{in};$

# From Abstract RTN to Concrete RTN to Control Sequences

- **The ability to begin with an abstract description, then describe a hardware design and resulting concrete RTN and control sequence is powerful.**
- **We shall use this method in Chapter 4 to develop various hardware designs for SRC.**

# Chapter 2 Summary

- **Classes of computer ISAs**
- **Memory addressing modes**
- **SRC: a complete example ISA**
- **RTN as a description method for ISAs**
- **RTN description of addressing modes**
- **Implementation of RTN operations with digital logic circuits**
- **Gates, strobos, and multiplexers**