

Chapter # 3: Multi-Level Combinational Logic

Contemporary Logic Design

Randy H. Katz
University of California, Berkeley

June 1993

No. 3-1

Chapter Overview

- ***Multi-Level Logic***

- Conversion to NAND-NAND and NOR-NOR Networks

- DeMorgan's Law and Pushing Bubbles

- AND-OR-Invert Building Blocks

- CAD Tools for Multi-Level Optimization

- ***Time Response in Combinational Networks***

- Gate Delays and Timing Waveforms

- Hazards/Glitches and How To Avoid Them

No. 3-2

Boolean Algebra

Commutative Laws:

$$a + b = b + a$$

$$a \cdot b = b \cdot a$$

Associative Laws:

$$(a+b)+c = a+(b+c)$$

$$(ab)c = a(bc)$$

Identities:

$$a + 0 = a$$

$$a \cdot 0 = 0$$

$$a \cdot 1 = a$$

$$a + 1 = 1$$

Distributive Laws:

$$a + (b \cdot c) = (a+b) \cdot (b+c)$$

$$a \cdot (b+c) = (a \cdot b) + (a \cdot c)$$

No. 3-3

Boolean Algebra

Complement:

$$a + a = 1$$

$$a \cdot a = 0$$

$$a + a = a$$

$$a \cdot a = a$$

Theorems:

$$a + ab = a$$

$$ab + ab = b$$

DeMorgan's Theorem:

$$a \cdot b = a + b$$

$$a + b = a \cdot b$$



No. 3-4

Multi-Level Logic: Advantages

Reduced sum of products form:

$$x = ADF + AEF + BDF + BEF + CDF + CEF + G$$

  6 x 3-input AND gates + 1 x 7-input OR gate (may not exist!)
25 wires (19 literals plus 6 internal wires)



Factored form:

$$x = (A + B + C) (D + E) F + G$$

1 x 3-input OR gate, 2 x 2-input OR gates,
1 x 3-input AND gate
10 wires (7 literals plus 3 internal wires)

No. 3-5

Multi-Level Logic: Conversion of Forms

NAND-NAND and NOR-NOR Networks

DeMorgan's Law: $(A + B)' = A' \cdot B'$; $(A \cdot B)' = A' + B'$


$$A + B = (A' \cdot B)'; \quad (A \cdot B) = (A' + B)'$$

In other words,

- OR is the same as NAND with complemented inputs
- AND is the same as NOR with complemented inputs
- NAND is the same as OR with complemented inputs
- NOR is the same as AND with complemented inputs

OR/NAND Equivalence

A	\bar{A}	B	\bar{B}	$A + B$	$\overline{A \cdot B}$	$\bar{A} + \bar{B}$	$\overline{A \cdot B}$
0	1	0	1	0	0	1	1
0	1	1	0	1	1	1	1
1	0	0	1	1	1	1	1
1	0	1	0	1	1	0	0

 


No. 3-6

Multi-Level Logic: Conversion Between Forms

AND/NOR Equivalence

A	\bar{A}	B	\bar{B}	$A \cdot B$	$\overline{A+B}$	$\bar{A} \cdot \bar{B}$	$\overline{A+B}$
0	1	0	1	0	0	1	1
0	1	1	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0

 


It is possible to convert from networks with ANDs and ORs to networks with NANDs and NORs by introducing the appropriate inversions ("bubbles")

To preserve logic levels, each introduced "bubble" must be matched with a corresponding "bubble"

No. 3-7



Multi-Level Logic: Conversion of Forms

Example: Map AND/OR network to NAND/NAND network

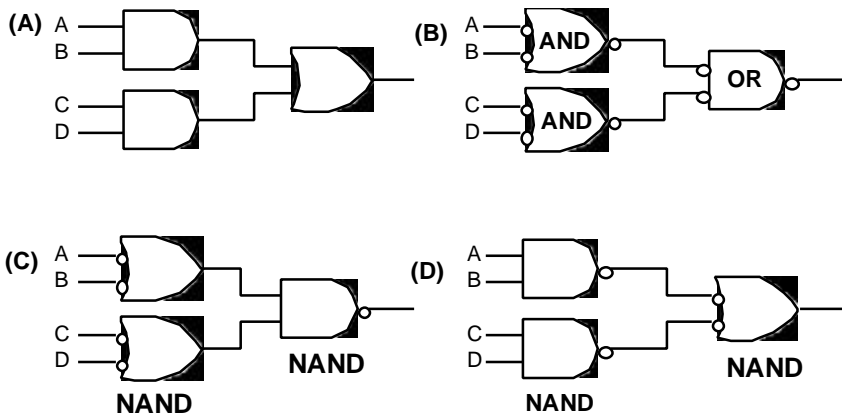

No. 3-8

  Example: Map AND/OR network to NAND/NAND network




$$\begin{aligned}
 Z &= [(A \cdot B)' (C \cdot D)']' \\
 &= [(A' + B') (C' + D')] \\
 &= [(A' + B')' \cdot (C' + D')'] \\
 &= (A \cdot B) + (C \cdot D) \quad ;
 \end{aligned}$$

This is the easy conversion!


No. 3-9

 Example: Map AND/OR network to NOR/NOR network



Conserve
"Bubbles"

Step 1

 


Conserve
"Bubbles"

Step 2

Z =

No. 3-10

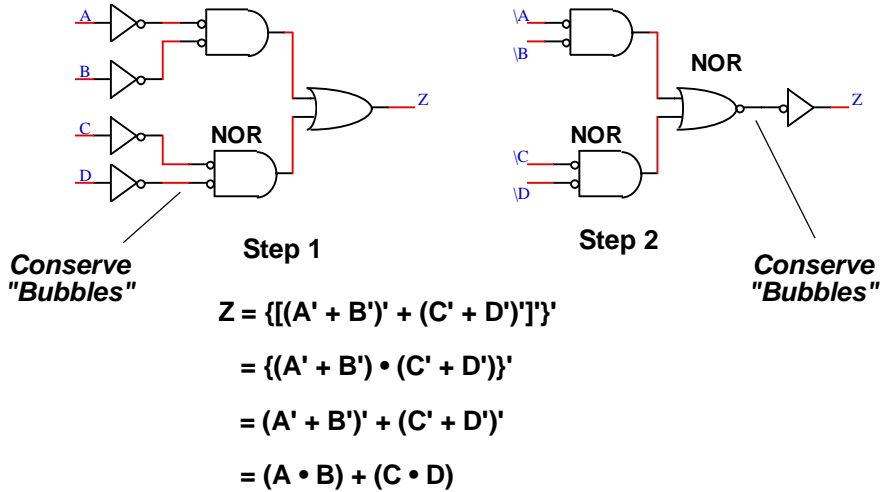
Example: Map AND/OR network to NOR/NOR network



This is the hard conversion!

AND/OR to NAND/NAND more natural


 
Example: Map OR/AND network to NOR/NOR network



Verify equivalence of the two forms

Z =

  Example: Map OR/AND network to NOR/NOR network





$$\begin{aligned}
 Z &= [(A + B)' + (C + D)']' \\
 &= \{(A + B)'\}' \cdot \{(C + D)'\}' \\
 &= (A + B) \cdot (C + D)
 \end{aligned}$$

This is the easy conversion!


No. 3-13

Example: Map OR/AND network to NAND/NAND network

 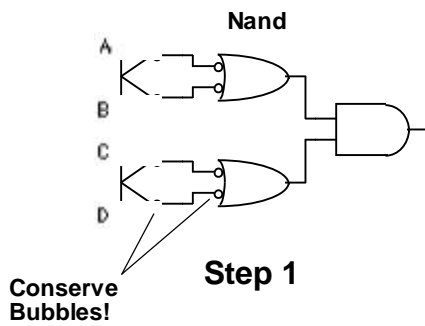

No. 3-14

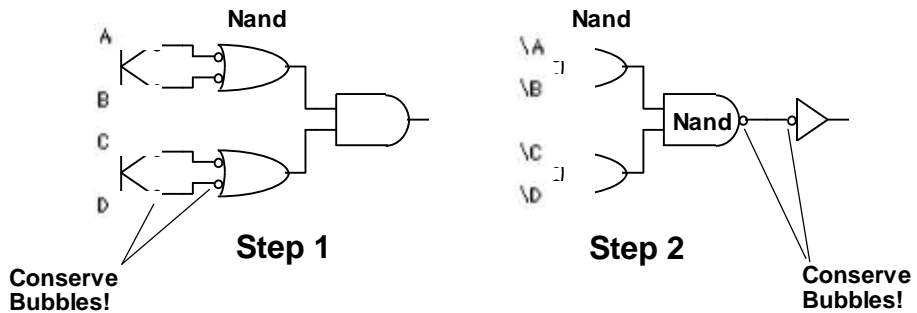Example: Map OR/AND network to NAND/NAND network



$$\begin{aligned}
 Z &= \{[(A' \cdot B') \cdot (C' \cdot D')]\}' \\
 &= \{(A' \cdot B') + (C' \cdot D')\}' \\
 &= (A' \cdot B')' \cdot (C' \cdot D')' \\
 &= (A + B) \cdot (C + D)
 \end{aligned}$$


This is the hard conversion!

OR/AND to NOR/NOR more natural

No. 3-15


Multi-Level Logic: More than Two Levels

$$f = A(B + CD) + B C'$$

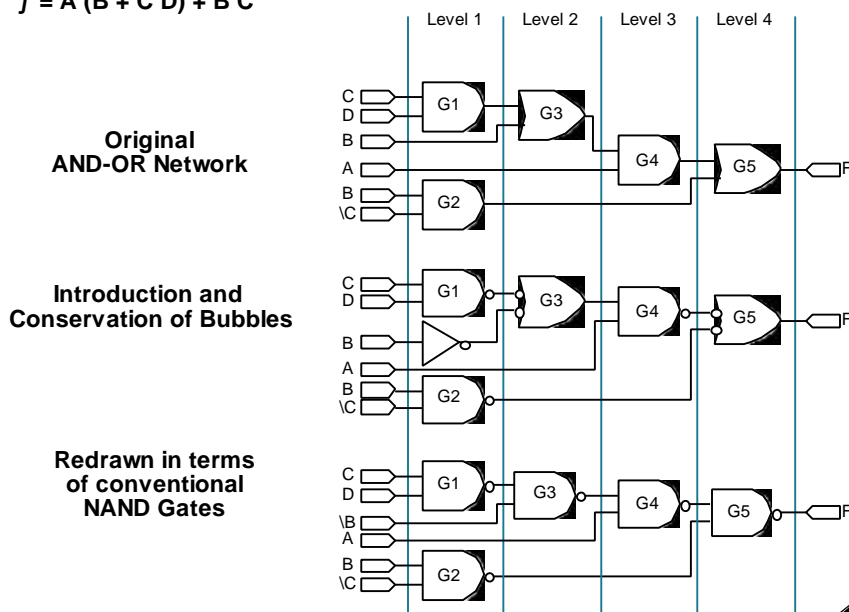


No. 3-16

Multi-Level Logic: More than Two Levels

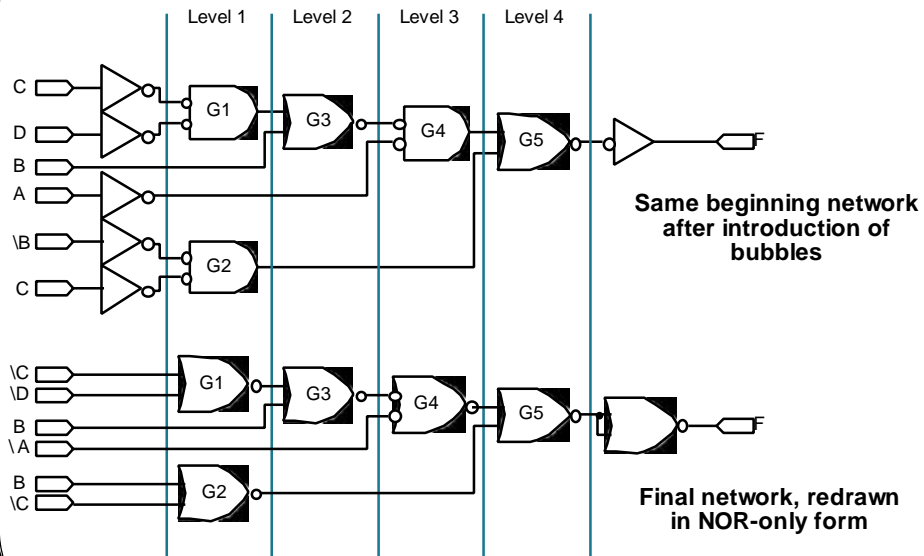

No. 3-17

Conversion Example

 


No. 3-18

Multi-Level Logic: AND-OR-Invert Block (AOI)


AOI Function: Three stage logic — AND, OR, Invert
Multiple gates "packaged" as a single circuit block

logical concept

 


AND OR Invert

two-input two-stack

 


Multi-Level Logic: AND-OR-Invert Block (AOI)

2x2 AOI Schematic Symbol

 

3x2 AOI Schematic Symbol

 

Example: XOR implementation

$$A \text{ xor } B = A' B + A B'$$

AOI form

$$= (?)'$$

$$(A' B + A B')$$

$$(A + B') (A' + B)$$

$$(A B + A' B')$$

General procedure to place in AOI form:

Compute the complement in Sum of Products form by circling the 0's in the K-map!

$$f = (A' B' + A B)'$$

No. 3-21

Example:

		A			
	AB	00	01	11	10
C	0	1	0	0	0
	1	1	1	0	1
		B			

$$F = B C' + A C' + A B$$

$$F' = A' B' + A' C + B' C$$

2-input 3-stack AOI gate

F K-map

$$F = (A + B) (A + C') (B + C')$$

$$F' = (B' + C) (A' + C) (A' + B')$$

2-input 3-stack OAI gate

No. 3-22


Example: 4-bit Equality Function

$$Z = (A_0 B_0 + A_0' B_0') (A_1 B_1 + A_1' B_1') (A_2 B_2 + A_2' B_2') (A_3 B_3 + A_3' B_3')$$

Each implemented in single 2x2 AOI gate

No. 3-23

Example: AOI Implementation of a 4-Bit Equality Tester

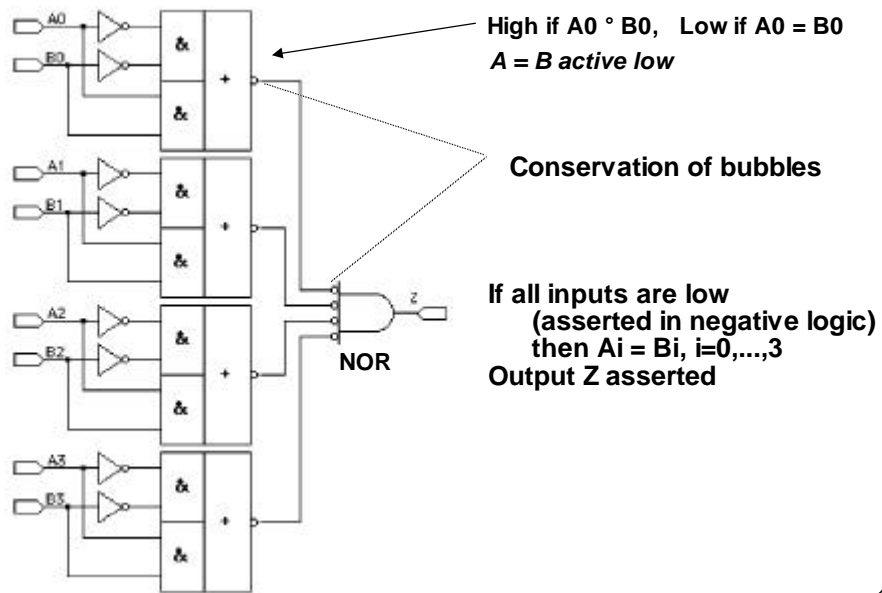

No. 3-24


Multi-Level Logic: CAD Tools for Simplification

Multi-Level Optimization:

1. Factor out common sublogic (reduce fan-in, increase gate levels), subject to timing constraints
2. Map factored form onto library of gates
3. Minimize number of literals (correlates with number of wires)

Factored Form:

sum of products of sum of products . . .

 

$$X = (A B + B' C) (C + D (E + A C')) + (D + E)(F G)$$

No. 3-25

Multi-Level Logic: CAD Tools for Simplification

Operations on Factored Forms:

- Decomposition
 - Extraction
 - Factoring
 - Substitution
 - Collapsing
- Manipulate network by interactively issuing the appropriate instructions
- There exists no algorithm that guarantees "optimal" multi-level network will be obtained

No. 3-26

Time Response in Combinational Networks

- emphasis on timing behavior of circuits
- waveforms to visualize what is happening
- simulation to create these waveforms
- momentary change of signals at the outputs: **hazards**
 - can be useful— pulse shaping circuits
 - can be a problem — **glitches**: incorrect circuit operation

Terms:



gate delay - time for change at input to cause change at output
minimum delay vs. typical/nominal delay vs. maximum delay
careful designers design for the worst case!

rise time - time for output to transition from low to high voltage

fall time - time for output to transition from high to low voltage

No. 3-27

Pulse Shaping Circuit

  


D remains high for
three gate delays after
A changes from low to high

F is not always 0!

No. 3-28

Another Pulse Shaping Circuit

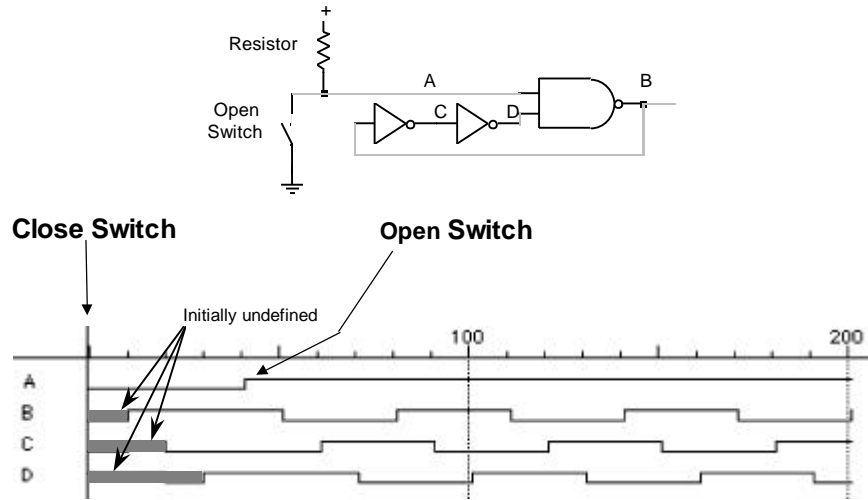

No. 3-29

Hazards/Glitches and How to Avoid Them

Unwanting switching at the outputs

Occur because delay paths through the circuit experience different propagation delays

Danger if logic "makes a decision" while output is unstable
OR hazard output controls an *asynchronous* input (these respond immediately to changes rather than waiting for a synchronizing signal called a *clock*)

Usual solutions:

- wait until signals are stable (by using a clock)
- never, never, never use circuits with asynchronous inputs
- design hazard-free circuits


Suggest that first two approaches be used, but we'll tell you about hazard-free design anyway!

No. 3-30


Hazards/Glitches and How to Avoid Them



 Input change causes output to go from **1 to 0 to 1**



 Input change causes output to go from **0 to 1 to 0**




Input change causes a double change from **0 to 1 to 0 to 1** OR from **1 to 0 to 1 to 0**

Kinds of Hazards

No. 3-31


Glitch Example

 

input change within product term

AB		A			
		00	01	11	10
CD	00	0	0	1	1
	01	1	1	1	1
	11	1	1	0	0
	10	0	0	0	0
		B		D	

$$F = A'D + AC'$$

 

input change that spans product terms
output changes from 1 to 0 to 1

No. 3-32

Glitch Example

General Strategy: add redundant terms

$$F = A' D + A C' \text{ becomes } A' D + A C' + C' D$$

This eliminates 1-hazard? How about 0-hazard?


Re-express F in PoS form:

$$F = (A' + C')(A + D)$$

Glitch present!

$$\text{Add term: } (C' + D)$$

This expression is equivalent to the hazard-free SoP form of F

 

No. 3-33

Glitch Example

Start with expression that is free of static 1-hazards

$$F = A C' + A' D + C' D$$

Work with complement:

$$F' = (A C' + A' D + C' D)'$$

$$= (A' + D) (A + D') (C + D')$$

$$= A C + A C D' + C D' + A' C D' + A' D'$$

$$= A C + C D' + A' D'$$

covers all the adjacent 0's in the K-map

free of static-1 and static-0 hazards!

No. 3-34

Detecting Static Hazards in Multi-Level Circuits

Calculate transient output function

variables and complements are treated as independent variables

cannot use $X + X' = 1$ or $X \cdot X' = 0$ for simplifications

Example:

$$F = A B C + (A + D) (A' + C')$$

$$F_1 = A B C + A A' + A C' + A' D + C' D \quad \text{2-level form}$$

		A				
		00	01	11	10	
C	AB	00	0	0	1	1
	01	1	1	1	1	
	11	1	1	1	0	
	10	0	0	1	0	
		D				

ABCD: 1111 to 1110, covered by term ABC, so no 1-hazard present

ABCD: 1110 to 1100, term ABC goes low while term AC' goes high

some static hazards are present!


No. 3-35

Static 1-hazards

Solution:

Add redundant terms to insure all adjacent transitions are covered by terms

$$F_2 = A C' + A' D + C' D + A B + B D$$

 

1's hazards in F corrected in F₂

No. 3-36

Static 0-Hazards

Similar to previous case, but work with the complement of F

If terms of the transient output function cover all 0 transitions, then no 0-hazards are present

$$\bar{F} = [A B C + (A + D) (A' + C')]'$$

$$= (A' + B' + C') (A' D' + A C)$$

$$= A' D' + A' B D' + A' C D' + A B' C$$

$$= A' D' + A B' C + B' C D'$$

		A			
		00	01	11	10
CD	00	0	0	1	1
	01	1	1	1	1
	11	1	1	1	0
	10	0	0	1	0
		B		D	

$$F = (A + D) (A' + B + C') (B + C' + D)$$


0-hazard free

equivalent to F2 on last slide

0-hazard on transition from 1010 to 0010

No. 3-37

Static 0-Hazards

 


0-Hazard Corrected in F3

No. 3-38

Designing Networks for Hazard-free operation

Simply place transient output function in a form that guarantees that all adjacent ones are covered by a term

 no term of the transient output function contains both a variable and its complement




$$F(A,B,C,D) = \sum m(1,3,5,7,8,9,12,13,14,15)$$

$$F = A B + A' D + B D + A C' + C' D$$

$$= (A' + B + C') D + A (B + C')$$

(factored by distributive law, which does not introduce hazards since it does not depend on the complementarity laws for its validity)

Dynamic Hazards

 

Three different paths from B or B' to output

ABC = 000, F = 1 to ABC = 010, F = 0

different delays along the paths:
G1 slow, G4 very slow

Handling dynamic hazards very complex

Beyond our scope

Elements of a Data Sheet

A data sheet contains all the relevant documentation that you need to use the component:

1. Description of Function
2. A function/truth table
3. A logic schematic with labeled I/Os
4. Boolean expression of function in terms of I/Os
5. Alternative package pin-outs
6. Internal transistor schematics
7. Operating specifications
8. Recommended operating conditions
9. Electrical characteristics.
10. Switching characteristics.

No. 3-41

Operating Specifications: the absolute worst-case conditions under which the component can operate or be stored. Max input volt: 7v, Temp: 0 to 70 C.

Recommended Operating Conditions: the normal operating conditions for the supply voltage, input voltages, output currents, and temperature.

V_{HI} : min input volt recognized as a logic 1 (2v)

V_{IL} : max input volt recognized as a logic 0 (0.8v)

I_{OH} : max current gate can supply to maintain volt of logic 1 (-0.4 mA)

I_{OL} : min current gate can supply to maintain volt of logic 0 (8 mA)

No. 3-42

Electrical Characteristics: voltages and currents that can be observed at the inputs and outputs.

V_{OH} : min output high volt (2.7v min, 3.4v typical)

V_{OL} : max output low volt (0.4v max, 0.25v typical)

I_{IH} : max current into input when high (20uA)

I_{IL} : max current into input when low (-0.4 mA)

The voltages determine the **noise margin**: 0.7v margin on logic 1, and 0.4v on logic 0.

Switching Characteristics: the typical and maximum gatdelays under specified test conditions.

t_{PLH} : delay from low to high (9ns typical, 15ns worst)

t_{PHL} : delay from high to low (10ns typical, 15ns worst)

No. 3-43

Fan-Out: a given output can drive only a finite number of inputs before the output signal levels become degraded and are no longer recognized as good logic 1/0s.

To determine the **fan-out** examine the I_{OH} of the driving gate. This value must exceed the sum of the I_{IH} values of the inputs that the gate is driving.

Similarly, the I_{OL} of the gate must exceed the sum of the I_{IL} values of the inputs to which it is connected.

Example: I_{IH} : 20uA, I_{OH} : -0.4mA

I_{IL} : -0.4mA, I_{OL} : 8mA

It can drive **20** gates to logic **1** and to logic **0**.

No. 3-44

Technology Metrics

There are differences in the underlying technologies that may make one technology more attractive than another. The main technology metrics are:

1. Gate Delay: the time delay between the changes. On general, bipolar techs are faster than MOS (ECL the fastest).

2. Degree of Integration: the area required to implement a given function in the underlying tech. MOS pack much more densely than bipolar.

SSI: up to 10 gates

MSI: up to 100 gates (not important)

LSI / VLSI: up to 1000 gates (MOS has advantage)

No. 3-45

3. Power Dissipation: the power consumption and heat generated that must be dissipated.

- Bipolar generate more heat and consume more power
- ECL consume the most power
- MOS, especially CMOS, consume very little power

4. Noise Margin: the max volt that can be added to or subtracted from the logic voltages and still have the ckt interpret the voltage as the correct logic value.

- Modern TTL / CMOS have good noise margins
- ECL has tighter noise margin

5. Component Cost: TTL, MOS, ECL

No. 3-46