 



# Using Voltages “Digitally”

- Key idea: don't allow “0” to be mistaken for a “1” or vice versa
- Use the same “uniform representation convention”, for every component and wire in our digital system
- To implement devices with high reliability, we outlaw “close calls” via a representation convention which forbids a range of voltages between “0” and “1”.



CONSEQUENCE:

 
Notion of “VALID” and “INVALID” logic levels



# A Digital Processing Element


- A *combinational device* is a circuit element that has
  - one or more *digital inputs*
  - one or more *digital outputs*
  - a *functional specification* that details the value of each output for every possible combination of valid input values
  - a *timing specification* consisting (at minimum) of an upper bound  $t_{pd}$  on the required time for the device to compute the specified output values from an arbitrary set of stable, valid input values

**Static discipline**

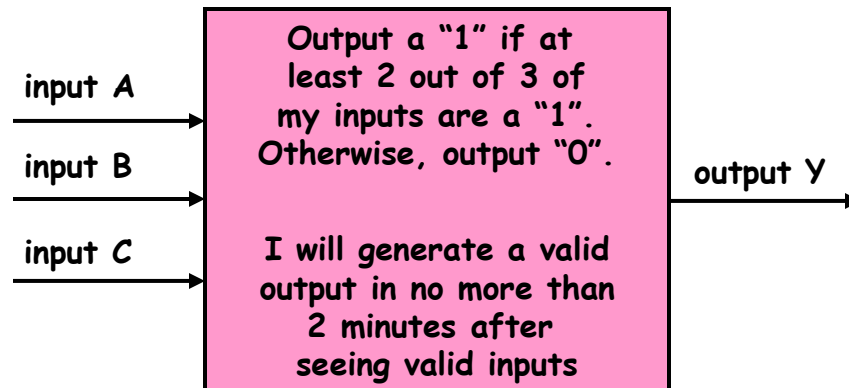

# Wires: theory vs. practice

Does a wire obey the static discipline?

 


Questions to ask ourselves:

*In digital systems, where does noise come from?*


*How big an effect are we talking about?*

# Needed: Noise Margins!

Does a wire obey the static discipline?


 


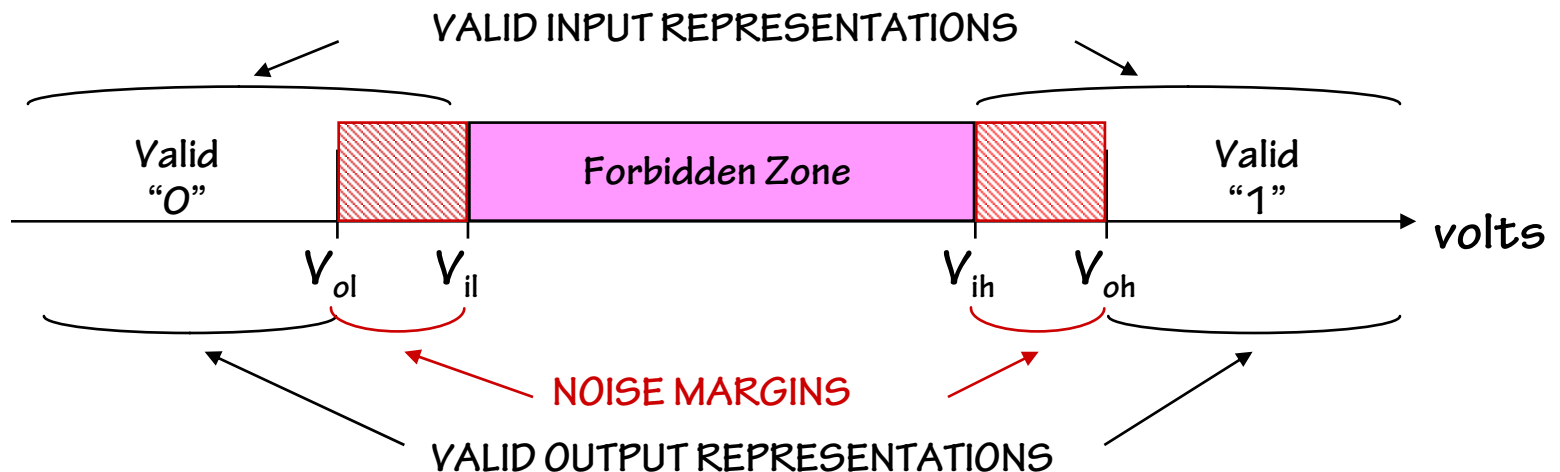No! A combinational device must restore marginally valid signals. It must accept marginal inputs and provide unquestionable outputs (i.e., to leave room for noise).



# A Buffer

A simple BUFFER:

  

**Voltage Transfer Characteristic (VTC):**

Plot of  $V_{out}$  vs.  $V_{in}$  where each measurement is taken after any transients have died out.


*Note: VTC does not tell you anything about how fast a device is— it measures static behavior not dynamic behavior*

Static Discipline requires that we avoid the shaded regions (aka “forbidden zones”), which correspond to *valid* inputs but *invalid* outputs. Net result:

combinational devices must have **GAIN > 1** and be **NONLINEAR**.
 
# Can this be a combinational device?

Suppose that you measured the voltage transfer curve of the device shown below.  
 Could we build a logic family using it as a single-input combinational device?



Hmmm, it had better be an *INVERTER*...

The device must be able to actually produce the desired output level. Thus,  $V_{OL}$  can be no lower than 0.5 V.

Try  $V_{OL} = 0.5$  V

$V_{IH}$  must be high enough to produce  $V_{OL}$

Try  $V_{IH} = 3$  V

Now, choose noise margins – find an  $N$  and set

$$V_{OH} = V_{IH} + N$$

$$V_{IL} = V_{OL} + N$$

Such that

$V_{IH}$  IN generates  $V_{OL}$  or less out; AND


$V_{IL}$  IN generates  $V_{OH}$  or more out.

Try  $N = 0.5$  V

# Building Bits from Atoms

## We Need Three Things:

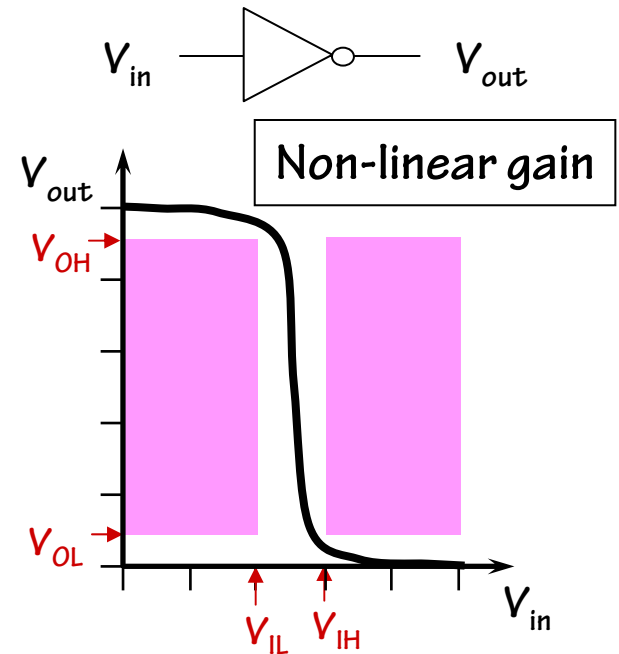
1. Represent and communicate bits
2. Transform bits (Invert, AND, OR,...)
3. Remember bits (storage)



...subject to the fundamentals of physics:

Uncertainty, Noise,  $c$ , Thermodynamics,...

# MOSFETS: Gain & non-linearity

 


MOSFETs (metal-oxide-semiconductor field-effect transistors) are four-terminal voltage-controlled switches. Current flows between the diffusion terminals if the voltage on the gate terminal is large enough to create a conducting “channel”, otherwise the mosfet is off and the diffusion terminals are not connected.

Why are MOS devices King?


 
# FETs as switches

The four terminals of a Field Effect Transistor (gate, source, drain and bulk) connect to conducting surfaces that generate a complicated set of electric fields in the channel region which depend on the relative voltages of each terminal.






## INVERSION:

A sufficiently strong vertical field will attract enough electrons to the surface to create a conducting n-type channel between the source and drain.


## CONDUCTION:

If a channel exists, a horizontal field will cause a drift current from the drain to the source.

# CMOS Inverter

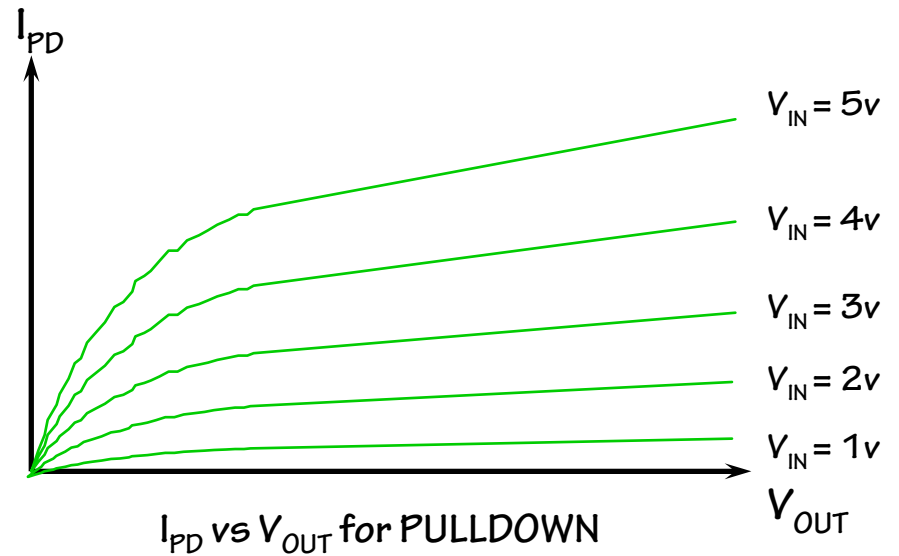 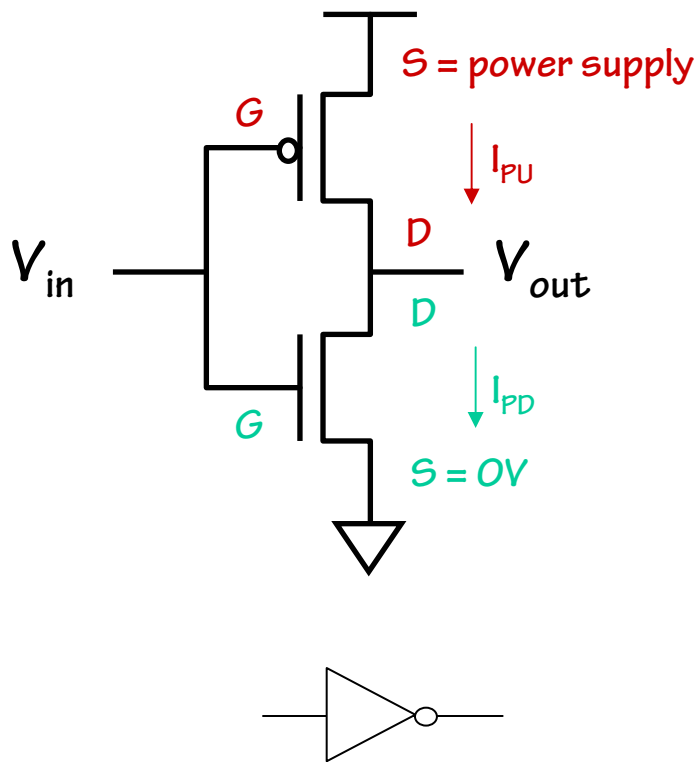


# Think Switches

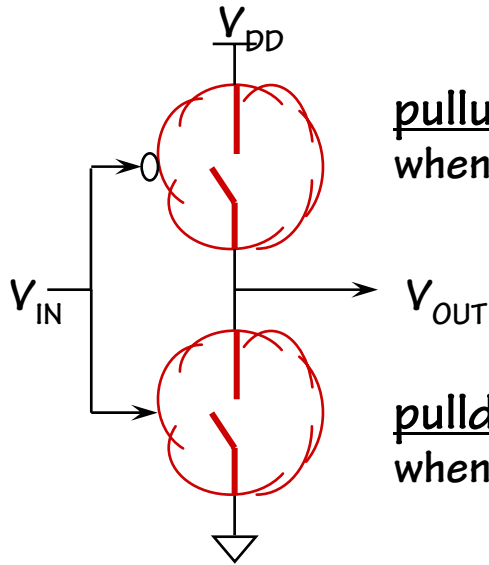


pullup: make this connection  
when  $V_{IN}$  near 0 so that  $V_{OUT} = V_{DD}$

 pulldown: make this connection  
when  $V_{IN}$  near  $V_{DD}$  so that  $V_{OUT} = 0$





# CMOS complements


What a nice  $V_{OH}$  you have...

 


Thanks. It runs in the family...

  


conducts when  $V_{GS}$  is high

 


conducts when  $V_{GS}$  is low

 

 
conducts when A is high  
and B is high:  $A \cdot B$



 conducts when  $\overline{A}$  is low  
or B is low:  $\overline{A+B} = \overline{A} \cdot \overline{B}$



 
conducts when A is high  
or B is high:  $A+B$




conducts when A is low  
and B is low:  $\overline{A \cdot B} = \overline{A+B}$
 
# General CMOS gate recipe


Step 1. Figure out pull-down network that does what you want, e.g.,  $F = A*(B+C)$   
(What combination of inputs generates a low output)



 Step 2. Walk the hierarchy replacing nfets with pfets, series subnets with parallel subnets, and parallel subnets with series subnets



 Step 3. Combine pfet pullup network from Step 2 with nfet pull-down network from Step 1 to form fully-complementary CMOS gate.



But isn't it hard to wire it all up?

