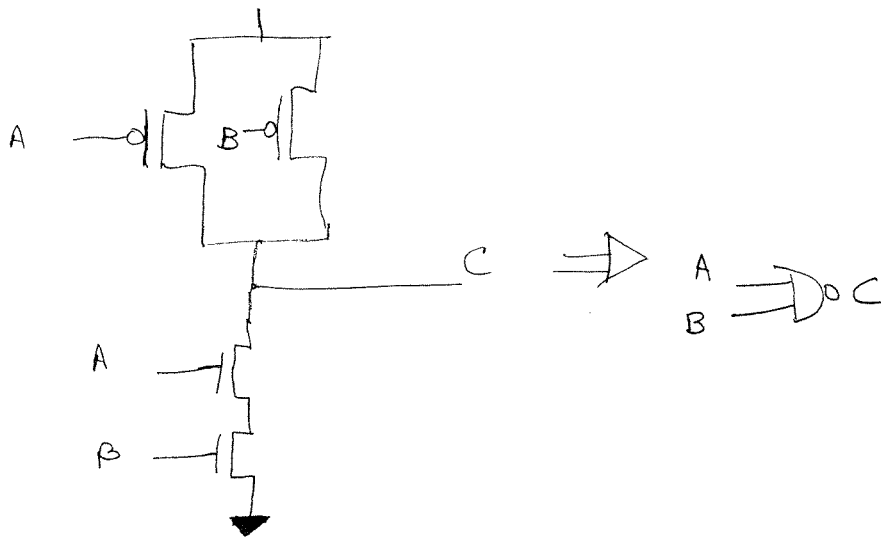


NAND


A	B	C
0	0	1
0	1	1
1	0	1
1	1	0



UNIVERSAL

NOR


A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

 

UNIVERSAL

INVERTER WITH NAND'S

A	B
0	1
1	0

 


AND




N - INPUT

NAND - NOR

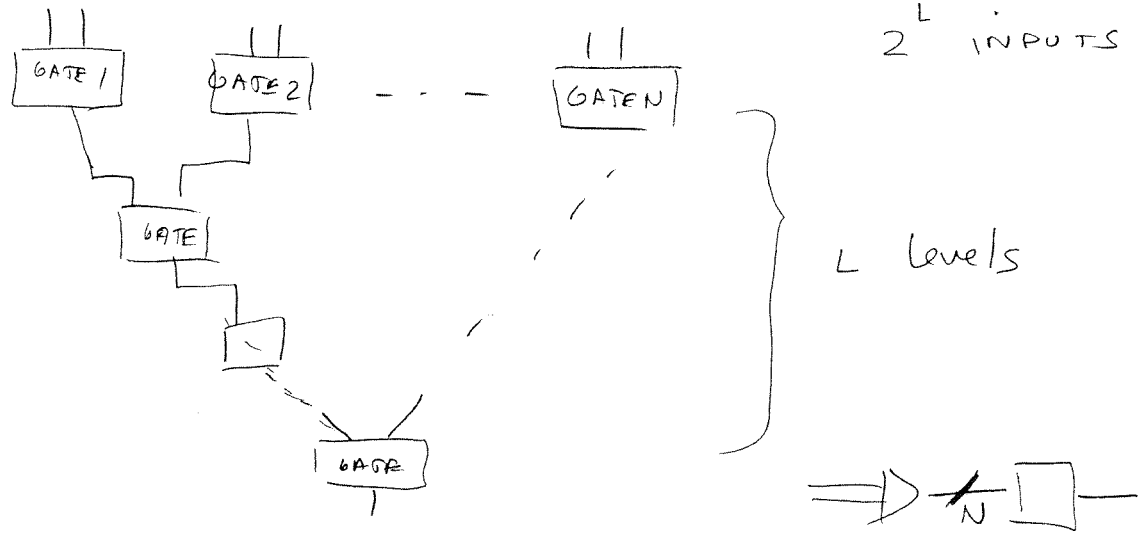


2-1 MUX.

A	B	Sel	ϕ
0	x	0	0
1	x	0	1
x	0	1	0
x	1	1	1


 


ADDER (1 bit)

A	B	Cin	ϕ	Count
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

 



ADDER (N BIT)

  

Bit Slice Design



ALU (1 bit)

M ₁ M ₀	A	B	C	Count
00			A+B+C	
01			A	
11			\bar{A}	
10			Cin	A

  




MEMORY AND SEQUENTIAL CIRCUITS

R-S latch

  



R	S	Q_t	Q_{t+1}
0	0	X	INVALID
1	1	0	0
1	1	1	1
0	1	X	1
1	0	X	0

D Flip-Flop

   


Master-Slave D-Flip flop. (Edge-triggered)


Race Condition

  

Register N-Bit

 

2-4 Decoder

 

A_1	A_0	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	1	0	0	0	1
1	0	0	0	1	0

4 x 8 memory

