

**Universidad de Puerto Rico  
Recinto Universitario de Mayagüez**

**INEL 4206 – Microprocesadores  
Primavera 2002**

**Ejercicios de práctica  
Examen Parcial I**

1. **Processor Implementation.** Add an instruction BrL (Branch and link) to the Easy I processor designed in class. You must provide any necessary additions/modifications to the Easy I datapaths, flowcharts and state transition table. The instruction has the following functionality:

Symbolic Name	Assembler Example	Action
BrL	BrL sort	MEM[X-2] <- PC PC <- X

2. **Processor Implementation.** Add an instruction RtL (Return using link) to the Easy I processor designed in class. You must provide any necessary additions/modifications to the Easy I datapaths, flowcharts and state transition table. The instruction has the following functionality:

Symbolic Name	Operands	Action
RtL	RtL sort	PC <- MEM[X-2]

3. **Combinational Logic.** Provide two alternative designs for a combinational circuit to control a Dice LED display. The display has one input for each of 7 LED lights. The combinational circuit must map three inputs encoding a binary representation of a number between 0 and 6 into the 7 control signals controlling the LED's. Design one should use traditional K-Map techniques and should be based on logic gates. The second design should use a ROM or PLA.

