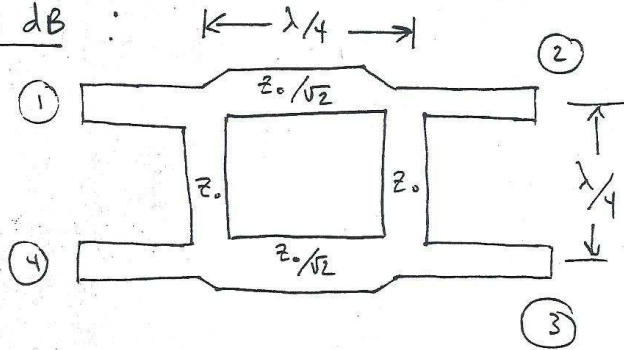



# "Branch Line Coupler"

- 4 puertos
- simétrica → "even-odd mode"
- ancho de banda estrecho
- acoplamiento "fuerte" (12.7 dB)

Diseño 3 dB :



Circuitos normalizados :

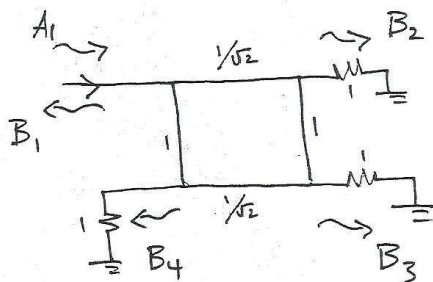


$$S_{11} = \frac{B_1}{A_1}$$

$$S_{21} = \frac{B_2}{A_1}$$


$$S_{31} = \frac{B_3}{A_1}$$

$$S_{41} = \frac{B_4}{A_1}$$

Make  $A_1 = 1$

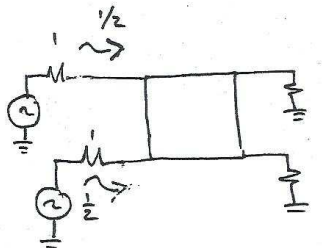


Even-Mode

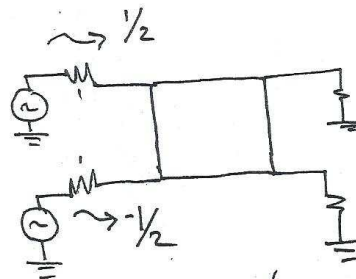

odd-Mode

Even Mode

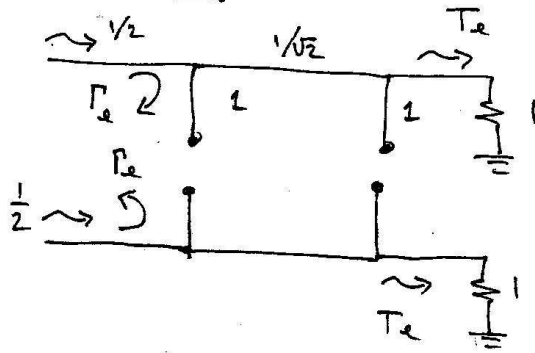

$$\frac{B_1}{A_1} = \frac{B_2}{1} = \frac{1}{2} \Gamma_e + \frac{1}{2} \Gamma_0$$


$$B_2 = \frac{1}{2} T_e + \frac{1}{2} T_0$$

$$B_3 = \frac{1}{2} T_e - \frac{1}{2} T_0$$

$$B_4 = \frac{1}{2} \Gamma_e - \frac{1}{2} \Gamma_0$$


- Superposición respuestas modo par + modo impar

Odd Mode

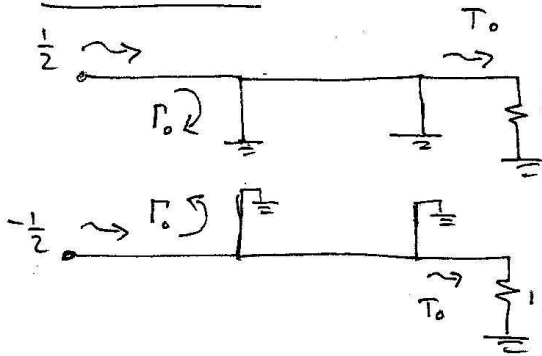

Usando matriz ABCD podemos determinar

$\Gamma_e, T_e$  y  $\Gamma_o, T_o$

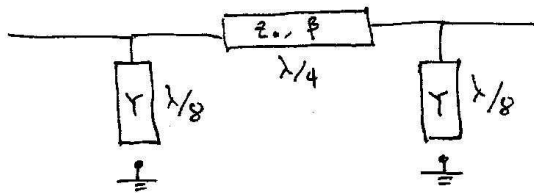

donde

$$Z_0 \frac{\lambda}{4} = \frac{1}{\sqrt{2}}$$

$$Y = 1$$

$$\begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \cdot \begin{bmatrix} \text{capl } jZ_0 \text{ simpl} \\ jY \text{ simpl capl} \end{bmatrix} \cdot \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

ABCD "stub"

ABCD línea

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\text{even}} = \begin{bmatrix} 1 & 0 \\ j & 1 \end{bmatrix} \begin{bmatrix} 0 & j\sqrt{2} \\ j\sqrt{2} & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ j & 1 \end{bmatrix} \quad 3$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_e = \frac{1}{\sqrt{2}} \begin{bmatrix} -1 & j \\ j & -1 \end{bmatrix}$$

De la misma forma

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\text{odd}} = \frac{1}{\sqrt{2}} \begin{bmatrix} 1 & j \\ j & 1 \end{bmatrix}$$

Transformo  $[A B C D]_{\text{even}} \Rightarrow [S]_{\text{even}}$

$[A B C D]_{\text{odd}} \Rightarrow [S]_{\text{odd}}$

donde

$$[S]_{\text{even}} = \begin{bmatrix} \Gamma_e & T_e \\ T_e & \Gamma_e \end{bmatrix}$$

$$[S]_{\text{odd}} = \begin{bmatrix} \Gamma_o & T_o \\ T_o & \Gamma_o \end{bmatrix}$$

De tabla 5-2

$$\Gamma_e = 0, \quad \Gamma_o = 0, \quad T_e = -\frac{(1+j)}{\sqrt{2}}, \quad T_o = \frac{(1-j)}{\sqrt{2}}$$

De aquí;  $B_1 = 0, \quad B_2 = \frac{-j}{\sqrt{2}}, \quad B_3 = \frac{-1}{\sqrt{2}}, \quad B_4 = 0$

$$[S] = \frac{-1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix}$$



Matriz  $[S]$  para híbrido de cuadratura  
("Branch line coupler")

# 3dB Branch Line Coupler

$$f_c = 3 \text{ GHz}$$

$$\epsilon_r = 2.33 \quad h = 4 \text{ mils}$$

Line calc:

$$l_{\lambda/4} = 700 \text{ mils}$$

$$W_{50\Omega} = 133 \text{ mils}$$

$$W_{35.35} = 218 \text{ mils}$$

