

Clase #3 INEL 5306

$$V_n(z) = V_{on}^+ e^{-j\beta z} + V_{on}^- e^{+j\beta z}$$


$$V_n(z) = V_n^+ + V_n^-$$

Puerto #1 : $V_1 = V_1^+ + V_1^-$

#2 : $V_2 = V_2^+ + V_2^-$

[S] \rightarrow describe completamente el circuito reemplazando voltajes incidentes con reflejados en los puertos del circuito. Son # complejos!!

$$S_{11} = |S_{11}| \angle \theta_{S_{11}}$$

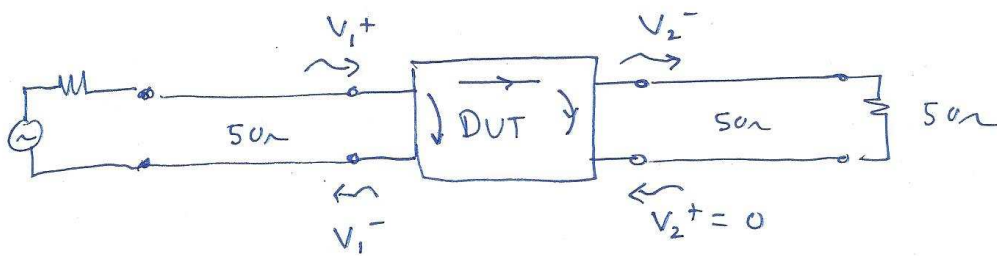

$$S_{11} = \frac{V_1^-}{V_1^+} \Big|_{V_2^+ = 0}$$

$$S_{21} = \frac{V_2^-}{V_1^+} \Big|_{V_2^+ = 0}$$

De la misma forma:

$$S_{22} = \frac{V_2^-}{V_2^+} \Big|_{V_1^+ = 0}$$

$$S_{12} = \frac{V_1^-}{V_2^+} \Big|_{V_1^+ = 0}$$

$$V_1^- = S_{11}V_1^+ + S_{12}V_2^+$$

$$V_2^- = S_{21}V_1^+ + S_{22}V_2^+$$

$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \underbrace{\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}}_{[S]} \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

En general :

$$S_{ij} = \frac{V_i^-}{V_j^+} \Big|_{V_k^+ = 0 \quad (k \neq j)}$$

← sale por parte

↑
mudateen parte j

$$\begin{bmatrix} V_1^- \\ V_2^- \\ \vdots \\ V_n^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \dots & S_{1n} \\ S_{21} & S_{22} & \dots & S_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ S_{n1} & S_{n2} & \dots & S_{nn} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \\ \vdots \\ V_n^+ \end{bmatrix}$$


↑
 V_1^+

↑
 V_2^+

Uso de decibelios:

— Razones de potencia la expresamos en dB

$$10 \log \frac{P_1}{P_2} \text{ dB}$$

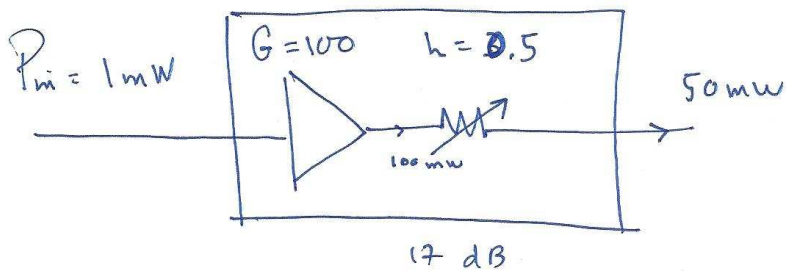

$$G_{dB} = 10 \log 100 = 20 \text{ dB}$$

$$L_{dB} = 10 \log(0.5) = -3 \text{ dB}$$

Usaremos referencia para expresar en dB valores absolutos.

$$P_{in \text{ dBm}} = 10 \log \frac{P_{in}}{1mW} \text{ dBm}$$

$$= 10 \log \frac{1mW}{1mW} = \underline{\underline{0 \text{ dBm}}}$$

$$P_{out} \text{ dBm} = 0 \text{ dBm} + 20 - 3 = \underline{17 \text{ dBm}}$$



$$\implies 10 \log \frac{P_{out}}{1 \text{ mW}} = 17 \text{ dBm}$$

$$P_{out} = (10^{1.7}) (1 \text{ mW}) = \underline{\underline{50 \text{ mW}}}$$

$$\implies 10 \log \frac{P}{1 \text{ W}} \quad \underline{\underline{\text{dBW}}}$$

100 mW	→	20 dBm
20 mW	→	13 dBm
8 mW	→	9 dBm
4 mW	→	6 dBm
2 mW	→	3 dBm
1 mW	→	0 dBm
0.5 mW	→	-3 dBm
0.25 mW	→	-6 dBm


Exemplo :

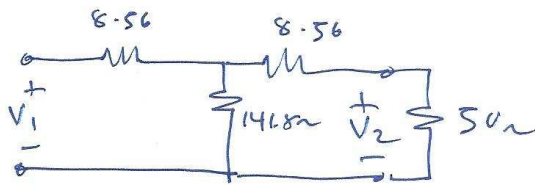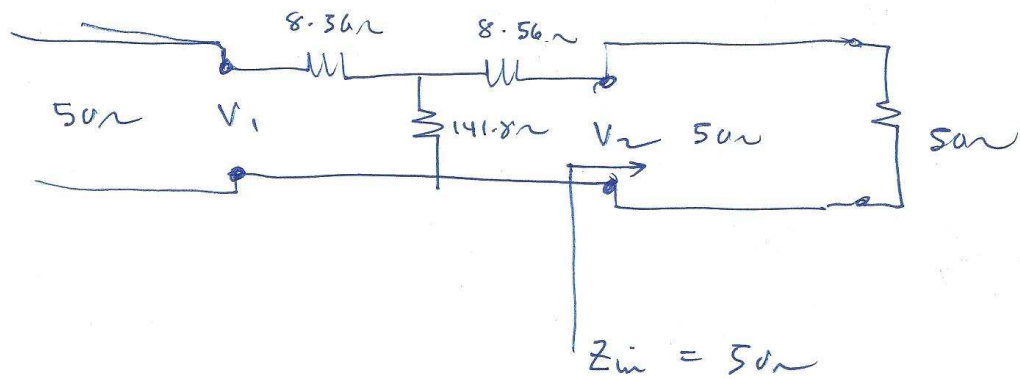

$$V_1 = V_1^+ + V_1^-$$

$$V_2 = V_2^+ + V_2^-$$

S₁₁

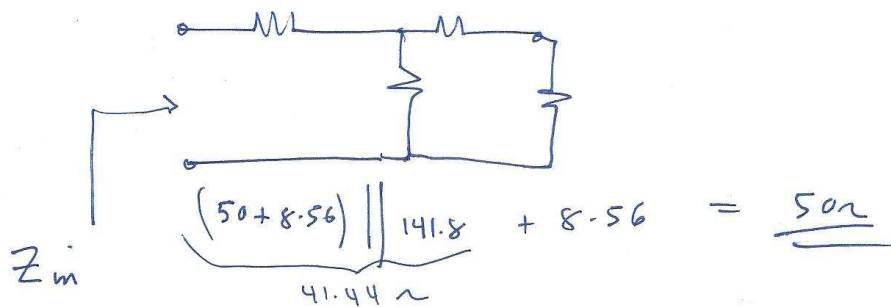


$$\therefore S_{11} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{0}{100} = 0$$

$$V_1^{\neq} = V_{1+} + \cancel{V_{1-}^0} = V_{1+}$$

$$= V_{1+} (1 + \cancel{S_{11}}) = V_{1+}$$

$$V_2 = \cancel{V_{2+}^0} + V_{2-} = V_{2-}$$
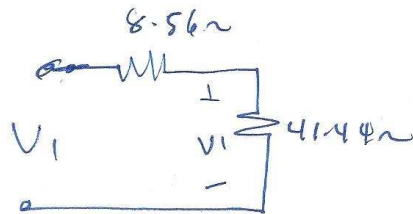
$$\therefore S_{21} = \frac{V_{2-}}{V_{1+}}$$



$$V' = \frac{(V_1)(41.44)}{41.44 + 8.56} = \frac{41.44}{50} V_{1+}$$



$$V_2 = \frac{(V')(50)}{50 + 8.56} = \frac{\left(\frac{41.44}{50} V_{1+}\right)(50)}{50 + 8.56} = .707 V_{1+}$$

$$\frac{V_{2-}}{V_{1+}} = S_{21} = .707$$

$$|S_{21}| = .707$$

$$\theta = 0$$

$$|S_{21}|_{dB} = 20 \log .707 = -3 dB$$

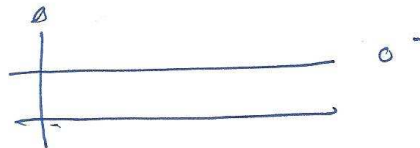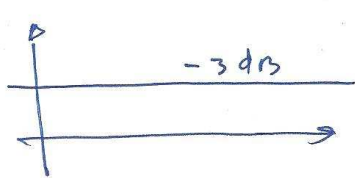


De la misma forma

$$S_{12} = .707 \quad S_{22} = 0$$



$$[S] = \begin{bmatrix} 0 & .707 \\ .707 & 0 \end{bmatrix}$$

Asignación:

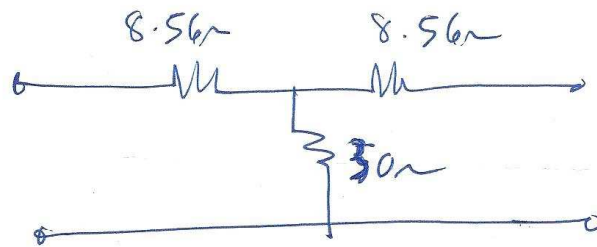

$$[S] = \begin{bmatrix} -.275 & .432 \\ .432 & -.275 \end{bmatrix}$$

[S] para línea de transmisión

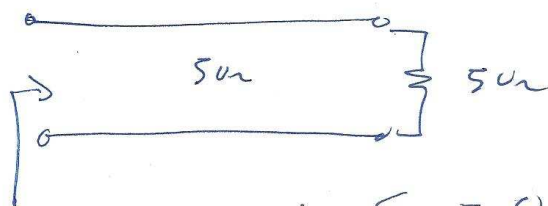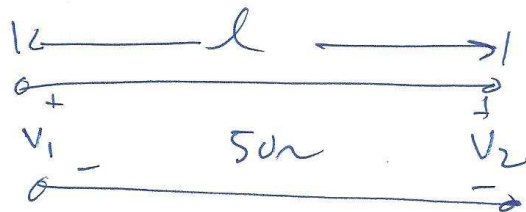

$$z_{in} = 50\Omega \quad \therefore S_{11} = 0$$

$$S_{22} = 0$$



En línea $V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$

$$V_1 = V(z=l) = V_0^+ e^{j\beta l} + 0$$

$$V_1 = V_1^+ + V_1^- = V_1^+ = V_0^+ e^{+j\beta l}$$

$$V_2 = \cancel{V_2^+} + V_2^- = V_2^- = V(z=0) = V_0^+ e^{j0} = V_0^+$$
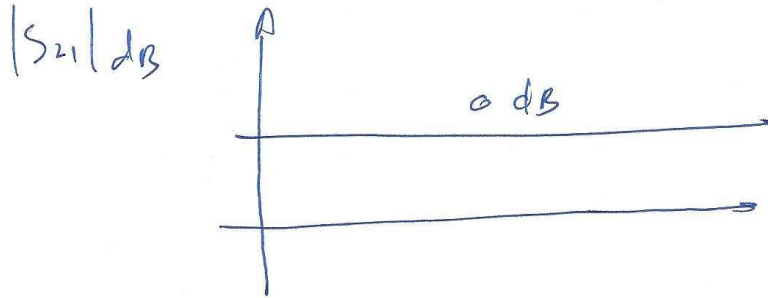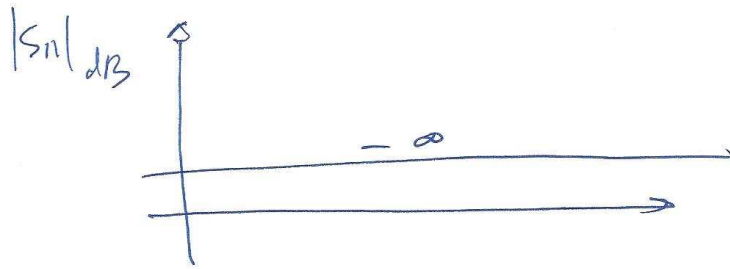
$$\therefore \frac{V_2^-}{V_1^+} = \frac{V_0^+}{V_0^+ e^{j\beta l}} = e^{-j\beta l}$$





$\theta_{S_{21}}$

$$= -\beta l$$

$$= -\frac{2\pi}{\lambda} l$$

$$= -\frac{2\pi}{c} f l$$

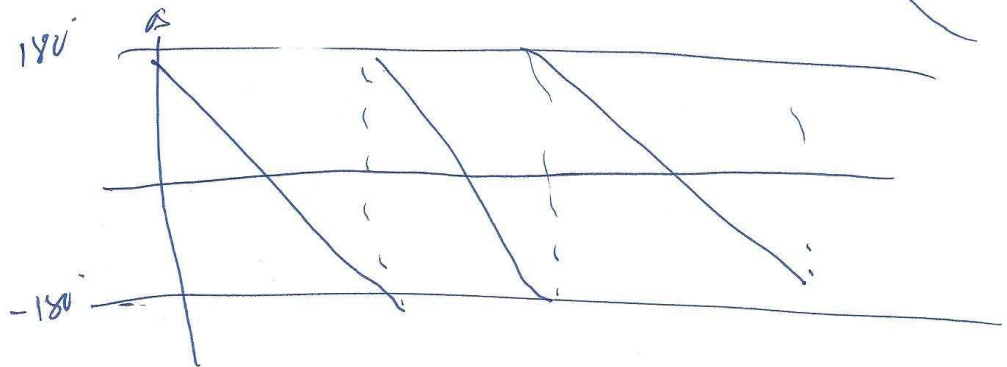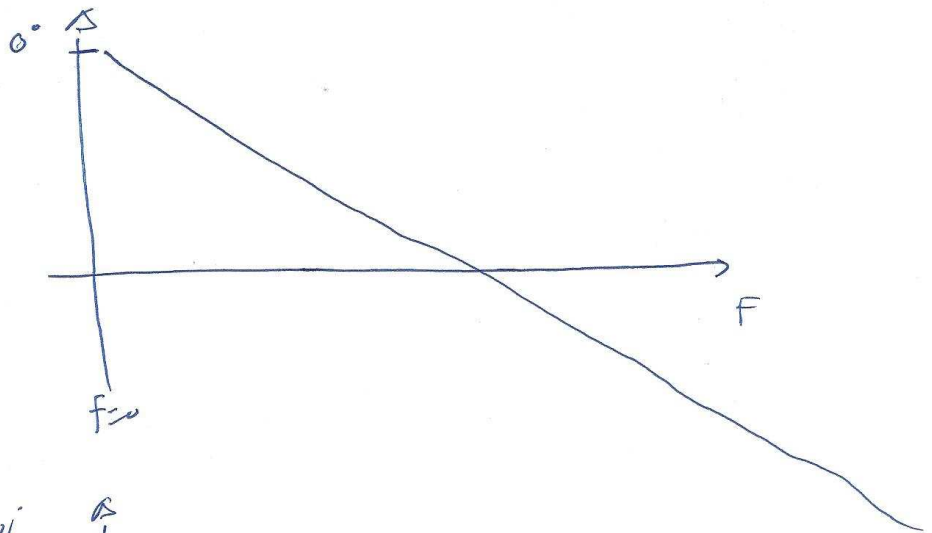

Symmetry

$$S_{nm} = S_{mn}$$


$$[S] = [S]^t$$

$$[S] = \begin{bmatrix} .1 \angle 0^\circ & .8 \angle 90^\circ \\ .8 \angle 90^\circ & .2 \angle 0^\circ \end{bmatrix}$$

$$[S]^t = \begin{bmatrix} .1 \angle 0^\circ & .8 \angle 90^\circ \\ .8 \angle 90^\circ & .2 \angle 0^\circ \end{bmatrix} \checkmark$$

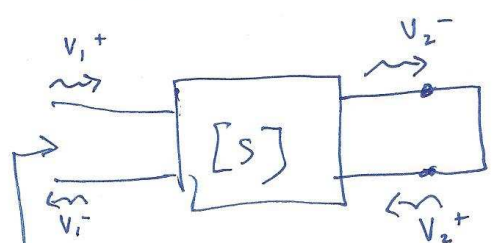Example

~~$$[S] = \begin{bmatrix} 0.1 \angle 0^\circ & 0.8 \angle 90^\circ \\ 0.8 \angle 90^\circ & 0.2 \angle 0^\circ \end{bmatrix}$$~~



$$\Gamma_z = -1$$

$$\frac{V_2^+}{V_2^-} = -1$$

$$\Gamma_{11} = ? \quad \frac{V_1^-}{V_1^+}$$

$$V_1^- = 0.1V_1^+ + j0.8V_2^+$$

$$V_2^- = j0.8V_1^+ + 0.2V_2^+$$

$$V_1^- = 0.1V_1^+ - j0.8V_2^-$$

$$V_2^- = j0.8V_1^+ - 0.2V_2^-$$

$$V_2^- = \frac{j0.8V_{1+}}{1.2}$$

$$V_1^- = 0.1V_{1+} - j0.8 \left(\frac{j0.8V_{1+}}{1.2} \right)$$

$$\frac{V_1^-}{V_{1+}} = \Gamma_{11} = \underline{\underline{0.633}}$$