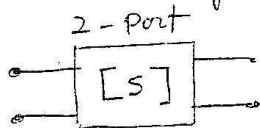


## INEL 5306 - Microondas

$$\sum_{n=1}^N |V_n^-|^2 = \sum_{n=1}^N |V_n^+|^2$$

Para circuito de dos puertos:



$$|V_1^-|^2 + |V_2^-|^2 = |V_1^+|^2 + |V_2^+|^2$$

$$\left. \begin{aligned} V_1^- &= S_{11} V_1^+ + S_{12} V_2^+ \\ V_2^- &= S_{21} V_1^+ + S_{22} V_2^+ \end{aligned} \right\} \text{Definición}$$

Entonces:

$$|S_{11} V_1^+ + S_{12} V_2^+|^2 + |S_{21} V_1^+ + S_{22} V_2^+|^2 = |V_1^+|^2 + |V_2^+|^2$$

Si hacemos  $V_2^+ = 0$

$$|S_{11} V_1^+|^2 + |S_{21} V_1^+|^2 = |V_1^+|^2$$

De aquí;  $|S_{11}|^2 + |S_{21}|^2 = 1$

$$S_{11} S_{11}^* + S_{21} S_{21}^* = 1$$

$$\sum_{k=1}^N S_{ki} S_{ki}^* = 1$$

La suma del producto punto de una columna por su conjugado tiene que ser  $= \underline{1}$

$$\text{se } |V_1^-|^2 + |V_2^-|^2 = |V_1^+|^2 + |V_2^+|^2 \quad \underline{2}$$

Podemos decir también que,

$$\begin{aligned} & (S_{11}V_1^+ + S_{12}V_2^+)(S_{11}V_1^+ + S_{12}V_2^+)^* + (S_{21}V_1^+ + S_{22}V_2^+)(S_{21}V_1^+ + S_{22}V_2^+)^* \\ &= |V_1^+|^2 + |V_2^+|^2 \end{aligned}$$

Multiplicando,

$$\begin{aligned} & |S_{11}V_1^+|^2 + S_{11}V_1^+S_{12}^*V_2^{+*} + S_{12}V_2^+S_{11}^*V_1^{+*} + |S_{12}V_2^+|^2 \\ &+ |S_{21}V_1^+|^2 + S_{21}V_1^+S_{22}^*V_2^{+*} + S_{22}V_2^+S_{21}^*V_1^{+*} + |S_{22}V_2^+|^2 \\ &= |V_1^+|^2 + |V_2^+|^2 = |S_{11}V_1^+|^2 + |S_{21}V_1^+|^2 + |S_{22}V_2^+|^2 + |S_{12}V_2^+|^2 \end{aligned}$$

Si decimos que  $V_1^+ = V_2^+ = V^+$

$$|V^+|^2 (S_{11}S_{12}^* + S_{12}S_{11}^* + S_{21}S_{22}^* + S_{22}S_{21}^*) = 0$$

$$A = S_{11}S_{12}^* + S_{21}S_{22}^*$$

$$|V^+|^2 (A + A^*) = 0$$

$$\text{Si } V_1^+ = V^+ \quad V_2^+ = jV^+$$

$$j|V^+|^2 (A^* - A) = 0$$

De aquí podemos inferir que  $A = 0$

$$\sum_{k=1}^N S_{ki}S_{kj}^* = 0 \quad i \neq j$$

otro punto

de una columna multiplicada por conjugado de otra = 0 !!


$$\begin{bmatrix} 0.1 \angle 90^\circ & 0.6 \angle -45^\circ & 0.6 \angle 45^\circ & 0 \\ 0.6 \angle -45^\circ & 0 & 0 & 0.6 \angle 45^\circ \\ 0.6 \angle -45^\circ & 0 & 0 & 0.6 \angle -45^\circ \\ 0 & 0.6 \angle 45^\circ & 0.6 \angle -45^\circ & 0 \end{bmatrix}$$

3

$$|S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 + |S_{14}|^2 = 1$$

$$(-1)^2 + (.6)^2 + (.6)^2 + 0 = 0.73 \neq 1$$

Desplazamiento del plano de referencia

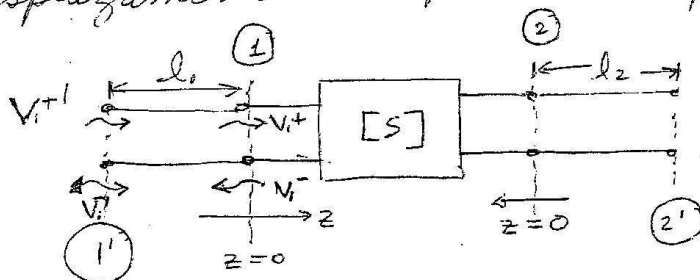

- Matriz se midió con respecto a terminales 1 y 2. ahora se desea mover el plano de referencia a 1' y 2', ¿cómo se afecta [S]?

$$V_1^{+1} = V_1^+ e^{j\beta l_1} = V_1^+ e^{j\theta_1}$$

$$V_1^{-1} = V_1^- e^{-j\theta_1}$$

$$V_2^{+1} = V_2^+ e^{j\theta_2}$$

$$V_2^{-1} = V_2^- e^{-j\theta_2}$$

yo se que (tomando referencia 1 y 2):

$$V_1^- = S_{11} V_1^+ + S_{12} V_2^+$$

$$V_2^- = S_{21} V_1^+ + S_{22} V_2^+$$

Puedo decir que:

$$V_1^- = V_1'^- e^{j\theta_1}; V_2^- = V_2'^- e^{j\theta_2}; V_1^+ = V_1'^+ e^{-j\theta_1}; V_2^+ = V_2'^+ e^{-j\theta_2}$$

stetuyendo,

$$V_1^- e^{j\theta_1} = S_{11} V_1^+ e^{-j\theta_1} + S_{12} V_2^+ e^{-j\theta_2}$$


$$V_2^- e^{j\theta_2} = S_{21} V_1^+ e^{-j\theta_1} + S_{22} V_2^+ e^{-j\theta_2}$$

$$V_1^- = S_{11} V_1^+ e^{-j2\theta_1} + S_{12} V_2^+ e^{-j(\theta_1 + \theta_2)}$$

$$V_2^- = S_{21} V_1^+ e^{-j(\theta_1 + \theta_2)} + S_{22} V_2^+ e^{-j2\theta_2}$$

$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} e^{-j2\theta_1} & S_{12} e^{-j(\theta_1 + \theta_2)} \\ S_{21} e^{-j(\theta_1 + \theta_2)} & S_{22} e^{-j2\theta_2} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

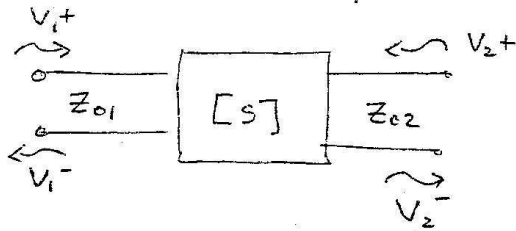Matriz - S, usando componentes normalizados



$$a_1 = \frac{V_1^+}{\sqrt{Z_{01}}}$$

$$b_1 = \frac{V_1^-}{\sqrt{Z_{01}}}$$

$$a_2 = \frac{V_2^+}{\sqrt{Z_{02}}}$$

$$b_2 = \frac{V_2^-}{\sqrt{Z_{02}}}$$

$$V_1 = V_1^+ + V_1^- = \sqrt{Z_{01}} (a_1 + b_1)$$

$$I_1 = \frac{V_1^-}{Z_{01}} - \frac{V_1^+}{Z_{01}} = \frac{1}{\sqrt{Z_{01}}} (a_1 - b_1)$$

Potencia :

5

$$\begin{aligned} P_{ave} &= \frac{1}{2} \operatorname{Re} \{ V I^* \} \\ &= \frac{1}{2} \operatorname{Re} \{ |a_1|^2 - |b_1|^2 + (b_1 a_1^* - b_1^* a_1) \} \\ &= \frac{1}{2} (|a_1|^2 - |b_1|^2) \end{aligned}$$

En general;  $S_{ij} = \frac{b_i}{a_j} \Big|_{a_k=0} \quad k \neq j$

$$S_{ij} = \frac{V_i^- \sqrt{Z_{0j}}}{V_j^+ \sqrt{Z_{0i}}} \Big|_{V_k^+ = 0}$$

$$V_1 = \sqrt{Z_{01}} (a_1 + b_1)$$

$$I_1 = \frac{1}{\sqrt{Z_{01}}} (a_1 - b_1) \Rightarrow b_1 = a_1 - \sqrt{Z_{01}} I_1$$

$$\therefore V_1 = \sqrt{Z_{01}} (a_1 + a_1 - \sqrt{Z_{01}} I_1)$$

$$V_1 = 2\sqrt{Z_{01}} a_1 - Z_{01} I_1$$

$$\Rightarrow a_1 = \frac{V_1 + Z_{01} I_1}{2\sqrt{Z_{01}}}$$


$$b_1 = \frac{V_1 - Z_{01} I_1}{2\sqrt{Z_{01}}}$$

$$b_2 = \frac{V_2 - Z_{02} I_2}{2\sqrt{Z_{02}}}$$

$$a_2 = \frac{V_2 + Z_{02} I_2}{2\sqrt{Z_{02}}}$$

## Matriz de Transmisión (ABCD)


16

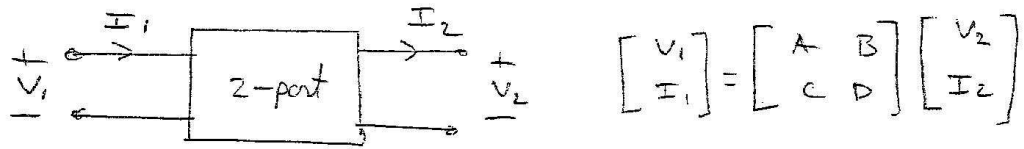

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$V_1 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$

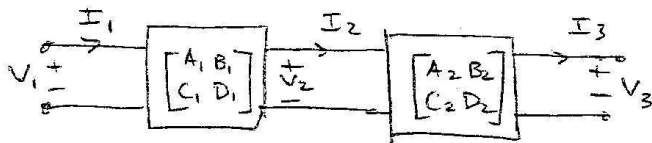

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$


$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \underbrace{\begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}}_{\begin{bmatrix} A_3 & B_3 \\ C_3 & D_3 \end{bmatrix}} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} A_3 & B_3 \\ C_3 & D_3 \end{bmatrix}$$


||
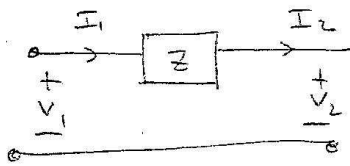
$$\begin{bmatrix} A_1 A_2 + B_1 C_2 & A_1 B_2 + B_1 D_2 \\ C_1 A_2 + D_1 C_2 & C_1 B_2 + D_1 D_2 \end{bmatrix}$$



$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

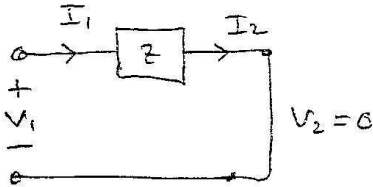
$$I_2 = I_1 = 0 \implies V_1 = V_2 \implies \underline{A = 1}$$



$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

$$V_1 = Z I_2$$

$$B = \frac{V_1}{I_2} = \underline{Z}$$

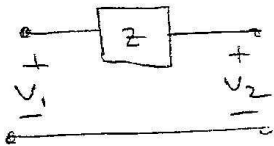

$$I_1 = I_2 = 0$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$\text{Since } I_1 = 0 \quad C = 0$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

$$\text{Como } I_1 = I_2 \implies \underline{D = 1}$$

$$[ABCD] = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$