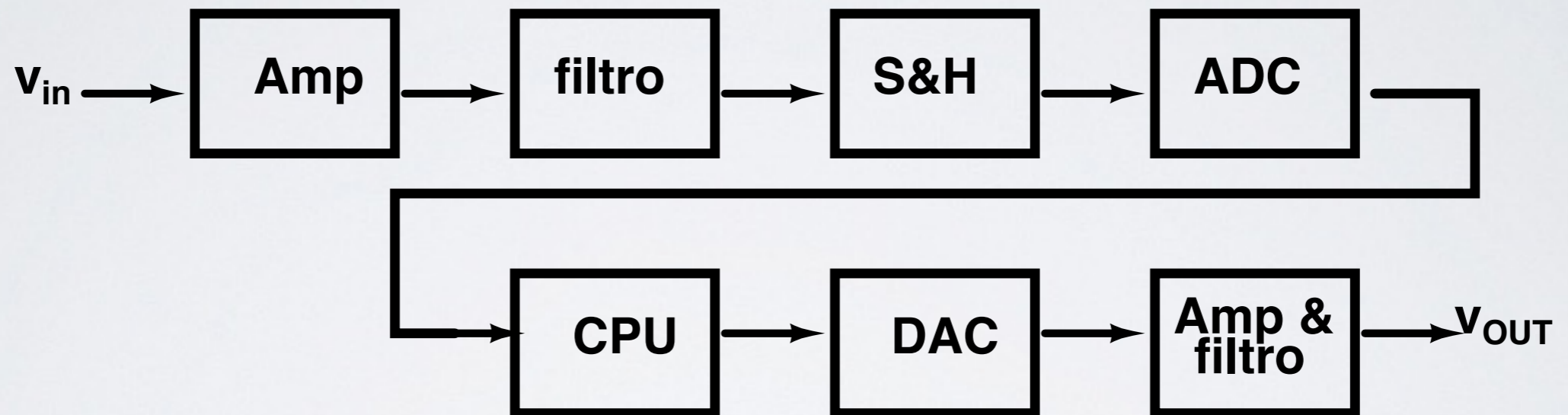



ADC/DAC

INEL 4207 Digital Electronics


MIXED-SIGNAL SYSTEM




INVERTING AMPLIFIER

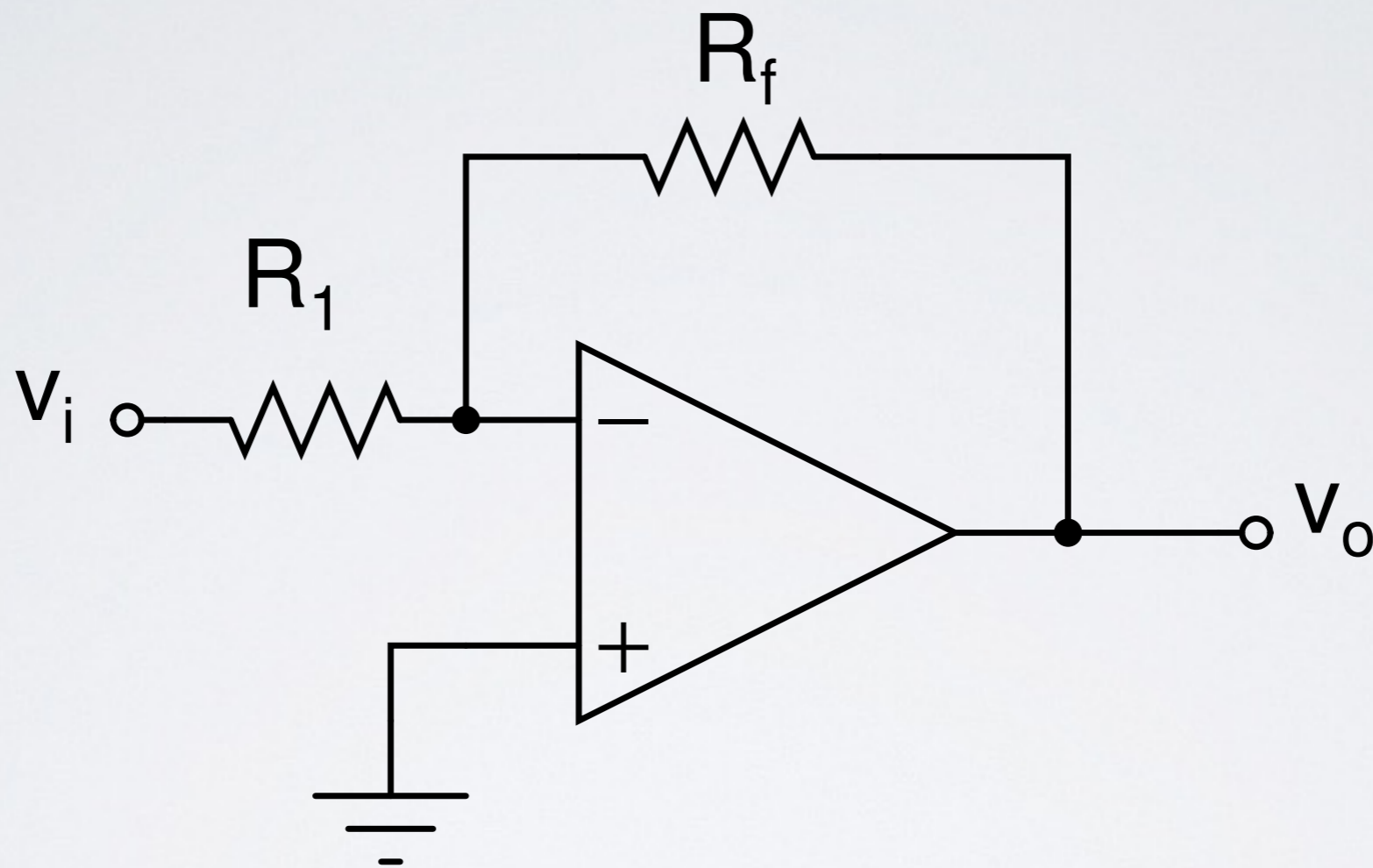


NON-INVERTING AMPLIFIER

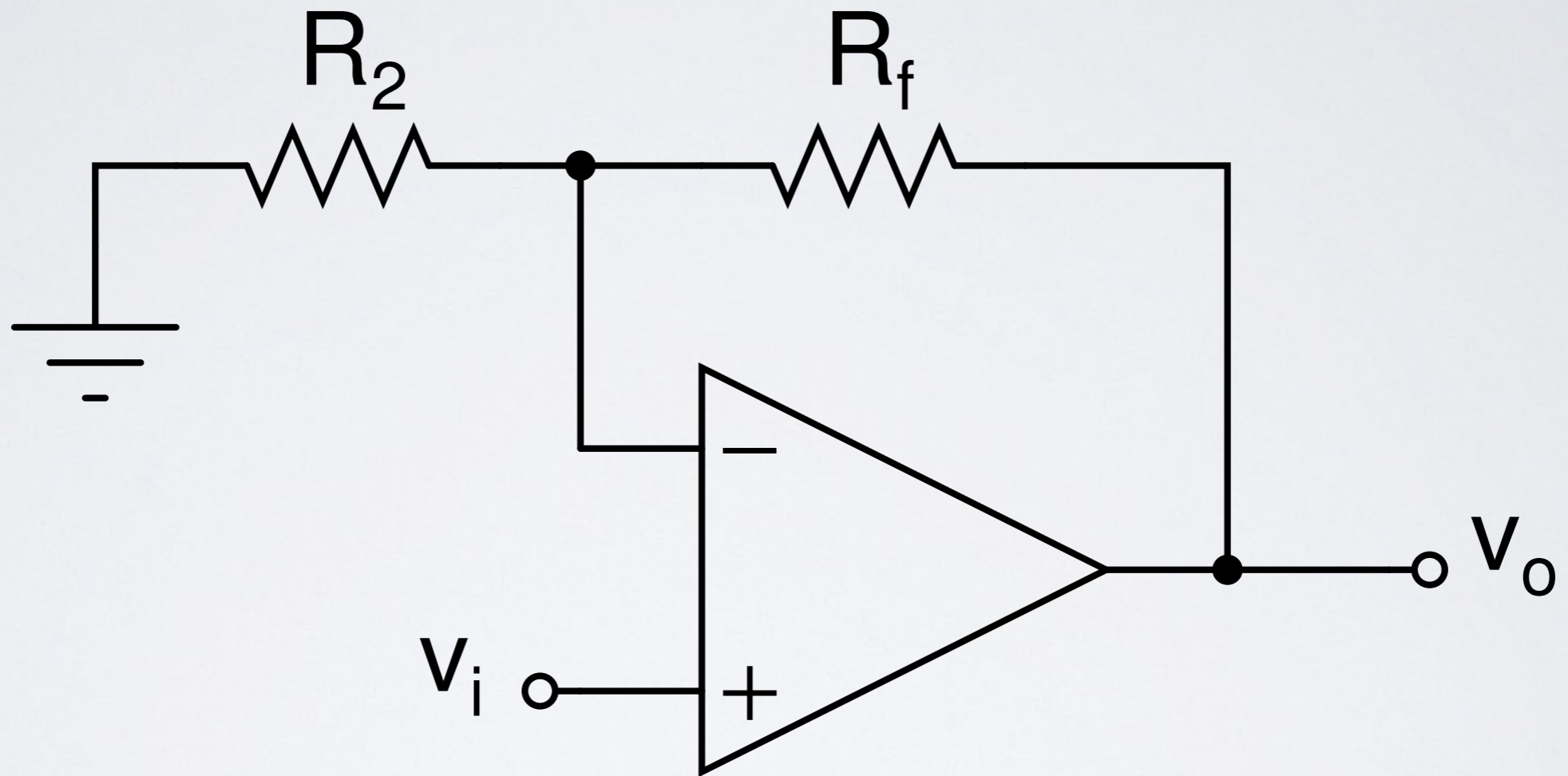



BUFFER AMPLIFIER

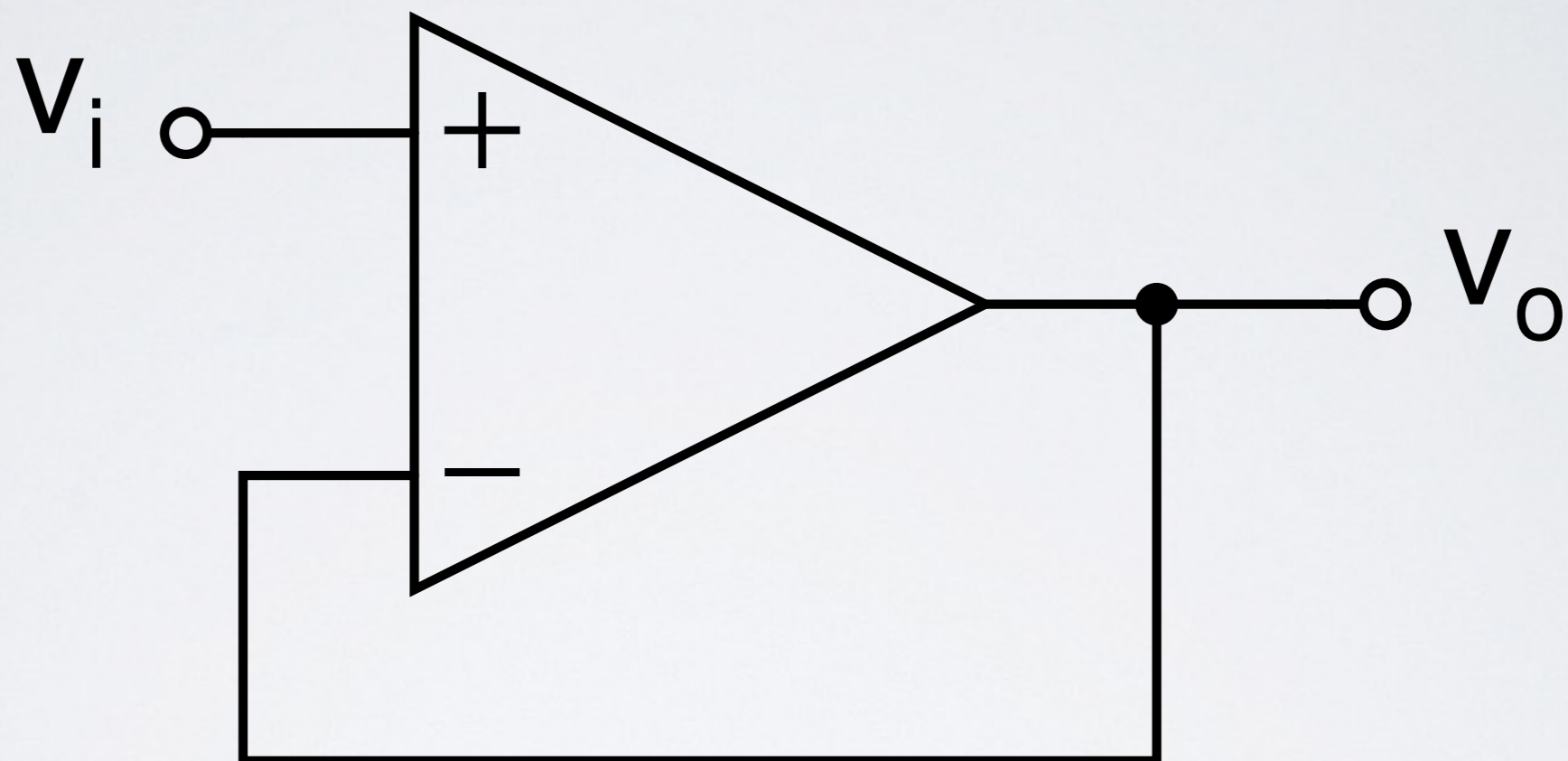


SUMMING AMPLIFIER

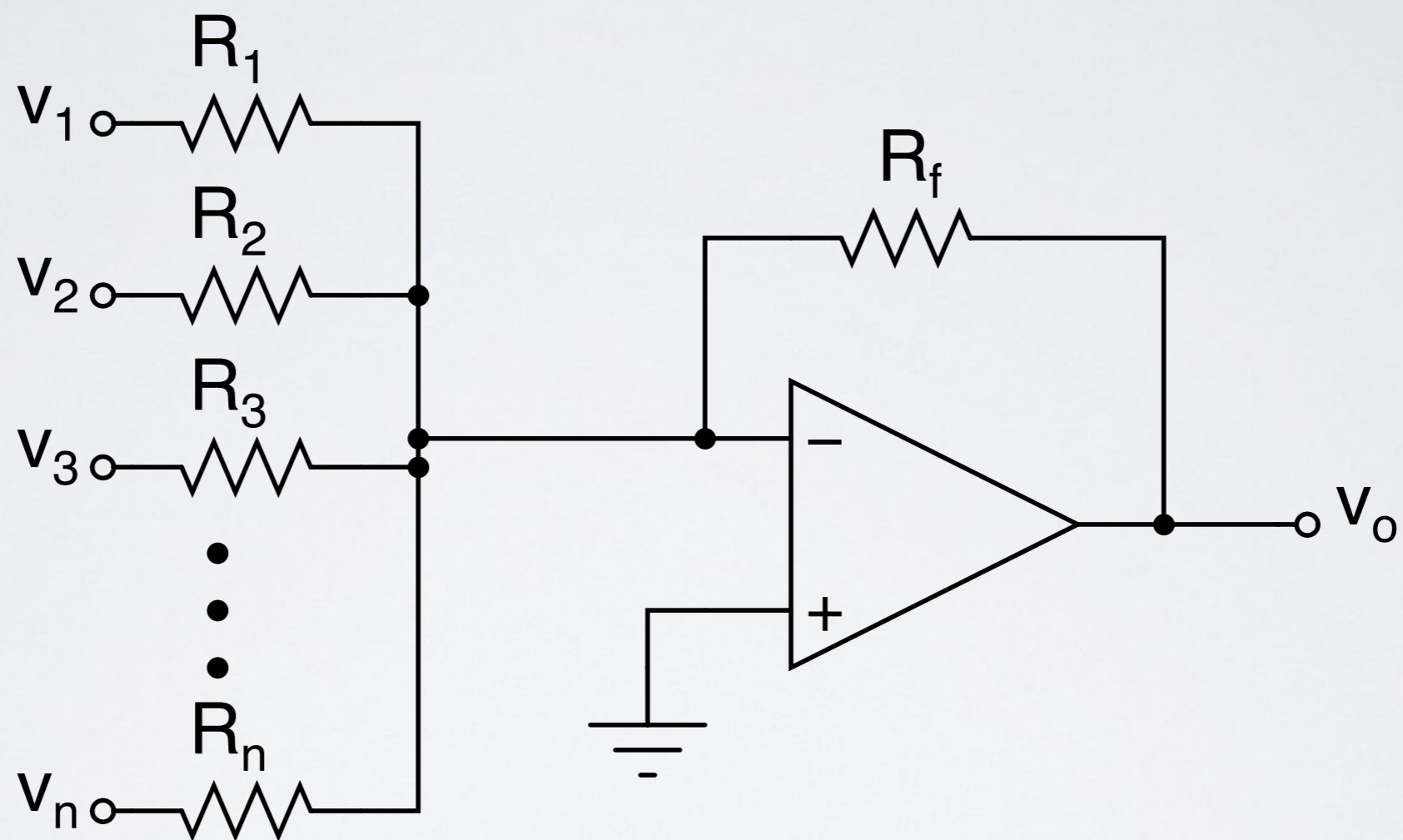

SAMPLE AND HOLD

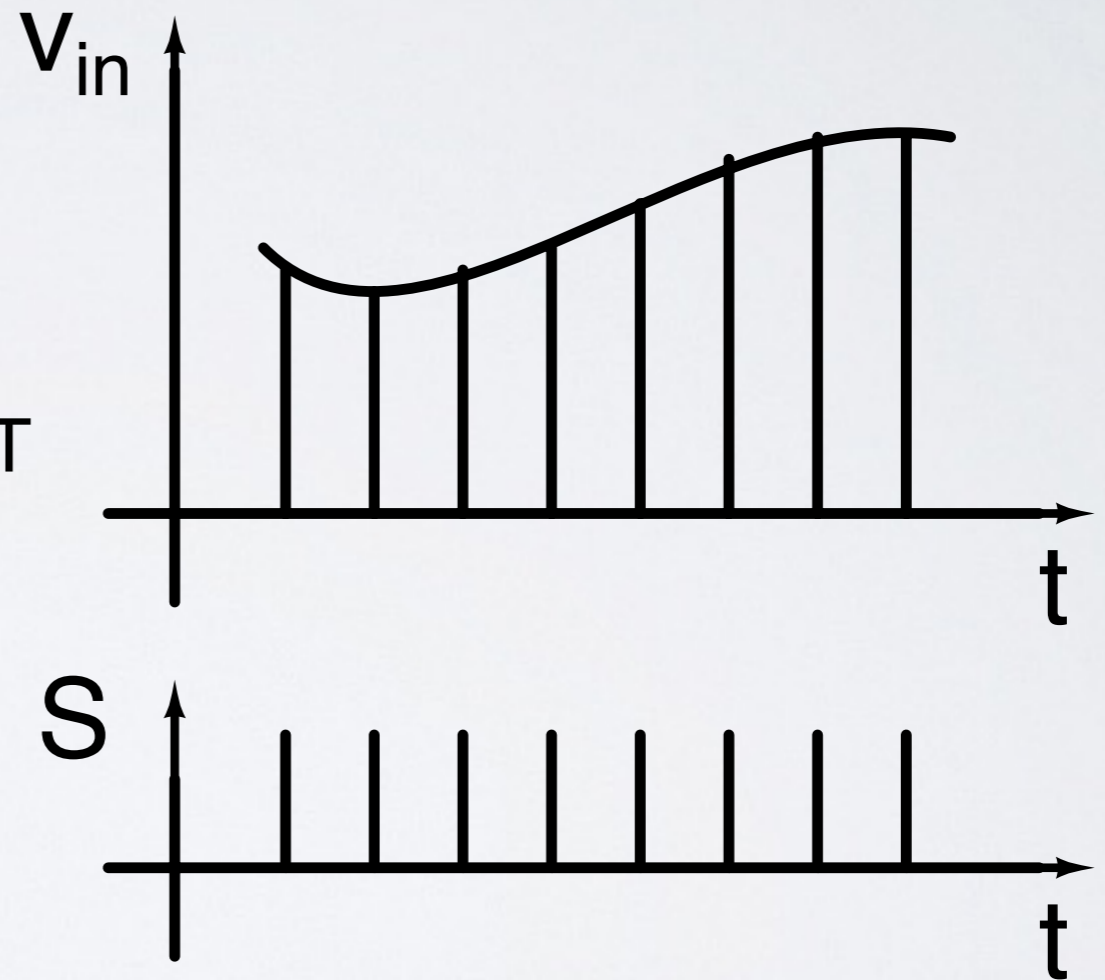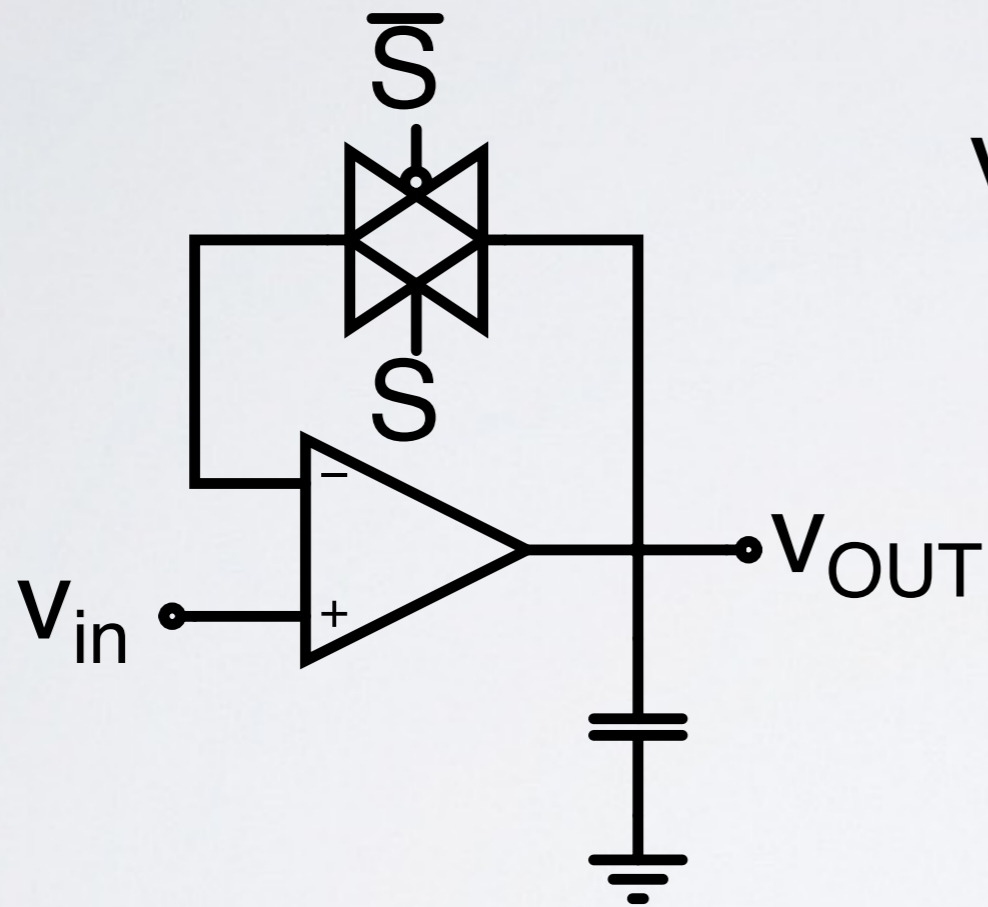

DAC

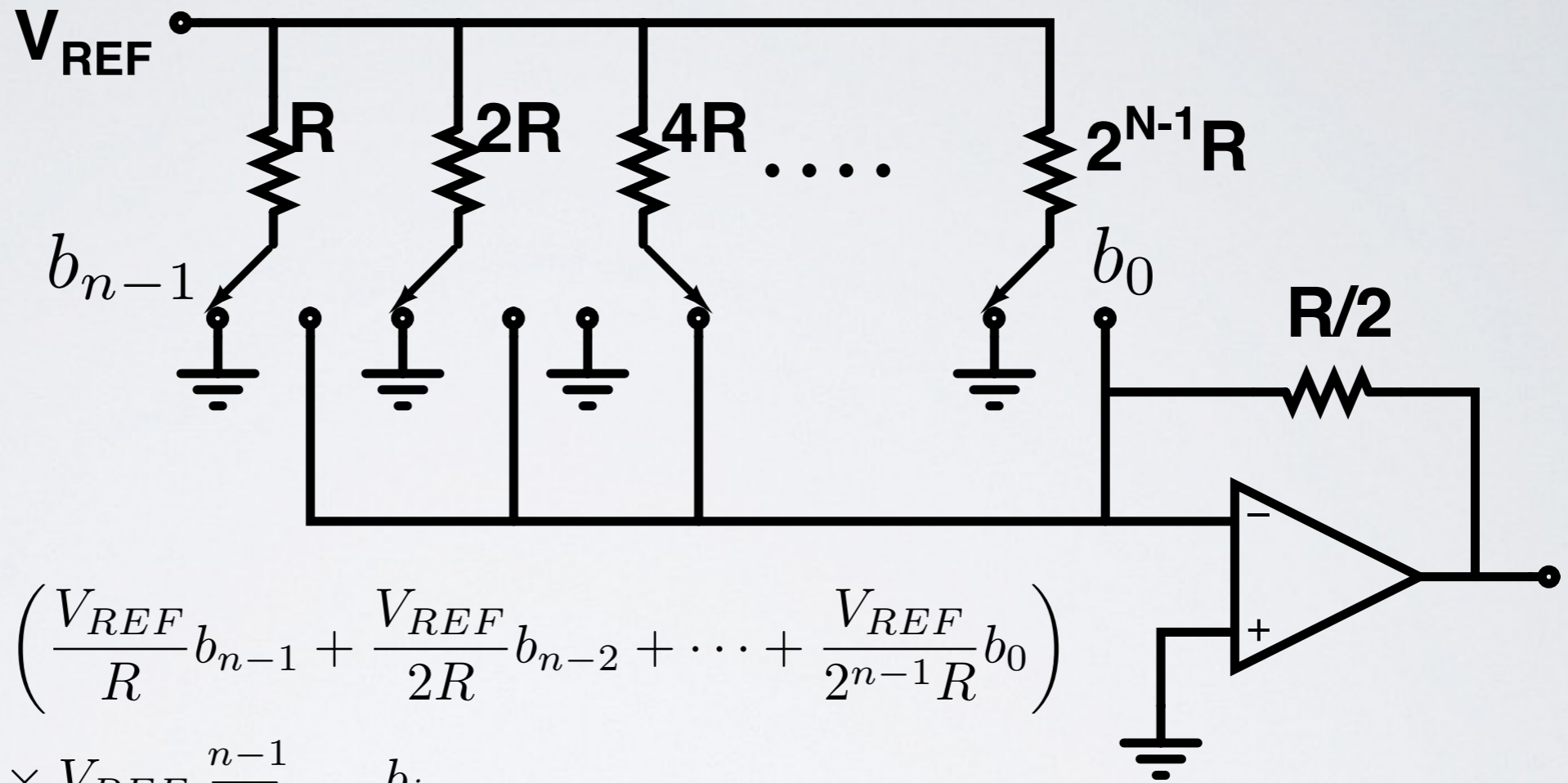


$$v_{OUT} = -\frac{R}{2} \left(\frac{V_{REF}}{R} b_{n-1} + \frac{V_{REF}}{2R} b_{n-2} + \dots + \frac{V_{REF}}{2^{n-1}R} b_0 \right)$$


$$= -\frac{R \times V_{REF}}{2} \sum_{i=0}^{n-1} \frac{b_i}{2^{n-i-1}R}$$

$$= -V_{REF} \sum_{i=0}^{n-1} \frac{b_i}{2^{n-i}}$$


DAC

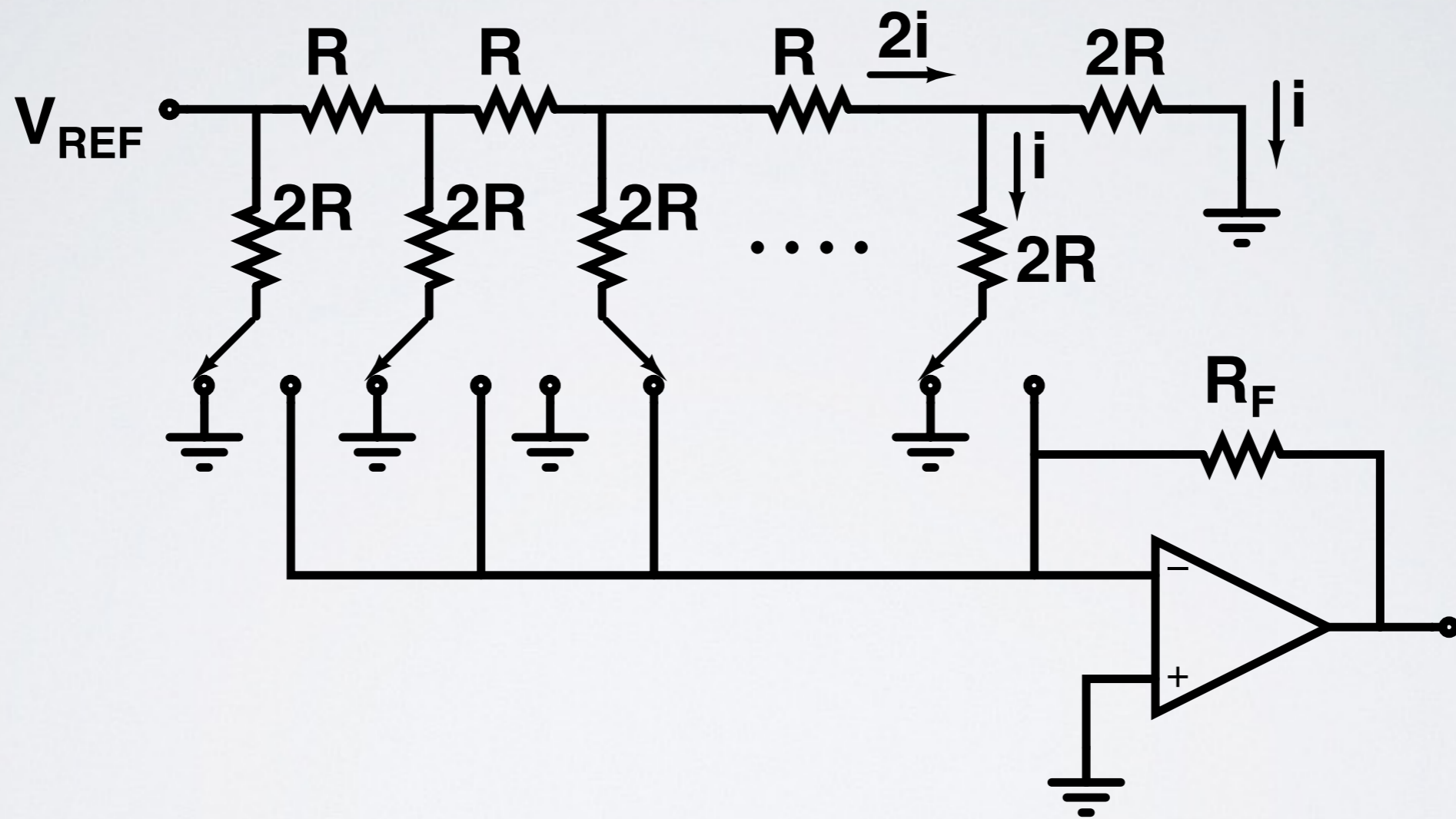


SIMPLE ADC

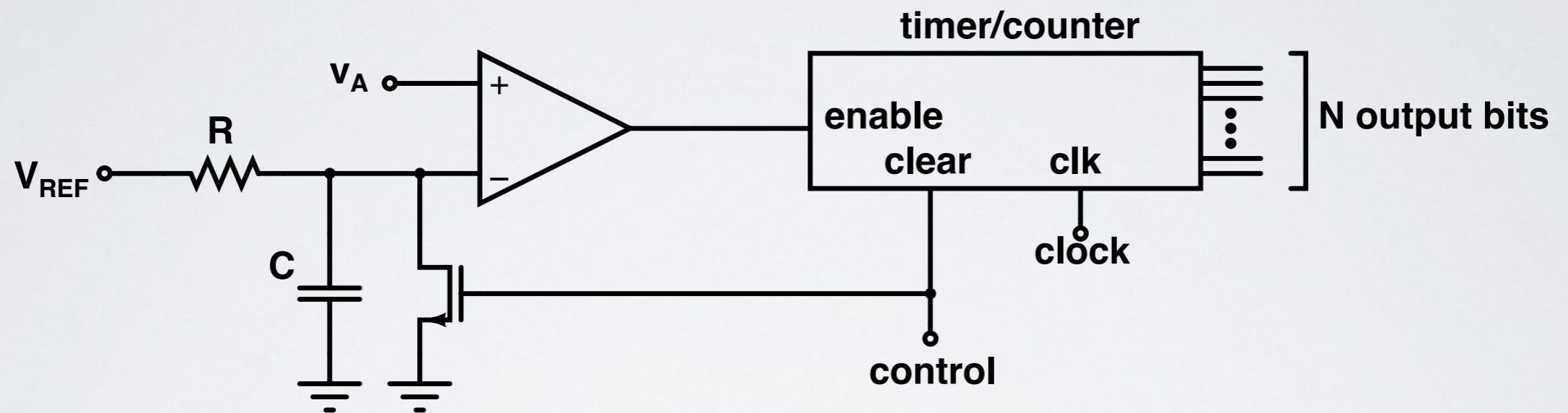

INTEGRATOR

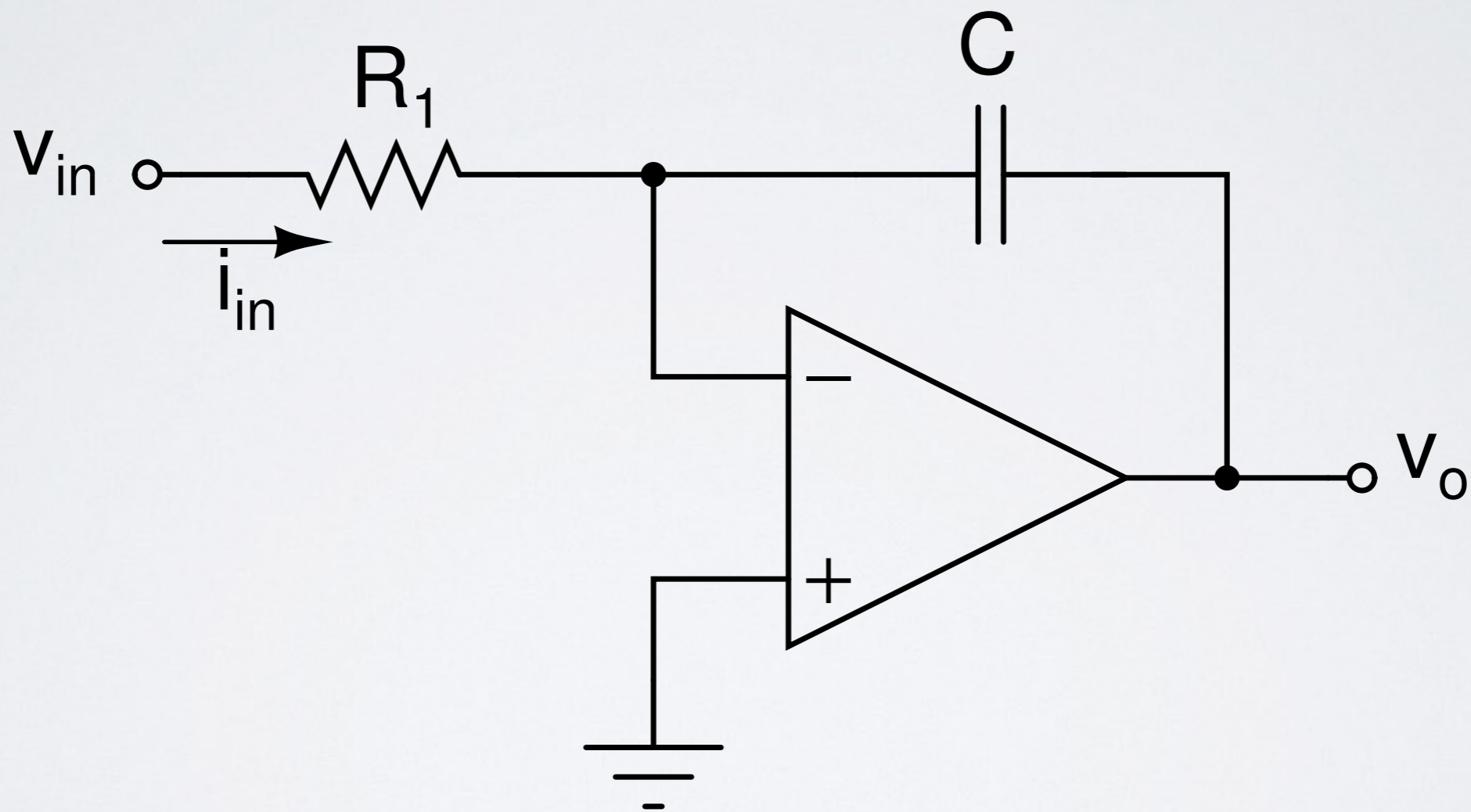


DOUBLE-SLOPE ADC

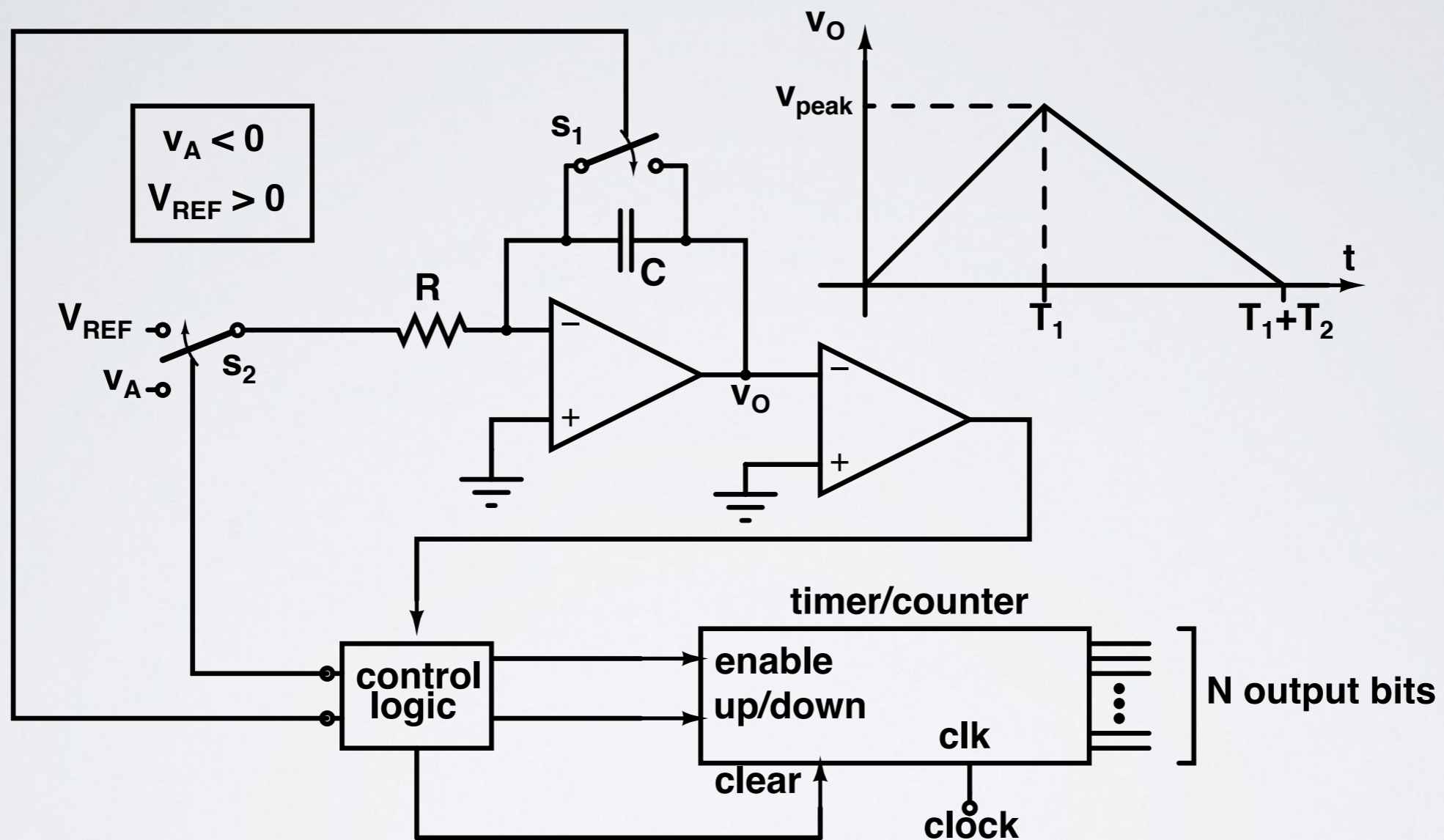

At $t=0$ capacitor C is discharged and s_2 is connected to v_A . At $t=T_1$ s_2 is switched to V_{REF}

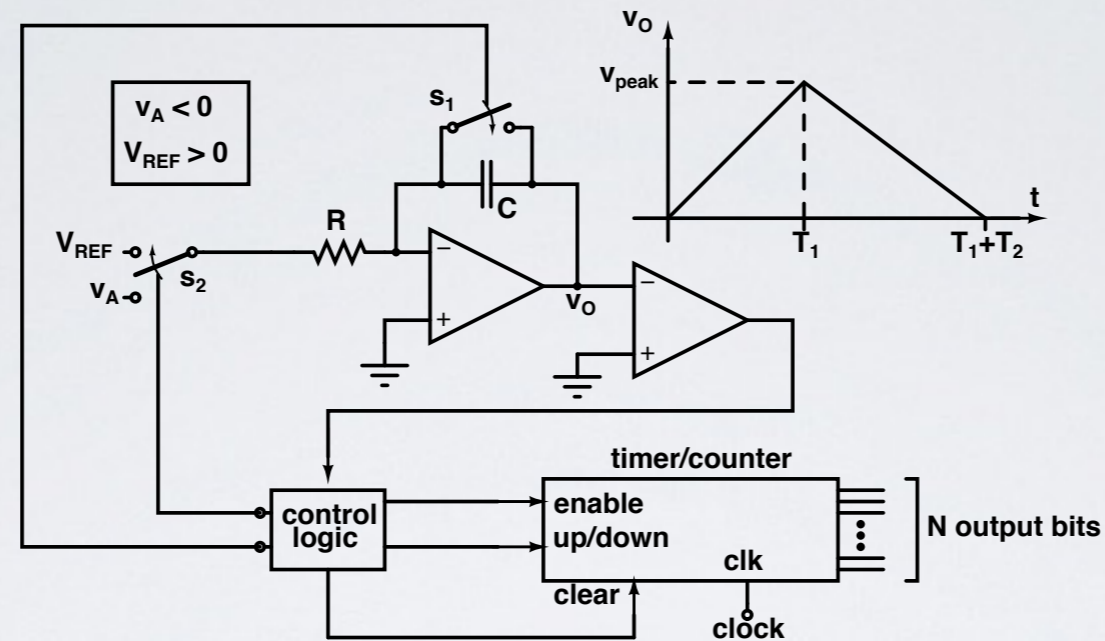1. A 12-bit dual-slope ADC of the type illustrated below



At $t=0$ capacitor C is discharged and s_2 is connected to v_A . At $t=T_1$ s_2 is switched to V_{REF} .

utilises a 1-MHz clock and has $V_{ref} = 10V$. Its analog input is in the range 0 to $-10V$. The fixed interval T_1 is the time taken for the counter to accumulate a count 2^N .

- (10 points) What is the time required to convert an input voltage equal to the full-scale value?
- (10 points) If the peak voltage reach at the output of the integrator is $10V$, what is the integrator time constant?
- (10 points) If through ageing, R increases by 2% and C decreases by 1%, what does V_{peak} become?

67

10

$$T_c = \frac{1}{f_{clk}} = 1 \mu s$$

$$T_1 = 2^{12} T_c = \underline{\underline{4.096 \text{ ms}}}$$

$$T = T_1 + T_2 = T_1 \left(1 + \frac{V_A}{V_{ref}} \right)$$

$$\Rightarrow 2 T_1 = \underline{\underline{8.19 \text{ ms}}}$$

$$V_{peak} = 10 = \frac{V_A}{\tau} T_1$$


$$\Rightarrow \tau = \frac{V_A}{V_{peak}} T_1 = \underline{\underline{4.096 \text{ ms}}}$$

$\Delta \tau = -1\%$ and causes a -1% change in V_{peak}

$$\Rightarrow V_{peak} = \underline{\underline{9.9 \text{ V}}}$$

No . Final count does not depend on τ

1. The following diagram

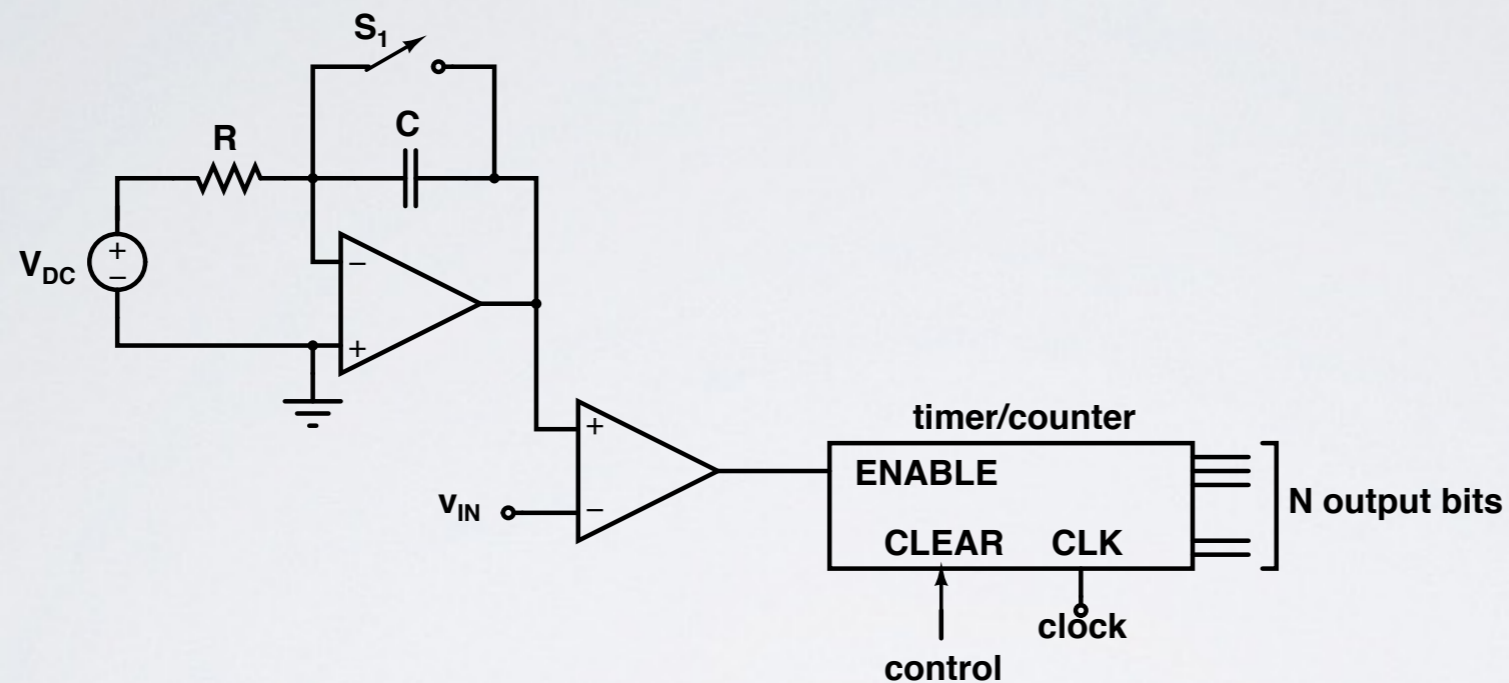

sketches an ADC. Prior to $t = 0$, capacitor C is discharged and the counter is erased by the control signal. At $t = 0$, s_1 opens and the counter is allowed to count. The analog input voltage, v_{IN} , is in the range of $0V$ to $5V$. If $V_{DC} = -10V$,

- (20 points) Find R and C so that the maximum conversion time equals $0.1ms$.
- (10 points) If a 10 MHz clock ($1\text{ MHz} = 10^6\text{ Hz}$) is used, what is the number of bits of resolution?

a) (20 points) Find R and C so that the maximum conversion time equals $0.1ms$.

ANSWER: The capacitor charges with a constant current $i = V_{DC}/R$, so for the opamp,

$$\frac{dv_{O1}}{dt} = \frac{10V}{RC}$$

A conversion will be done when $v_{O1} = v_{IN}$, so when $v_{IN} = 5V$,


$$\frac{5V}{0.1ms} = \frac{10V}{RC} \Rightarrow RC = 0.2ms$$

Any appropriate values will work. For example, select $R = 10k\Omega$ and $C = 20nF$.

b) (10 points) If a 10 MHz clock (1 MHz = 1024 kHz) is used, what is the number of bits of resolution?

ANSWER: There will be $10.24 \times 10^6 \times 0.1 \times 10^{-3} = 1.024 \times 10^7 \times 10^{-4} = 1024$ clock pulses per conversion, for a resolution of 10 bits ($2^{10} = 1024$).

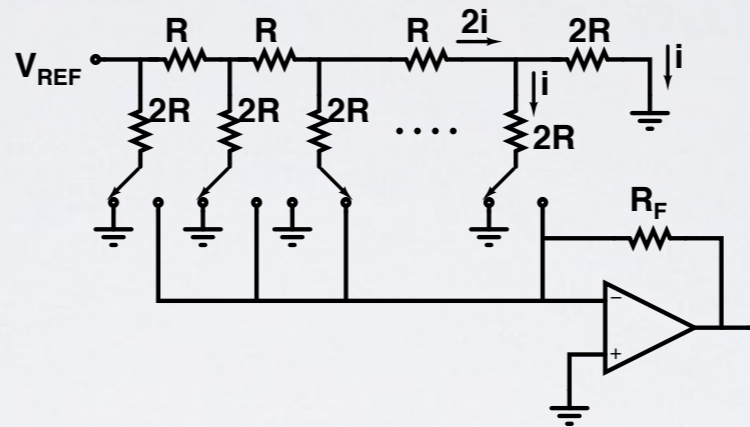
3. The following sketch shows a $R - 2R$ digital-to-analog converter (DAC).



If the circuit uses 10 bits, $R = 1k\Omega$ and $V_{REF} = -5V$,

- (a) (20 points) find the value of R_F that should be used to have an output voltage range from $0V$ to $10V$.
- (b) (20 points) for the value of R_F found in part (a), what is the output voltage for a binary input equal to 0100011101 ?

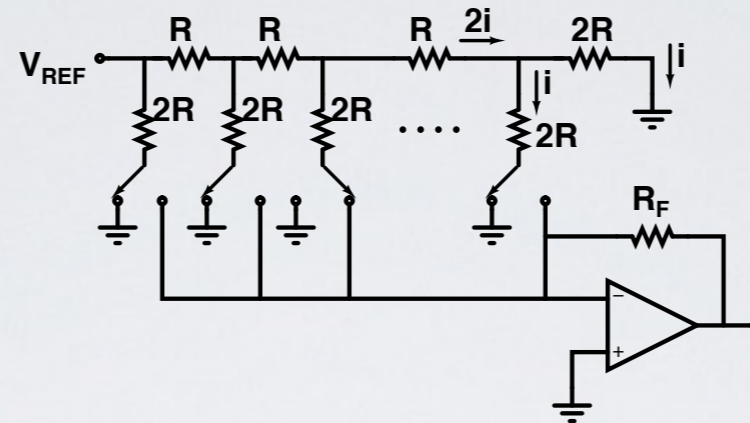3. The following sketch shows a $R - 2R$ digital-to-analog converter (DAC).



If the circuit uses 10 bits, $R = 1k\Omega$ and $V_{REF} = -5V$,

- (a) (20 points) find the value of R_F (to within 0.1%) that should be used to have an output voltage range from $0V$ to $10V$.

ANSWER: The maximum current, which flows through R_F when all input bits are logic-1, can be expressed as

$$i_{max} = \frac{5V}{1k\Omega} \left(\frac{2^{10} - 1}{2^{10}} \right) = 4995.12\mu A$$

so

$$10V = 4995.12\mu A \times R_F \Rightarrow R_F = 10V/4995.12\mu A = 2002\Omega$$

- (b) (20 points) for the value of R_F found in part (a), what is the output voltage for a binary input equal to 0100011101?

ANSWER:

$$v_{out} = 2002\Omega \times 2.5mA (2^{-10} + 2^{-8} + 2^{-7} + 2^{-6} + 2^{-2}) = 1.393V$$