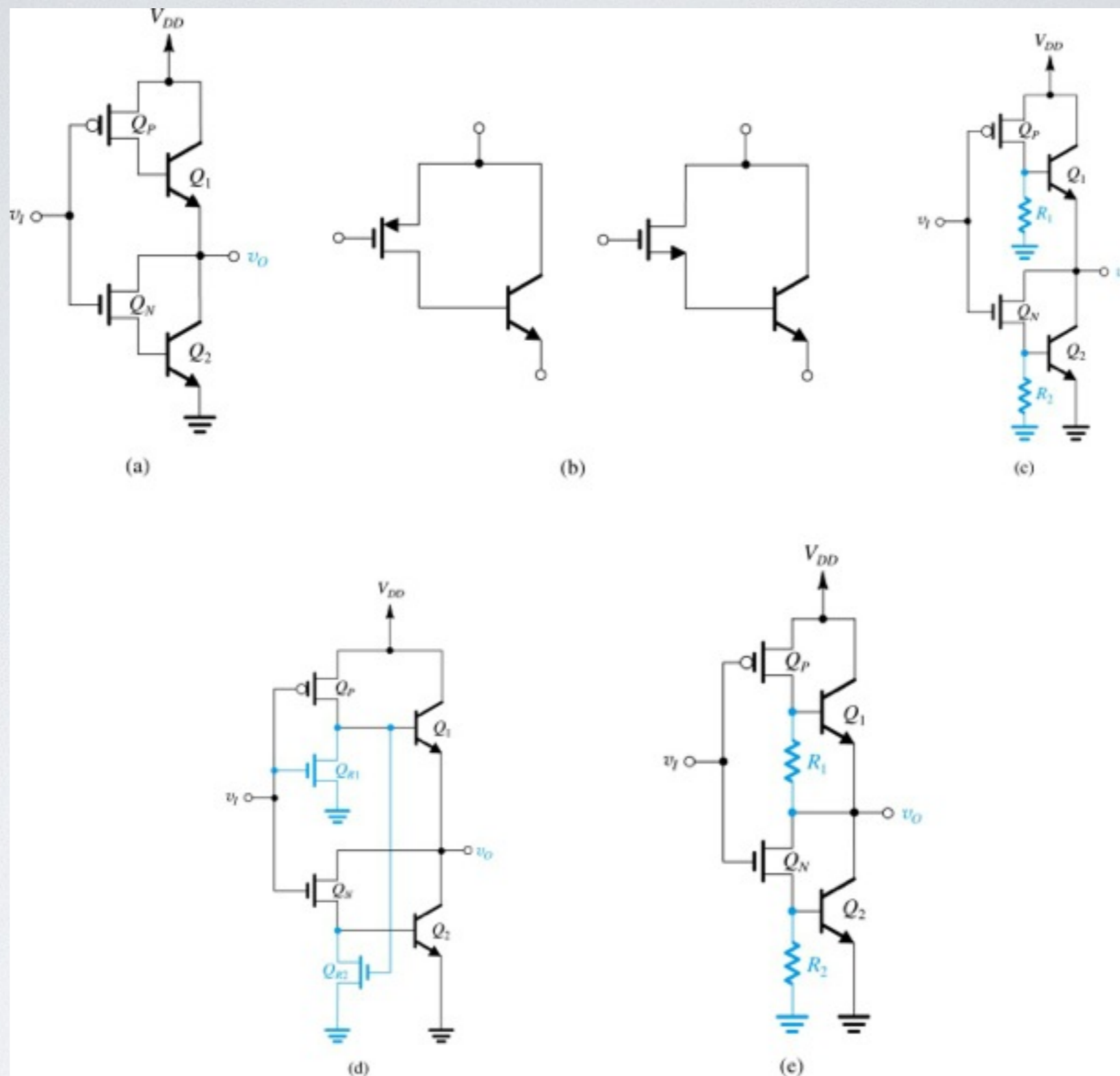



# BICMOS

INEL 4207 - M.Toledo





**Figure 15.37** Development of the BiCMOS inverter circuit. **(a)** The basic concept is to use an additional bipolar transistor to increase the output current drive of each of  $Q_N$  and  $Q_P$  of the CMOS inverter. **(b)** The circuit in **(a)** can be thought of as utilizing these composite devices. **(c)** To reduce the turn-off times of  $Q_1$  and  $Q_2$ , “bleeder resistors”  $R_1$  and  $R_2$  are added. **(d)** Implementation of the circuit in **(c)** using NMOS transistors to realize the resistors. **(e)** An improved version of the circuit in **(c)** obtained by connecting the lower end of  $R_1$  to the output node.

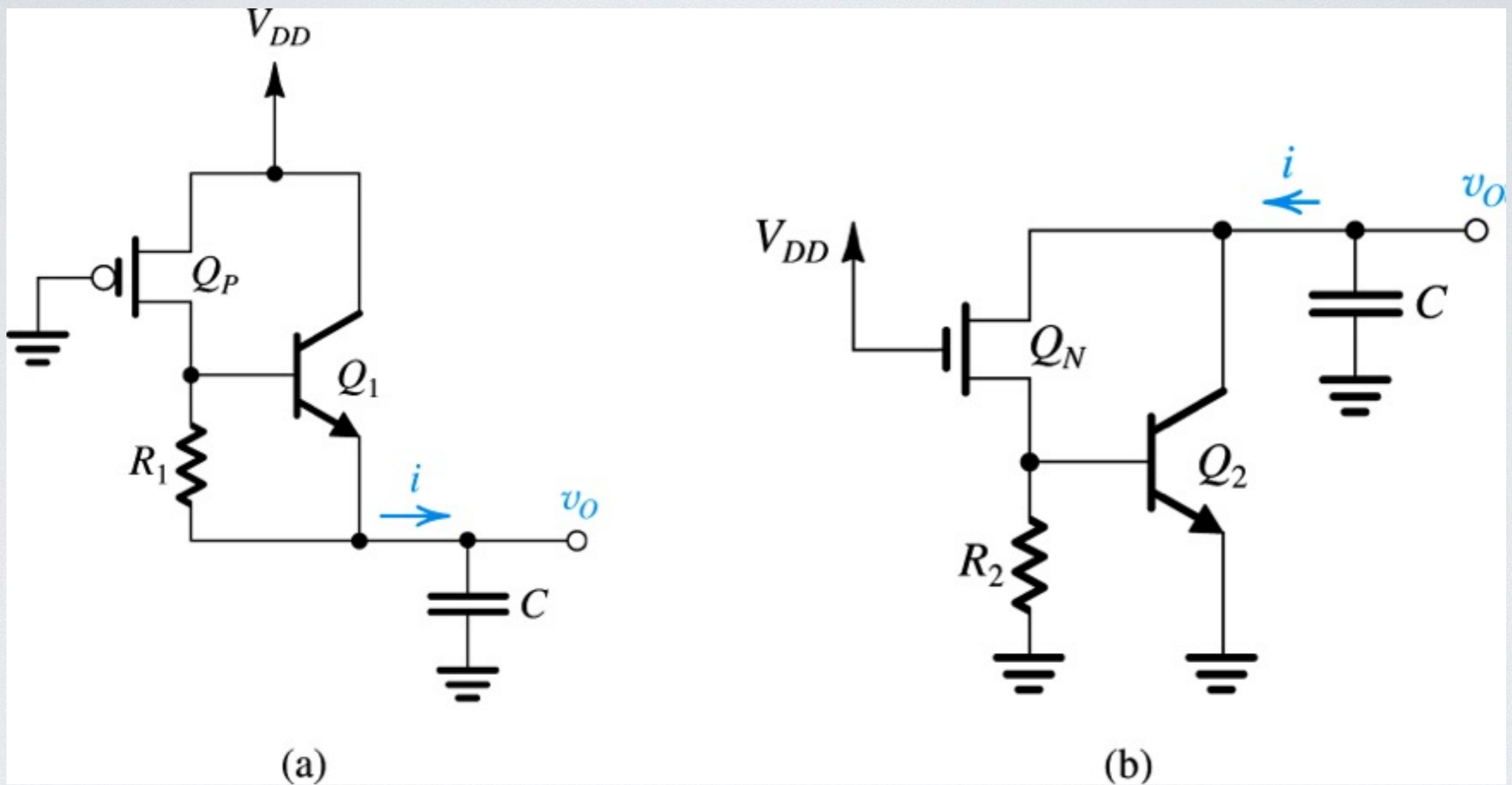

**Figure 15.38** Equivalent circuits for charging and discharging a load capacitance  $C$ . Note that  $C$  includes all the capacitances present at the output node.




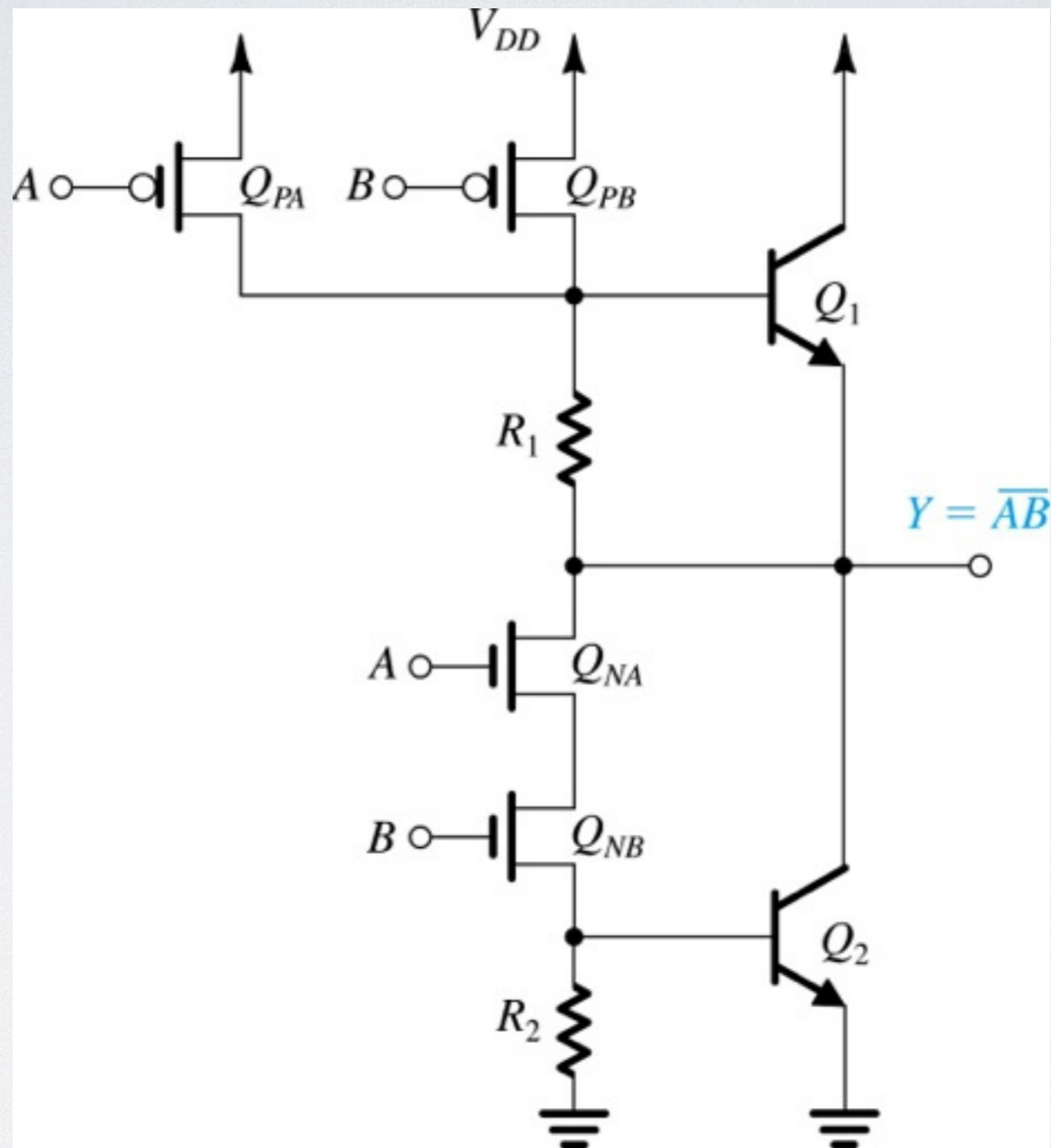



Figure 15.39 A BiCMOS two-input NAND gate.

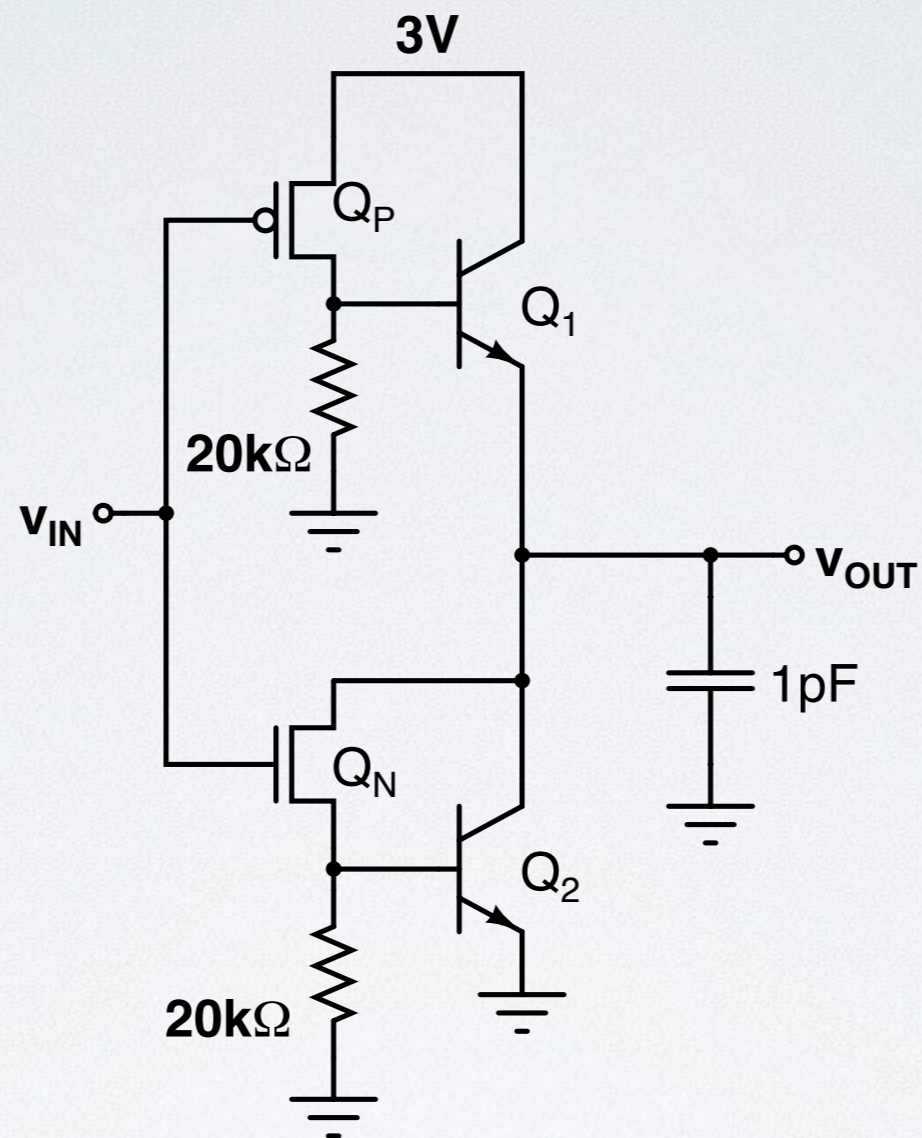



For the above BiCMOS circuit, estimate the time  $t_d$  that it takes to discharge  $C_L$  from its initial voltage  $v_{out,i}$  (the largest value of  $v_{out}$  that the circuit can reach) to  $v_{out,i}/2$ . Assume that  $v_{BE} = 0.7V$  and  $\beta = 20$  for the bipolar transistors,  $k_n = 300\mu A/V^2$  for  $Q_N$  and  $k_p = 100\mu A/V^2$  for  $Q_P$ . For both MOSFETs the threshold voltage is  $|V_{t0}| = 0.5V$  and  $\gamma = 0$ . Use  $v_{IN} = 3V$ .



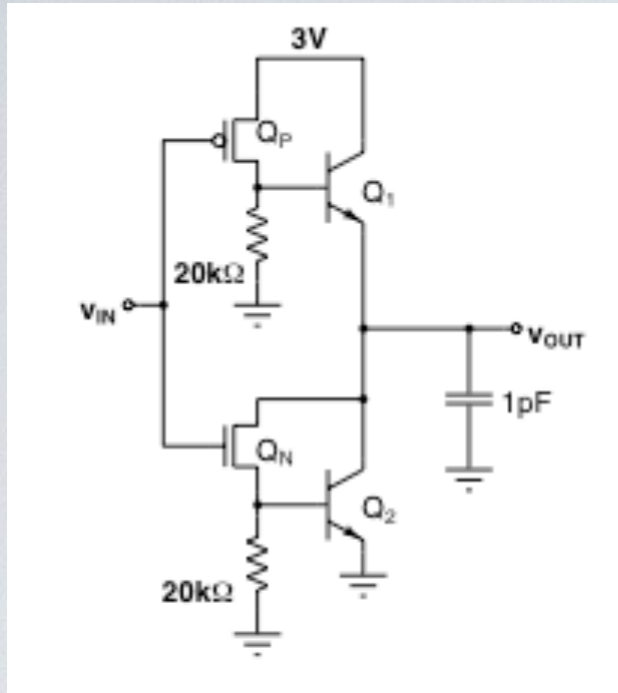

1. Find  $v_{out,i}$

$$i_{C1} = 0 \rightarrow i_{B1} = 0 \rightarrow i_{D,P} = i_{20k\Omega}$$

$$\frac{3V - v_{SD,P}}{20k\Omega} = (0.1mA/V^2) (2(3V - 0.5V)v_{DS,P} - v_{DS,P}^2)$$

$$\frac{3V - v_{SD,P}}{2} = 5v_{DS,P} - v_{DS,P}^2$$

$$v_{SD,P} = 5.2V, \boxed{0.29V} \Rightarrow \boxed{v_{OUT} \simeq 3V - 0.3V - 0.7 = 2V}$$

2. Find the initial capacitor current

The initial voltage across the capacitor is  $\boxed{v_{out,i} = 2.0V}$ . At point 1,  $v_{OUT} = 2.0V$  and

$$v_{DS,N} = 2.0V - 0.7V = 1.3V$$

$$v_{GS,N} - V_{t0} = 3V - 0.7V - 0.5V = 1.8V$$

$$i_{D1} = (0.3mA/V^2)[2(1.8V)1.3V - (1.3V)^2] = 0.897mA$$

$$i_1 = \beta(i_{D1} - 0.7V/20k\Omega) + i_{D1} = 20(0.897mA - 0.035mA) + 0.897 = \boxed{18.147mA}$$



3. Find the capacitor current when  $v_{out} = v_{out,i} / 2$

At point 2,  $v_{out} = 2.0V/2 = 1.0V$  and

$$\begin{aligned}v_{DS,N} &= 1.0V - 0.7V = 0.3V \\v_{GS,N} - V_{t0} &= 3V - 0.7V - 0.5V = 1.8V \\i_{D2} &= (0.3mA/V^2)[2(1.8V)0.3V - (0.3V)^2] \simeq 0.3mA \\i_2 &= \beta(i_{D2} - 0.7V/20k\Omega) + i_{D2} \\&= 20(0.3mA - 0.035mA) + 0.3mA = \boxed{5.6mA}\end{aligned}$$

4. Find  $i_{ave}$  and  $t_d$

$$\begin{aligned}i_{av} &= \frac{18.15mA + 5.6mA}{2} \simeq 11.9mA \\t_d &= 1pF \frac{1.0V}{11.9mA} = \boxed{84.2ps}\end{aligned}$$



The threshold voltage of the BiCMOS inverter of Fig. 15.37(e) is the value of  $v_I$  at which both  $Q_N$  and  $Q_P$  are conducting equal currents and operating in the saturation region. At this value of  $v_I$ ,  $Q_2$  will be on, causing the voltage at the source of  $Q_N$  to be approximately 0.7 V. It is required to design the circuit so that the threshold voltage is equal to  $V_{DD}/2$ . For  $V_{DD} = 5$  V,  $|V_t| = 0.6$  V, and assuming equal channel lengths for  $Q_N$  and  $Q_P$  and that  $\mu_n \approx 2.5 \mu_p$ , find the required ratio of widths,  $W_p/W_n$ .



The threshold voltage of the BiCMOS inverter of Fig. 15.37(e) is the value of  $v_I$  at which both  $Q_N$  and  $Q_P$  are conducting equal currents and operating in the saturation region. At this value of  $v_I$ ,  $Q_2$  will be on, causing the voltage at the source of  $Q_N$  to be approximately 0.7 V. It is required to design the circuit so that the threshold voltage is equal to  $V_{DD}/2$ . For  $V_{DD} = 5$  V,  $|V_t| = 0.6$  V, and assuming equal channel lengths for  $Q_N$  and  $Q_P$  and that  $\mu_n \approx 2.5 \mu_p$ , find the required ratio of widths,  $W_p/W_n$ .

**Ans.** 1

$$v_I = 2.5V$$

$$v_{SG,P} - |V_t| = 5V - 2.5V - 0.6V = 1.9V$$

$$v_{GS,N} - V_t = 2.5V - 0.7V - 0.6V = 1.2V$$

$$\frac{2.5\mu_p C_{ox}}{2} \frac{W_n}{L} (1.2V)^2 = \frac{\mu_p C_{ox}}{2} \frac{W_p}{L} (1.9V)^2$$

$$\frac{W_p}{W_n} = \boxed{0.997}$$