

RS FLIP FLOP

BASIC OPERATION

INEL 4207 Digital Electronics - M.Toledo


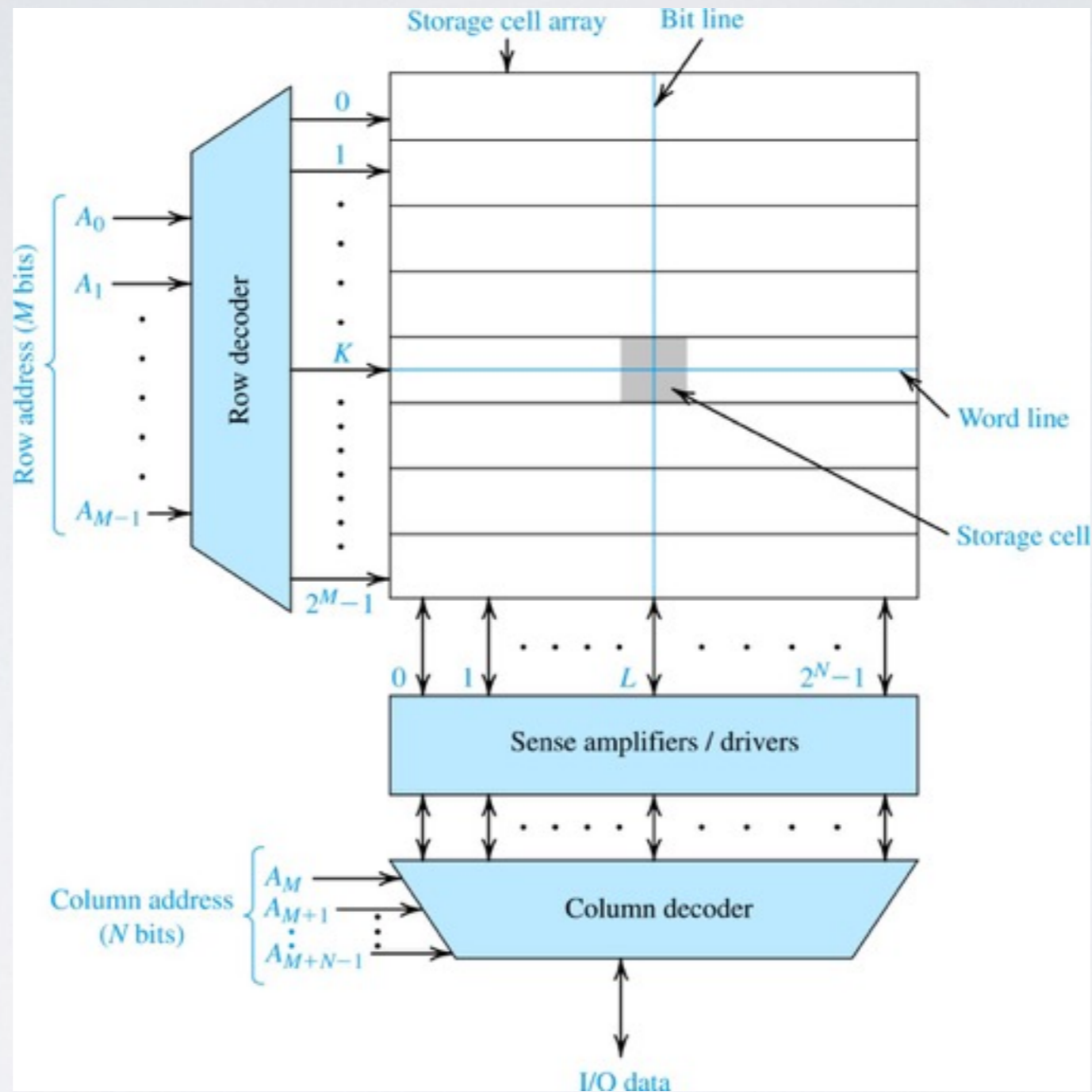


Figure 16.11 A 2^{M+N} -bit memory chip organized as an array of 2^M rows \times 2^N columns.

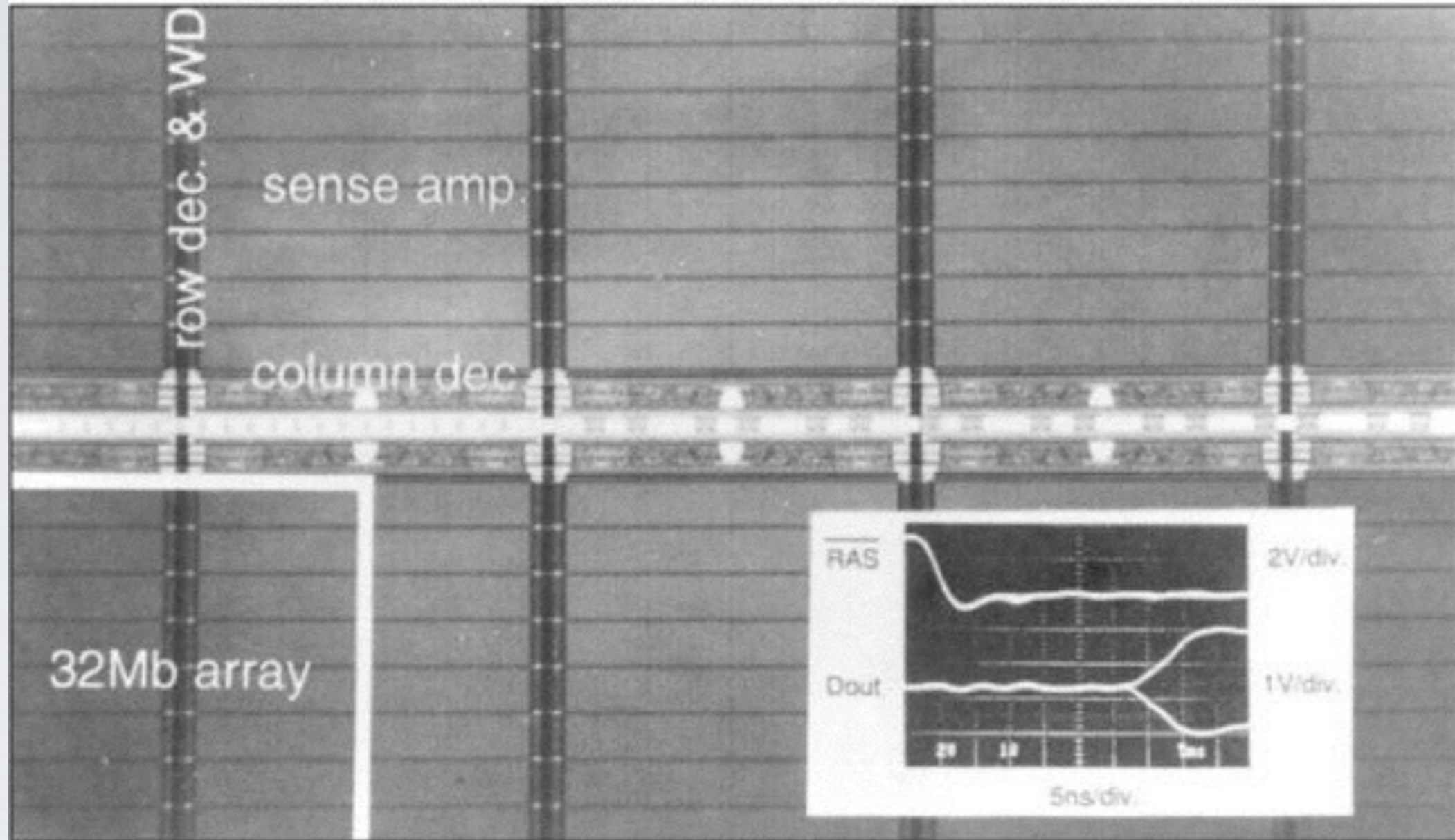

(a)



 


Figure 16.1 (a) Basic latch. (b) The latch with the feedback loop opened. (c) Determining the operating point(s) of the latch.

 

 

R	S	Q_{n+1}
0	0	Q_n
0	1	1
1	0	0
1	1	Not used

(b)

Figure 16.3 (a) The set/reset (SR) flip-flop and (b) its truth table.

 
 
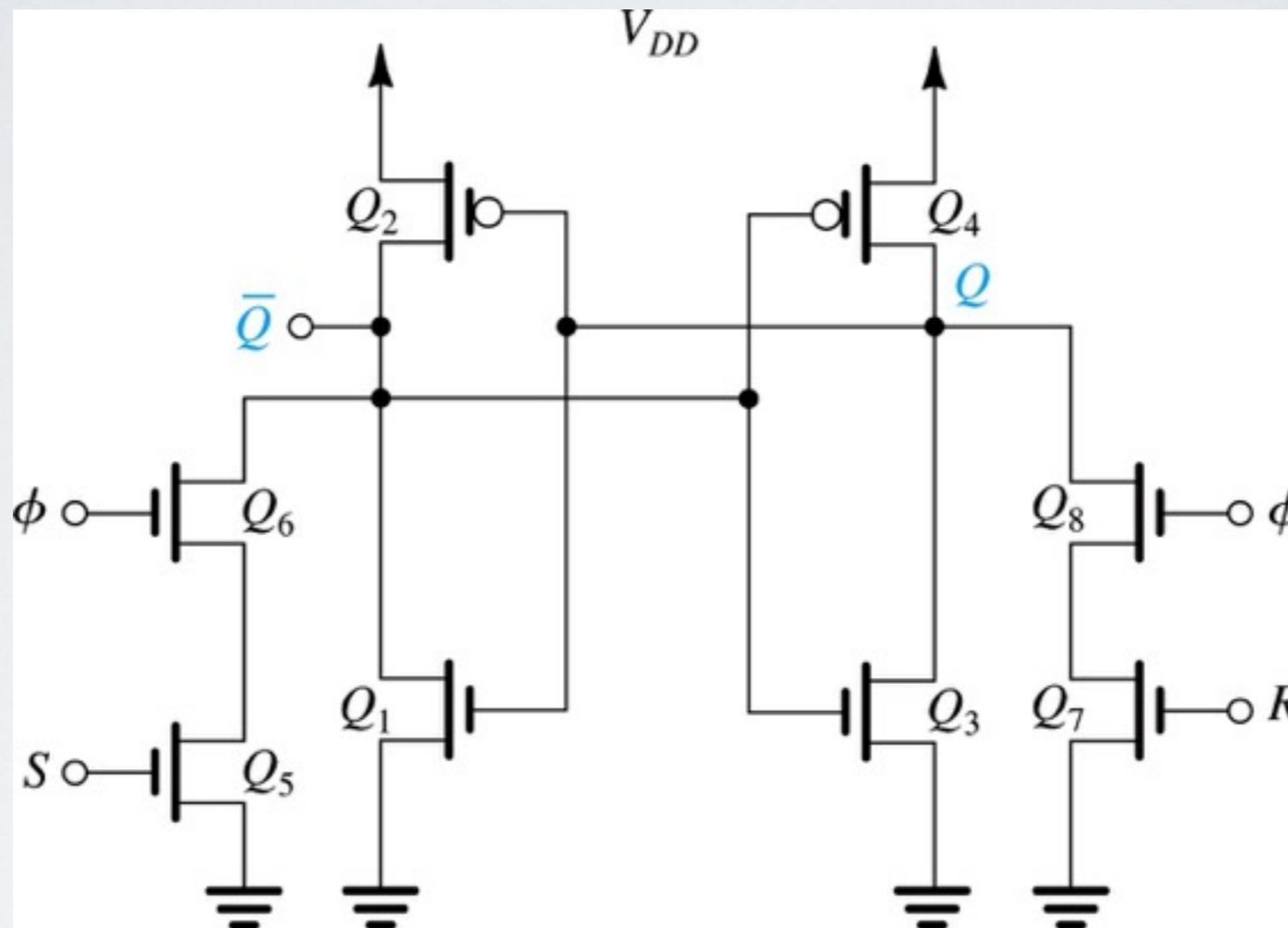


Fig. 16.4 CMOS implementation of a clocked SR flip-flop. The clock signal is denoted by ϕ .

Assume $Q=0, Q'=1$

 
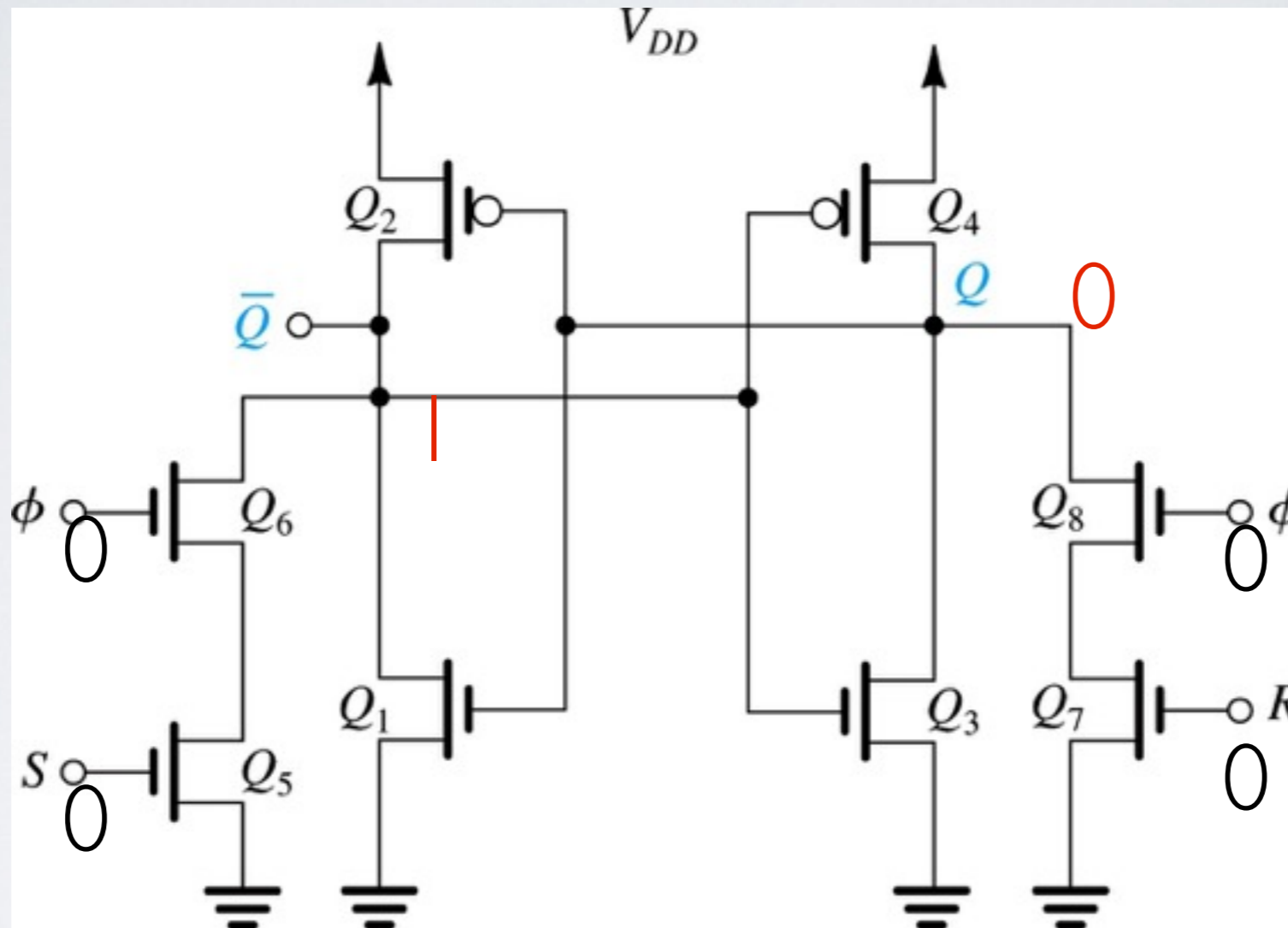


Fig. 16.4 CMOS implementation of a clocked SR flip-flop. The clock signal is denoted by ϕ .

Assume $Q=0, \bar{Q}' = 1$
 Clock and S go high

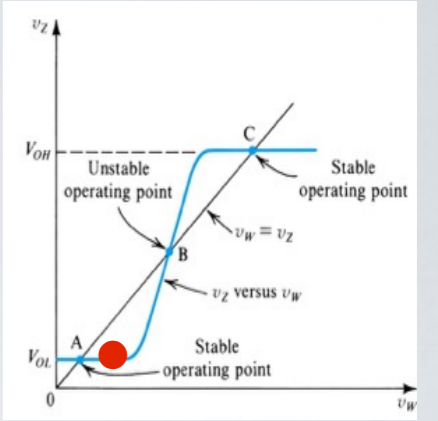
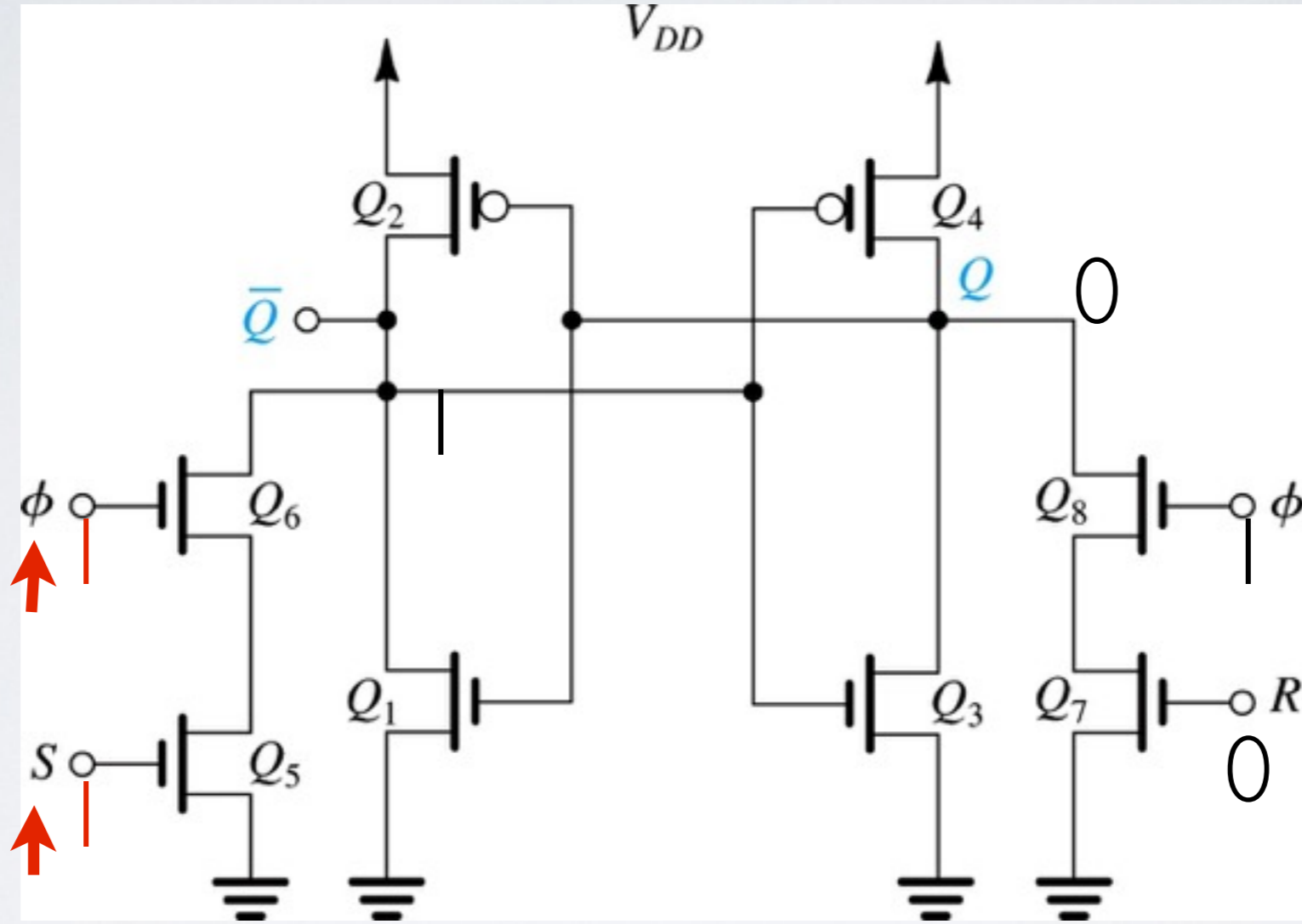


Fig. 16.4 CMOS implementation of a clocked SR flip-flop. The clock signal is denoted by ϕ .

Assume $Q=0$, $Q' = 1$
 Clock and S go high
 Q' is pulled down

 
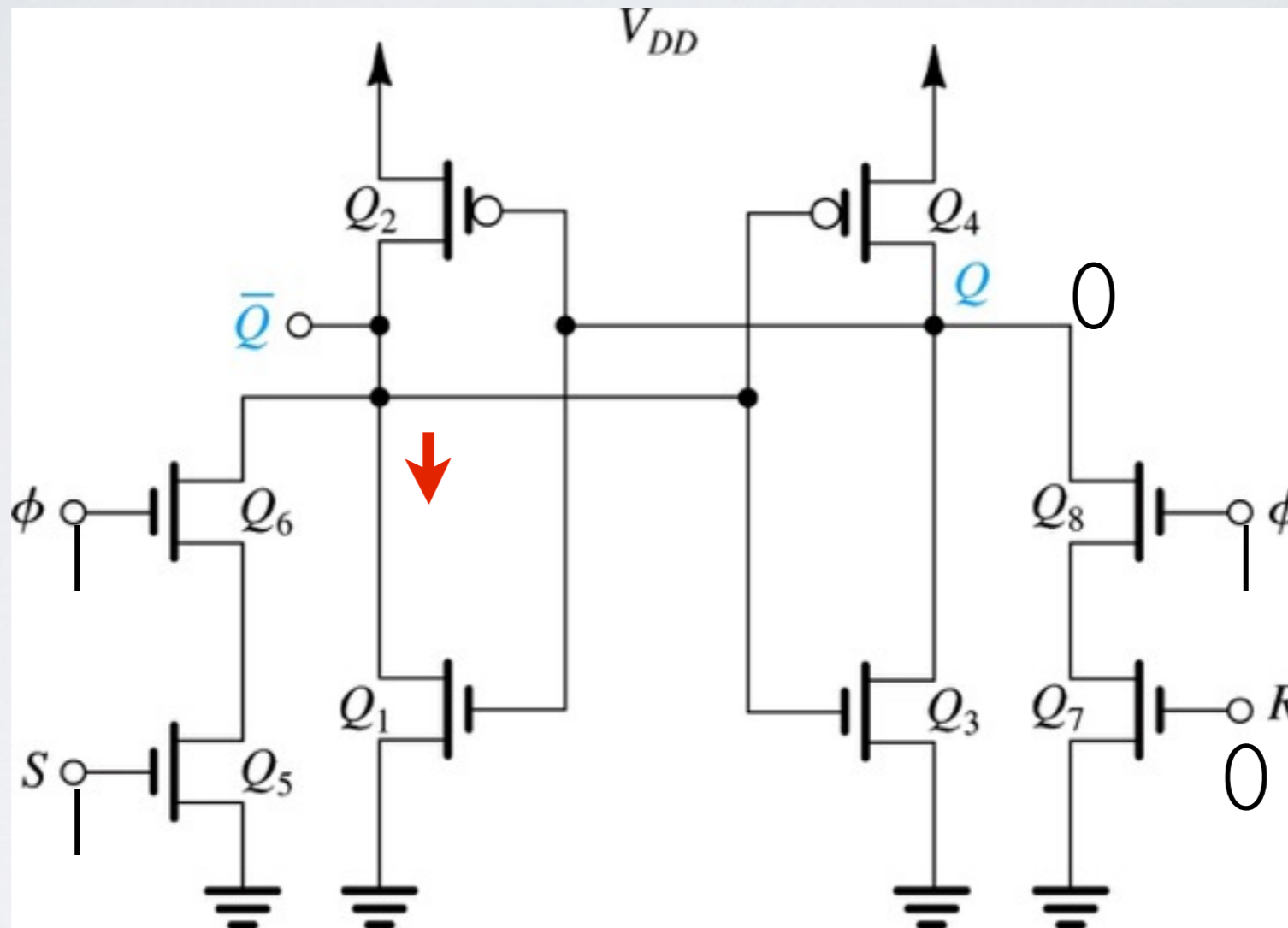


Fig. 16.4 CMOS implementation of a clocked SR flip-flop. The clock signal is denoted by ϕ .

Assume $Q=0$, $Q' = 1$
 Clock and S go high
 Q' is pulled down
 voltage at Q increases

 
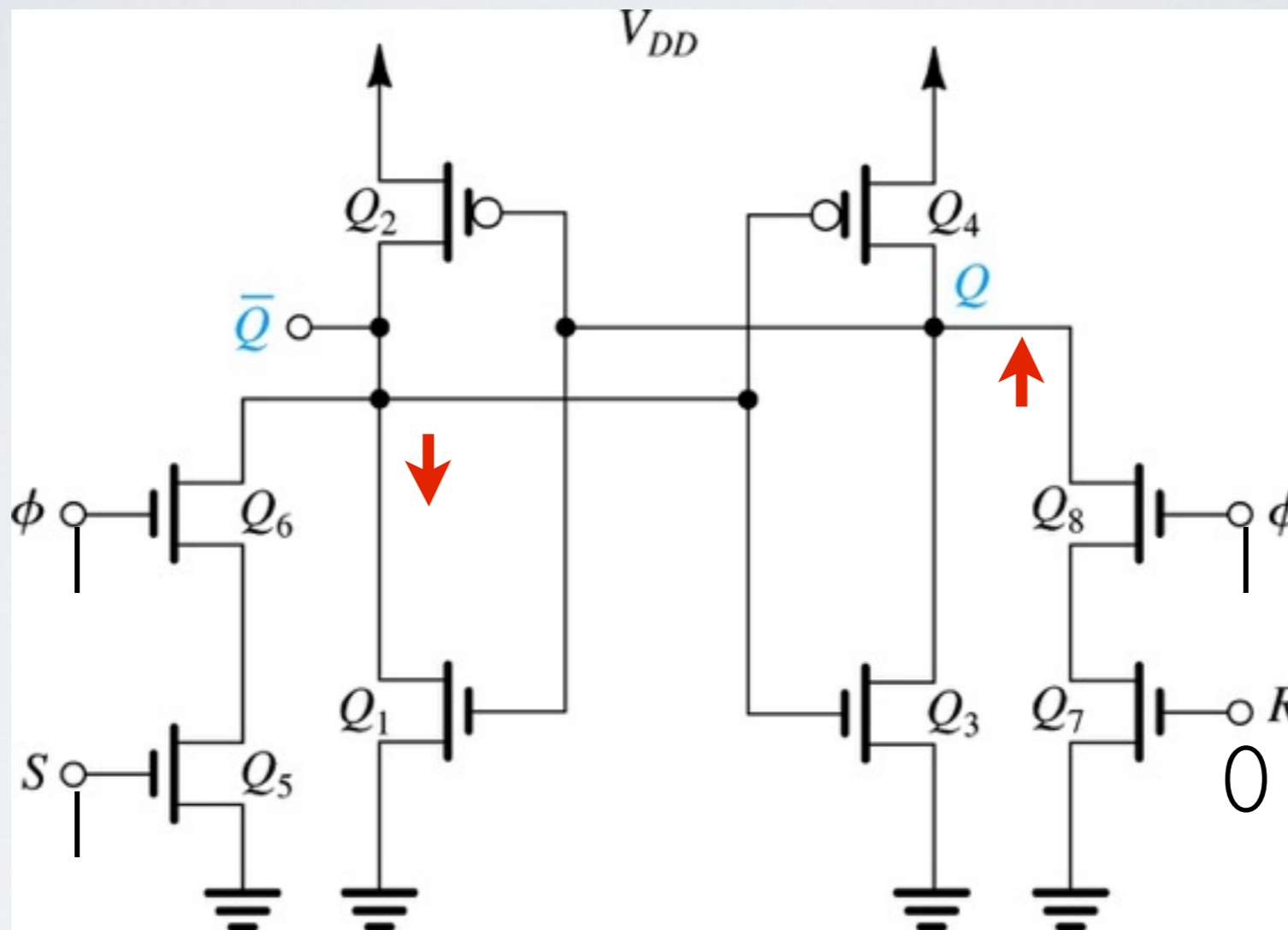


Fig. 16.4 CMOS implementation of a clocked SR flip-flop. The clock signal is denoted by ϕ .

Assume $Q=0$, $Q' = 1$
 Clock and S go high
 Q' is pulled down
 voltage at Q increases
 Q' reaches critical point

 
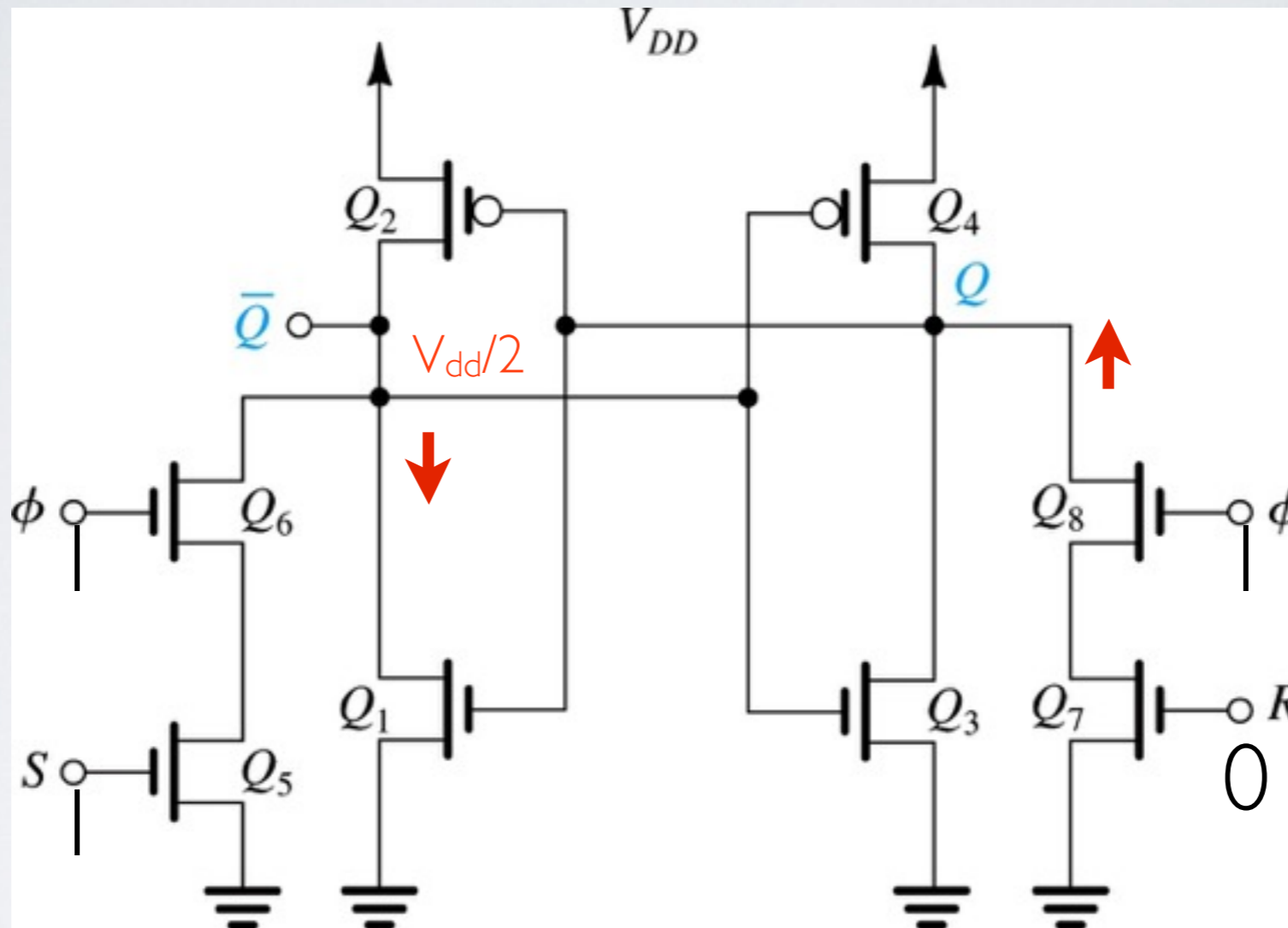


Fig. 16.4 CMOS implementation of a clocked SR flip-flop. The clock signal is denoted by ϕ .

Assume $Q=0$, $Q' = 1$
 Clock and S go high
 Q' is pulled down
 voltage at Q increases
 Q' reaches critical point
 Q reaches critical point

 
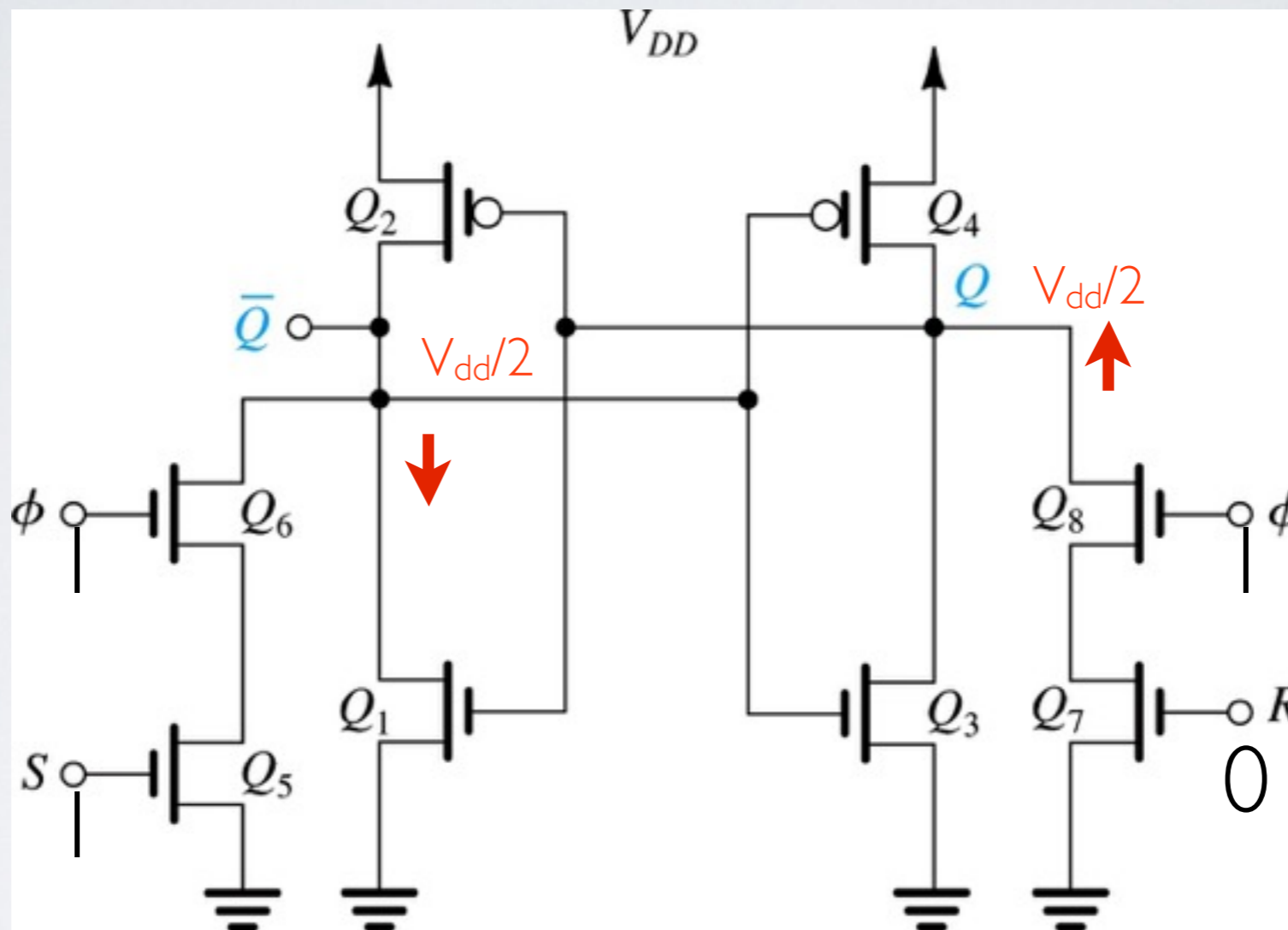


Fig. 16.4 CMOS implementation of a clocked SR flip-flop. The clock signal is denoted by ϕ .

Assume $Q=0, Q' = 1$
Clock and S go high
 Q' is pulled down
voltage at Q increases
 Q' reaches critical point
Q reaches critical point
S is be removed

 
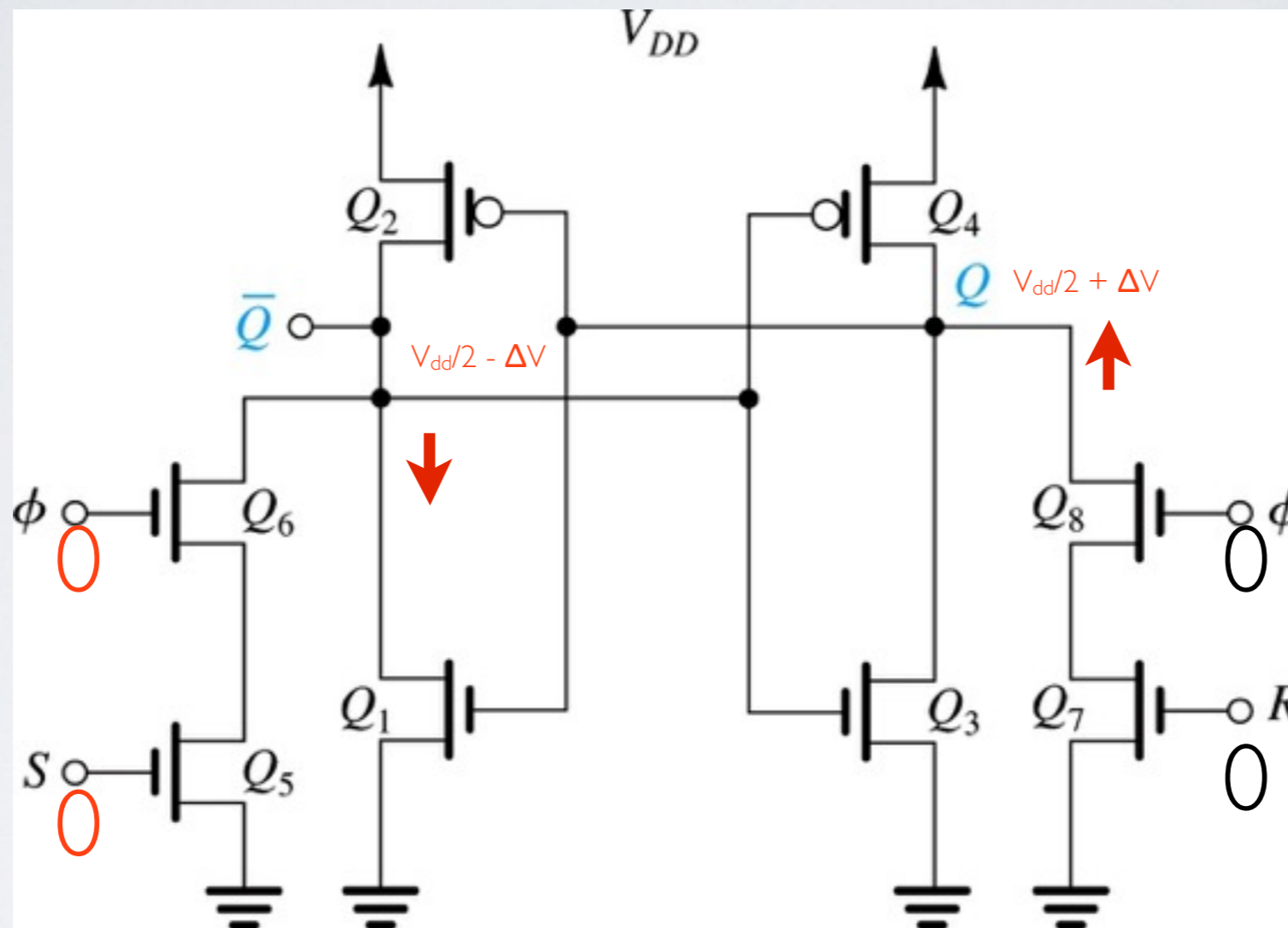


Fig. 16.4 CMOS implementation of a clocked SR flip-flop. The clock signal is denoted by ϕ .

Assume $Q=0$, $Q' = 1$
 Clock and S go high
 Q' is pulled down
 voltage at Q increases
 Q' reaches critical point
 Q reaches critical point
 S is be removed

Regenerative action restore levels

 
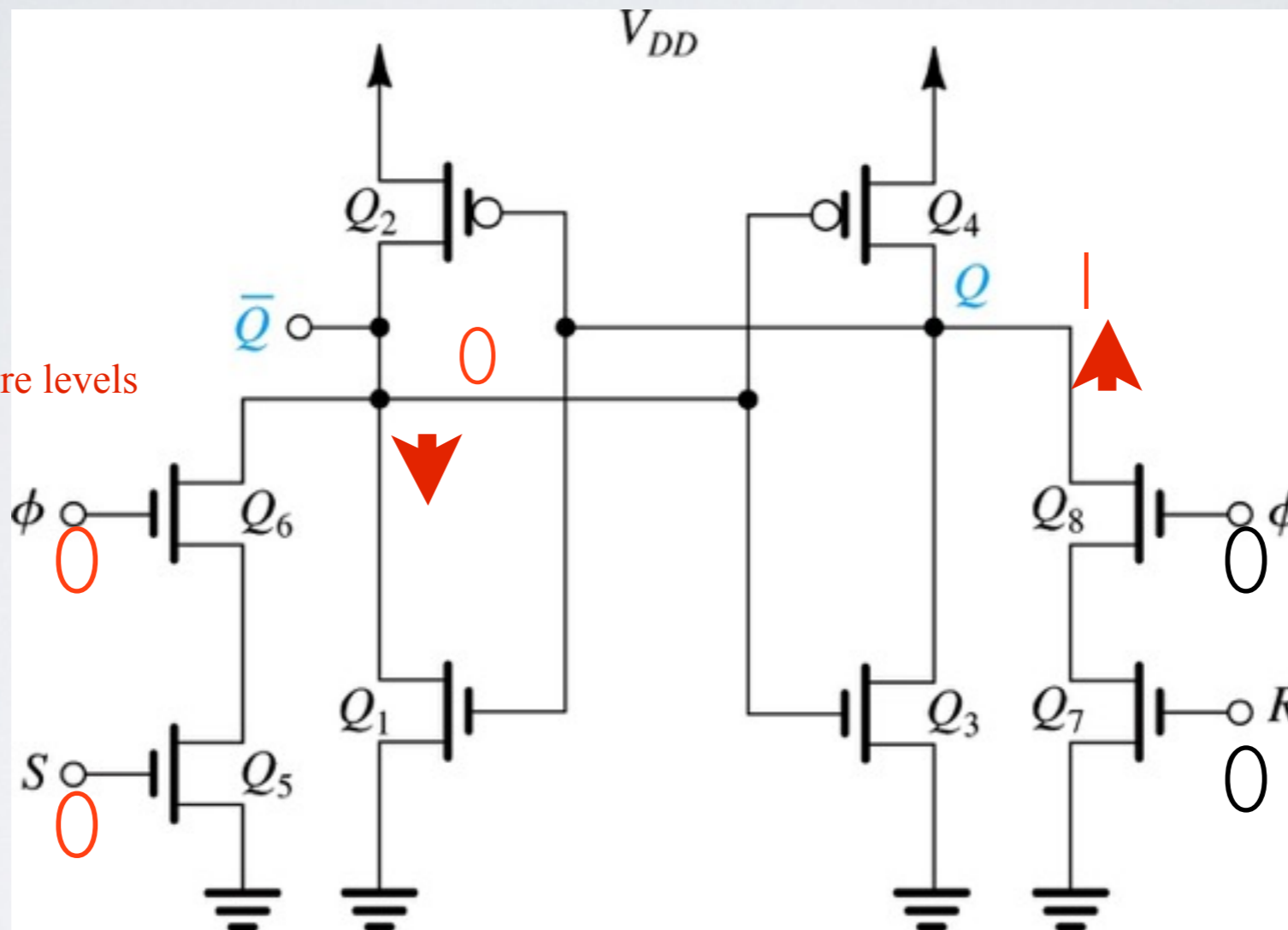


Fig. 16.4 CMOS implementation of a clocked SR flip-flop. The clock signal is denoted by ϕ .

Assume $Q=0, Q' = 1$
 Clock and S go high
 Q' is pulled down
 voltage at Q increases
 Q' reaches critical point
 Q reaches critical point
 S is removed
 Regenerative action restore levels
FF is SET


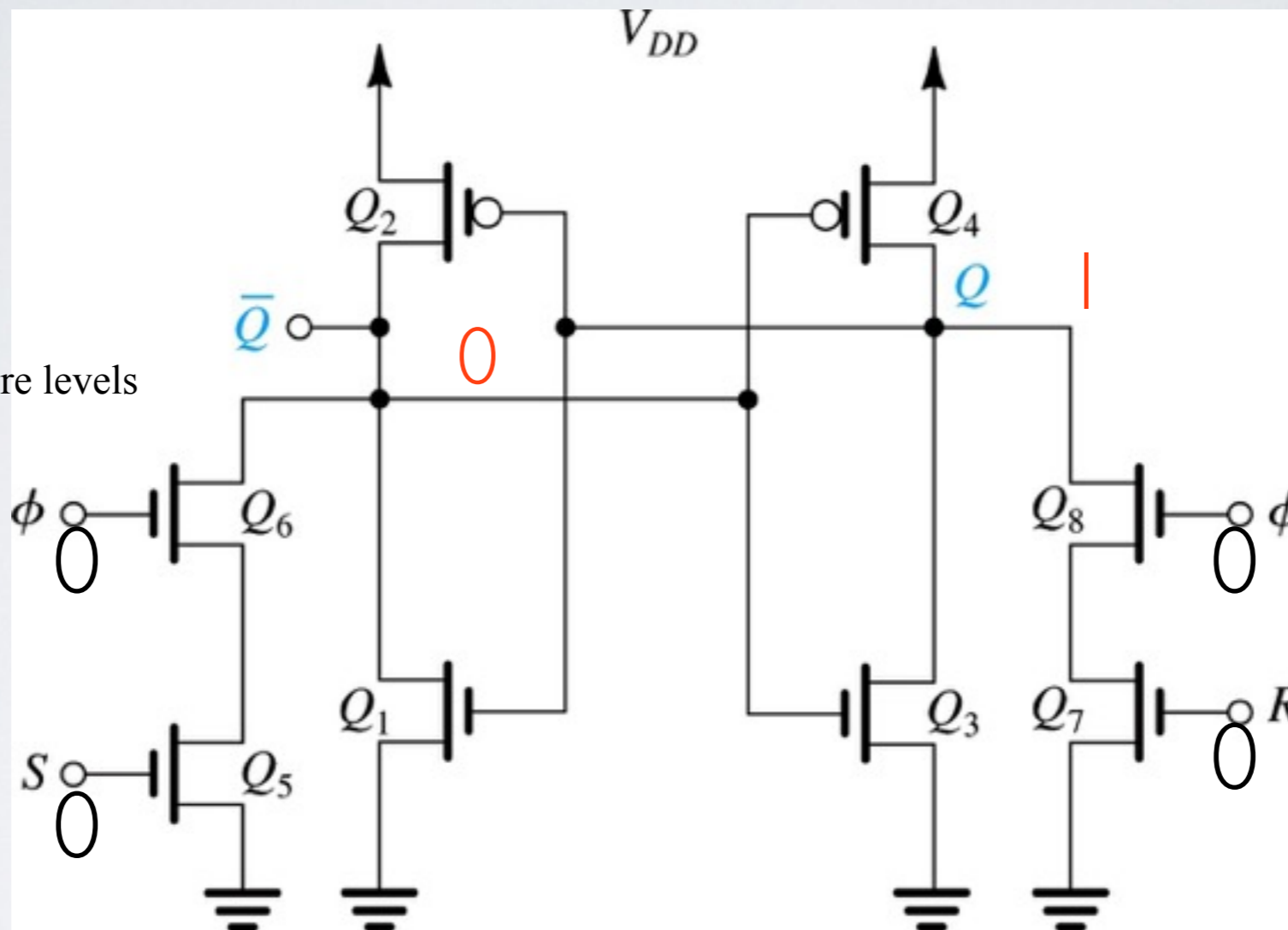


Fig. 16.4 CMOS implementation of a clocked SR flip-flop. The clock signal is denoted by ϕ .

EXAMPLE

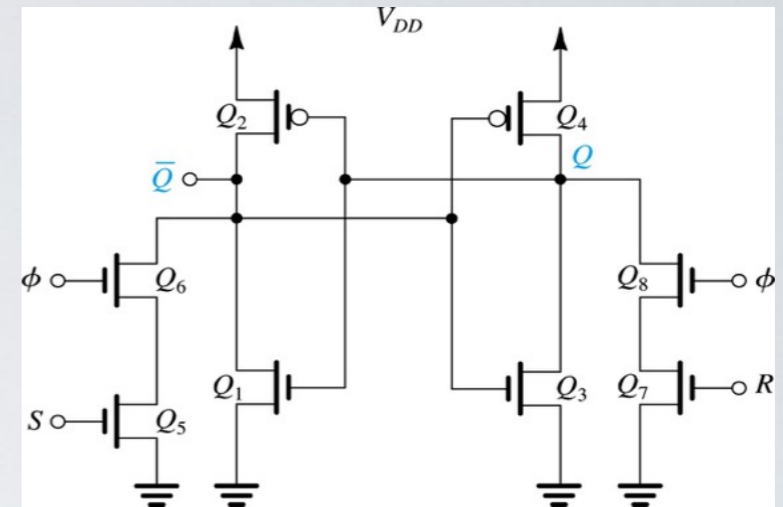

The CMOS SR flip-flop in Fig. 16.4 is fabricated in a 0.18- μm process for which $\mu_n C_{ox} = 4 \mu_p C_{ox} = 300 \mu\text{A}/\text{V}^2$, $V_{tn} = |V_{tp}| = 0.5\text{V}$, and $V_{DD} = 1.8\text{V}$. The inverters have $(W/L)_n = 0.27\mu\text{m}/0.18\mu\text{m}$ and $(W/L)_p = 4 (W/L)_n$. The four NMOS transistors in the set-reset circuit have equal W/L ratios.

(a) Determine the minimum value required for this ratio to ensure that the flip-flop will switch.

(b) Also, determine the minimum width the set pulse must have for the case in which the W/L ratio of each of the four transistors in the set-reset circuit is selected at twice the minimum value found in (a). Assume that the total capacitance at each of the Q and \bar{Q} nodes and ground is **20fF**.

EXAMPLE

$\mu_n C_{ox} = 4 \mu_p C_{ox} = 300 \mu A/V^2$, $V_{tn} = |V_{tp}| = 0.5V$, and $V_{DD} = 1.8V$. The inverters have $(W/L)_n = 0.27\mu m/0.18\mu m$ and $(W/L)_p = 4 (W/L)_n$. (a) Determine the minimum value of $(W/L)_{5,6,7,8}$ required to ensure that the flip-flop will switch.


Solution:

- Assume $Q = 0$ and that you want to *Set* the flip flop
- Replace Q_5 and Q_6 with an equivalent transistor Q_{eq} for which $(W/L)_{eq} = (W/L)_{5,6}/2$
- Assume that v_Q does not change, i.e. remains fixed at $0V$
- Observe that Q_2 operates in triode mode when $V_{\bar{Q}} = V_{DD}/2 = 0.9V$ because $v_{SD,2} = 0.9V < v_{SG,2} - V_{tp} = 1.8V - 0.5V = 1.3V$. Likewise, Q_{eq} operates in triode mode.
- Equate $i_{D,2}$ and $i_{D,eq}$

$$\frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_{eq} [2(1.3V)0.9V - (0.9V)^2] = \frac{1}{4} \frac{\mu_n C_{ox}}{2} \left(\frac{0.27\mu m}{0.18\mu m} \right) (4) [2(1.3V)0.9V - (0.9V)^2]$$

- Simplify to obtain
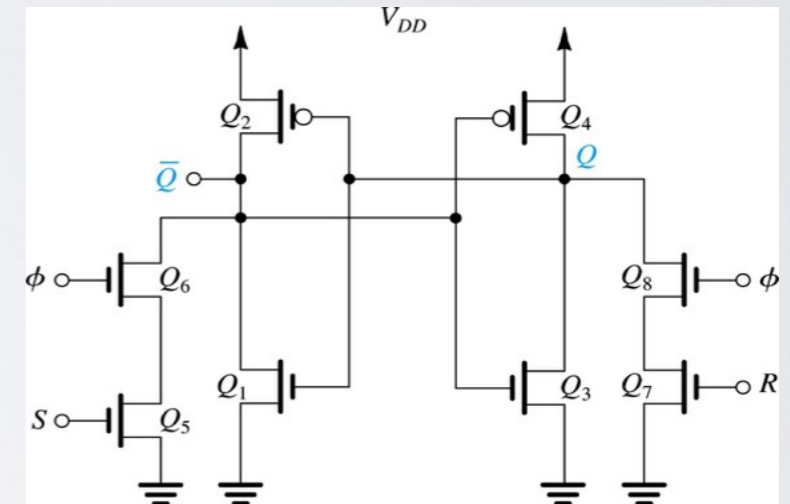
$$\boxed{\left(\frac{W}{L} \right)_{eq} = \frac{1}{2} \left(\frac{W}{L} \right)_{5,6,7,8} = \frac{0.27\mu m}{0.18\mu m}}$$



EXAMPLE

(b) Also, determine the minimum width the set pulse must have for the case in which the W/L ratio of each of the four transistors in the set-reset circuit is selected at twice the minimum value found in (a). Assume that the total capacitance at each of the Q and \bar{Q} nodes and ground is **20fF**.

Solution: Set $(W/L)_5 = (W/L)_6 = (W/L)_7 = (W/L)_8 = 1.08\mu\text{m}/0.18\mu\text{m}$.

Set

$$t_S = t_{PHL} + t_{PLH}$$

where

t_{PHL} is the time it takes for $v_{Q'}$ to go from V_{DD} to $V_{DD}/2$



and


t_{PLH} is the time it takes for v_Q to go from 0V to $V_{DD}/2$

To find t_{PHL} , use $i_C = i_{D,eq} - i_{D2}$. At $t = 0$, $v_{Q'} = V_{DD}$ and Q_2 is off, Q_{eq} is saturated and $i_{C1} = 760.5\mu\text{A}$. At $t = t_{PHL}$, $v_{Q'} = V_{DD}/2$, $i_{D2} = 344.25\mu\text{A}$, $i_{Deq} = 688.5\mu\text{A}$ and $i_{C2} = 344.25\mu\text{A}$. So $i_{C,AVE} = 552.4\mu\text{A}$ and $t_{PHL} = (20\text{fF})(0.9\text{V})/552\mu\text{A} = 32.6\text{ps}$.

To find t_{PLH} , you can use the formula from ch. 14 that use α to get $t_{PLH} = 49.5\text{ps}$.
 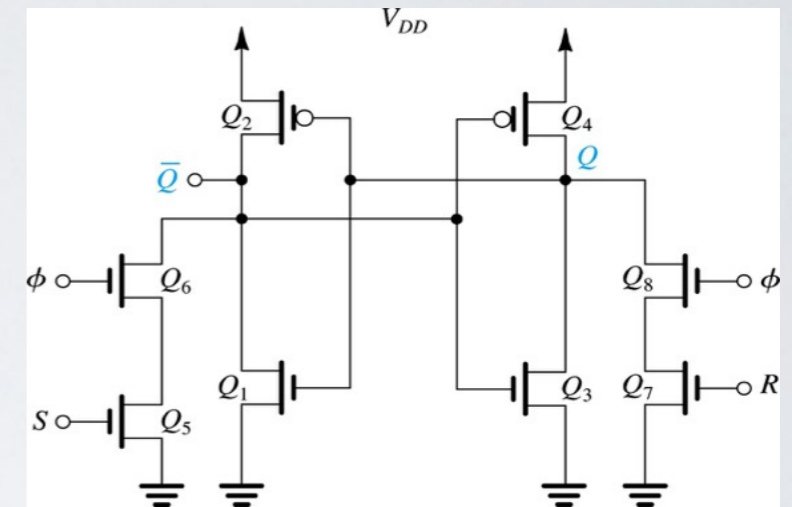
$$T_{\min} = t_{PHL} + t_{PLH} = 82.1\text{ps}$$



 

A simpler CMOS implementation of the clocked SR flip-flop. This circuit is popular as the basic cell in the design of static random-access memory (SRAM) chips.

 


Figure 16.8 A block diagram representation of the D flip-flop.

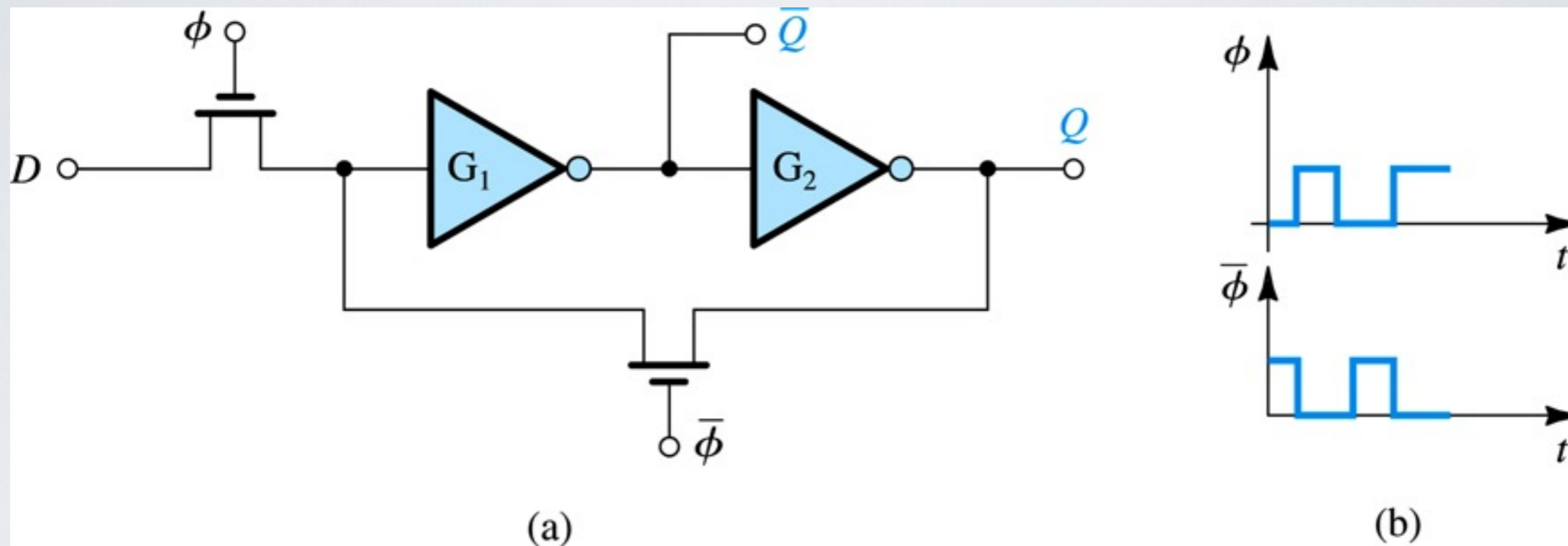


Figure 16.9 A simple implementation of the D flip-flop. The circuit in (a) utilizes the two-phase non-overlapping clock whose waveforms are shown in (b).

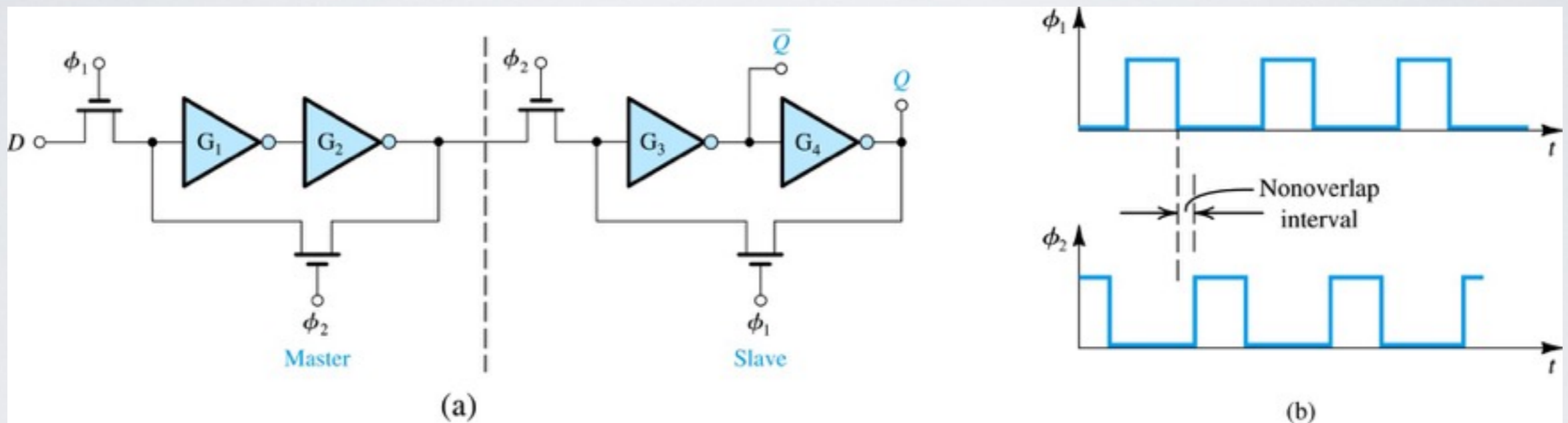


Figure 16.10 (a) A master–slave D flip-flop. The switches can be, and usually are, implemented with CMOS transmission gates. (b) Waveforms of the two-phase non-overlapping clock required.