

### 14.3 TRANSISTOR-TRANSISTOR LOGIC (TTL OR T<sup>2</sup>L)

For more than two decades (late 1960s to late 1980s) TTL enjoyed immense popularity. Indeed, the bulk of digital systems applications employing SSI and MSI packages were designed using TTL.

We shall begin this section with a study of the evolution of TTL from DTL. In this way we shall explain the function of each of the stages of the complete TTL gate circuit. Characteristics of standard TTL gates will be studied in Section 14.4. Standard TTL, however, has now been virtually replaced with more advanced forms of TTL that feature improved performance. These will be discussed in Section 14.5.

#### Evolution of TTL from DTL

The basic DTL gate circuit in discrete form was discussed in the previous section (see Fig. 14.6). The integrated-circuit form of the DTL gate is shown in Fig. 14.7 with only one input indicated. As a prelude to introducing TTL, we have drawn the input diode as a diode-connected transistor ( $Q_1$ ), which corresponds to how diodes are made in IC form.

This circuit differs from the discrete DTL circuit of Fig. 14.6 in two important aspects. First, one of the steering diodes is replaced by the base-emitter junction of a transistor ( $Q_2$ ) that is either cut off (when the input is low) or in the active mode (when the input is high). This is done to reduce the input current and thereby increase the fan-out capability of the gate. A detailed explanation of this point, however, is not relevant to our study of TTL. Second, the resistance  $R_B$  is returned to ground rather than to a negative supply, as was done in the earlier discrete circuit. An obvious advantage of this is the elimination of the additional power supply. The disadvantage, however, is that the reverse base current available to remove the excess charge stored in the base of  $Q_3$  is rather small. We shall elaborate on this point below.

 


FIGURE 14.7 IC form of the DTL gate with the input diode shown as a diode-connected transistor ( $Q_1$ ). Only one input terminal is shown.

#### EXERCISE

- 14.4 Consider the DTL gate circuit shown in Fig. 14.7 and assume that  $\beta(Q_2) = \beta(Q_3) = 50$ . (a) When  $v_i = 0.2$  V, find the input current. (b) When  $v_i = +5$  V, find the base current of  $Q_3$ .  
**Ans.** (a) 1.1 mA; (b) 1.6 mA

#### Reasons for the Slow Response of DTL

The DTL gate has relatively good noise margins and reasonably good fan-out capability. Its response, however, is rather slow. There are two reasons for this: first, when the input goes low and  $Q_2$  and D turn off, the charge stored in the base of  $Q_3$  has to leak through  $R_B$  to ground. The initial value of the reverse base current that accomplishes this “base discharging” process is approximately  $0.7$  V/ $R_B$ , which is about 0.14 mA. Because this current is quite small in comparison to the forward base current, the time required for the removal of base charge is rather long, which contributes to lengthening the gate delay.

The second reason for the relatively slow response of DTL derives from the nature of the output circuit of the gate, which is simply a common-emitter transistor. Figure 14.8 shows the output transistor of a DTL gate driving a capacitive load  $C_L$ . The capacitance  $C_L$  represents the input capacitance of another gate and/or the wiring and parasitic capacitances that are inevitably present in any circuit. When  $Q_3$  is turned on, its collector voltage cannot instantaneously fall because of the existence of  $C_L$ . Thus  $Q_3$  will not immediately saturate but rather will operate in the active region. The collector of  $Q_3$  will therefore act as a constant-current source and will sink a relatively large current ( $\beta I_B$ ). This large current will rapidly discharge  $C_L$ . We thus see that the common-emitter output stage features a short turn-on time. However, turnoff is another matter.

Consider next the operation of the common-emitter output stage when  $Q_3$  is turned off. The output voltage will not rise immediately to the high level ( $V_{CC}$ ). Rather,  $C_L$  will charge up to  $V_{CC}$  through  $R_C$ . This is a rather slow process, and it results in lengthening the DTL gate delay (and similarly the RTL gate delay).

Having identified the two reasons for the slow response of DTL, we shall see in the following how these problems are remedied in TTL.

#### Input Circuit of the TTL Gate

Figure 14.9 shows a conceptual TTL gate with only one input terminal indicated. The most important feature to note is that the input diode has been replaced by a transistor. One can

 


FIGURE 14.8 The output circuit of a DTL gate driving a capacitive load  $C_L$ .

 


FIGURE 14.9 Conceptual form of TTL gate. Only one input terminal is shown.

 


FIGURE 14.10 Analysis of the conceptual TTL gate when the input is high.

think of this simply as if the short circuit between base and collector of  $Q_1$  in Fig. 14.7 has been removed.

To see how the conceptual TTL circuit of Fig. 14.9 works, let the input  $v_i$  be high (say,  $v_i = V_{CC}$ ). In this case current will flow from  $V_{CC}$  through  $R$ , thus forward-biasing the base-collector junction of  $Q_1$ . Meanwhile, the base-emitter junction of  $Q_1$  will be reverse-biased. Therefore  $Q_1$  will be operating in the **inverse active mode**—that is, in the active mode but with the roles of emitter and collector interchanged. The voltages and currents will be as indicated in Fig. 14.10, where the current  $I$  can be calculated from

$$I = \frac{V_{CC} - 1.4}{R}$$

In actual TTL circuits  $Q_1$  is designed to have a very low reverse  $\beta$  ( $\beta_R \approx 0.02$ ). Thus the gate input current will be very small, and the base current of  $Q_3$  will be approximately equal to  $I$ . This current will be sufficient to drive  $Q_3$  into saturation, and the output voltage will be low (0.1 to 0.2 V).

Next let the gate input voltage be brought down to the logic-0 level (say,  $v_i \approx 0.2$  V). The current  $I$  will then be diverted to the emitter of  $Q_1$ . The base-emitter junction of  $Q_1$  will become forward-biased, and the base voltage of  $Q_1$  will therefore drop to 0.9 V. Since  $Q_3$  was in saturation, its base voltage will remain at +0.7 V pending the removal of the excess charge stored in the base region. Figure 14.11 indicates the various voltage and current values immediately after the input is lowered. We see that  $Q_1$  will be operating in the normal

 


FIGURE 14.11 Voltage and current values in the conceptual TTL circuit immediately after the input voltage is lowered.

 


FIGURE 14.12 An emitter-follower output stage with capacitive load.

active mode<sup>3</sup> and its collector will carry a large current ( $\beta_F I$ ). This large current rapidly discharges the base of  $Q_3$  and drives it into cutoff. We thus see the action of  $Q_1$  in speeding up the turn-off process.

As  $Q_3$  turns off, the voltage at its base is reduced, and  $Q_1$  enters the saturation mode. Eventually the collector current of  $Q_1$  will become negligibly small, which implies that its  $V_{CEsat}$  will be approximately 0.1 V and the base of  $Q_3$  will be at about 0.3 V, which keeps  $Q_3$  in cutoff.

### Output Circuit of the TTL Gate

The above discussion illustrates how one of the two problems that slow down the operation of DTL is solved in TTL. The second problem, the long rise time of the output waveform, is solved by modifying the output stage, as we shall now explain.

First, recall that the common-emitter output stage provides fast discharging of load capacitance but rather slow charging. The opposite is obtained in the emitter-follower output stage shown in Fig. 14.12. Here, as  $v_i$  goes high, the transistor turns on and provides a low output resistance (characteristic of emitter followers), which results in fast charging of  $C_L$ . On the other hand, when  $v_i$  goes low, the transistor turns off and  $C_L$  is then left to discharge slowly through  $R_E$ .

<sup>3</sup> Although the collector voltage of  $Q_1$  is lower than its base voltage by 0.2 V, the collector-base junction will in effect be cut off and  $Q_1$  will be operating in the active mode.

 


FIGURE 14.13 The totem-pole output stage.

It follows that an optimum output stage would be a combination of the common-emitter and the emitter-follower configurations. Such an output stage, shown in Fig. 14.13, has to be driven by two complementary signals  $v_{I1}$  and  $v_{I2}$ . When  $v_{I1}$  is high  $v_{I2}$  will be low, and in this case  $Q_3$  will be on and saturated, and  $Q_4$  will be off. The common-emitter transistor  $Q_3$  will then provide the fast discharging of load capacitance and in steady state provide a low resistance ( $R_{CEsat}$ ) to ground. Thus when the output is low, the gate can sink substantial amounts of current through the saturated transistor  $Q_3$ .

When  $v_{I1}$  is low and  $v_{I2}$  is high,  $Q_3$  will be off and  $Q_4$  will be conducting. The emitter-follower  $Q_4$  will then provide fast charging of load capacitance. It also provides the gate with a low output resistance in the high state and hence with the ability to source a substantial amount of load current.

Because of the appearance of the circuit in Fig. 14.13, with  $Q_4$  stacked on top of  $Q_3$ , the circuit has been given the name **totem-pole output stage**. Also, because of the action of  $Q_4$  in pulling up the output voltage to the high level,  $Q_4$  is referred to as the **pull-up transistor**. Since the pulling up is achieved here by an active element ( $Q_4$ ), the circuit is said to have an **active pull-up**. This is in contrast to the **passive pull-up** of RTL and DTL gates. Of course, the common-emitter transistor  $Q_3$  provides the circuit with **active pull-down**. Finally, note that a special **driver circuit** is needed to generate the two complementary signals  $v_{I1}$  and  $v_{I2}$ .

**EXAMPLE 14.1**

We wish to analyze the circuit shown together with its driving waveforms in Fig. 14.14 to determine the waveform of the output signal  $v_O$ . Assume that  $Q_3$  and  $Q_4$  have  $\beta = 50$ .

**Solution**

Consider first the situation before  $v_{I1}$  goes high—that is, at time  $t < 0$ . In this case  $Q_3$  is off and  $Q_4$  is on, and the circuit can be simplified to that shown in Fig. 14.15. In this simplified circuit we have replaced the voltage divider ( $R_1, R_2$ ) by its Thévenin equivalent. In the steady state,  $C_L$  will be charged to the output voltage  $v_O$ , whose value can be obtained as follows:

$$5 = 10 \times I_B + V_{BE} + I_E \times 0.5 + 2.5$$

Substituting  $V_{BE} \approx 0.7$  V and  $I_B = I_E/(\beta + 1) = I_E/51$  gives  $I_E = 2.59$  mA. Thus the output voltage  $v_O$  is given by

$$v_O = 2.5 + I_E \times 0.5 = 3.79$$
 V

 


FIGURE 14.14 Circuit and input waveforms for Example 14.1.

 


FIGURE 14.15 The circuit of Fig. 14.14 when  $Q_3$  is off.

We next consider the circuit as  $v_{I1}$  goes high and  $v_{I2}$  goes low. Transistor  $Q_3$  turns on and transistor  $Q_4$  turns off, and the circuit simplifies to that shown in Fig. 14.16. Again we have used the Thévenin equivalent of the divider ( $R_1, R_2$ ). We shall also assume that the switching times of the transistors are negligibly small. Thus at  $t = 0+$  the base current of  $Q_3$  becomes

$$I_B = \frac{5 - 0.7}{10} = 0.43$$
 mA

Since at  $t = 0$  the collector voltage of  $Q_3$  is 3.79 V, and since this value cannot change instantaneously because of  $C_L$ , we see that at  $t = 0+$  transistor  $Q_3$  will be in the active mode. The collector current of  $Q_3$  will be  $\beta I_B$ , which is 21.5 mA, and the circuit will have the equivalent shown in Fig. 14.17(a). A simpler version of this equivalent circuit, obtained using Thévenin's theorem, is shown in Fig. 14.17(b).

The equivalent circuit of Fig. 14.17 applies as long as  $Q_3$  remains in the active mode. This condition persists while  $C_L$  is being discharged and until  $v_O$  reaches about +0.3 V, at which time  $Q_3$  enters saturation. This is illustrated by the waveform in Fig. 14.18. The time for the output

 


FIGURE 14.16 The circuit of Fig. 14.14 when  $Q_4$  is off.

 


FIGURE 14.17 (a) Equivalent circuit for the circuit in Fig. 14.16 when  $Q_3$  is in the active mode. (b) Simpler version of the circuit in (a) obtained using Thévenin's theorem.

 


FIGURE 14.18 Details of the output voltage waveform for the circuit in Fig. 14.14.

voltage to fall from +3.79 V to +0.3 V, which can be considered the **fall time**  $t_f$ , can be obtained from

$$-8.25 - (-8.25 - 3.79)e^{-t_f/\tau} = 0.3$$

which results in

$$t_f \approx 0.34\tau$$

where

$$\tau = C_L \times 0.5 \text{ k}\Omega = 10 \text{ ns}$$

Thus  $t_f = 3.4 \text{ ns}$ .

After  $Q_3$  enters saturation, the capacitor discharges further to the final steady-state value of  $V_{CEsat} (\approx 0.2 \text{ V})$ . The transistor model that applies during this interval is more complex; since the interval in question is quite short, we shall not pursue the matter further.

Consider next the situation as  $v_{i1}$  goes low and  $v_{i2}$  goes high at  $t = T$ . Transistor  $Q_3$  turns off as  $Q_4$  turns on. We shall assume that this occurs immediately, and thus at  $t = T+$  the circuit simplifies to that in Fig. 14.15. We have already analyzed this circuit in the steady state and thus know that eventually  $v_O$  will reach +3.79 V. Thus  $v_O$  rises exponentially from +0.2 V toward +3.79 V with a time constant of  $C_L(0.5 \text{ k}\Omega // [10 \text{ k}\Omega / (\beta + 1)])$ , where we have neglected the emitter resistance  $r_e$ . Denoting this time constant  $\tau_r$ , we obtain  $\tau_r = 2.8 \text{ ns}$ . Defining the rise time  $t_r$  as the time for  $v_O$  to reach 90% of the final value, we obtain  $3.79 - (3.79 - 0.2)e^{-t_r/\tau_r} = 0.9 \times 3.79$ , which results in  $t_r = 6.4 \text{ ns}$ . Figure 14.18 illustrates the details of the output voltage waveform.

### The Complete Circuit of the TTL Gate

Figure 14.19 shows the complete TTL gate circuit. It consists of three stages: the input transistor  $Q_1$ , whose operation has already been explained, the driver stage  $Q_2$ , whose function is to generate the two complementary voltage signals required to drive the totem-pole circuit,

 


FIGURE 14.19 The complete TTL gate circuit with only one input terminal indicated.

which is the third (output) stage of the gate. The totem-pole circuit in the TTL gate has two additional components: the 130-Ω resistance in the collector circuit of  $Q_4$  and the diode D in the emitter circuit of  $Q_4$ . The function of these two additional components will be explained shortly. Notice that the TTL gate is shown with only one input terminal indicated. Inclusion of additional input terminals will be considered in Section 14.4.

Because the driver stage  $Q_2$  provides two complementary (that is, out-of-phase) signals, it is known as a **phase splitter**.

We shall now provide a detailed analysis of the TTL gate circuit in its two extreme states: one with the input high and one with the input low.


### Analysis When the Input Is High

When the input is high (say, +5 V), the various voltages and currents of the TTL circuit will have the values indicated in Fig. 14.20. The analysis illustrated in Fig. 14.20 is quite straightforward, and the order of the steps followed is indicated by the circled numbers. As expected, the input transistor is operating in the inverse active mode, and the input current, called the **input high current**  $I_{IH}$ , is small; that is,


$$I_{IH} = \beta_R I \approx 15 \mu\text{A}$$

where we assume that  $\beta_R \approx 0.02$ .

The collector current of  $Q_1$  flows into the base of  $Q_2$ , and its value is sufficient to saturate the phase-splitter transistor  $Q_2$ . The latter supplies the base of  $Q_3$  with sufficient current to drive it into saturation and lower its output voltage to  $V_{CEsat}$  (0.1 to 0.2 V). The voltage at the collector of  $Q_2$  is  $V_{BE3} + V_{CEsat}(Q_2)$ , which is approximately +0.9 V. If diode D were not included, this voltage would be sufficient to turn  $Q_4$  on, which is contrary to the proper operation of the totem-pole circuit. Including diode D ensures that both  $Q_4$  and D remain off.

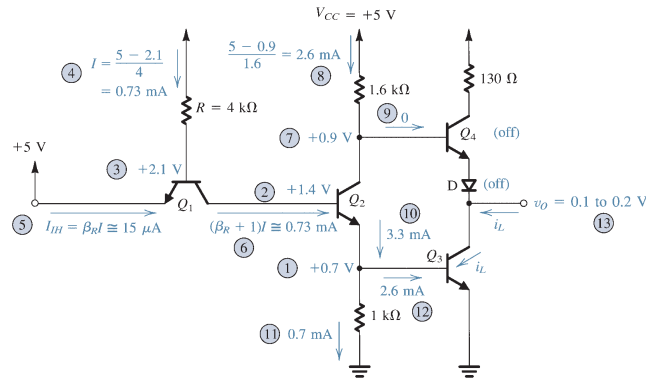

**FIGURE 14.20** Analysis of the TTL gate with the input high. The circled numbers indicate the order of the analysis steps.

 

**FIGURE 14.21** The  $v_O$ - $i_L$  characteristic of the TTL gate when the output is low.

The saturated transistor  $Q_3$  then establishes the low output voltage of the gate ( $V_{CEsat}$ ) and provides a low impedance to ground.

In the low-output state the gate can sink a load current  $i_L$ , provided that the value of  $i_L$  does not exceed  $\beta \times 2.6$  mA, which is the maximum collector current that  $Q_3$  can sustain while remaining in saturation. Obviously the greater the value of  $i_L$ , the greater the output voltage will be. To maintain the logic-0 level below a certain specified limit, a corresponding limit has to be placed on the load current  $i_L$ . As will be seen shortly, it is this limit that determines the maximum fan-out of the TTL gate.

Figure 14.21 shows a sketch of the output voltage  $v_O$  versus the load current  $i_L$  of the TTL gate when the output is low. This is simply the  $v_{CE}-i_C$  characteristic curve of  $Q_3$  measured with a base current of 2.6 mA. Note that at  $i_L = 0$ ,  $v_O$  is the offset voltage, which is about 100 mV.

### EXERCISE


- 14.5 Assume that the saturation portion of the  $v_O$ - $i_L$  characteristic shown in Fig. 14.21 can be approximated by a straight line (of slope = 8 Ω) that intersects the  $v_O$  axis at 0.1 V. Find the maximum load current that the gate is allowed to sink if the logic-0 level is specified to be  $\leq 0.3$  V.

Ans. 25 mA

### Analysis When the Input Is Low

Consider next the operation of the TTL gate when the input is at the logic-0 level (=0.2 V). The analysis is illustrated in Fig. 14.22, from which we see that the base-emitter junction of  $Q_1$  will be forward-biased and the base voltage will be approximately +0.9 V. Thus the current  $I$  can be found to be approximately 1 mA. Since 0.9 V is insufficient to forward-bias the series combination of the collector-base junction of  $Q_1$  and the base-emitter junction of  $Q_2$  (at least 1.2 V would be required), the latter will be off. Therefore the collector current of  $Q_1$  will be almost zero and  $Q_1$  will be saturated, with  $V_{CEsat} \approx 0.1$  V. Thus the base of  $Q_2$  will be at approximately +0.3 V, which is indeed insufficient to turn  $Q_2$  on.

The gate input current in the low state, called **input-low current**  $I_{IL}$ , is approximately equal to the current  $I$  ( $\approx 1$  mA) and flows out of the emitter of  $Q_1$ . If the TTL gate is driven

 

**FIGURE 14.22** Analysis of the TTL gate when the input is low. The circled numbers indicate the order of the analysis steps.

by another TTL gate, the output transistor  $Q_3$  of the driving gate should sink this current  $I_{IL}$ . Since the output current that a TTL gate can sink is limited to a certain maximum value, the maximum fan-out of the gate is directly determined by the value of  $I_{IL}$ .

**EXERCISES**

- 14.6 Consider the TTL gate analyzed in Exercise 14.5. Find its maximum allowable fan-out using the value of  $I_{IL}$  calculated above.  
Ans. 25
- 14.7 Use Eq. (4.114) to find  $V_{CEsat}$  of transistor  $Q_1$  when the input of the gate is low (0.2 V). Assume that  $\beta_F = 50$  and  $\beta_R = 0.02$ .  
Ans. 98 mV

Let us continue with our analysis of the TTL gate. When the input is low, we see that both  $Q_2$  and  $Q_3$  will be off. Transistor  $Q_4$  will be on and will supply (source) the load current  $i_L$ . Depending on the value of  $i_L$ ,  $Q_4$  will be either in the active mode or in the saturation mode.

With the gate output terminal open, the current  $i_L$  will be very small (mostly leakage) and the two junctions (base–emitter junction of  $Q_4$  and diode D) will be barely conducting. Assuming that each junction has a 0.65-V drop and neglecting the voltage drop across the 1.6-k $\Omega$  resistance, we find that the output voltage will be

$$v_O \approx 5 - 0.65 - 0.65 = 3.7 \text{ V}$$

As  $i_L$  is increased,  $Q_4$  and D conduct more heavily, but for a range of  $i_L$ ,  $Q_4$  remains in the active mode, and  $v_O$  is given by

$$v_O = V_{CC} - \frac{i_L}{\beta + 1} \times 1.6 \text{ k}\Omega - V_{BE4} - V_D \tag{14.4}$$

If we keep increasing  $i_L$ , a value will be reached at which  $Q_4$  saturates. Then the output voltage becomes determined by the 130- $\Omega$  resistance according to the approximate relationship

$$v_O \approx V_{CC} - i_L \times 130 - V_{CEsat}(Q_4) - V_D \tag{14.5}$$

**Function of the 130- $\Omega$  Resistance**

At this point the reason for including the 130- $\Omega$  resistance should be evident: It is simply to limit the current that flows through  $Q_4$ , especially in the event that the output terminal is accidentally short-circuited to ground. This resistance also limits the supply current in another circumstance, namely, when  $Q_4$  turns on while  $Q_3$  is still in saturation. To see how this occurs, consider the case where the gate input was high and then is suddenly brought down to the low level. Transistor  $Q_2$  will turn off relatively fast because of the availability of a large reverse current supplied to its base terminal by the collector of  $Q_1$ . On the other hand, the base of  $Q_3$  will have to discharge through the 1-k $\Omega$  resistance, and thus  $Q_3$  will take some time to turn off. Meanwhile  $Q_4$  will turn on, and a large current pulse will flow through the series combination of  $Q_4$  and  $Q_3$ . Part of this current will serve the useful purpose of charging up any load capacitance to the logic-1 level. The magnitude of the current pulse will be limited by the 130- $\Omega$  resistance to about 30 mA.

The occurrence of these current pulses of short duration (called **current spikes**) raises another important issue. The current spikes have to be supplied by the  $V_{CC}$  source and, because of its finite source resistance, will result in voltage spikes (or “glitches”) superimposed on  $V_{CC}$ . These voltage spikes could be coupled to other gates and flip-flops in the digital system and thus might produce false switching in other parts of the system. This effect, which might loosely be called **crosstalk**, is a problem in TTL systems. To reduce the size of the voltage spikes, capacitors (called bypass capacitors) should be connected between the supply rail and ground at frequent locations. These capacitors lower the impedance of the supply-voltage source and hence reduce the magnitude of the voltage spikes. Alternatively, one can think of the bypass capacitors as supplying the impulsive current spikes.

**EXERCISES**

- 14.8 Assuming that  $Q_4$  has  $\beta = 50$  and that at the verge of saturation  $V_{CEsat} = 0.3 \text{ V}$ , find the value of  $i_L$  at which  $Q_4$  saturates.  
Ans. 4.16 mA
- 14.9 Assuming that at a current of 1 mA the voltage drops across the emitter–base junction of  $Q_4$  and the diode D are each 0.7 V, find  $v_O$  when  $i_L = 1 \text{ mA}$  and 10 mA. (Note the result of the previous exercise.)  
Ans. 3.6 V; 2.7 V
- 14.10 Find the maximum current that can be sourced by a TTL gate while the output high level ( $V_{OH}$ ) remains greater than the minimum guaranteed value of 2.4 V.  
Ans. 12.3 mA; or, more accurately, taking the base current of  $Q_4$  into account, 13.05 mA

### 14.4 CHARACTERISTICS OF STANDARD TTL

Because of its historical popularity and continued importance, TTL will be studied further in this and the next sections. In this section we shall consider some of the important characteristics of standard TTL gates. Special improved forms of TTL will be dealt with in Section 14.5.

#### Transfer Characteristic

Figure 14.23 shows the TTL gate together with a sketch of its voltage transfer characteristic drawn in a piecewise-linear fashion. The actual characteristic is, of course, a smooth curve. We shall now explain the transfer characteristic and calculate the various break-points and slopes. It will be assumed that the output terminal of the gate is open.

Segment *AB* is obtained when transistor  $Q_1$  is saturated,  $Q_2$  and  $Q_3$  are off, and  $Q_4$  and  $D$  are on. The output voltage is approximately two diode drops below  $V_{CC}$ . At point *B* the phase splitter ( $Q_2$ ) begins to turn on because the voltage at its base reaches  $0.6\text{ V}$  ( $0.5\text{ V} + V_{CEsat}$  of  $Q_1$ ).

Over segment *BC*, transistor  $Q_1$  remains saturated, but more and more of its base current  $I$  gets diverted to its base-collector junction and into the base of  $Q_2$ , which operates as a linear amplifier. Transistor  $Q_4$  and diode  $D$  remain on, with  $Q_4$  acting as an emitter follower. Meanwhile the voltage at the base of  $Q_3$ , although increasing, remains insufficient to turn  $Q_3$  on (less than  $0.6\text{ V}$ ).

Let us now find the slope of segment *BC* of the transfer characteristic. Let the input  $v_i$  increase by an increment  $\Delta v_i$ . This increment appears at the collector of  $Q_1$ , since the saturated  $Q_1$  behaves (approximately) as a three-terminal short circuit as far as signals are

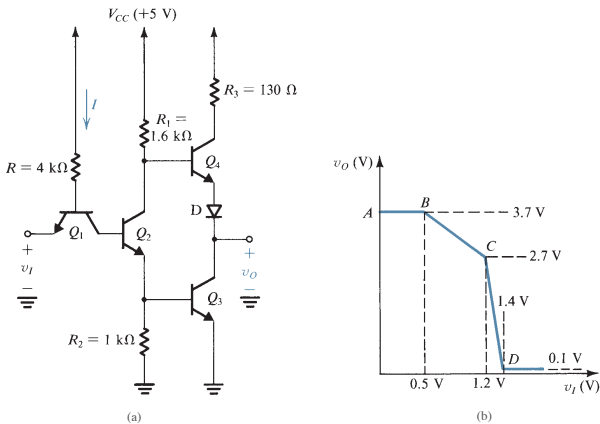


FIGURE 14.23 The TTL gate and its voltage transfer characteristic.

concerned. Thus at the base of  $Q_2$  we have a signal  $\Delta v_i$ . Neglecting the loading of emitter follower  $Q_4$  on the collector of  $Q_2$ , we can find the gain of the phase splitter from

$$\frac{v_{c2}}{v_{b2}} = \frac{-\alpha_2 R_1}{r_{e2} + R_2} \quad (14.6)$$

The value of  $r_{e2}$  will obviously depend on the current in  $Q_2$ . This current will range from zero (as  $Q_2$  begins to turn on) to the value that results in a voltage of about  $0.6\text{ V}$  at the emitter of  $Q_2$  (the base of  $Q_3$ ). This value is about  $0.6\text{ mA}$  and corresponds to point *C* on the transfer characteristic. Assuming an average current in  $Q_2$  of  $0.3\text{ mA}$ , we obtain  $r_{e2} \approx 83\ \Omega$ . For  $\alpha = 0.98$ , Eq. (14.6) results in a gain value of  $1.45$ . Since the gain of the output follower  $Q_4$  is close to unity, the overall gain of the gate, which is the slope of the *BC* segment, is about  $-1.45$ .

As already implied, breakpoint *C* is determined by  $Q_3$  starting to conduct. The corresponding input voltage can be found from

$$\begin{aligned} v_i(C) &= V_{BE3} + V_{BE2} - V_{CEsat}(Q_1) \\ &= 0.6 + 0.7 - 0.1 = 1.2\text{ V} \end{aligned}$$

At this point the emitter current of  $Q_2$  is approximately  $0.6\text{ mA}$ . The collector current of  $Q_2$  is also approximately  $0.6\text{ mA}$ ; neglecting the base current of  $Q_4$ , the voltage at the collector of  $Q_2$  is

$$v_{c2}(C) = 5 - 0.6 \times 1.6 \approx 4\text{ V}$$

Thus  $Q_2$  is still in the active mode. The corresponding output voltage is

$$v_o(C) = 4 - 0.65 - 0.65 = 2.7\text{ V}$$

As  $v_i$  is increased past the value of  $v_i(C) = 1.2\text{ V}$ ,  $Q_3$  begins to conduct and operates in the active mode. Meanwhile,  $Q_1$  remains saturated, and  $Q_2$  and  $Q_4$  remain in the active mode. The circuit behaves as an amplifier until  $Q_2$  and  $Q_3$  saturate and  $Q_4$  cuts off. This occurs at point *D* on the transfer characteristic, which corresponds to an input voltage  $v_i(D)$  obtained from

$$\begin{aligned} v_i(D) &= V_{BE3} + V_{BE2} + V_{BC1} - V_{BE1} \\ &= 0.7 + 0.7 + 0.7 - 0.7 = 1.4\text{ V} \end{aligned}$$

Note that we have in effect assumed that at point *D* transistor  $Q_1$  is still saturated, but with  $V_{CEsat} \approx 0$ . To see how this comes about, note that from point *B* on, more and more of the base current of  $Q_1$  is diverted to its base-collector junction. Thus while the drop across the base-collector junction increases, that across the base-emitter junction decreases. At point *D* these drops become almost equal. For  $v_i > v_i(D)$  the base-emitter junction of  $Q_1$  cuts off; thus  $Q_1$  leaves saturation and enters the inverse active mode.

Calculation of gain over the segment *CD* is a relatively complicated task. This is due to the fact that there are two paths from input to output: one through  $Q_3$  and one through  $Q_4$ . A simple but gross approximation for the gain of this segment can be obtained from the coordinates of points *C* and *D* in Fig. 14.23(b), as follows:

$$\begin{aligned} \text{Gain} &= -\frac{v_o(C) - v_o(D)}{v_i(D) - v_i(C)} \\ &= -\frac{2.7 - 0.1}{1.4 - 1.2} = -13\text{ V/V} \end{aligned}$$

From the transfer curve of Fig. 14.23(b) we can determine the critical points and the noise margins as follows:  $V_{OH} = 3.7$  V;  $V_{IL}$  is somewhere in the range of 0.5 V to 1.2 V, and thus a conservative estimate would be 0.5 V;  $V_{OL} = 0.1$  V;  $V_{IH} = 1.4$  V;  $NM_H = V_{OH} - V_{IH} = 2.3$  V; and  $NM_L = V_{IL} - V_{OL} = 0.4$  V. It should be noted that these values are computed assuming that the gate is not loaded and without taking into account power-supply or temperature variations.

**EXERCISE**

14.11 Taking into account the fact that the voltage across a forward-biased *pn* junction changes by about  $-2$  mV/°C, find the coordinates of points A, B, C, and D of the gate transfer characteristic at  $-55^\circ\text{C}$  and at  $+125^\circ\text{C}$ . Assume that the characteristic in Fig. 14.23(b) applies at  $25^\circ\text{C}$ , and neglect the small temperature coefficient of  $V_{CEsat}$ .  
**Ans.** At  $-55^\circ\text{C}$ : (0, 3.38), (0.66, 3.38), (1.52, 2.16), (1.72, 0.1); at  $+125^\circ\text{C}$ : (0, 4.1), (0.3, 4.1), (0.8, 3.46), (1.0, 0.1)

**Manufacturers' Specifications**

Manufacturers of TTL usually provide curves for the gate transfer characteristic, the input *i-v* characteristic, and the output *i-v* characteristic, measured at the limits of the specified operating temperature range. In addition, guaranteed values are usually given for the parameters  $V_{OL}$ ,  $V_{OH}$ ,  $V_{IL}$ , and  $V_{IH}$ . For standard TTL (known as the 74 series) these values are  $V_{OL} = 0.4$  V,  $V_{OH} = 2.4$  V,  $V_{IL} = 0.8$  V, and  $V_{IH} = 2$  V. These limit values are guaranteed for a specified tolerance in power-supply voltage and for a maximum fan-out of 10. From our discussion in Section 14.3 we know that the maximum fan-out is determined by the maximum current that  $Q_3$  can sink while remaining in saturation and while maintaining a saturation voltage lower than a guaranteed maximum ( $V_{OL} = 0.4$  V). Calculations performed in Section 14.3 indicate the possibility of a maximum fan-out of 20 to 30. Thus the figure specified by the manufacturer is appropriately conservative.

The parameters  $V_{OL}$ ,  $V_{OH}$ ,  $V_{IL}$ , and  $V_{IH}$  can be used to compute the noise margins as follows:

$$NM_H = V_{OH} - V_{IH} = 0.4 \text{ V}$$

$$NM_L = V_{IL} - V_{OL} = 0.4 \text{ V}$$

**EXERCISES**

14.12 In Section 14.3 we found that when the gate input is high, the base current of  $Q_3$  is approximately 2.6 mA. Assume that this value applies at  $25^\circ\text{C}$  and that at this temperature  $V_{BE} \approx 0.7$  V. Taking into account the  $-2$ -mV/°C temperature coefficient of  $V_{BE}$  and neglecting all other changes, find the base current of  $Q_3$  at  $-55^\circ\text{C}$  and at  $+125^\circ\text{C}$ .  
**Ans.** 2.2 mA; 3 mA

14.13 Figure E14.13 shows sketches of the  $i_L-v_O$  characteristics of a TTL gate when the output is low. Use these characteristics together with the results of Exercise 14.12 to calculate the value of  $\beta$  of transistor  $Q_3$  at  $-55^\circ\text{C}$ ,  $+25^\circ\text{C}$ , and  $+125^\circ\text{C}$ .

 


FIGURE E14.13

**Ans.** 16; 25; 28

**Propagation Delay**

The propagation delay of TTL gates is defined conventionally as the time between the 1.5-V points of corresponding edges of the input and output waveforms. For standard TTL (also known as *medium-speed* TTL)  $t_p$  is typically about 10 ns.

As far as power dissipation is concerned it can be shown (see Exercise 14.14) that when the gate output is high the gate dissipates 5 mW, and when the output is low the dissipation is 16.7 mW. Thus the average dissipation is 11 mW, resulting in a delay-power product of about 100 pJ.

**EXERCISE**

14.14 Calculate the value of the supply current ( $I_{CC}$ ), and hence the power dissipated in the TTL gate, when the output terminal is open and the input is (a) low at 0.2 V (see Fig. 14.22) and (b) high at +5 V (see Fig. 14.20).

**Ans.** (a) 1 mA, 5 mW; (b) 3.33 mA, 16.7 mW

**Dynamic Power Dissipation**

In Section 14.3 the occurrence of supply current spikes was explained. These spikes give rise to additional power drain from the  $V_{CC}$  supply. This **dynamic power** is also dissipated in the gate circuit. It can be evaluated by multiplying the average current due to the spikes by  $V_{CC}$ , as illustrated by the solution of Exercise 14.15.



**EXERCISE**

14.15 Consider a TTL gate that is switched on and off at the rate of 1 MHz. Assume that each time the gate is turned off (that is, the output goes high) a supply-current pulse of 30-mA amplitude and 2-ns width occurs. Also assume that no current spike occurs when the gate is turned on. Calculate the average supply current due to the spikes, and the dynamic power dissipation.

Ans. 60  $\mu$ A; 0.3 mW

**The TTL NAND Gate**

Figure 14.24 shows the basic TTL gate. Its most important feature is the **multiemitter transistor**  $Q_1$  used at the input. Figure 14.25 shows the structure of the multiemitter transistor.

It can be easily verified that the gate of Fig. 14.24 performs the NAND function. The output will be high if one (or both) of the inputs is (are) low. The output will be low in only

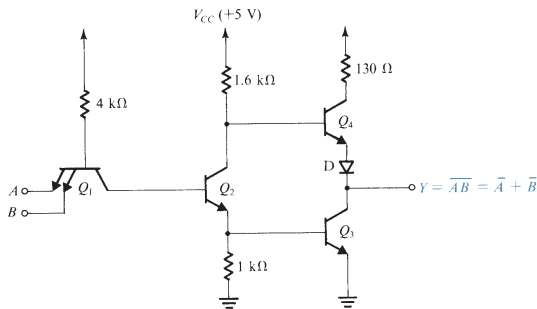


FIGURE 14.24 The TTL NAND gate.

 


FIGURE 14.25 Structure of the multiemitter transistor  $Q_1$ .

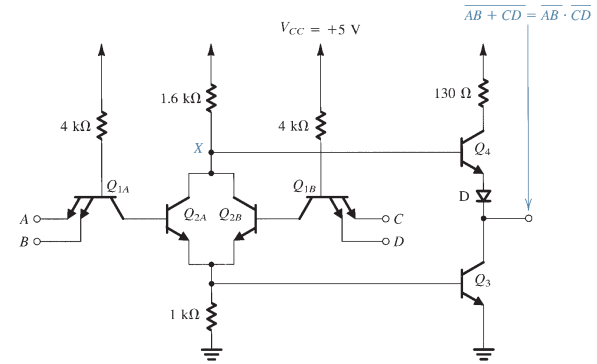


FIGURE 14.26 A TTL AND-OR-INVERT gate.

one case: when both inputs are high. Extension to more than two inputs is straightforward and is achieved by diffusing additional emitter regions.

Although theoretically an unused input terminal may be left open-circuited, this is generally not a good practice. An open-circuit input terminal acts as an “antenna” that “picks up” interfering signals and thus could cause erroneous gate switching. An unused input terminal should therefore be connected to the positive power supply *through a resistance* (of, say, 1 k $\Omega$ ). In this way the corresponding base-emitter junction of  $Q_1$  will be reverse-biased and thus will have no effect on the operation of the gate. The series resistance is included in order to limit the current in case of breakdown of the base-emitter junction due to transients on the power supply.

**Other TTL Logic Circuits**

On a TTL MSI chip there are many cases in which logic functions are implemented using “stripped-down” versions of the basic TTL gate. As an example we show in Fig. 14.26 the TTL implementation of the AND-OR-INVERT function. As shown, the phase-splitter transistors of two gates are connected in parallel, and a single output stage is used. The reader is urged to verify that the logic function realized is as indicated.

At this point it should be noted that the totem-pole output stage of TTL does *not* allow connecting the output terminals of two gates to realize the AND function of their outputs (known as the wired-AND connection). To see the reason for this, consider two gates whose outputs are connected together, and let one gate have a high output and the other have a low output. Current will flow from  $Q_4$  of the first gate through  $Q_3$  of the second gate. The current value will fortunately be limited by the 130- $\Omega$  resistance. Obviously, however, no useful logic function is realized by this connection.


The lack of wired-AND capability is a drawback of TTL. Nevertheless, the problem is solved in a number of ways, including doing the paralleling at the phase-splitter stage, as illustrated in Fig. 14.26. Another solution consists of deleting the emitter-follower transistor

altogether. The result is an output stage consisting solely of the common-emitter transistor  $Q_3$  without even a collector resistance. Obviously, one can connect the outputs of such gates together to a common collector resistance and achieve a wired-AND capability. TTL gates of this type are known as **open-collector TTL**. The obvious disadvantage is the slow rise time of the output waveform.

Another useful variant of TTL is the **tristate** output arrangement explored in Exercise 14.16.

**EXERCISE**

**14.16** The circuit shown in Fig. E14.16 is called tristate TTL. Verify that when the terminal labeled **Third state** is high, the gate functions normally and that when this terminal is low, both transistors  $Q_3$  and  $Q_4$  cut off and the output of the gate is an open circuit. The latter state is the third state, or the high-output-impedance state.

 

**FIGURE E14.16**

Tristate TTL enables the connection of a number of TTL gates to a common output line (or bus). At any particular time the signal on the bus will be determined by the one TTL gate

that is *enabled* (by raising its third-state input terminal). All other gates will be in the third state and thus will have no control of the bus.

**14.5 TTL FAMILIES WITH IMPROVED PERFORMANCE**


The standard TTL circuits studied in the two previous sections were introduced in the mid-1960s. Since then, several improved versions have been developed. In this section we shall discuss some of these improved TTL subfamilies. As will be seen the improvements are in two directions: increasing speed and reducing power dissipation.

The speed of the standard TTL gate of Fig. 14.24 is limited by two mechanisms: first, transistors  $Q_1$ ,  $Q_2$ , and  $Q_3$  saturate, and hence we have to contend with their finite storage time. Although  $Q_2$  is discharged reasonably quickly because of the active mode of operation of  $Q_1$ , as already explained, this is not true for  $Q_3$ , whose base charge has to leak out through the 1-k $\Omega$  resistance in its base circuit. Second, the resistances in the circuit, together with the various transistor and wiring capacitances, form relatively long time constants, which contribute to lengthening the gate delay.

It follows that there are two approaches to speeding up the operation of TTL. The first is to prevent transistor saturation and the second is to reduce the values of all resistances. Both approaches are utilized in the Schottky TTL circuit family.

**Schottky TTL**

In Schottky TTL, transistors are prevented from saturation by connecting a low-voltage-drop diode between base and collector, as shown in Fig. 14.27. These diodes, formed as a metal-to-semiconductor junction, are called Schottky diodes and have a forward voltage drop of about 0.5 V. We have briefly discussed Schottky diodes in Section 3.9. Schottky diodes<sup>4</sup> are easily fabricated and do not increase chip area. In fact, the Schottky TTL fabrication process has been designed to yield transistors with smaller areas and thus higher  $\beta$  and  $f_T$  than those produced by the standard TTL process. Figure 14.27 also shows the symbol used to represent the combination of a transistor and a Schottky diode, referred to as a Schottky transistor.

 

**FIGURE 14.27** (a) A transistor with a Schottky diode clamp. (b) Circuit symbol for the connection in (a), known as a Schottky transistor.

<sup>4</sup> Note that silicon Schottky diodes exhibit voltage drops of about 0.5 V, whereas GaAs Schottky diodes (Section 5.12) exhibit voltage drops of about 0.7 V.