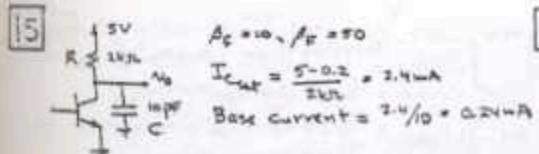


## Probs. sugeridos: 16-21 y 23

- 14.16** Consider the circuit of Fig. 14.9 with a 5-V supply,  $R = 4 \text{ k}\Omega$ ,  $R_C = 2 \text{ k}\Omega$ ,  $V_{BE} = 0.7 \text{ V}$ ,  $V_{CEsat}(Q_3) \approx 0.2 \text{ V}$ ,  $\beta_F = 20$ , and  $\beta_R = 0.1$ . What input current flows with input high ( $\geq 1.4 \text{ V}$ )? with input low (at 0.2 V)? What is the value of  $V_{OH}$  with no load? For what fan-out of similar circuits does  $V_{OH}$  decrease by 2 V?
- 14.17** Consider the circuit of Fig. 14.9 with  $V_{CC} = 3 \text{ V}$ ,  $R = 3 \text{ k}\Omega$ , and  $R_C = 1 \text{ k}\Omega$ , as the input rises slowly from 0 V. If  $V_{CEsat}$  of  $Q_1$  is 0.1 V, and if  $Q_3$  turns on when its  $V_{BE}$  reaches 0.6 V, at what value of input voltage does  $Q_3$  begin to conduct? This is a good estimate of  $V_{IL}$ .
- \*14.18** A variant of the T<sup>2</sup>L gate shown in Fig. 14.19 is being considered in which all resistances are tripled. For input high, estimate all node voltages and branch currents with  $\beta_F = 30$ ,  $\beta_R = 0.01$ ,  $V_{BE} = 0.7 \text{ V}$ , and a load of 1 k $\Omega$  connected to the 5-V supply.
- \*14.19** Repeat the analysis of the circuit suggested in Problem 14.18 with input low (at +0.2 V) and a resistor of 1 k $\Omega$  connected from the output to ground.
- \*14.20** Two TTL gates of the type described in Problem 14.18, one with input high and one with input low, have their outputs accidentally joined. What output voltage results? What current flows in the short circuit?
- \*14.21** A transistor for which  $\beta_F = 50$  and  $\beta_R = 5$  is used for  $Q_3$  in Fig. 14.20. For a base current of 2.5 mA, what is  $V_{CEsat}$  for  $i_L = 0, 1, 10$ , and 100 mA? Estimate  $R_{CEsat}$  at 0.5, 5, and 50 mA.
- 14.22** Consider the output circuit of the gate in Fig. 14.22. What is the output voltage when a current of 2 mA is extracted? What is the (small-signal) output resistance at this current level? Use  $\beta = 50$ .
- 14.23** Consider the output circuit of the gate in Fig. 14.22. For  $\beta = \infty$  and  $V_{CEsat} = 0.2 \text{ V}$ , at what output current does  $Q_4$  saturate? For  $\beta = 20$ , at what current does saturation occur?
- 14.24** If the output of the circuit in Fig. 14.22 is short-circuited to ground, what current flows? Assume high  $\beta$ ,  $V_{CEsat} = 0.2 \text{ V}$ , and  $V_{BE} = V_D = 0.7 \text{ V}$ . What is the minimum value of  $\beta$  for which your analysis holds?



For fall time (on turn-on):  $I_C = 50 \cdot 0.24 = 12mA$   
 $N_0 = 5 - (2k\Omega)(12mA)(1 - e^{-t/RC}) = 19 + 24e^{-t/RC}$   
 Now,  $N_0 = 0.2 + 0.1(5 - 0.2) = 0.68V$ , when  
 $0.68 = 19 + 24e^{-t/RC}$ , or  $e^{-t/RC} = \frac{19.32}{24} = 0.82$   
 or  $-t/RC = -0.198$ , or  $t = 0.198RC$   
 That is,  $t_f = 0.198 \times 2 \times 10^3 \times 10 \times 10^{-12} = 3.97 \mu s$

For rise time (on turn-off):  
 $V_0 = 0.2 + (5 - 0.2)(1 - e^{-t/RC}) = 5 - 4.8e^{-t/RC}$   
 Now,  $N_0$  reaches  $0.2 + 0.1(5 - 0.2) = 0.68V$ , when  
 $0.68 = 5 - 4.8e^{-t/RC}$ , or  $t = -20 \times 10^{-12} \ln \frac{4.32}{4.8} = 2.1$   
 and reaches  $5 - 0.1(5 - 0.2) = 4.52V$ , when  
 $4.52 = 5 - 4.8e^{-t/RC}$ , or  $t = -20 \times 10^{-12} \ln \frac{0.48}{4.8} = 4.60 \mu s$   
 That is,  $t_r = 4.60 - 2.1 = 4.39 \mu s$

[6] For input high:  $I_{B1} = \frac{5-0.7-0.7}{4k\Omega} = 0.9mA$   
 and  $I_{in} = \beta_F I_{B1} = 0.1(0.9) = 90\mu A$   
 $V_o = 0.2V$ , but more precisely:  
 $I_{B3} = 0.7 - 0.09 = 0.61mA$ ;  $I_{C3} = \frac{5-0.2}{2k\Omega} = 2.4mA$   
 $i.e. \beta_F = 2.4/0.61 = 3.92$   
 That  $V_{o1} = V_{C_{sat}} = V_T \ln \left( \frac{1 + (2.4/0.61)/0.1}{1 - 2.4/0.61} \right) = 923mV$

[14]  $I_{B2} = 0.63 + 0.242 = 1.105mA$   
 $I_{B3} = 1.105 - \frac{0.7/3k}{2k\Omega} = 0.812mA$   
 Now, for  $V_{out} = 0.2V$ ,  $I_{C3} = \frac{5-0.2}{1k\Omega} = 4.8mA$   
 $\beta_{F11} = \frac{0.63}{0.812} = 5.52$   
 $i.e. V_{C_{sat}} = 25 \ln \left( \frac{1 + (5.52+1)/0.01}{1 - 5.52/30} \right) = 167mV$   
 ie  $V_{C3} = V_0 = 0.17V$   
 and  $V_{C4} = 0.5V$ ,  $I_{in} = 0.725 \times 0.01 = 7.25\mu A$ .

[19] All resistors in Fig 14.19 are tripled  
 For  $v_T$  low ( $0.2V$ ):  
 $V_{C1} = 0.2V, V_{B1} = 0.9V, I_{B1} = \frac{5-0.2}{3k\Omega} = 0.72mA$   
 Also  $I_{C1} = \beta_F = 0, V_{C2} = 25 \ln \left( \frac{1 + (0.72/0.01)}{1 - 0.72} \right) = 157mV$   
 $i.e. V_1 = 0.2 + 0.015 = 0.215V = V_{B2}$   
 and  $V_{E2} = 0V$

$\therefore V_o = \frac{1}{1.155} \times 3.6 = 3.12V$   
 $V_{C4} = 3.82V$   
 $V_{B4} = 4.52V$   
 $I_{C4} = \frac{3.12}{1k\Omega} = 3.12mA$   
 $V_{C4} = 5 - 0.320(3.12) = 4.78V$ , Note saturated!  
 (next)

$$I_{E4} = \frac{5 - 1.4 - 0.7}{4.8} = \frac{2.6}{4.8} = 0.54 \text{ mA}$$

14

$$\therefore 0.75 - 0.202 V_T + 0.51 - 2.56 V_T = 11.24 - 2.77 V_T$$

Now,  $27.6 > 11.24 - 2.77 V_T$  for  $V_T > 0$ .

Thus  $Q_3$  must also saturate, and  $V_T = 0.2V = V_0$ , and the short-circuit current =  $11.24 - 2.77(0.2) / 10.7 = 10.7$

More precisely - for  $\beta_F = \frac{10.7}{0.921} = 11.62$  mA

$$\therefore V_{CE4sat} = V_T \ln \left( \frac{1 + (0.51 - 0.7) / 0.2}{1 - 11.62 / 10.7} \right)$$

$$= 25 \ln \left( \frac{13.2}{4.12} \right) = 191 \text{ mV}$$

$$\therefore V_0 = 0.191 \text{ V}$$

21 For  $i_L = 0$ ,  $\beta_F = 0$ , and

$$V_{CE1sat} = 25 \ln \left( \frac{1 + (0.41) / 5}{1 - 0.4 / 50} \right) = 25 \ln 1.12 = 4.56 \text{ mV}$$

For  $i_L = 1 \text{ mA}$ ,  $\beta_F = 1/2.5 = 0.4$ , and

$$V_{CE1sat} = 25 \ln \left( \frac{1 + (0.41 - 0.1) / 5}{1 - 0.4 / 50} \right) = 25 \ln \frac{1.32}{0.91} = 6.37 \text{ mV}$$

For  $i_L = 10 \text{ mA}$ ,  $\beta_F = 10/2.5 = 4$ , and

$$V_{CE1sat} = 25 \ln \left( \frac{1 + (4 - 0.1) / 5}{1 - 4 / 50} \right) = 25 \ln \frac{3.1}{0.91} = 19.4 \text{ mV}$$

For  $i_L = 100 \text{ mA}$ ,  $\beta_F = 100/2.5 = 40$ , and

$$V_{CE1sat} = 25 \ln \left( \frac{1 + (40 - 0.1) / 5}{1 - 40 / 50} \right) = 25 \ln \frac{5.1}{0.2} = 95 \text{ mV}$$

At  $0.5 \text{ mA}$ :  $R_{CE1sat} = \frac{1.37 - 0.5}{0.5} = 2.62 \text{ k}\Omega$

At  $5 \text{ mA}$ :  $R_{CE1sat} = \frac{19.4 - 0.5}{5} = 3.60 \text{ k}\Omega$


At  $50 \text{ mA}$ :  $R_{CE1sat} = \frac{95 - 0.5}{50} = 1.78 \text{ k}\Omega$

25 The value of  $R_2$  affects the output voltage for  $V_T = 1.2 \text{ V}$  (point C of Fig 14.23). 14

For  $R_2 = 1 \text{ k}\Omega$ ,  $V_0 = 2 \text{ V}$

For  $R_2 = 0.5 \text{ k}\Omega$ ,  $V_0$  falls twice as much, ie by  $2(3.7 - 2.7) = 2 \text{ V}$  to  $3.7 - 2.7 = 1.0 \text{ V}$

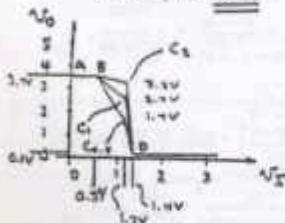For  $R_2 = 2.0 \text{ k}\Omega$ ,  $V_0$  falls by half as much, by  $0.5 \text{ V}$ , to  $2.2 \text{ V}$



Apparently  $R_2 = 2.0 \text{ k}\Omega$  gives the best transfer characteristic, being sharper (but is slow).

26 All but  $Q_1$  are active with  $V_{BE} = 0.7 \text{ V}$

(a)  $V_T = 0.7 + 0.7 - 0.1 = 1.2 \text{ V}$

Correspondingly -  $I_{E1} = (5 - 0.7 - 0.1) / 4 = 0.75 \text{ mA}$   
Drop in  $200 \text{ }\Omega$  resistor is  $(0.75)(0.77) = 0.56 \text{ V}$

$$\therefore V_0 = 1.2 - 0.56 = 0.64 \text{ V}$$


Correspondingly,  $V_{BE} = 0.15 \text{ V} + 0.7 + 0.1 = 1.0 \text{ V}$  and  $I_{E2} = (5 - 1.0) / 1.18 = 1.53 \text{ mA}$

Apparently  $Q_1$  and  $Q_3$  will be conducting a similar current,  $I$  in the collector of  $Q_3$ , and  $I = 0.75$  mA in the emitter of  $Q_4$ :

$$\text{i.e. } (1.53 - \frac{0.75 + 0.15}{1.18}) \frac{1}{100} = \frac{0.7}{1} \text{ mA} = I$$

14

22

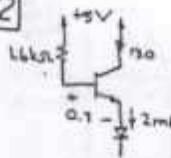

Assume linear operation:

$$V_B = 5 - \frac{1.6 \times 3}{51} = 4.94 \text{ V}$$

$$V_C = 5 - 0.13 \times 2 = 4.74 \text{ V}$$

$$V_E = 4.94 - 0.7 = 4.24 \text{ V}$$

$$V_O = 4.24 - 0.7 = 3.54 \text{ V}$$

14

Assume  $V_D = 0$  for the diode (ie it is a diode-connected transistor), and  $V_D + V_E = \frac{25}{51} \text{ V}$

$$\therefore R_{out} = \frac{25}{2} = \frac{25}{2} + \frac{1600}{51} = 12.5 + 31.2 = 31.4 \text{ }\Omega$$

$$= 56 \text{ m}\Omega$$

23

For  $\beta = \infty$ , saturation occurs when the drop across  $130 \text{ }\Omega$  is  $0.7 - 0.2 = 0.5 \text{ V}$ , ie

$$\text{for } I = 0.5 / 0.130 = 3.85 \text{ mA}$$

For  $\beta = 20$ , and output  $I$ ,

$$\frac{I}{21} = 1.6 + 0.7 - 0.2 = \frac{20}{21} I (0.13)$$

$$1.6 I = 10.5 = 2.6 I$$

$$I = 10.5 \text{ mA.}$$

24

For high  $\beta$ , short-circuit current is  $(5 - 0.7 - 0.2 - 0) / 130 \text{ }\Omega = 31.5 \text{ mA}$

Now, for the output at 0 V,  $I_{B4} = \frac{5 - 0.7 - 0.2}{1.18 \text{ }\Omega} = 2.25 \text{ mA}$

Thus,  $\beta$  for which saturation occurs is  $\frac{31.5}{2.25} = 14$   
That is, the minimum  $\beta$  for 31.5 mA is 14

$$\text{or } (1.516 - I / 50 - 0.7) 50 = I$$

$$(0.756 - I / 50) 50 = I, \quad 4.28 - I = I, \quad 2I = 4.28 \text{ mA}$$

Check saturation of  $Q_4$ :

$$V_{CE4} = 5 - 0.13(2.14 - 0.7) \frac{50}{51} = 2.31 \text{ V}$$

while  $V_{BE4} = 2.55 \text{ V}$ .

Thus  $V_{AC4} = 2.55 - 2.31 = 0.24$  shows  $Q_4$  to be active!

Overall:  $V_{C3} = 1.15 \text{ V}$ ,  $V_{E1} = 1.50 \text{ V}$ ,  $V_{B1} = 2.0 \text{ V}$ ,  $V_{C1} = 1.4 \text{ V}$ ,

$$V_{E2} = 0.7 \text{ V}$$
,  $V_{B2} = 1.15 \text{ V}$ ,  $V_{B4} = 2.55 \text{ V}$ ,  $V_{C4} = 2.31 \text{ V}$ ,

$$I_{E3} = 22.5 \text{ mA}$$
,  $I_{E4} = 21.1 \text{ mA}$ ,  $I_{E2} = 1.14 \text{ mA}$ ,

$$I_{E1} = 0.78 \text{ mA.}$$

(b) For  $Q_2$ ,  $V_{E2} = \frac{25}{1.14} = 21.9 \text{ }\Omega$ ,  $V_{T2} = 1.12 \text{ k}\Omega$

$$Q_2 : V_{E2} = \frac{25}{21.9} = 1.12 \text{ }\Omega \sim V_{T2} = 57.2 \text{ }\Omega$$

$$Q_1 : V_{E1} = \frac{25}{1.18} = 1.12 \text{ }\Omega \sim V_{T1} = 60.4 \text{ }\Omega$$

For gain: There are two paths to the output, one via  $Q_2$  and one via  $Q_4$ , in which output currents, and gains, add. The highest-gain path (and the one most affecting the voltage gain) is via  $Q_2$  and  $Q_4$ .

Thus, for a  $200 \text{ }\Omega$  load (the input, to which the  $200 \text{ }\Omega$  feedback resistor is connected, being a zero-ohm source); working from the output base:

$$\text{Gain } B_2 \text{ to } V_0 = \frac{200}{200 + 2(1.18)} = 0.988 \text{ V/V}$$

$$R_{out} = 51(200 + 2(1.18)) = 10.3 \text{ k}\Omega$$

$$\text{Gain } B_4 \text{ to } V_0 = \left( -\frac{25}{51} \frac{10.3}{1.14} \right) / (2.14 + 0.7) = -17.8 \text{ V/V}$$

Thus overall gain is about  $-0.99(17.8) = -17.6 \text{ V/V}$

14