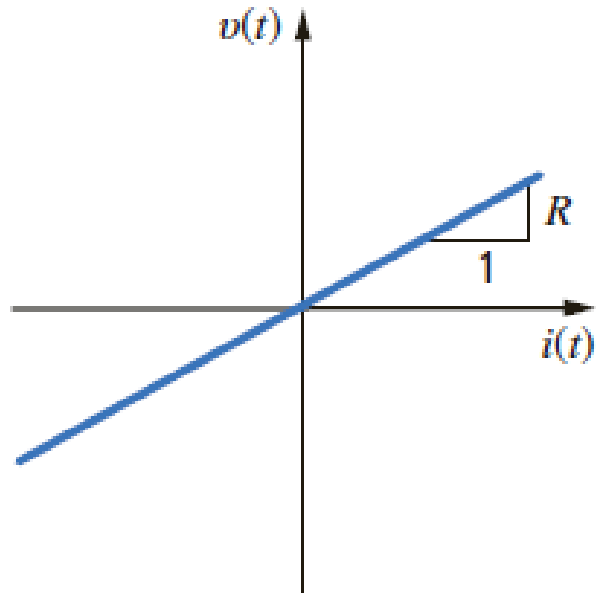



Last Lecture → Ohm's Law

8/16/2019

States that the voltage across a resistance is directly proportional to the current flowing through it.



$$v(t) = R \cdot i(t)$$

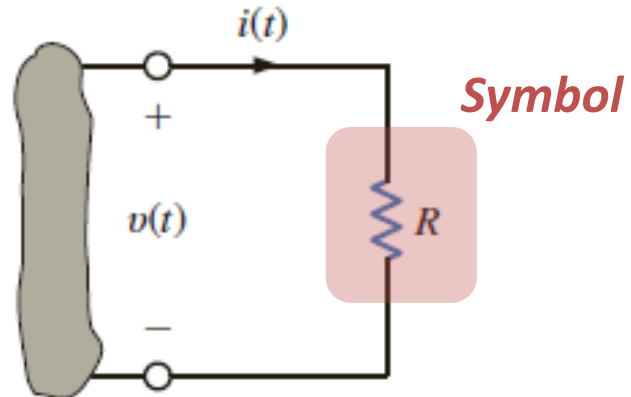

- **Resistance** [$\Omega = V/A$]

$$R = \frac{v(t)}{i(t)}$$

- **Conductance** [$S = A/V$]

$$G = \frac{1}{R} = \frac{i(t)}{v(t)}$$

- **Power Dissipation** [W]

$$\begin{aligned} p(t) &= v(t) \cdot i(t) = R \cdot i(t)^2 = \frac{v(t)^2}{R} \\ &= \frac{i(t)^2}{G} = G \cdot v(t)^2 \end{aligned}$$

Last Lecture → Kirchhoff's Laws

8/16/2019

KCL- the algebraic sum of the all the currents entering any node is zero

$$\sum_{h=1}^K i_h^{in}(t) = 0 \quad \longrightarrow \quad \sum_{j=1}^N i_j^{in}(t) = \sum_{i=1}^M i_i^{out}(t)$$


KVL- the algebraic sum of the voltages around any loop is zero

$$\sum_{h=1}^K v_h(t) = 0 \quad \longrightarrow \quad \sum_{j=1}^N v_j^{\uparrow}(t) = \sum_{i=1}^M v_i^{\downarrow}(t)$$

Learning Assessment E2.9


8/16/2019

... find the voltage V_{bd} .

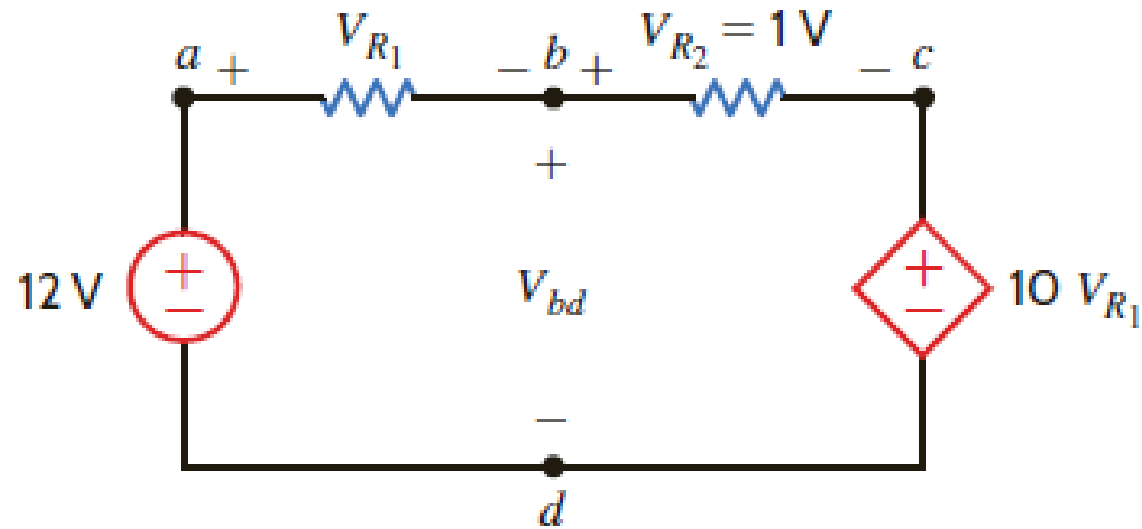

Single Loop Circuits → Voltage Division

8/16/2019

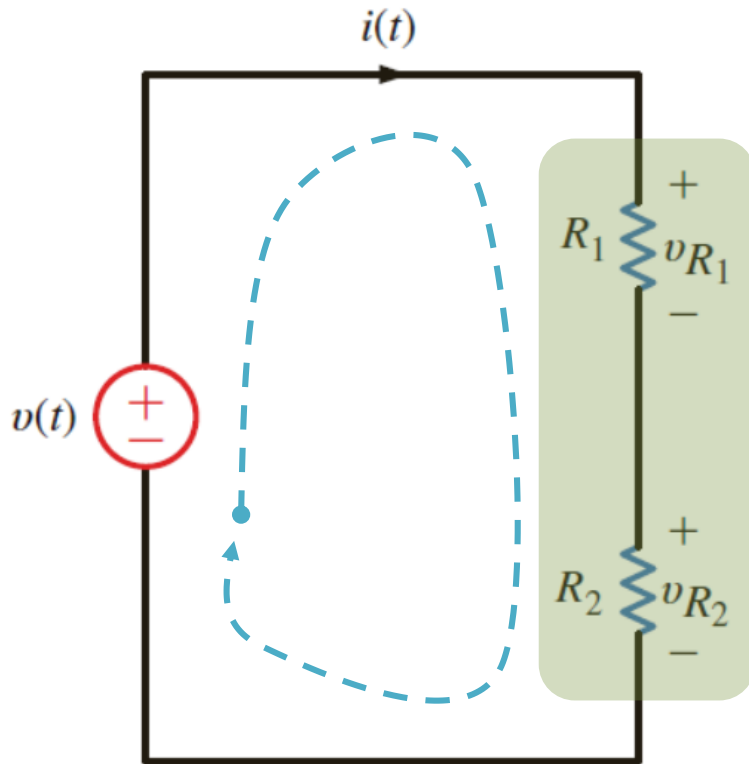

* $I_{R_1} = I_{R_2} = i(t)$
 $\therefore R_1$ and R_2 are in series


$$\begin{aligned}
 & \bullet \text{ KVL: } v(t) = v_{R_1} + v_{R_2} \\
 & \bullet \text{ Ohm's: } \begin{cases} v_{R_1} = R_1 \cdot i(t) \\ v_{R_2} = R_2 \cdot i(t) \end{cases} \quad \left. \begin{array}{l} v_{R_1} = ? \\ v_{R_2} = ? \end{array} \right\} \therefore i(t) = \frac{v(t)}{R_1 + R_2} \\
 & \therefore v_{R_1} = \frac{R_1}{R_1 + R_2} \cdot v(t) \\
 & \qquad \qquad \qquad v_{R_2} = \frac{R_2}{R_1 + R_2} \cdot v(t)
 \end{aligned}$$

The source voltage $v(t)$ is divided between the resistors R_1 and R_2 in direct proportion to their resistances.

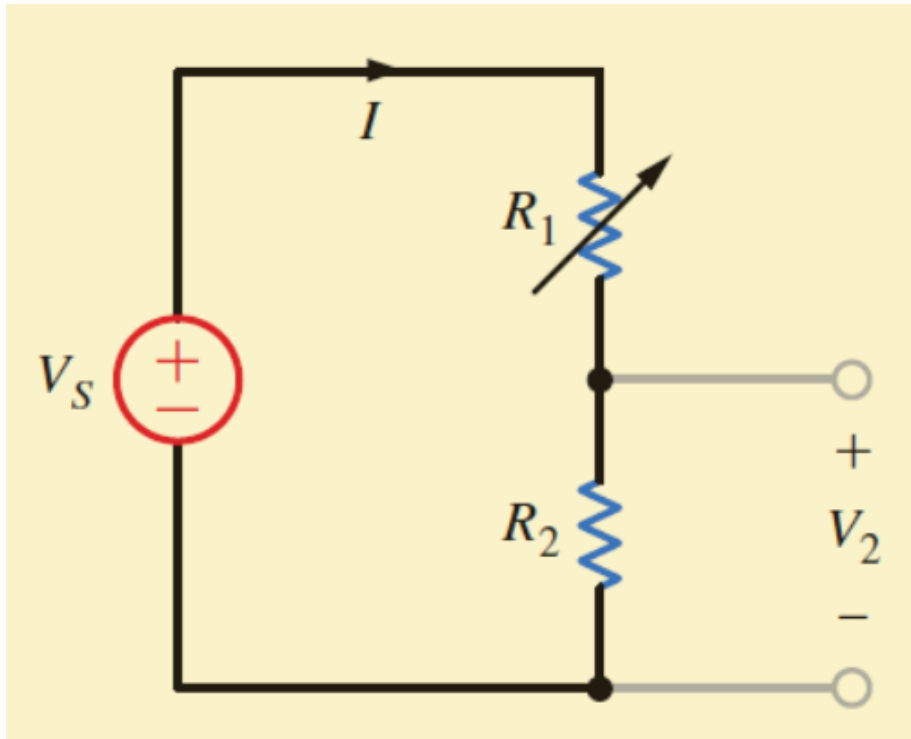Example 2.13

8/16/2019


Assuming $V_s=9\text{V}$, $R_1=90\text{k}\Omega$, and $R_2=30\text{k}\Omega$, examine the change in both the voltage across R_2 and the power absorbed in the resistor as R_1 is changed from $90\text{k}\Omega$ to $15\text{k}\Omega$.



Single Loop Circuits → Multiple Source/Resistor Networks

8/16/2019

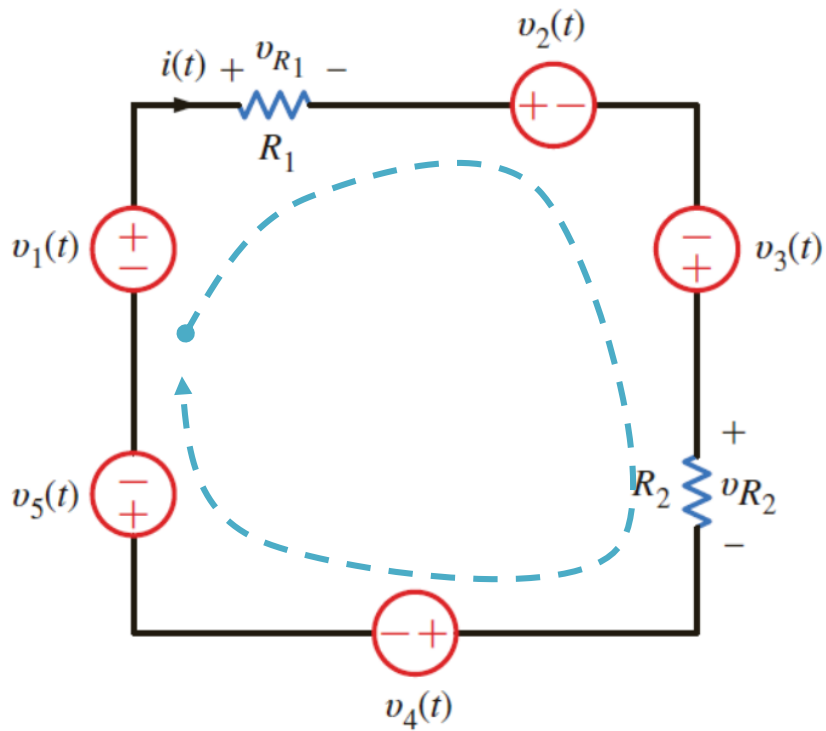- KVL: $v_1(t) - v_{R1} - v_2(t) + v_3(t) - v_{R2} - v_4(t) - v_5(t) = 0$




$$v_1(t) - v_2(t) + v_3(t) - v_4(t) - v_5(t) = v_{R1} + v_{R2}$$

$$v_1(t) - v_2(t) + v_3(t) - v_4(t) - v_5(t) = i(t) \cdot [R_1 + R_2]$$

$v(t)$

R_S


Equivalent Circuit

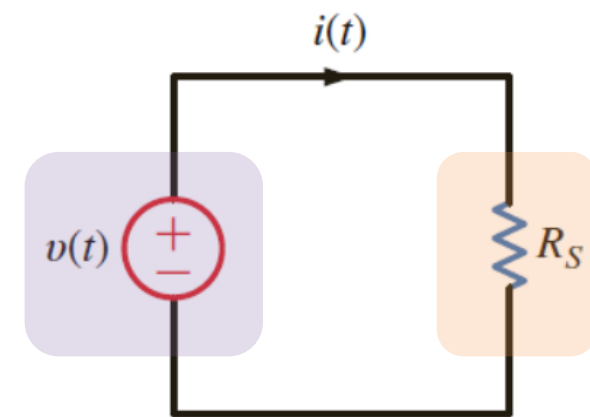


Single Loop Circuits → Multiple Source/Resistor Networks

8/16/2019

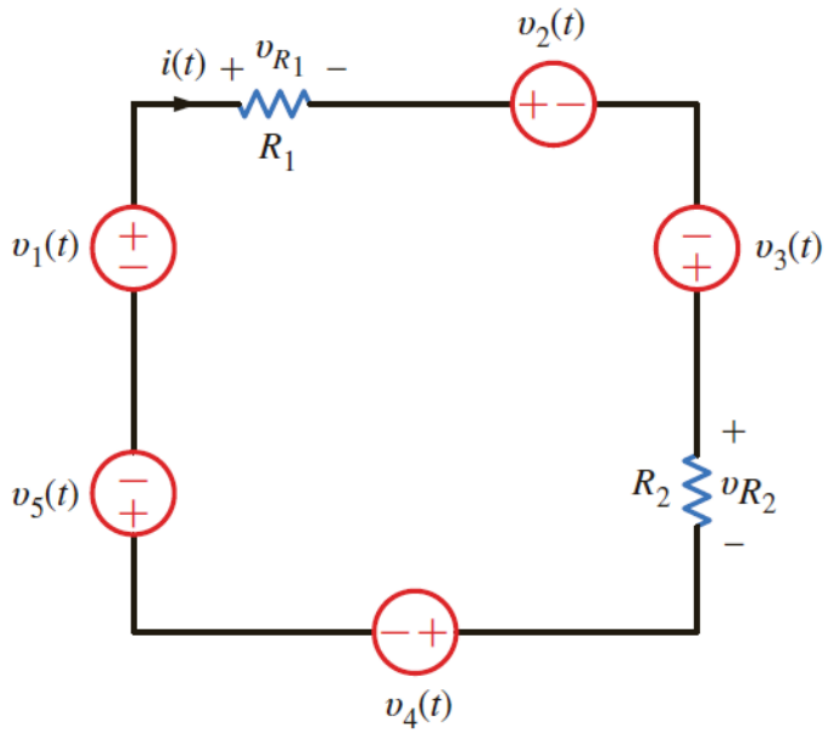- ∴ The sum of several voltage source in series can be replaced by one source whose value is the algebraic sum of the individual source
- ∴ The equivalent resistance of N resistors in series is simply the sum of the individual resistances.



$$R_S = \sum R_1 + R_2 + \dots + R_N$$

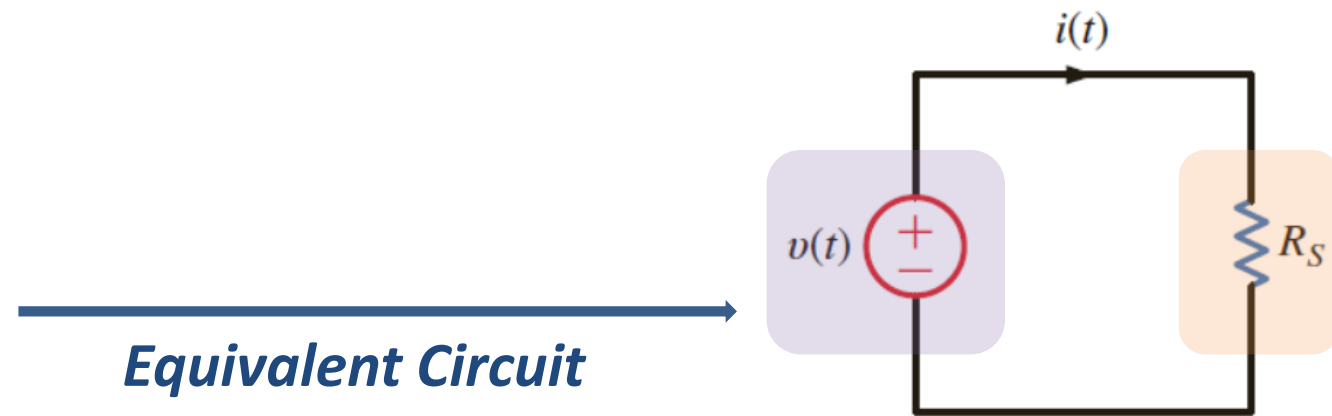


Equivalent Circuit

Learning Assessment E2.11


8/16/2019

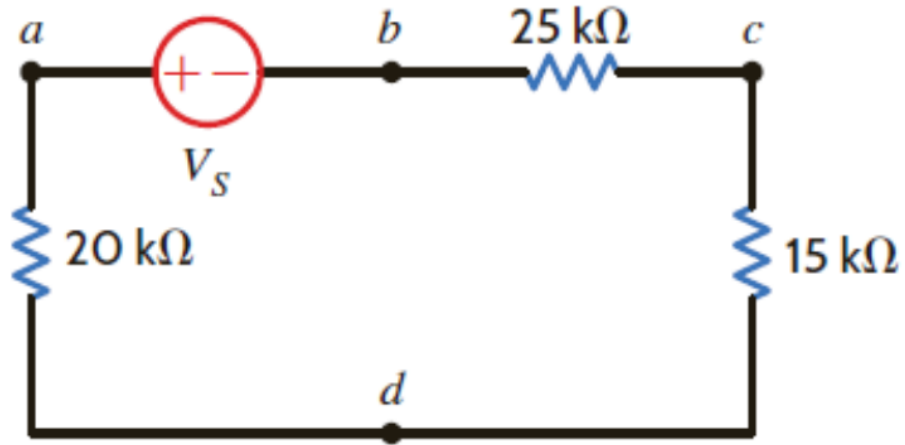In the network provided, if V_{ad} is 3V, find V_s .



Current Division

8/16/2019

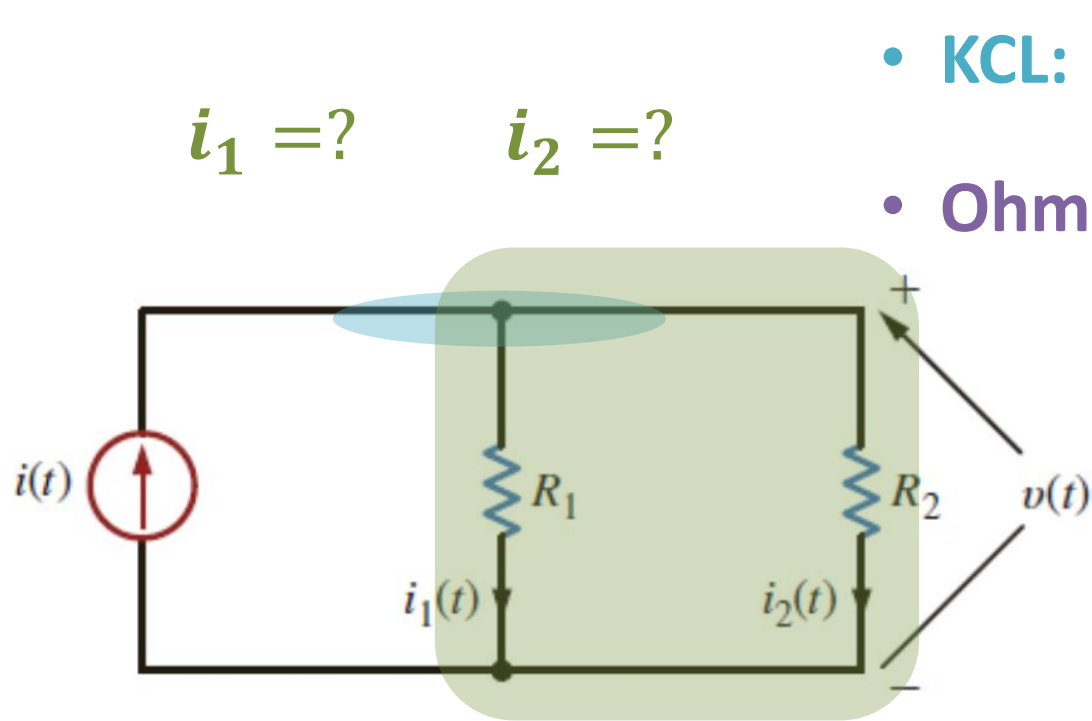

- KCL: $i(t) = i_1(t) + i_2(t)$

- Ohm's: $i_1(t) = \frac{v(t)}{R_1}$

- $i_2(t) = \frac{v(t)}{R_2}$

$$\therefore v(t) =$$

$$i(t) \cdot \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$\therefore i_1(t) = \frac{R_2}{R_1 + R_2} \cdot i(t)$$

$$i_2(t) = \frac{R_1}{R_1 + R_2} \cdot i(t)$$

* $V_{R_1} = V_{R_2} = v(t)$

$\therefore R_1$ and R_2 are in parallel


Single Loop Circuits → Multiple Source/Resistor Networks

8/16/2019

- KCL: $i_1(t) - i_2(t) - i_3(t) + i_4(t) - i_5(t) - i_6(t) = 0$

$$\hookrightarrow i_1(t) - i_3(t) + i_4(t) - i_6(t) = i_2(t) + i_5(t)$$
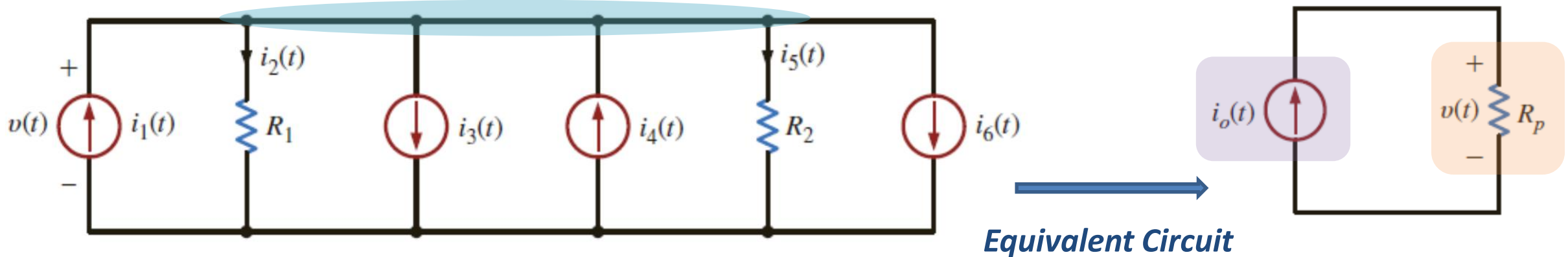
$$\underbrace{i_1(t) - i_3(t) + i_4(t) - i_6(t)}_{i_o(t)} = v(t) \cdot \underbrace{\left[\frac{1}{R_1} + \frac{1}{R_2} \right]}_{1/R_p}$$



Single Loop Circuits → Multiple Source/Resistor Networks


8/16/2019

- ∴ The sum of several current sources in parallel can be replaced by one source whose value is the algebraic sum of the individual source
- ∴ The reciprocal of the equivalent resistance of N resistors in parallel is equal to the sum of the reciprocal of the individual resistances.

$$\frac{1}{R_p} = \sum \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

For 2 resistances in parallel R_p can be expressed as...


$$R_p = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

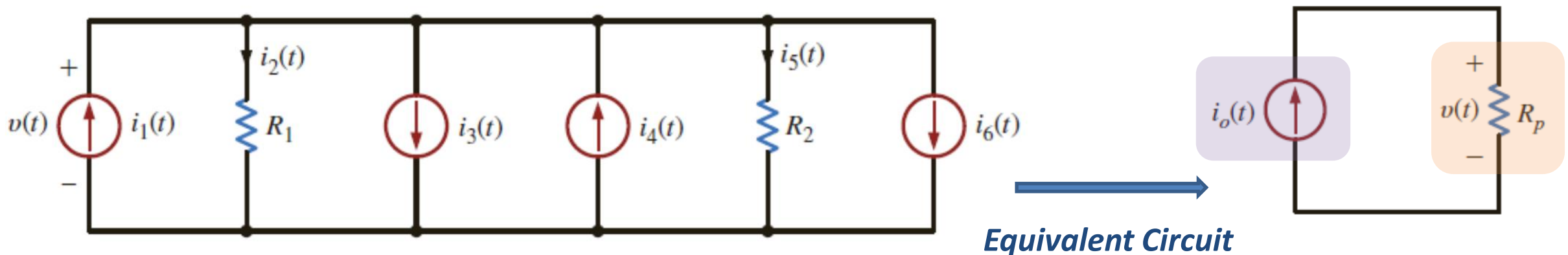

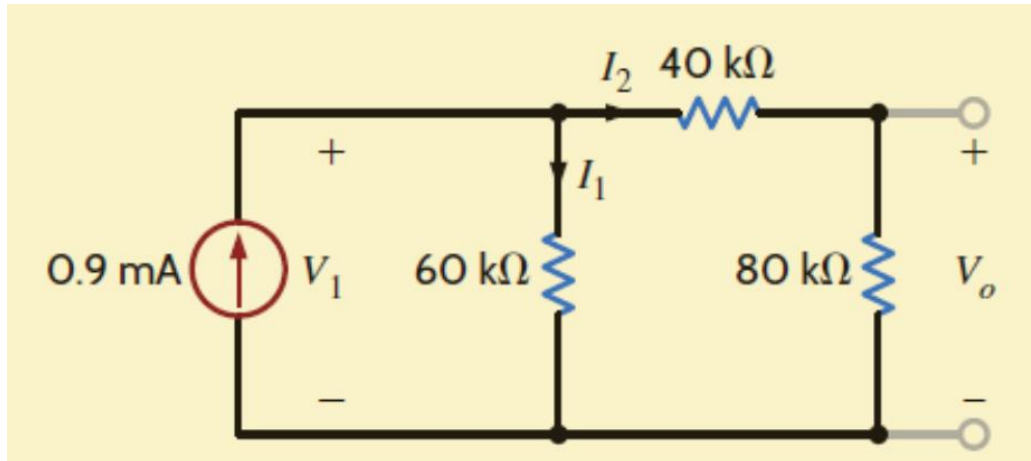Example 2.17

8/16/2019


For the given network find I_1 , I_2 , and V_o .



Series/Parallel Resistor Combinations

8/16/2019

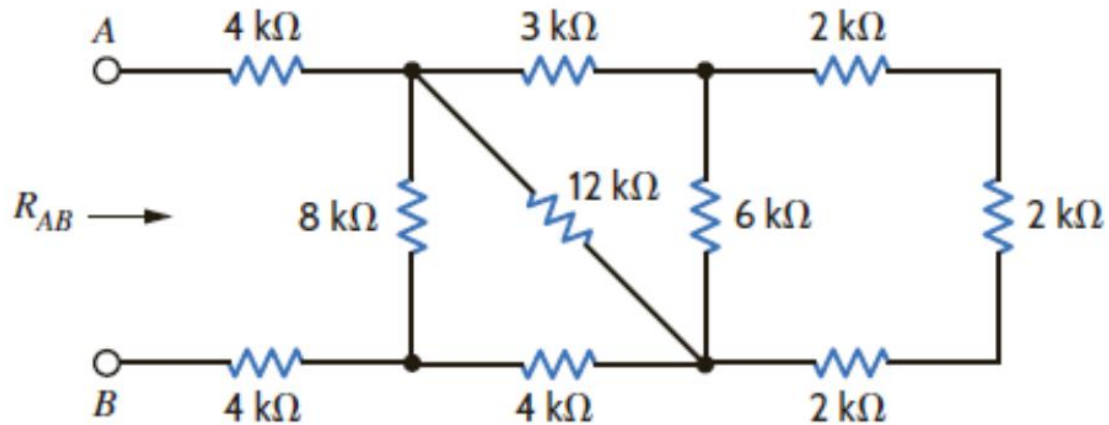E2.16: Find R_{AB} in the provided network.



- **Series:** $R_S = R_1 + R_2 + \dots + R_N$
- **Parallel:** $\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$

Learning Assessment E2.22

8/16/2019

Find V_0 , V_1 , and V_2 in the network provided.

