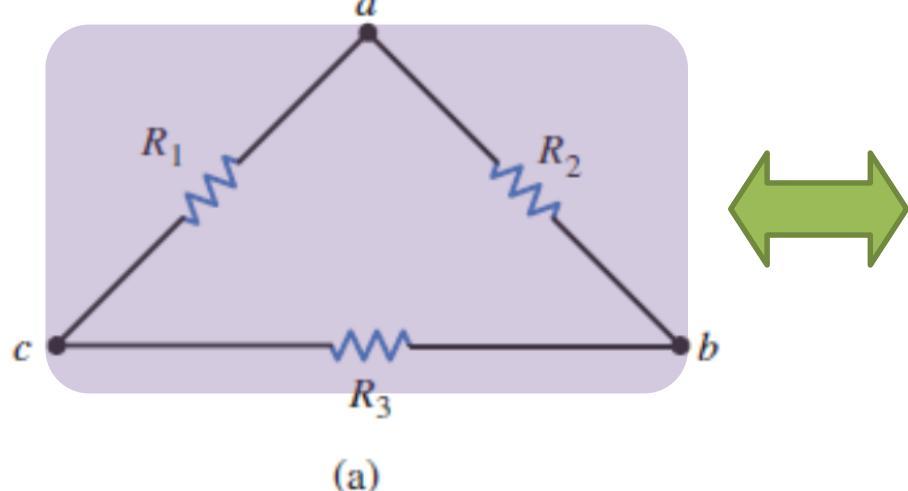


Last Lecture → Wye \leftrightarrow Delta Transformations

8/23/2019

For the two networks to be equivalent at each corresponding pair of terminals, it is necessary that the resistance at the corresponding terminals be equal (e.g., the resistance at terminals a and b with c open-circuited must be the same for both networks).



$$\Delta \leftarrow Y \quad \left\{ \begin{array}{l} R_1 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_b} \\ R_2 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_c} \\ R_3 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_a} \end{array} \right.$$

$$Y \leftarrow \Delta \quad \left\{ \begin{array}{l} R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3} \\ R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3} \\ R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3} \end{array} \right.$$


Last Lecture → Nodal Analysis

8/23/2019

- 1) Identify #of nodes: 3 node circuit
- 2) Select reference node: bottom node, 3
- 3) Label other node voltages: v_1, v_2
- 4) Identify branch currents: i_1, i_2, i_3
- 5) Apply KCL to nodes: 1, 2 → 2 independent equations

assume:

$I_A = 1mA$	$R_1 = 12k\Omega$
$I_B = 4mA$	$R_2 = 6k\Omega$
	$R_3 = 6k\Omega$

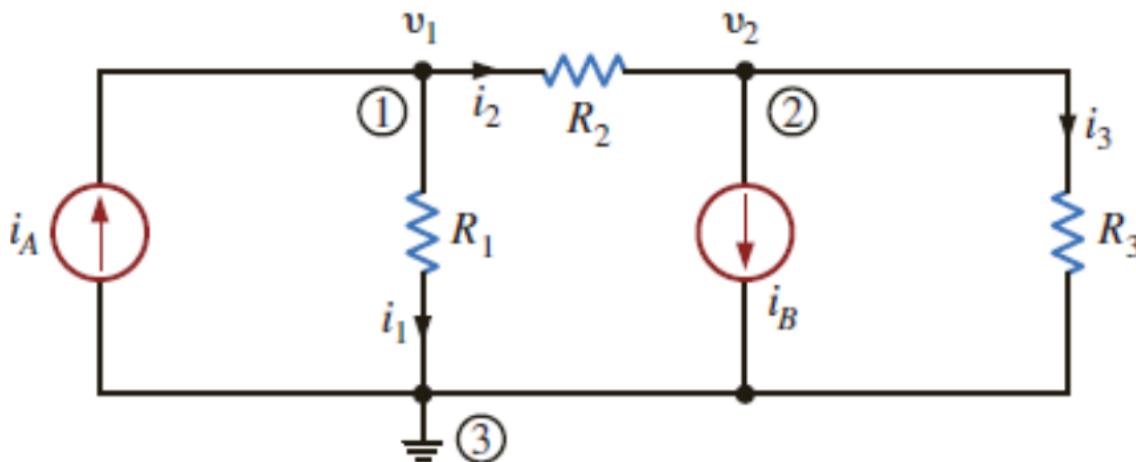

KCLs: $I_A = I_1 + I_2 = \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} = V_1 \left[\frac{1}{R_1} + \frac{1}{R_2} \right] - V_2 \left[\frac{1}{R_2} \right]$

$$I_B = I_2 + I_3 = \frac{V_1 - V_2}{R_2} - \frac{V_2}{R_3} = V_1 \left[\frac{1}{R_2} \right] - V_2 \left[\frac{1}{R_2} + \frac{1}{R_3} \right]$$

matrix eq.


$$\begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} \frac{1}{R_1 \parallel R_2} & -\frac{1}{R_2} \\ \frac{1}{R_2} & -\frac{1}{R_2 \parallel R_3} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

Nodal Analysis → Example 3.2

8/23/2019

Write the equations in matrix form for the provided circuit.

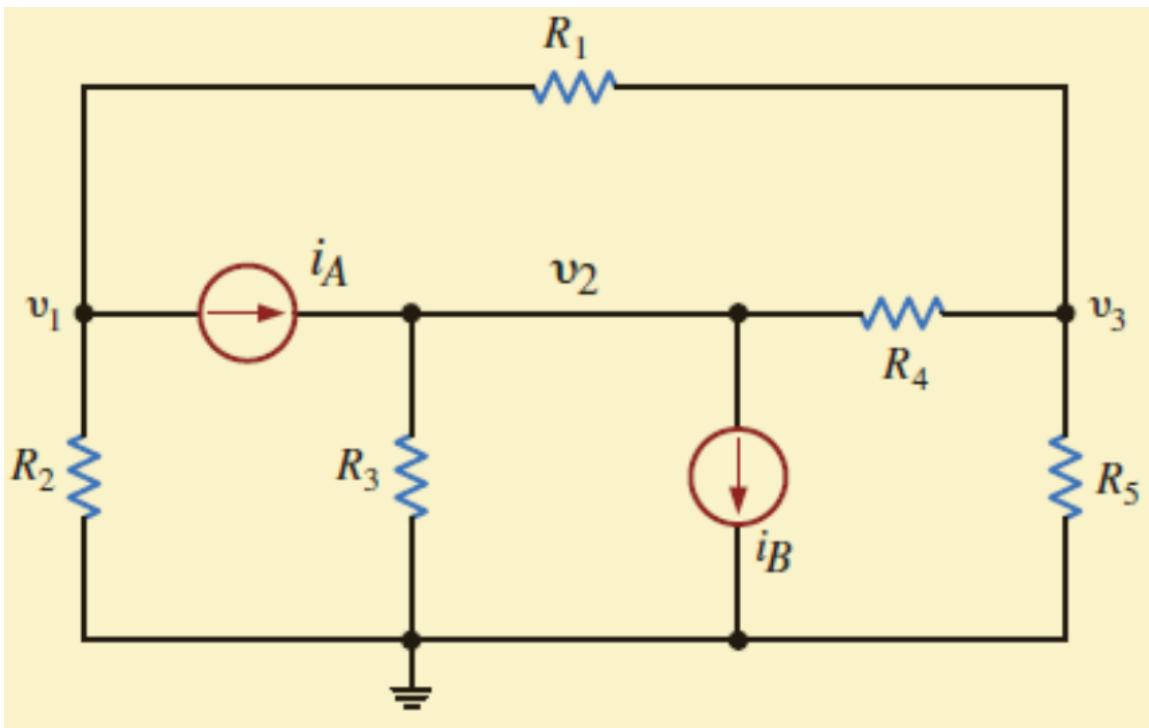Assume $R_1=R_2=2\text{k}\Omega$, $R_3=R_4=4\text{k}\Omega$, $R_5=1\text{k}\Omega$, $i_A=4\text{mA}$, and $i_B=2\text{mA}$.



- 1) Identify #of nodes
- 2) Select reference node
- 3) Label other node voltages
- 4) Identify branch currents
- 5) Apply KCL to nodes


matrix eq.

$$\begin{bmatrix} I_A \\ I_A - I_B \\ 0 \end{bmatrix} = \begin{bmatrix} -\frac{1}{R_1 \parallel R_2} & 0 & \frac{1}{R_1} \\ 0 & \frac{1}{R_3 \parallel R_4} & -\frac{1}{R_4} \\ \frac{1}{R_1} & \frac{1}{R_4} & -\frac{1}{R_1 \parallel R_4 \parallel R_5} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

Nodal Analysis → with Dependent Current Sources

8/23/2019

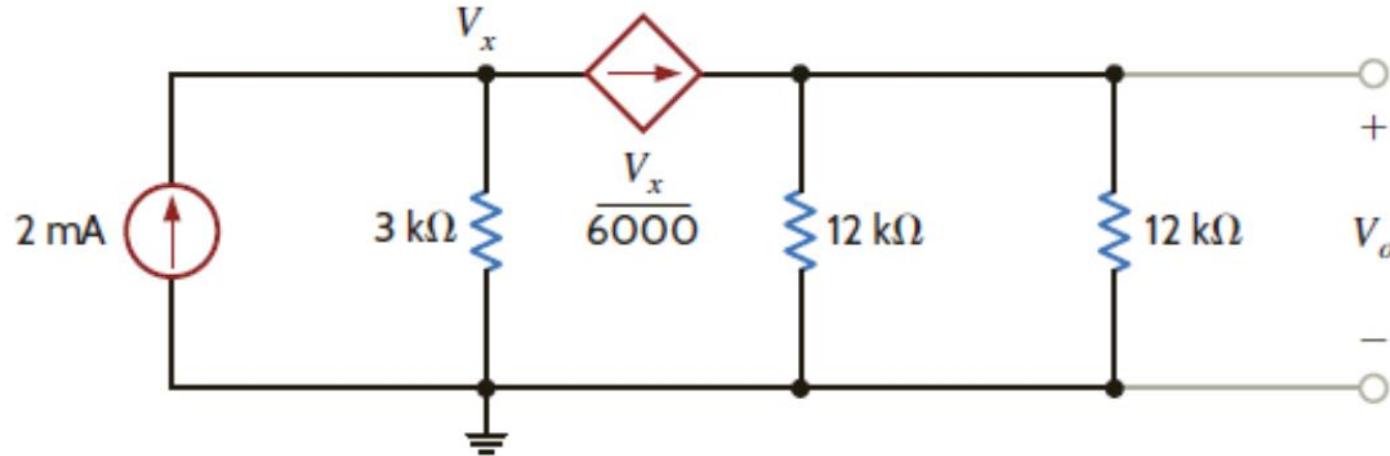E3.3: Find the voltage V_o in the network provided.




$$\left. \begin{aligned} KCL @ V_x &\rightarrow 2m - \frac{V_x}{3k} - \frac{V_x}{6k} = 0 \\ KCL @ V_0 &\rightarrow \frac{V_x}{6k} - \frac{V_0}{12k} - \frac{V_0}{12k} = 0 \end{aligned} \right\} \begin{aligned} V_x &= 4 V \\ V_0 &= V_x = 4 V \end{aligned}$$

Nodal Analysis → with Independent Voltage Sources

8/23/2019

Supernode: KCL at the surface (dashed) around the voltage source.

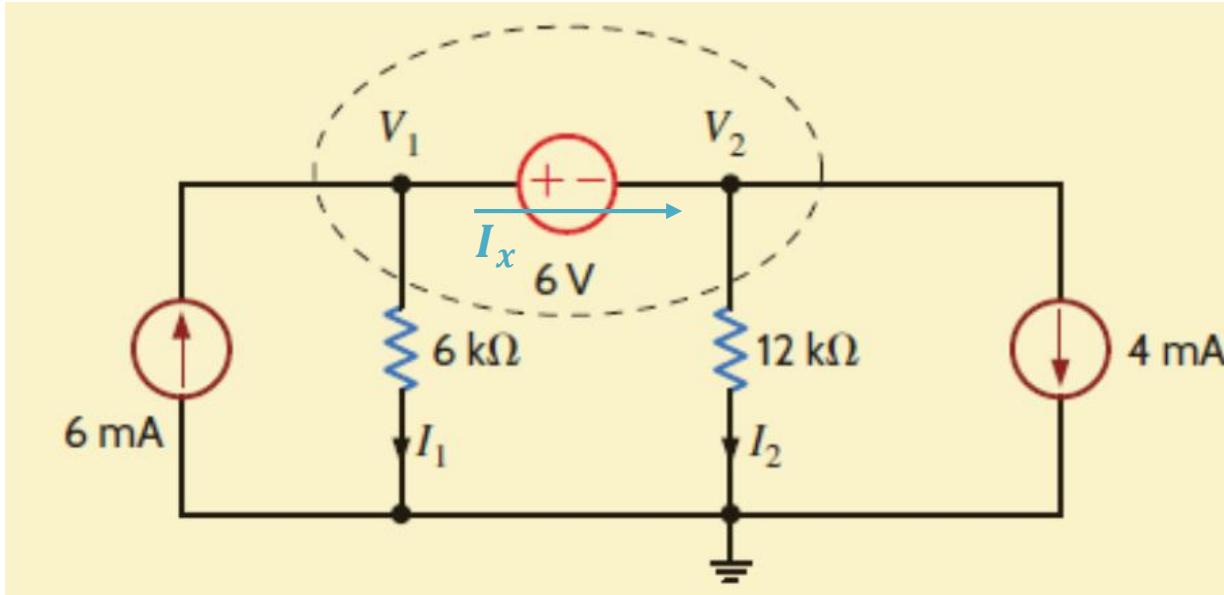Constraint equation: establishes the difference in potential between two nodes.



$$\left. \begin{aligned} KCL @ V_1 &\rightarrow 6m - \frac{V_1}{6k} - I_x = 0 \\ KCL @ V_2 &\rightarrow I_x - \frac{V_2}{12k} - 4m = 0 \end{aligned} \right\}$$

$$\begin{aligned} V_1 &= 10 \text{ V} \\ V_2 &= 4 \text{ V} \\ &\hline \end{aligned}$$


Constraint Eq. → 6 = V₁ - V₂

$$KCL @ Supernode \rightarrow 6m - \frac{V_1}{6k} - \frac{V_2}{12k} - 4m = 0$$

Nodal Analysis → with Independent Voltage Sources

8/23/2019

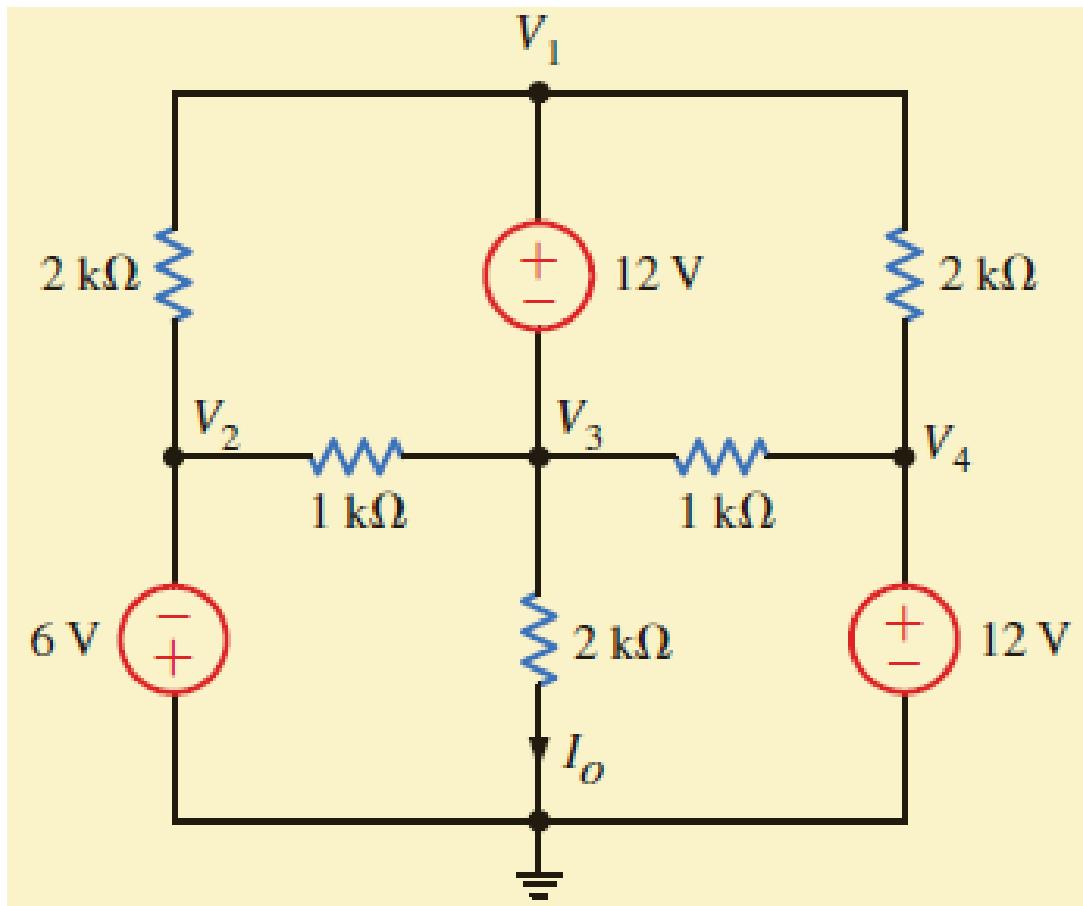Example 3.7: Determine the current I_0 in the provided network.



KCL @ supernode

$$\frac{-6 - V_1}{2k} + \frac{-6 - V_3}{1k} = \frac{V_1 - 12}{2k} + \frac{V_3 - 12}{1k} + \frac{V_3}{2k}$$

Constraint

$$12 = V_1 - V_3$$


$$V_3 = -\frac{6}{7} \text{ V}$$

$$I_0 = \frac{V_3}{2k} = -\frac{3}{7} \text{ mA}$$

Nodal Analysis → with Dependent Voltage Sources

8/23/2019

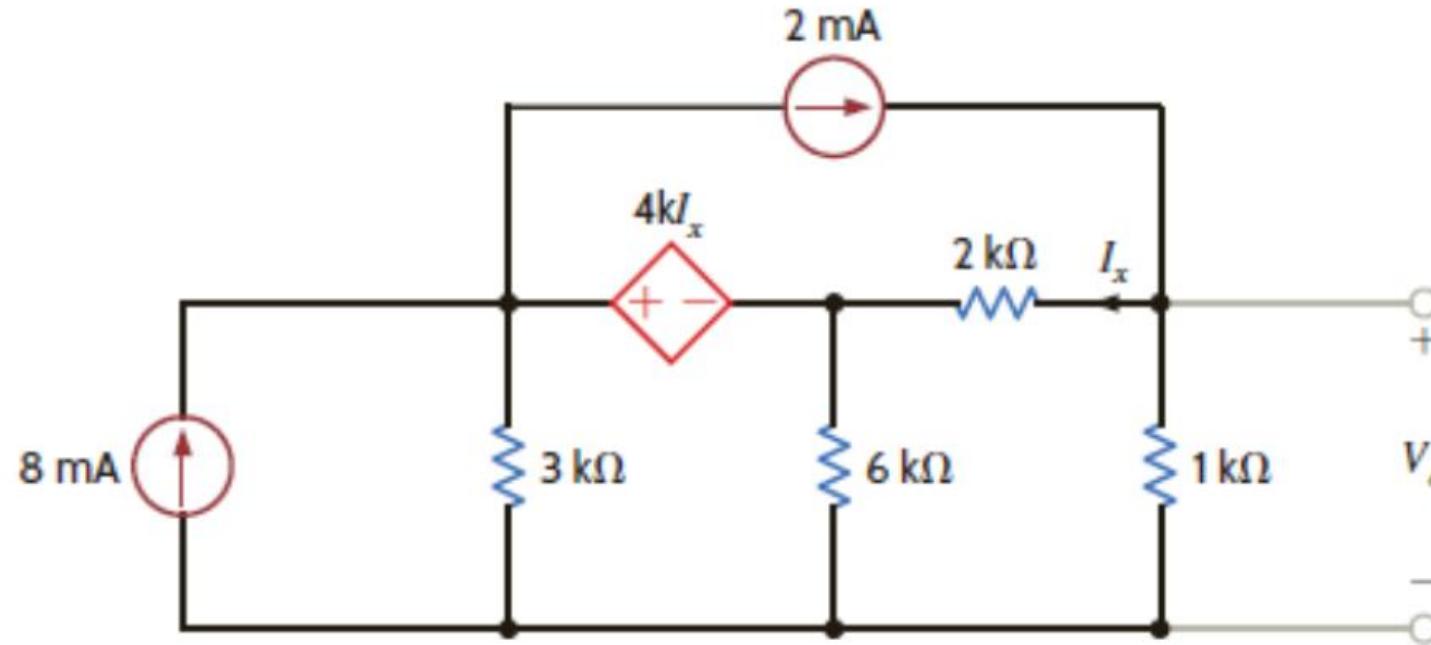E3.12: Determine the current V_0 in the provided network.



KCL @ supernode

$$8m - 2m = \frac{V_1}{3k} + \frac{V_2}{6k} + \frac{V_2 - V_0}{2k}$$

KCL @ node 2

$$2m = \frac{V_0}{1k} - \frac{V_2 - V_0}{2k}$$

Constraint

$$I_x = \frac{V_0 - V_2}{2k}$$

Dependent Source

$$V_1 - V_2 = 4k \cdot I_x$$

Mesh Analysis

8/23/2019

Alternative # 1

- $B \rightarrow \# \text{ of branches}$
- $N \rightarrow \# \text{ of nodes}$
- $B-N+1 \rightarrow \# \text{ independent simultaneous equations}$

Alternative # 2

- $M \rightarrow \# \text{ of independent loops in a planar circuit}$
- $M \rightarrow \# \text{ independent simultaneous equations}$



$$B = 8 \quad M = 4$$


$$N = 5$$

$$\# \text{ Eq.} = 4$$

Establish the currents
around the loops


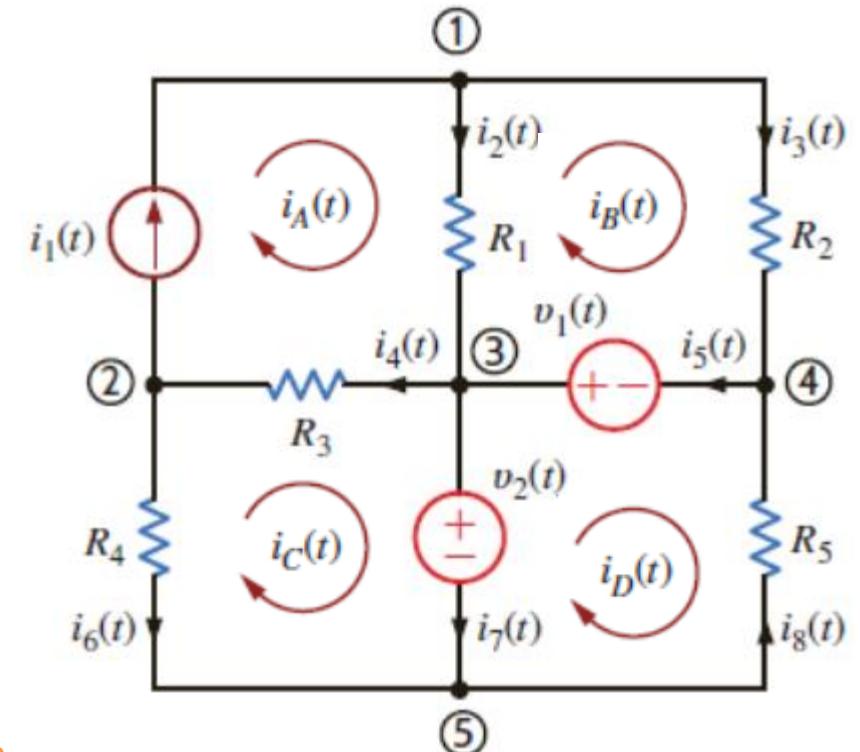
$$\begin{aligned} i_A(t) &= i_1(t) \\ v_1 &= V_{R_1} + V_{R_2} \\ -v_2 &= V_{R_3} + V_{R_4} \\ v_2 - v_1 &= V_5 \end{aligned}$$



Express voltages in terms of
currents: $i_A(t)$, $i_B(t)$, $i_C(t)$, and $i_D(t)$

KVLs according to the current around the loop