

Exam #1 → Tuesday Aug. 10, 2019 @ 7:00pm

9/4/2019

Concepts Chapter #1:

- Current/Charge Relationship
- Power/Energy/Current/Voltage Relationships
- Conservation of Energy

Location: Chardon 124

Concepts Chapter #2:

- Ohm's Law (passive sign convention)
- Kirchhoff's Current Law (KCL)
- Kirchhoff's Voltage Law (KVL)
- Voltage/Current Divider
- Equivalent Resistance
- Wye/Delta Transformations
- Solving Circuits

Exam #1 → Tuesday Aug. 10, 2019 @ 7:00pm

9/4/2019

Concepts Chapter #3:

Location: Chardon 124

1) Nodal Analysis

- Select node as reference
- # of Eq. = # of nodes – 1
- variables → voltages
- KCL → equations
- voltage source → constraint eq. (express in terms of variables)
- voltage source between 2 non-reference nodes → supernode

2) Loop Analysis


- # of Eq. = # of independent loops
- variables → currents (assign a loop current to each independent loop)
- KVL → equations
- current source → constraint eq. (express in terms of variables)

Last Lecture → Nodal Analysis

9/4/2019

Analysis Procedure

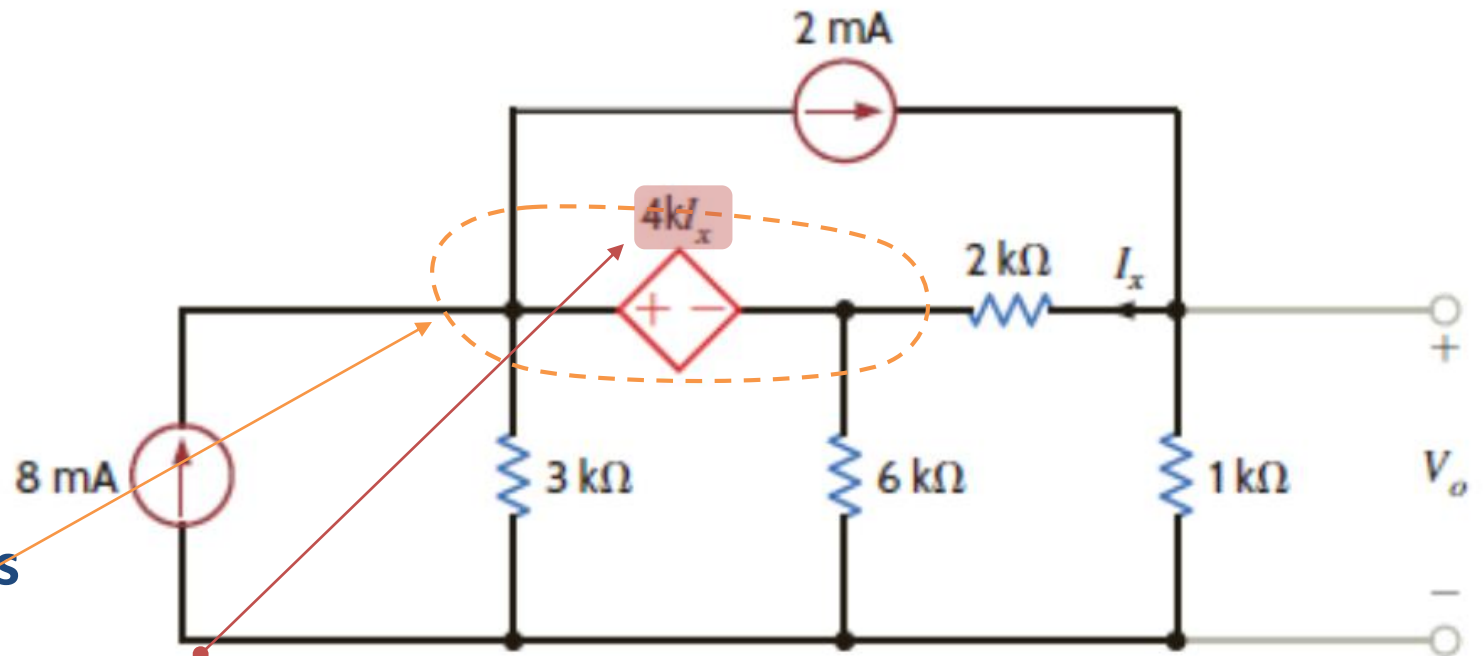- 1) Identify #of nodes
- 2) Select reference node
- 3) Label other node voltages
- 4) Identify branch currents
- 5) Identify **supernode** / **dependent sources**
- 6) Apply KCL to nodes and supernodes
- 7) Write constraint equation - **supernodes**
- 8) Write controlling equation - **dependent sources**
- 9) Solve equation system



$$V_1 - V_2 = 4k \cdot I_x$$

$$I_x = \frac{V_0 - V_2}{2k}$$

Mesh Analysis

9/4/2019

Alternative # 1

- $B \rightarrow$ # of branches
- $N \rightarrow$ # of nodes
- $B - N + 1 \rightarrow$ # independent simultaneous equations

Alternative # 2

- $M \rightarrow$ # of independent loops in a planar circuit
- $M \rightarrow$ # independent simultaneous equations



$$B = 8 \quad M = 4$$

$$N = 5$$

$$\# \text{ Eq.} = 4$$

Establish the currents
around the loops




$$i_A(t) = i_1(t)$$

$$v_1 = V_{R_1} + V_{R_2}$$

$$-v_2 = V_{R_3} + V_{R_4}$$

$$v_2 - v_1 = V_5$$

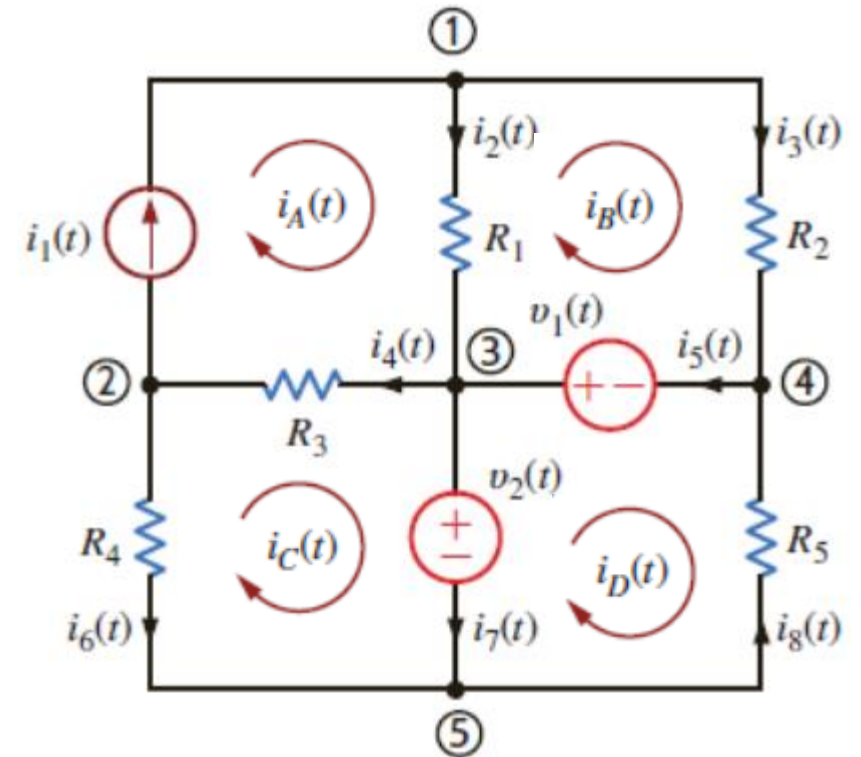


Express voltages in terms of
currents: $i_A(t)$, $i_B(t)$, $i_C(t)$, and $i_D(t)$

KVLs according to the current around the loop

Loop Analysis → with Independent Voltage Sources

9/4/2019

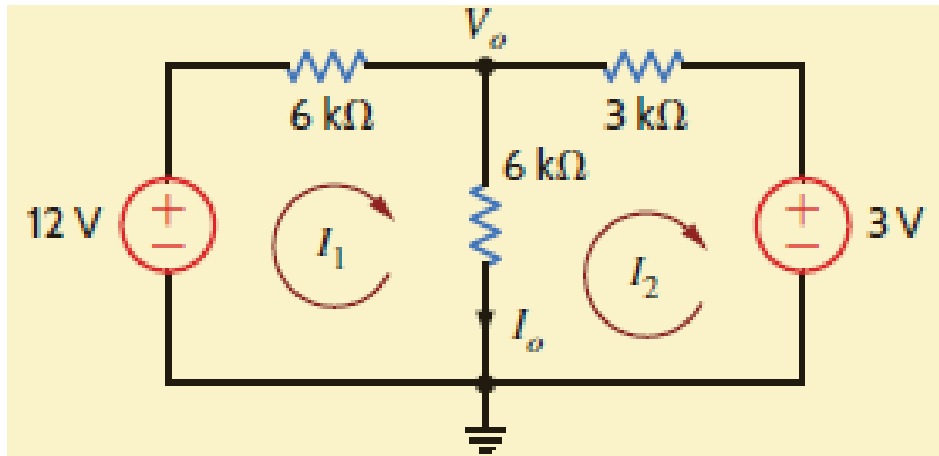***Use passive sign convention with respect the loop currents




$M = 2$
Eq. = 2

- KVLs in terms of I_1 and I_2

$$12 = 6k \cdot I_1 + 6k \cdot (I_1 - I_2)$$

$$-3 = 6k \cdot (I_2 - I_1) + 3k \cdot I_2$$

using the outer loop...

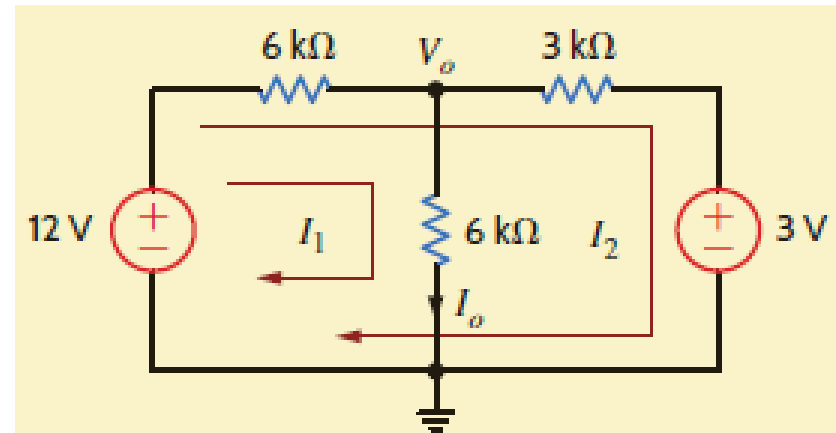


$$I_1 = \frac{1}{2} \text{ mA}$$

$$I_2 = \frac{5}{4} \text{ mA}$$

Loop Analysis → with Independent Current Sources

9/4/2019

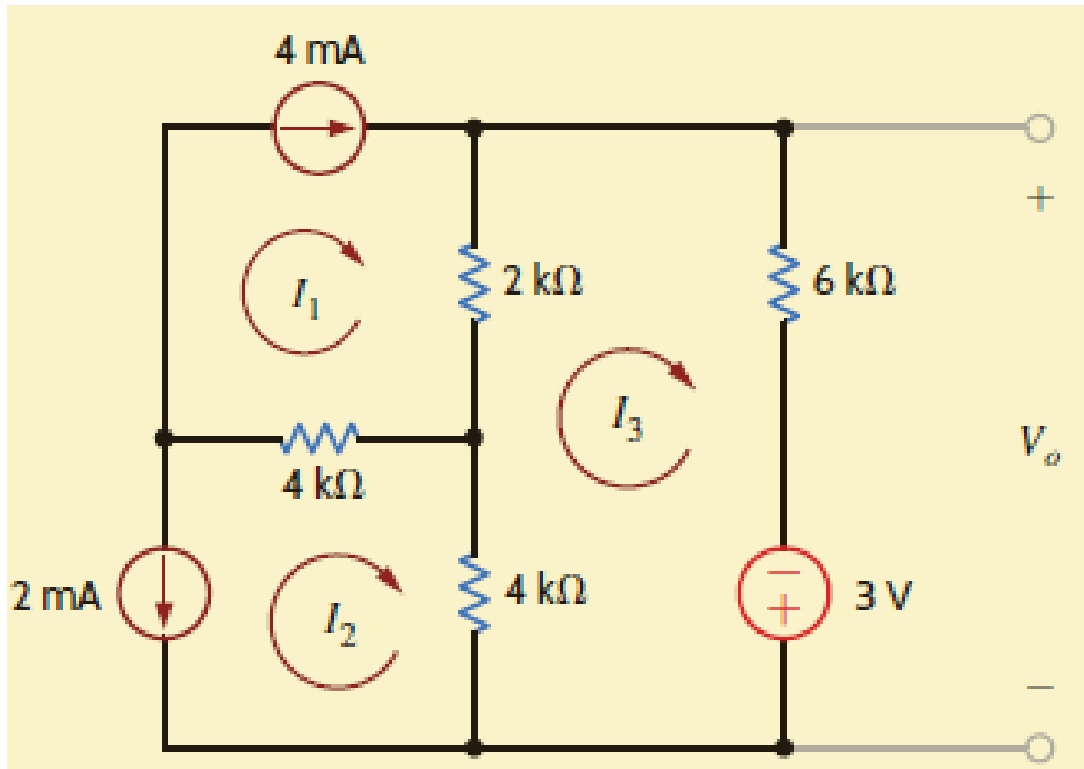*** The current source will determine loop current



$M = 3$
Eq. = 3

- Independent CS

$$I_1 = 4mA$$

$$I_2 = -2mA$$

- KVLs in terms of I_1 , I_2 , and I_3


$$3 = 4k \cdot (I_3 - I_2) + 2k \cdot (I_3 - I_1) + 6k \cdot I_3$$

$$\hookrightarrow I_1 = \frac{1}{4}mA$$

Loop Analysis → with Dependent Voltage Sources

9/4/2019

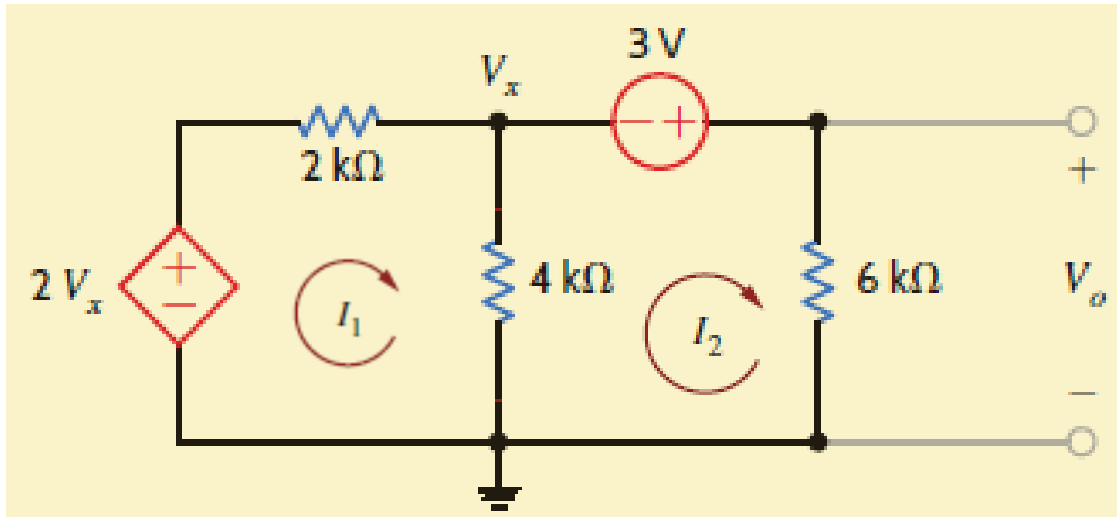*** After the KVLs, write the controlling equation for the dependent sources



$$I_1 = 3\text{mA}$$

$$I_2 = \frac{3}{2}\text{mA}$$

$$V_0 = 9\text{V}$$

$M = 2$
Eq. = 2

- KVLs in terms of I_1 and I_2


- Controlling Eq.

$$V_x = 4k \cdot [I_1 - I_2]$$

Loop Analysis → Super-mesh

9/4/2019

Learning Assessment – E3.23: Find V_o .

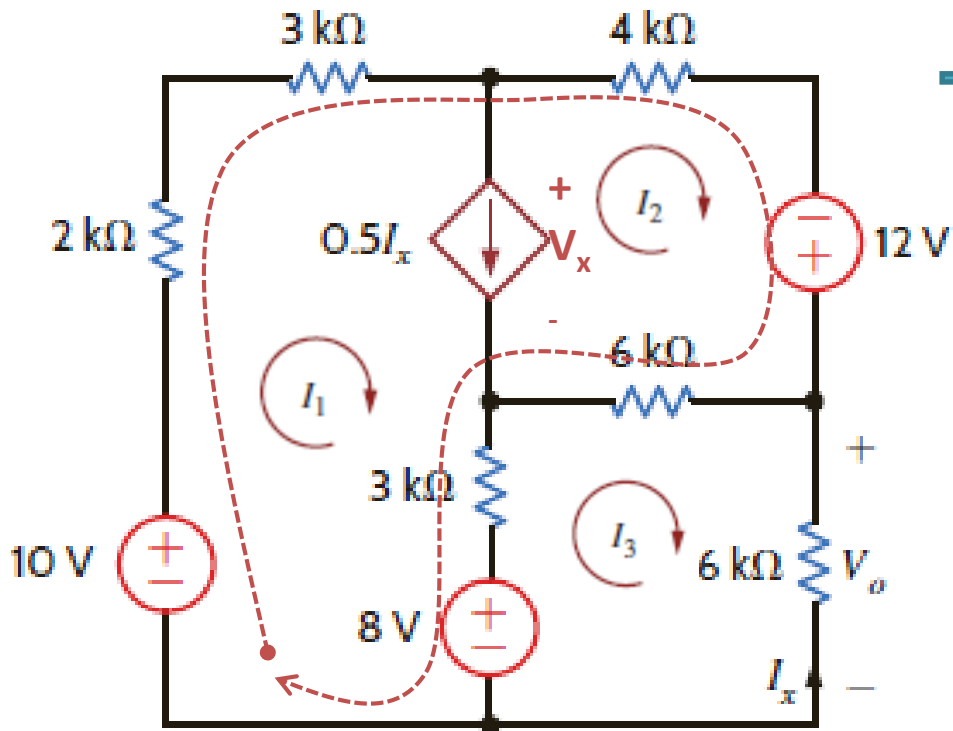

$M = 3$
Eq. = 3

- KVLs in terms of I_1 , I_2 and I_3

$$10 - 5k \cdot I_1 - V_x - 3k \cdot (I_1 - I_3) - 8 = 0$$

$$12 - 6k \cdot (I_2 - I_3) + V_x - 4k \cdot I_2 = 0$$




- KVLs @ Super-mesh

$$10 - 5k \cdot I_1 - 4k \cdot I_2 + 12 - 6k \cdot (I_2 - I_3) - 3k \cdot (I_1 - I_3) - 8 = 0$$

Loop Analysis → Super-mesh

9/4/2019

Learning Assessment – E3.23: Find V_o .

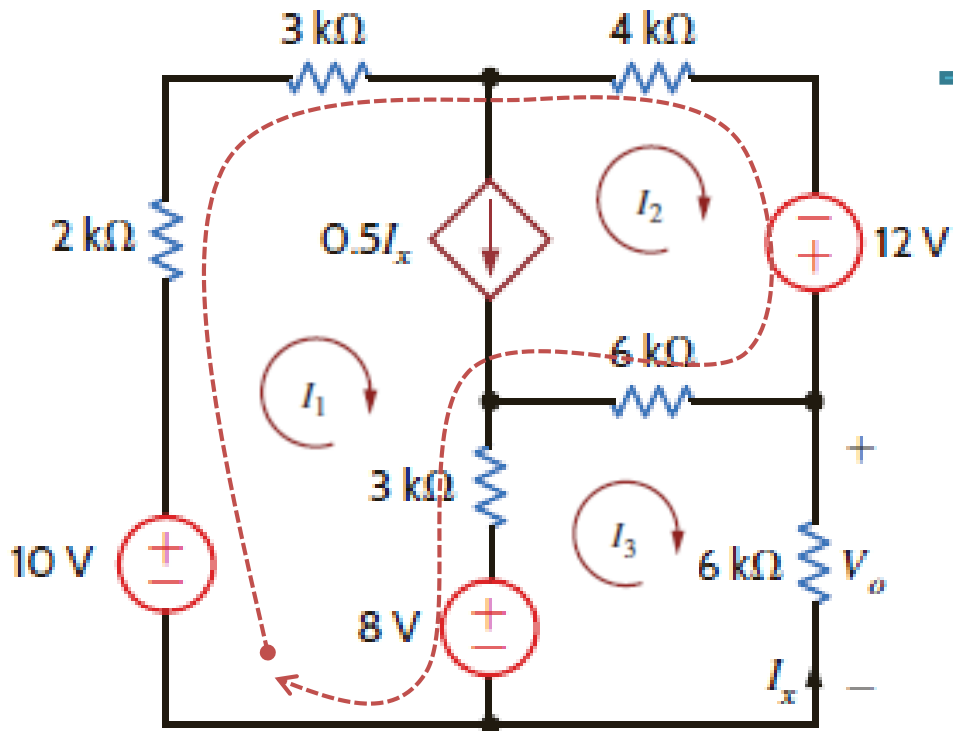

$M = 3$
Eq. = 3

- KVLs in terms of I_1 , I_2 and I_3

$$14 = 8k \cdot I_1 + 10k \cdot I_2 - 9k \cdot I_3$$

$$8 = -3k \cdot I_1 - 6k \cdot I_2 + 15k \cdot I_3$$

- Controlling Eq.

$$I_x = -I_3$$

- Constraint Eq.

$$I_1 - I_2 = \frac{1}{2} I_x$$

$$I_1 = \frac{10}{9} \text{ mA}$$

$$I_3 = \frac{3}{2} \text{ mA}$$

$$V_o = 9\text{V}$$

Problem → 3.124

9/4/2019

Find I_o using both nodal and mesh analysis