

Exam #1 → Tuesday Aug. 10, 2019 @ 7:00pm

9/4/2019

Concepts Chapter #1:

- Current/Charge Relationship
- Power/Energy/Current/Voltage Relationships
- Conservation of Energy

Location: Chardon 124

Concepts Chapter #2:

- Ohm's Law (passive sign convention)
- Kirchhoff's Current Law (KCL)
- Kirchhoff's Voltage Law (KVL)
- Voltage/Current Divider
- Equivalent Resistance
- Wye/Delta Transformations
- Solving Circuits

Exam #1 → Tuesday Aug. 10, 2019 @ 7:00pm

9/4/2019

Concepts Chapter #3:

Location: Chardon 124

1) Nodal Analysis

- Select node as reference
- # of Eq. = # of nodes – 1
- variables → voltages
- KCL → equations
- voltage source → constraint eq. (express in terms of variables)
- voltage source between 2 non-reference nodes → supernode

2) Loop Analysis

- # of Eq. = # of independent loops
- variables → currents (assign a loop current to each independent loop)
- KVL → equations
- current source → constraint eq. (express in terms of variables)


Last Lecture → Mesh Analysis

9/4/2019

- $M \rightarrow$ # of independent loops in a planar circuit
- $M \rightarrow$ # independent simultaneous equations

Analysis Procedure

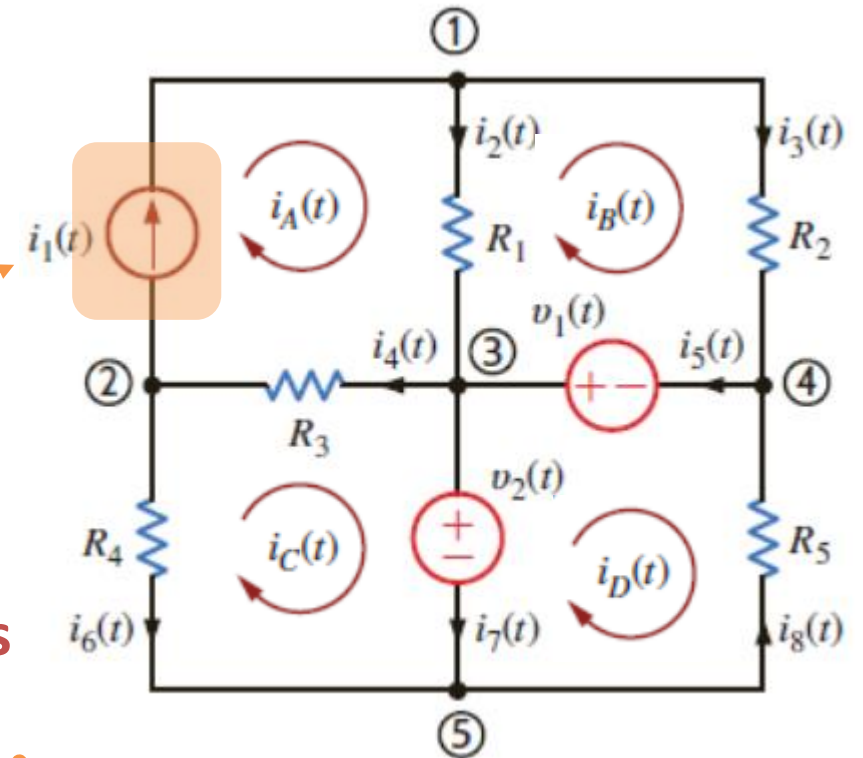- 1) Identify #of equations
- 2) Establish current around loops
- 3) Identify voltage drops according currents
- 4) Identify **current sources** / **dependent sources**
- 5) Apply KVL to loops
- 6) Write constraint equation – **current sources**
- 7) Write controlling equation – **dependent sources**
- 8) Solve equation system



$$I_A = I_1$$

Additional Analysis Techniques → Chapter #5


9/4/2019

- **Linearity and Equivalence**
- **Superposition**
- **Thevenin Equivalent Circuit**
- **Norton Equivalent Circuit**
- **Source Transformation**
- **Maximum Power Transfer**

Circuit Equivalence

9/4/2019

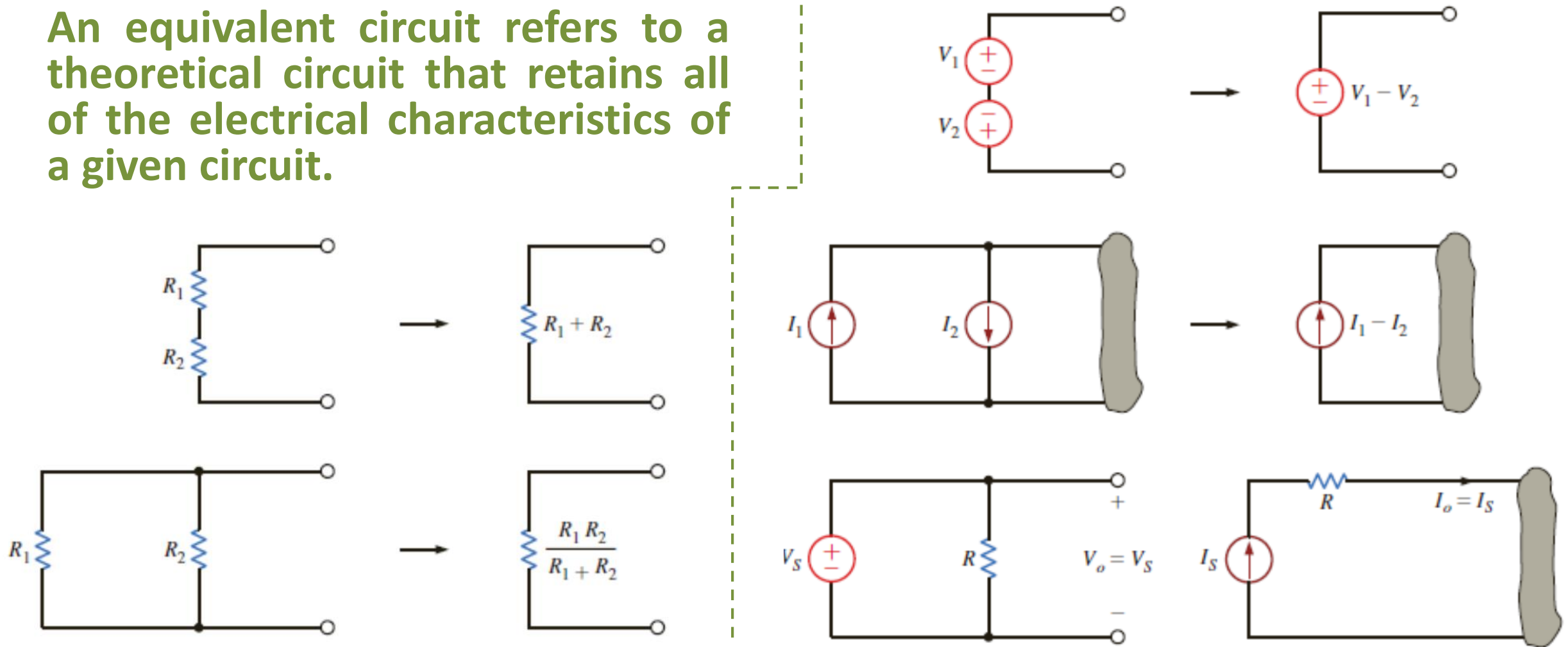
An equivalent circuit refers to a theoretical circuit that retains all of the electrical characteristics of a given circuit.



Circuit Linearity

9/4/2019

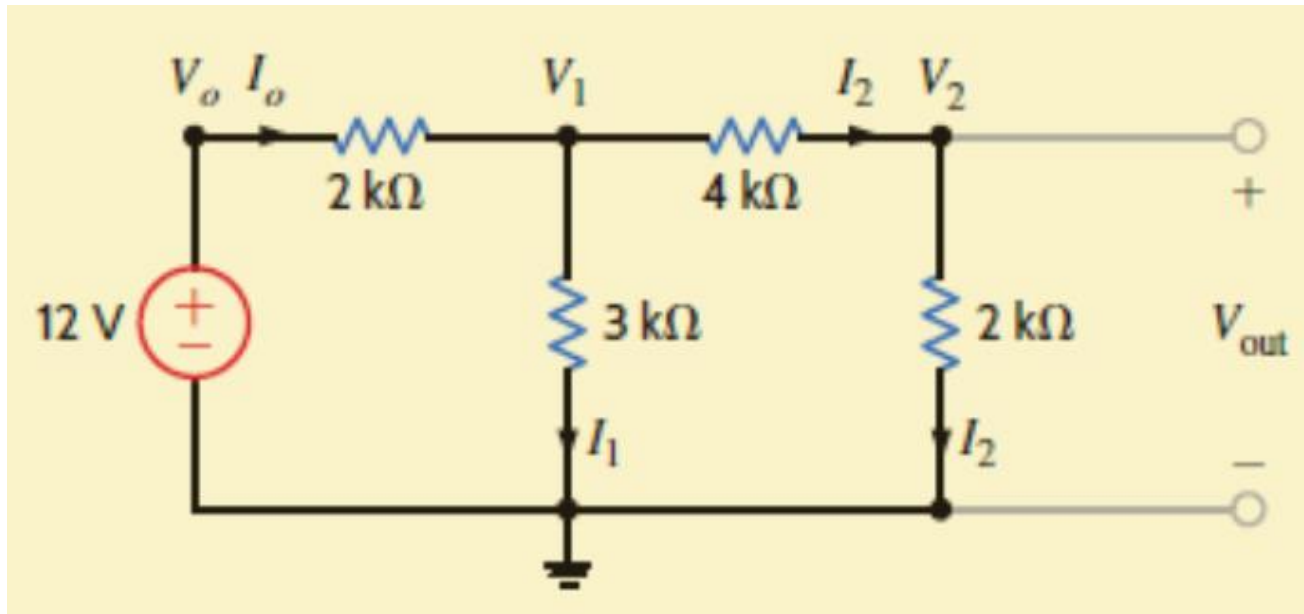Requires both additivity and homogeneity (scaling)



$$\frac{V_{out}}{V_0} = \frac{V_{out}'}{V_0'}$$

$$V_{out}' = 1V \rightarrow V_0' = 6V$$

$$\therefore V_{out} = V_0 \cdot \frac{V_{out}'}{V_0'} = V_0 \cdot \frac{1}{6} = 2V$$



Example 5.1: Find V_{out} ...

assuming $V_{out} = 1$, find V_0 and then use linearity to obtain V_{out} for $V_0 = 12V$.

Superposition

9/4/2019

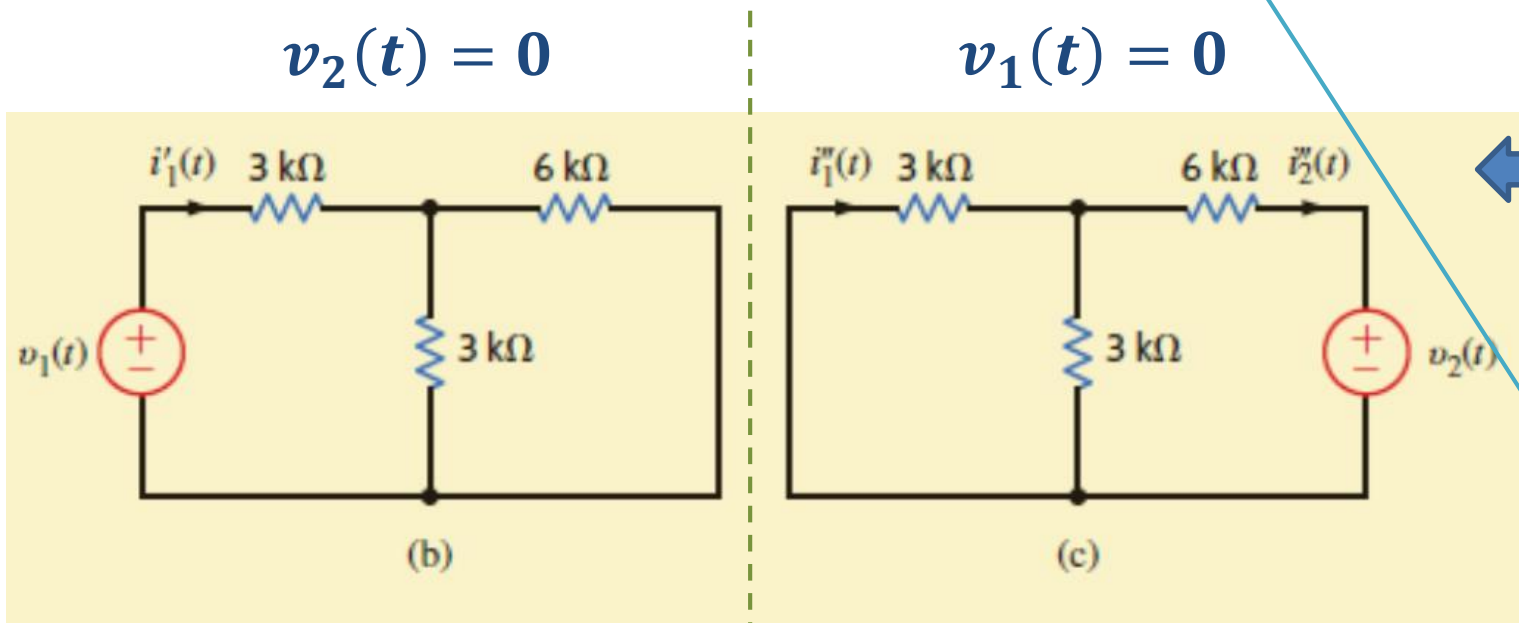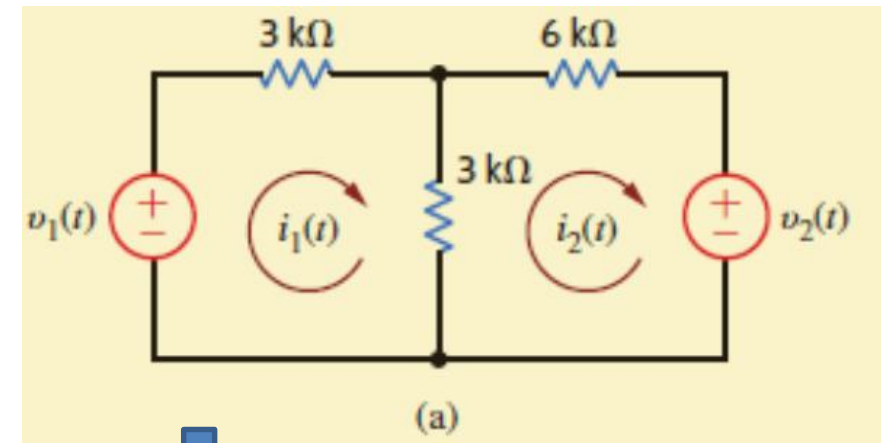In any linear circuit containing multiple independent sources, the current or voltage at any point in the network may be calculated as the algebraic sum of the individual contributions of each source acting alone.



$$i_1(t) = \frac{v_1(t)}{5k} - \frac{v_2(t)}{15k}$$

$$i_1'(t) = \frac{v_1(t)}{5k}$$

$$i_1''(t) = -\frac{v_2(t)}{15k}$$

$$i_1(t) = i_1'(t) + i_1''(t)$$

Superposition

9/4/2019

Each independent source can be applied independently with the remaining source turned off:




- *Turn off a voltage source* → *short circuit*
- *Turn off a current source* → *open circuit*

The final solution is the algebraic sum of the independent results!

Problem 2.65

9/4/2019


Find R_{AB} in the circuit provided.

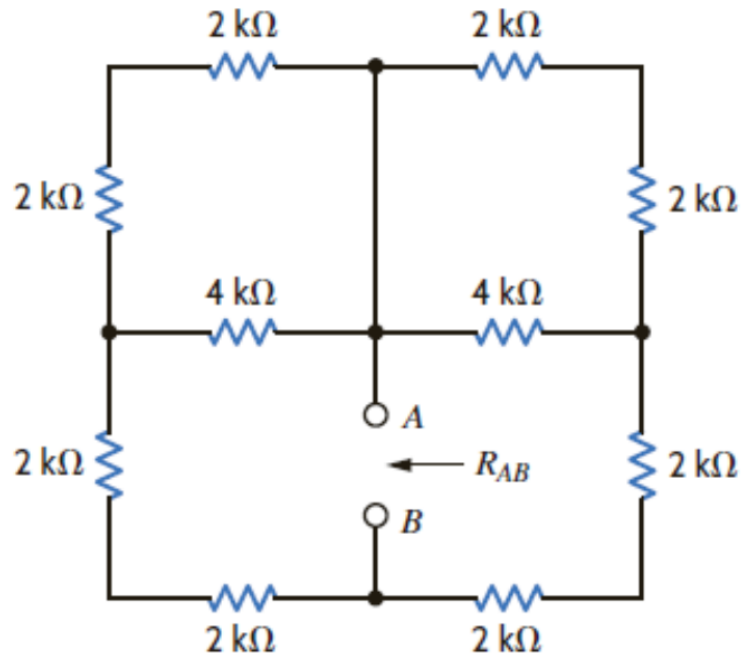

Learning Assessment E2.33

9/4/2019


If the power supplied by the 3A current source is 12W, find V_s and the power supplied by the 10V source.

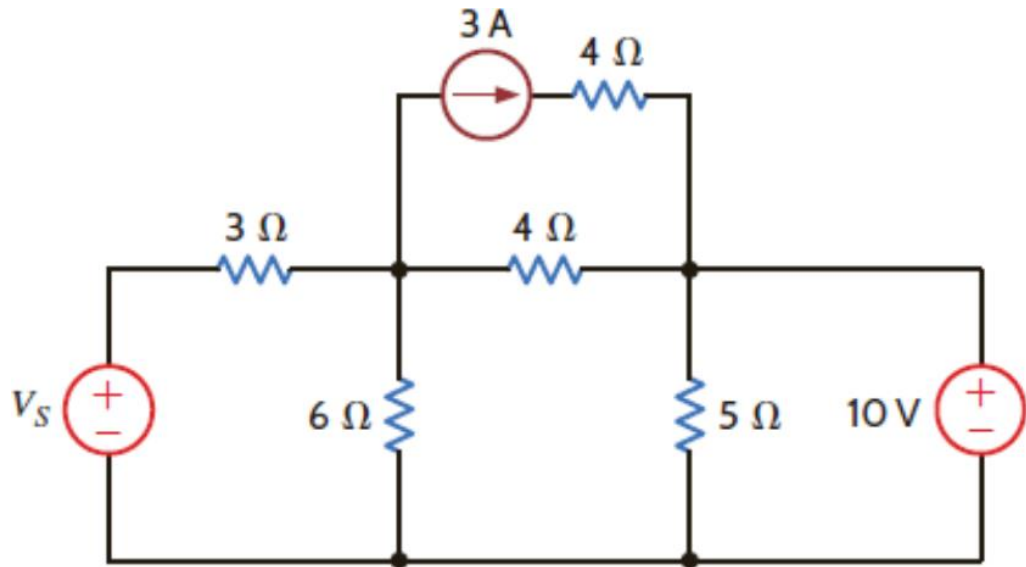

Problem 2.121

9/4/2019


Find V_o in the provided network.

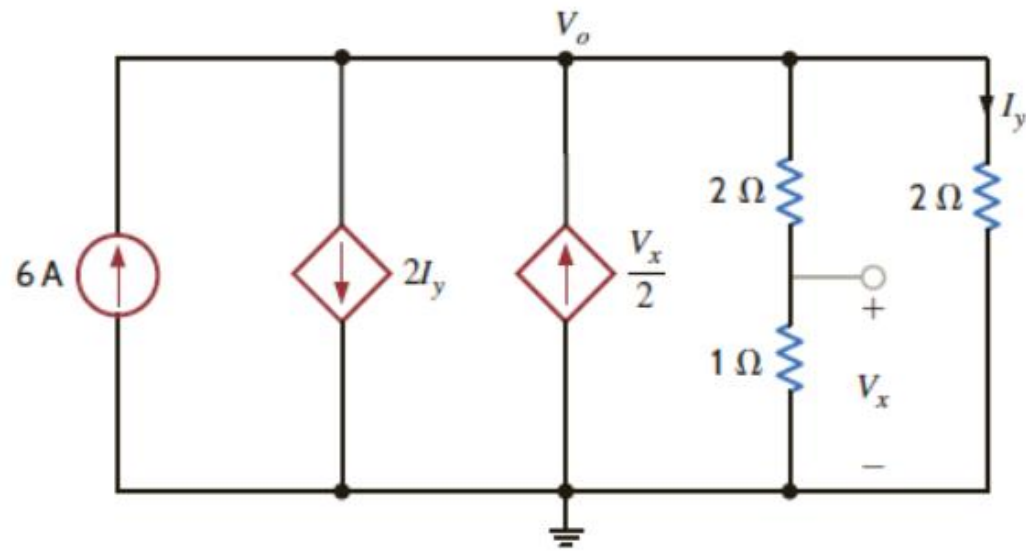

Problem → 3.31

9/4/2019

Find I_o using both nodal and mesh analysis

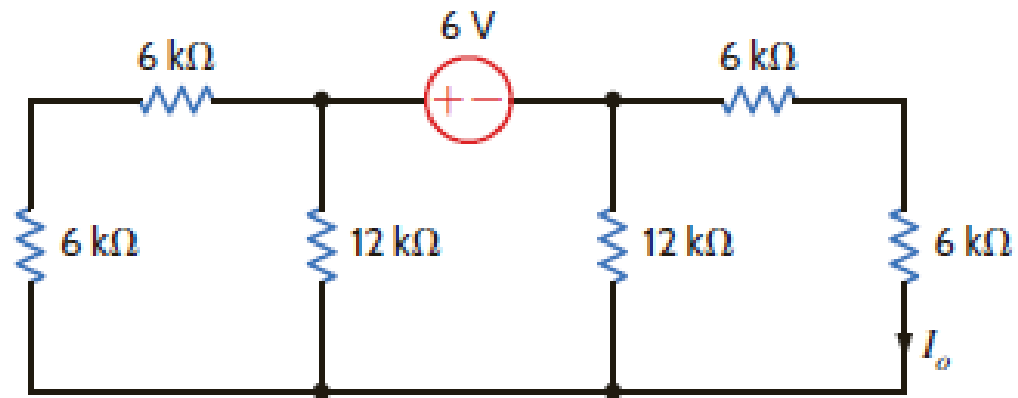

Circuits 1

Problem → 3.310

9/4/2019

Find V_o using both nodal and mesh analysis

