

Additional Analysis Techniques → Chapter #5


9/16/2019

- **Linearity and Equivalence**
- **Superposition**
- **Thevenin Equivalent Circuit**
- **Norton Equivalent Circuit**
- **Source Transformation**
- **Maximum Power Transfer**

Circuit Equivalence

9/16/2019

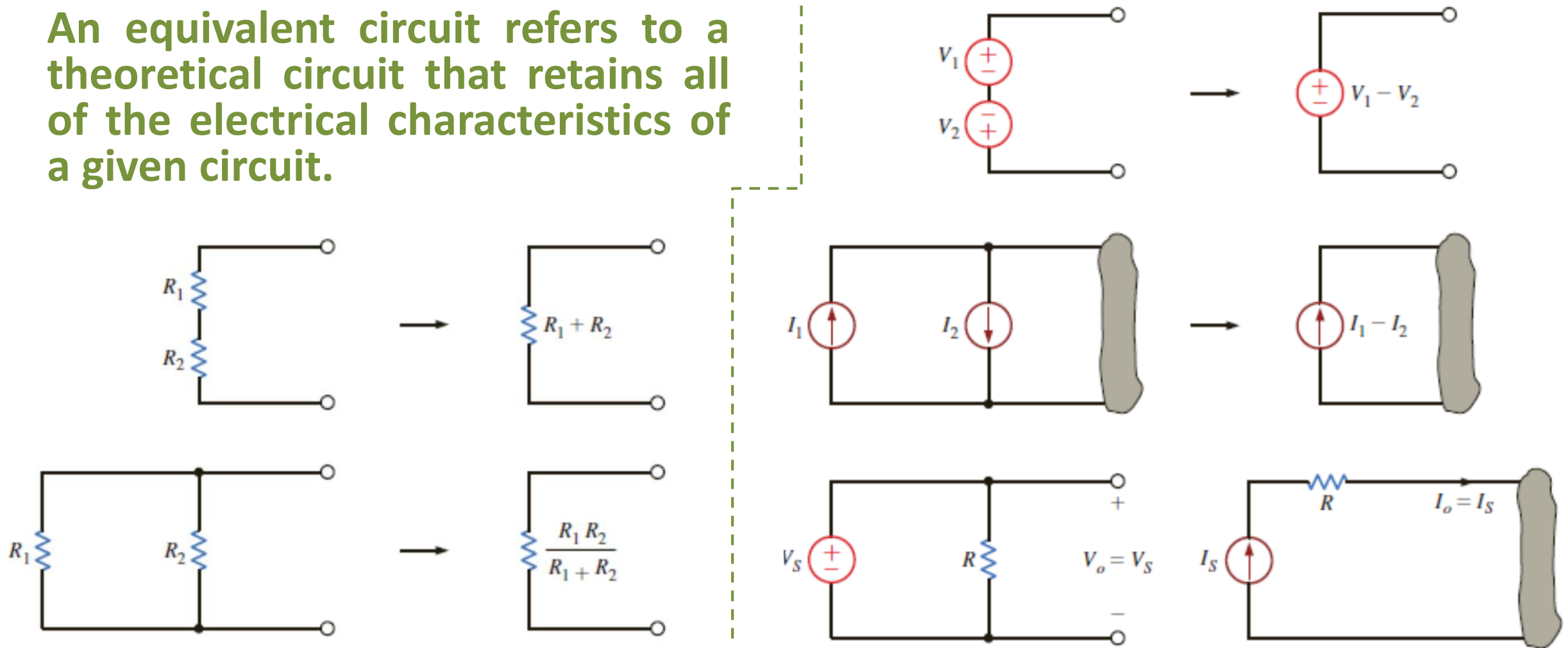
An equivalent circuit refers to a theoretical circuit that retains all of the electrical characteristics of a given circuit.



Circuit Linearity

9/16/2019

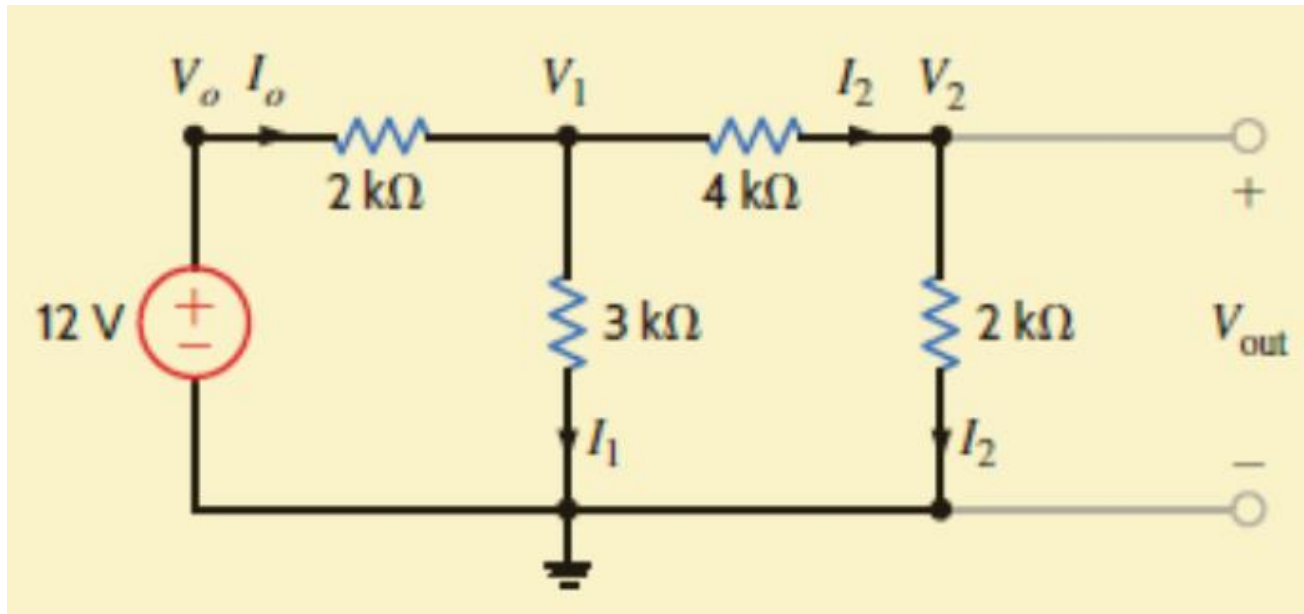Requires both additivity and homogeneity (scaling)



$$\frac{V_{out}}{V_0} = \frac{V_{out}'}{V_0'}$$

$$V_{out}' = 1V \rightarrow V_0' = 6V$$

$$\therefore V_{out} = V_0 \cdot \frac{V_{out}'}{V_0'} = V_0 \cdot \frac{1}{6} = 2V$$



Example 5.1: Find V_{out} ...

assuming $V_{out} = 1$, find V_0 and then use linearity to obtain V_{out} for $V_0 = 12V$.

Superposition

9/16/2019

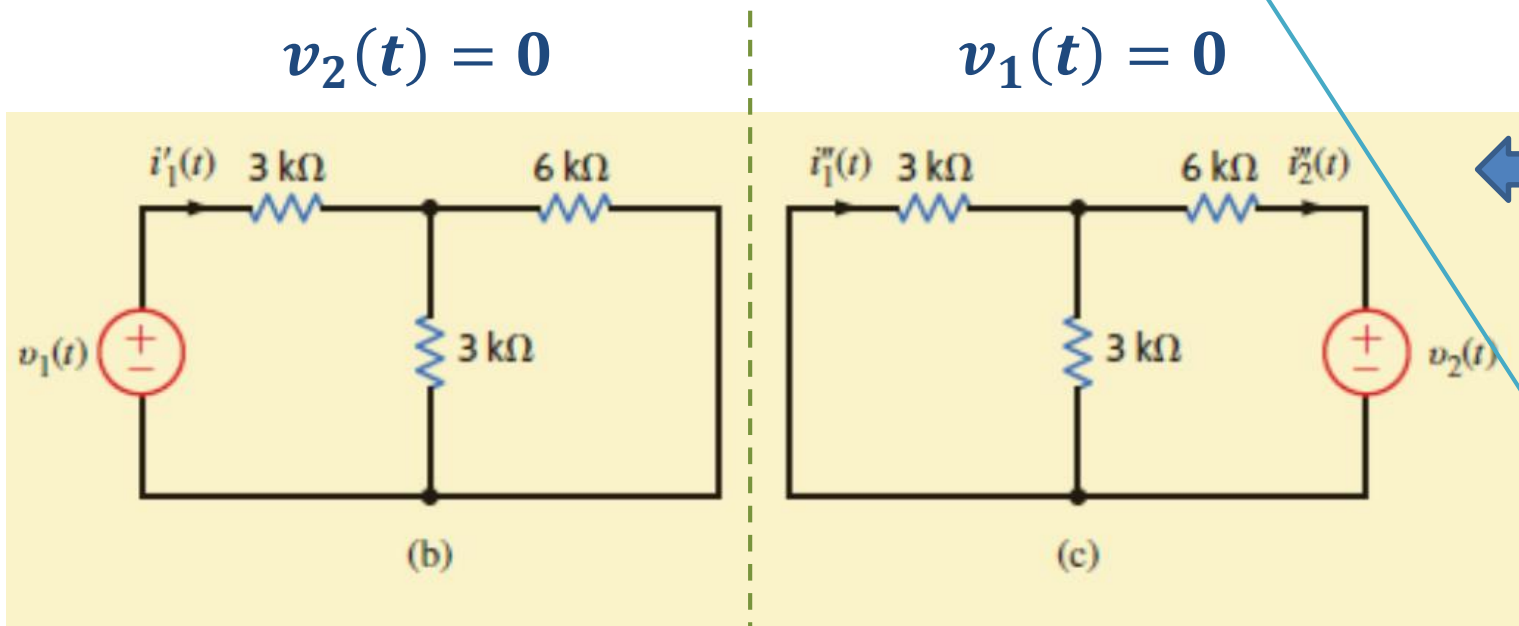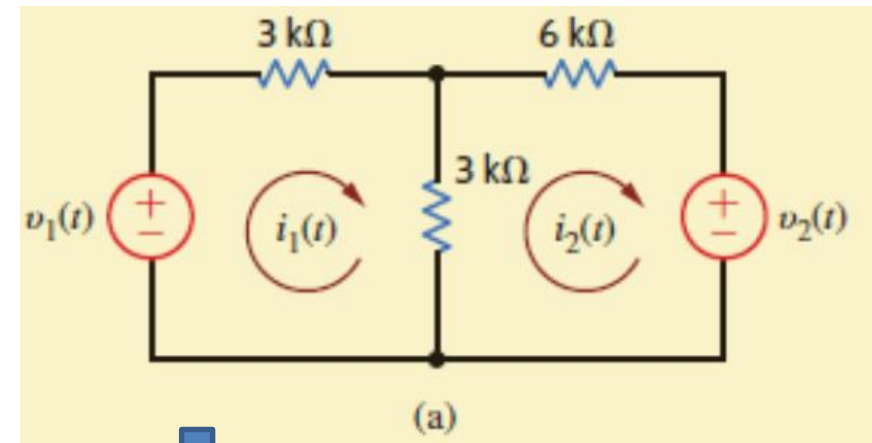In any linear circuit containing multiple independent sources, the current or voltage at any point in the network may be calculated as the algebraic sum of the individual contributions of each source acting alone.



$$i_1(t) = \frac{v_1(t)}{5k} - \frac{v_2(t)}{15k}$$

$$i_1'(t) = \frac{v_1(t)}{5k}$$

$$i_1''(t) = -\frac{v_2(t)}{15k}$$

$$i_1(t) = i_1'(t) + i_1''(t)$$

Superposition

9/16/2019

Each independent source can be applied independently with the remaining source turned off:




- *Turn off a voltage source* → *short circuit*
- *Turn off a current source* → *open circuit*

The final solution is the algebraic sum of the independent results!

Learning Assessment E.5.4

9/16/2019

Find V_o using superposition.

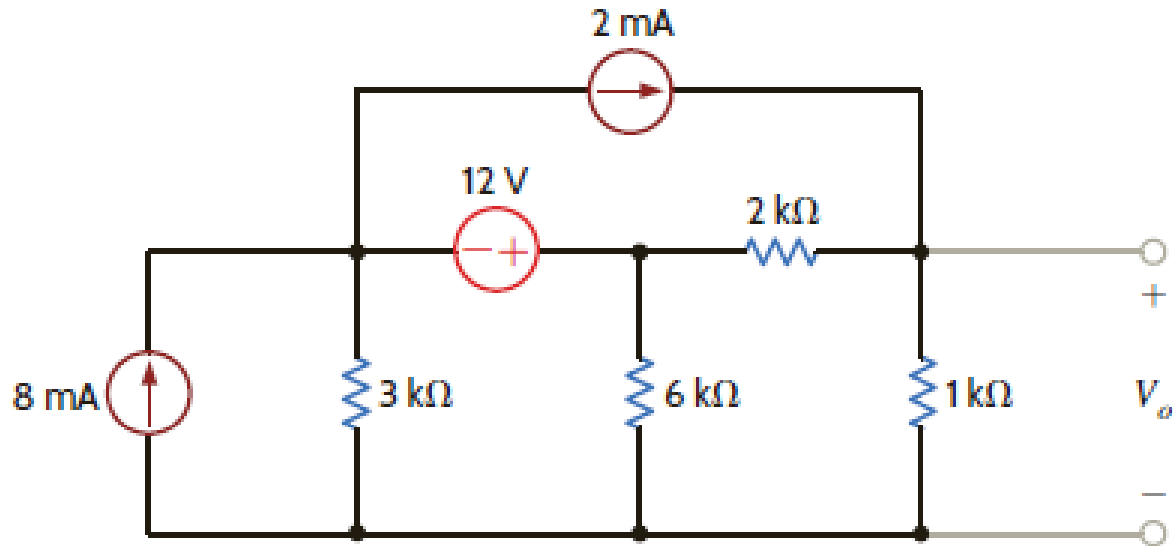

Thevenin's and Norton's Theorems


9/16/2019

Thevenin's Theorem: *an entire circuit or network can be replaced, exclusive of the load, by an equivalent circuit that contains only an independent voltage source in series with a resistor in such a way that the current-voltage relationship at the load is unchanged.*

Norton's Theorem: *an entire circuit or network can be replaced, exclusive of the load, by an equivalent circuit that contains only an independent current source in parallel with a resistor in such a way that the current-voltage relationship at the load is unchanged.*

Thevenin's and Norton's Theorems




9/16/2019

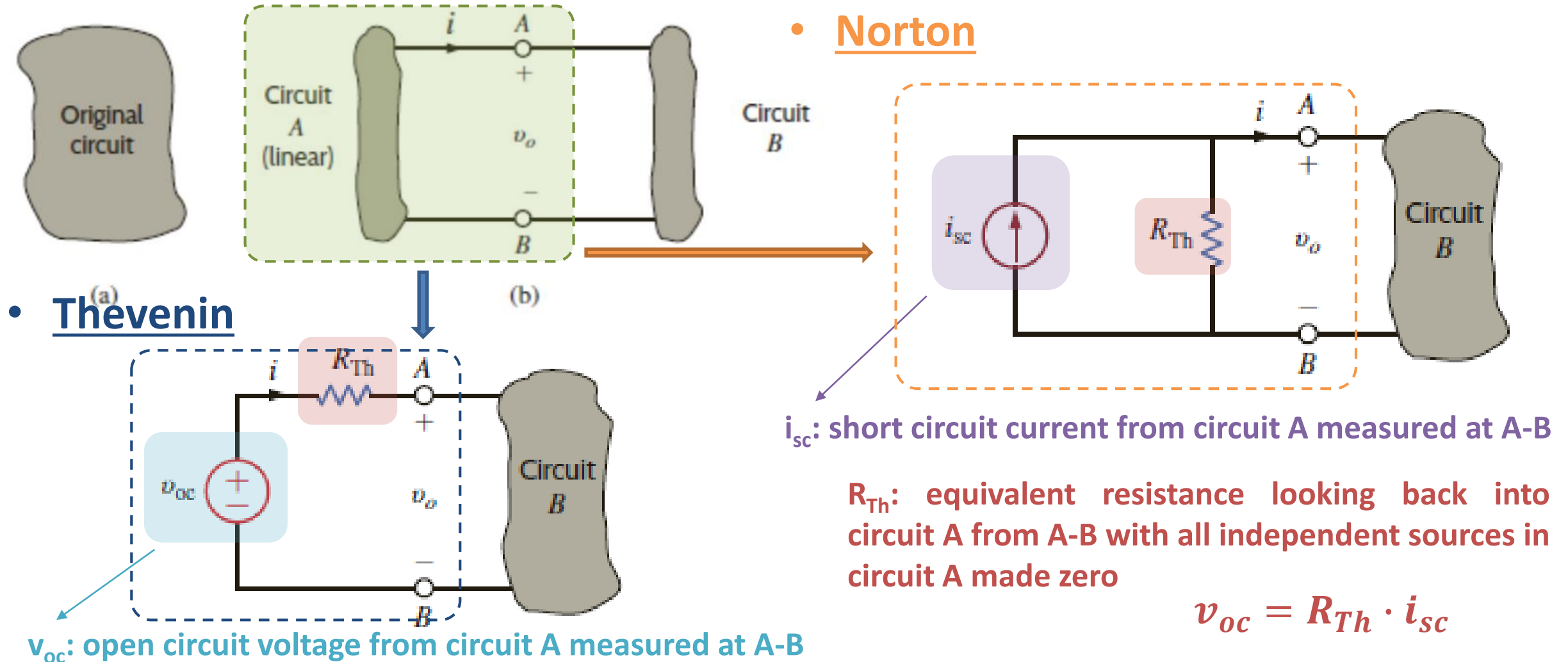

Thevenin's Theorem → Independent Sources Only

9/16/2019

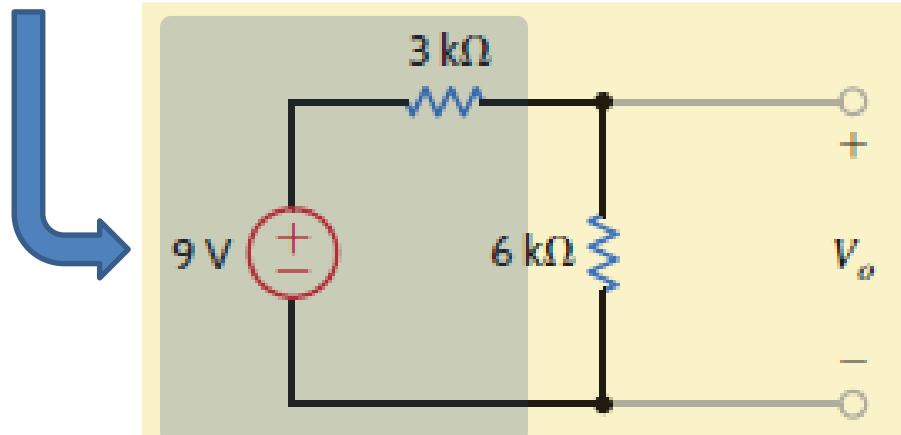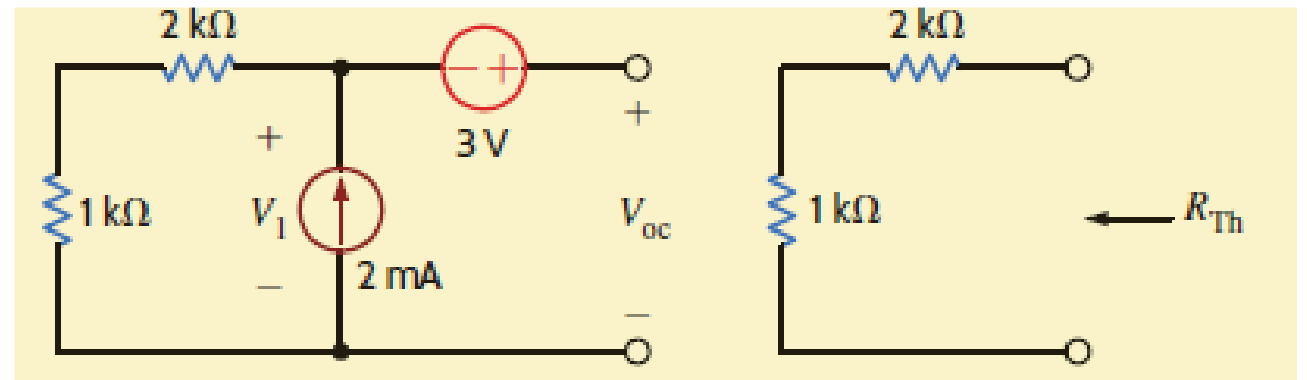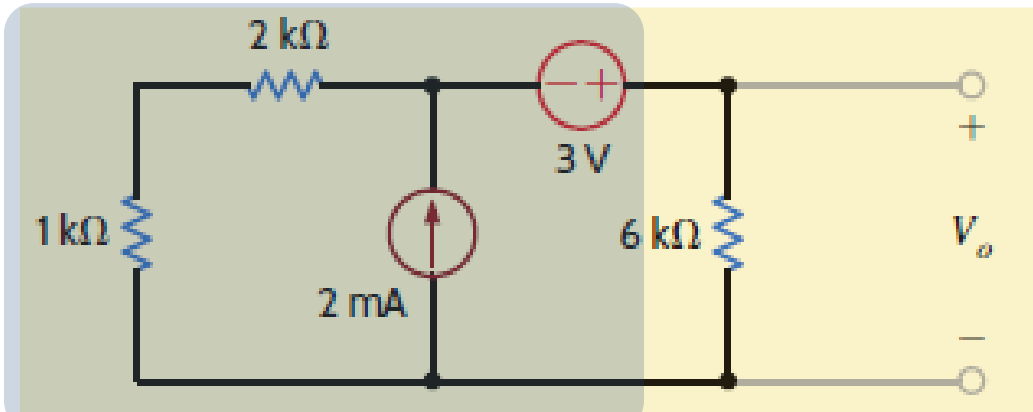Example 5.5: Use Thevenin's and Norton's theorems to find V_o in the network provided.



$$V_{oc} = 2m(1k + 2k) + 3 = 9V$$

$$R_{th} = 1k + 2k = 3k\Omega$$

$$V_o = 9 \frac{6k}{3k + 6k} = 6V$$