

Last Lecture → Superposition

10/2/2019

In any linear circuit containing multiple independent sources, the current or voltage at any point in the network may be calculated as the algebraic sum of the individual contributions of each source acting alone.




$$i_1(t) = i_1'(t) + i_1''(t)$$

Analysis:

Each independent source can be applied independently with the remaining source turned off:


- *Turn off a voltage source* → short circuit
- *Turn off a current source* → open circuit

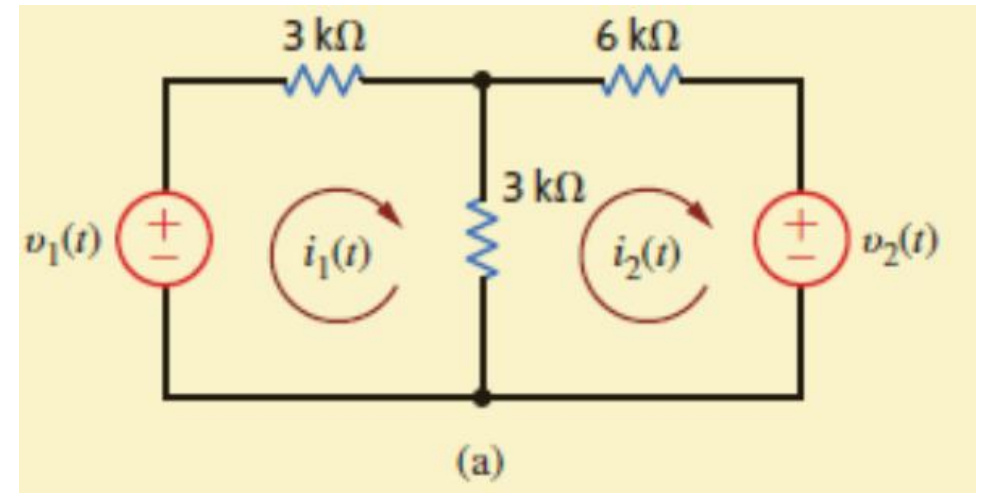The final solution is the algebraic sum of the independent results!.



Last Lecture → Thevenin & Norton




10/2/2019

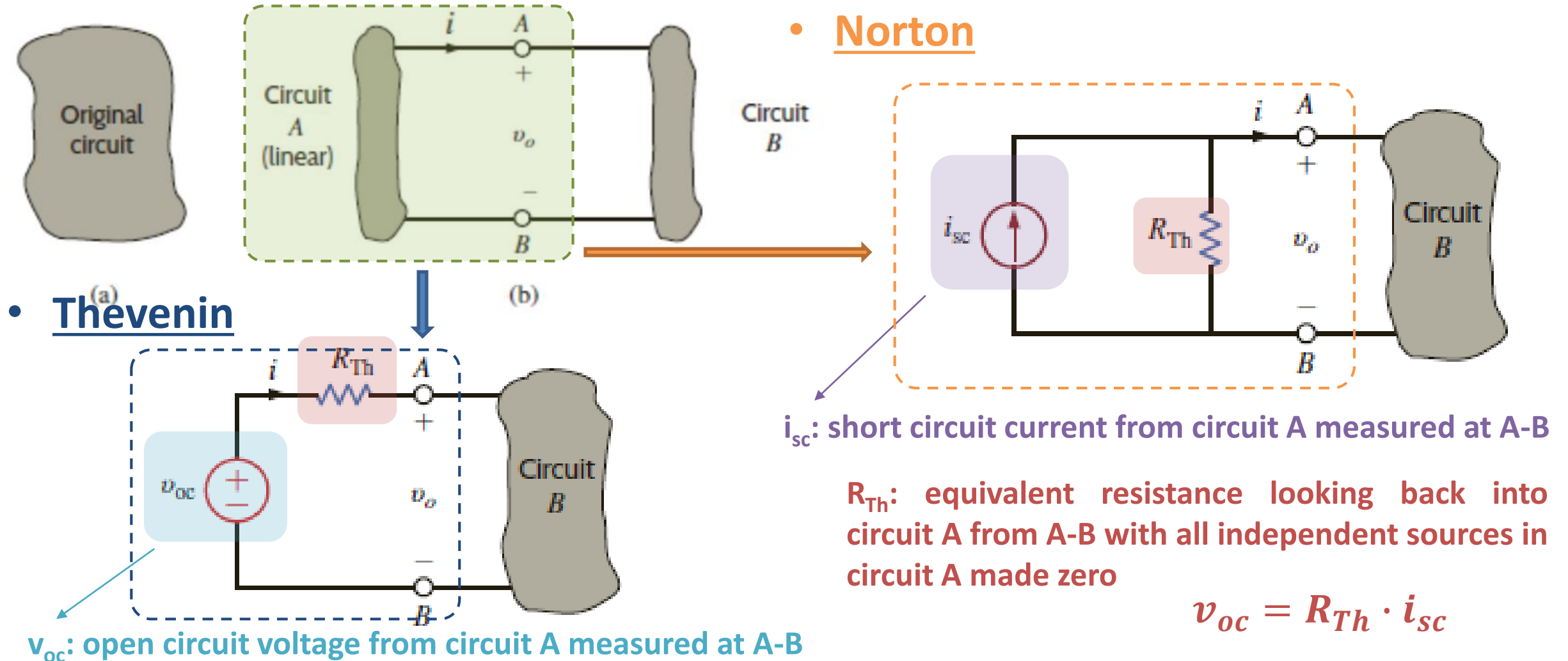

Last Lecture → Thevenin's Equivalent

10/2/2019

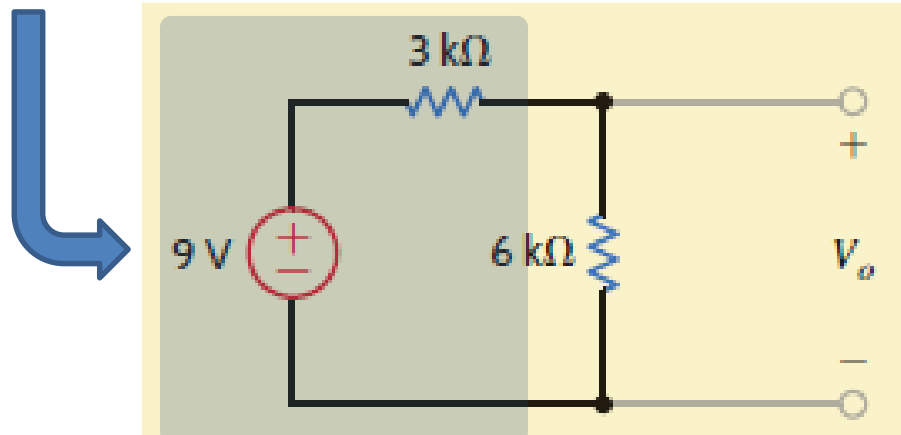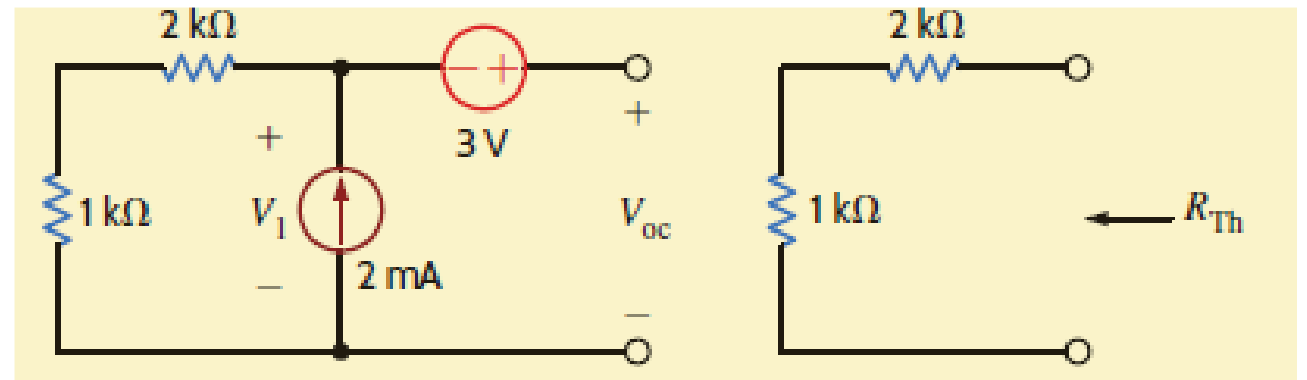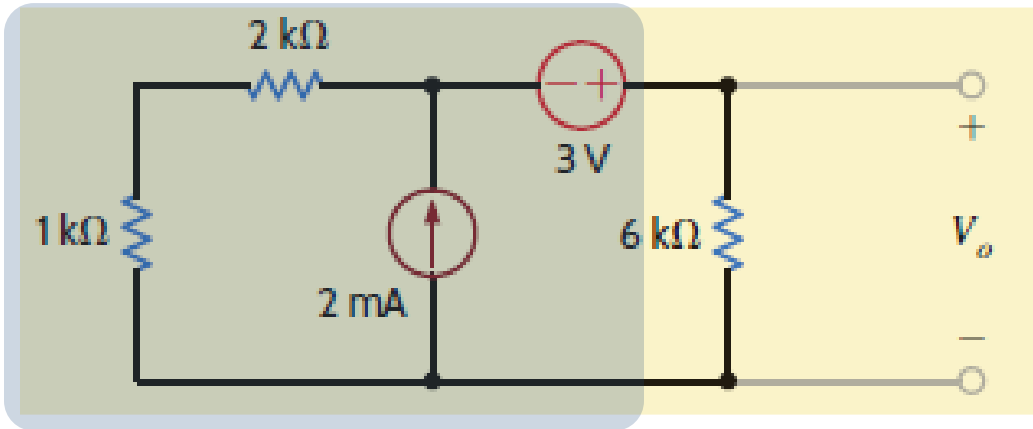Example 5.5: Use Thevenin's and Norton's theorems to find V_o in the network provided.



$$V_{oc} = 2m(1k + 2k) + 3 = 9V$$

$$R_{th} = 1k + 2k = 3k\Omega$$

$$V_o = 9 \frac{6k}{3k + 6k} = 6V$$

Thevenin and Norton Equivalent Circuits

10/2/2019

1) Independent Sources Only

- Find either V_{oc} or I_{sc}
- R_{Th} can be extrapolated directly from the network

2) Dependent Sources Only

- The equivalent circuit is R_{Th} only
- Find R_{th} through ohms law by placing an voltage/current source and measuring the current/voltage


3) Independent and Dependent Sources

- Must calculate both the V_{OC} and I_{SC} to calculate R_{TH} .
- Must not split the dependent source an its controlling variable


Thevenin's Theorem → Dependent Sources Only 10/2/2019

The Thevenin /Norton equivalent of a network containing only dependent sources is R_{th} !

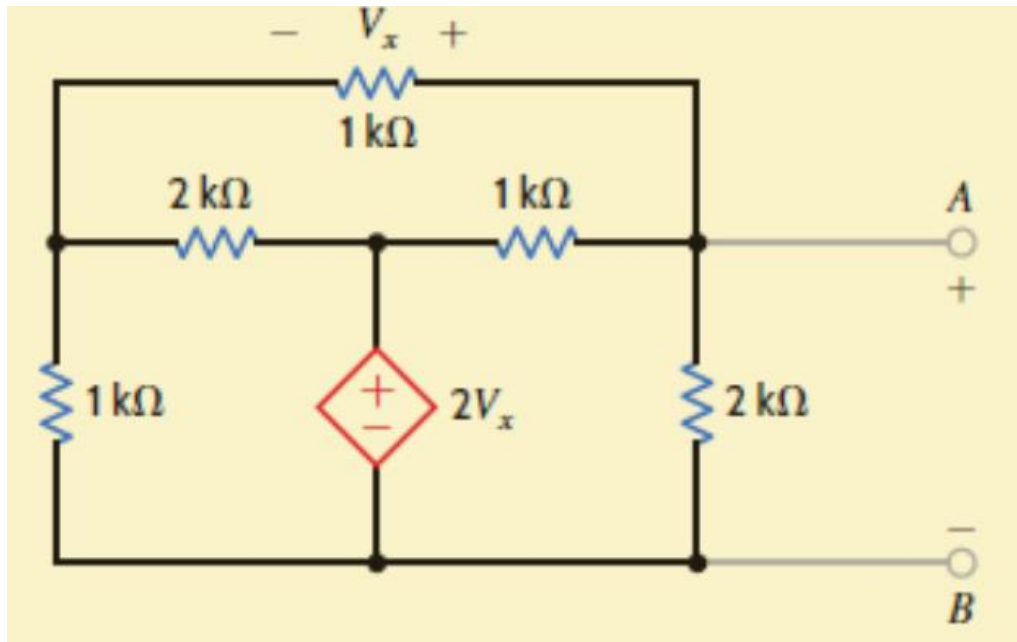Example 5.8:
Determine the Thevenin equivalent of the network provided at terminals A-B.



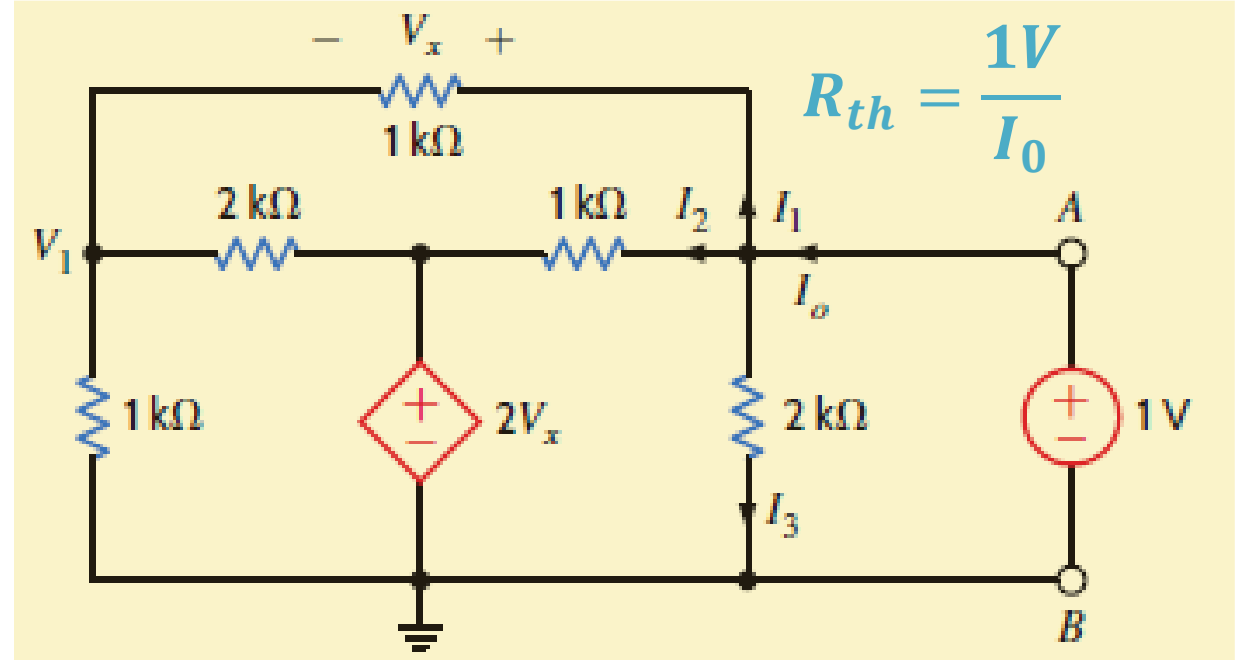↓
Measure R_{th} via a current or voltage source




Thevenin's Theorem → Independent & Dep. Sources

10/2/2019


- *Must calculate both the V_{OC} and I_{SC} to calculate R_{TH} .*
- *Must not split the dependent source on its controlling variable*

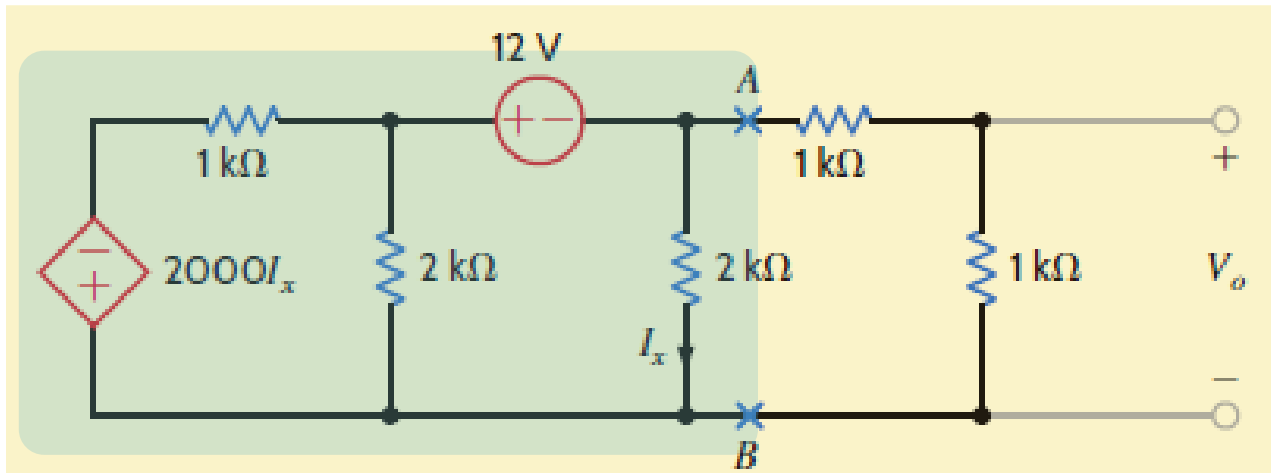Example 5.10:

Use Thevenin's theorem to find V_o in the network provided..



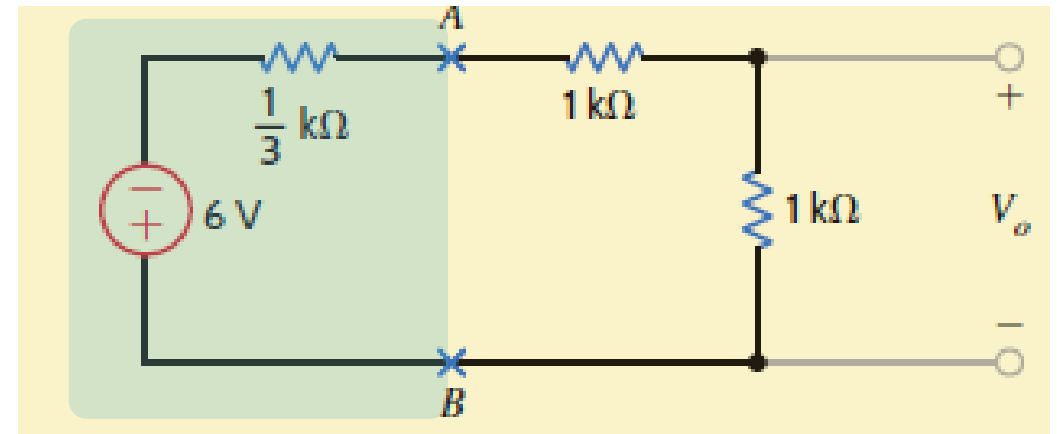
$$\left. \begin{aligned} I_{SC} &= -18 \text{ mA} \\ V_{OC} &= -6 \text{ V} \\ \therefore R_{th} &= \frac{1}{3} \text{ k}\Omega \end{aligned} \right\} V_o = -\frac{18}{7} \text{ V}$$



Learning Assessment → E5.6

10/2/2019

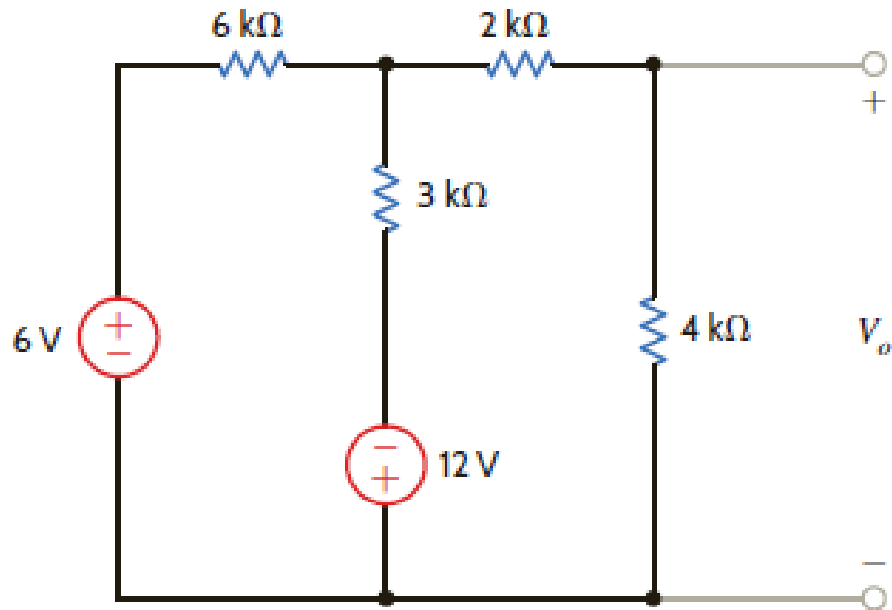
Use Thevenin's Theorem to find V_o in the network provided.



Learning Assessment → E5.13

10/2/2019

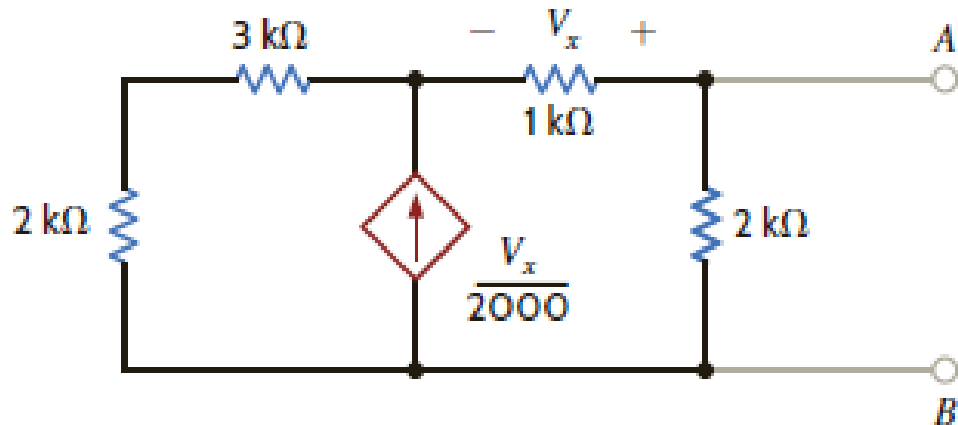
Find the Thevenin equivalent of the network at terminals A-B.




Source Transformation

10/2/2019

- Thevenin

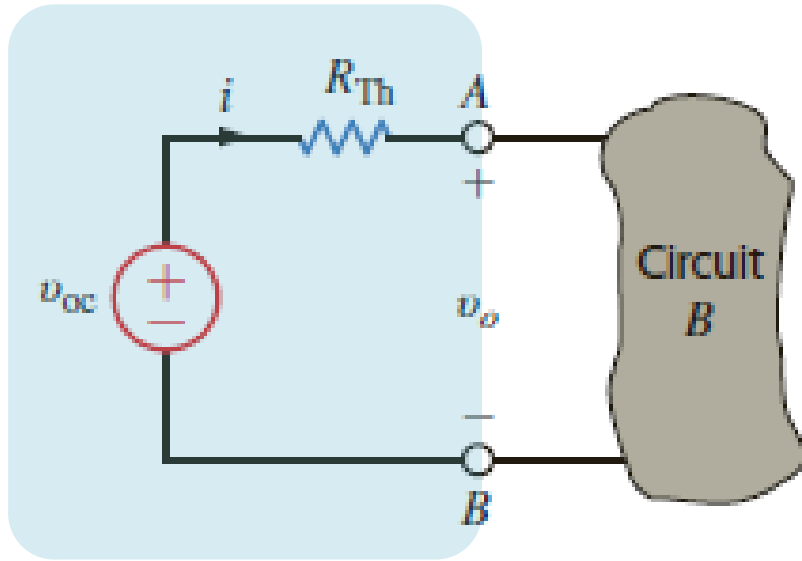

- Norton

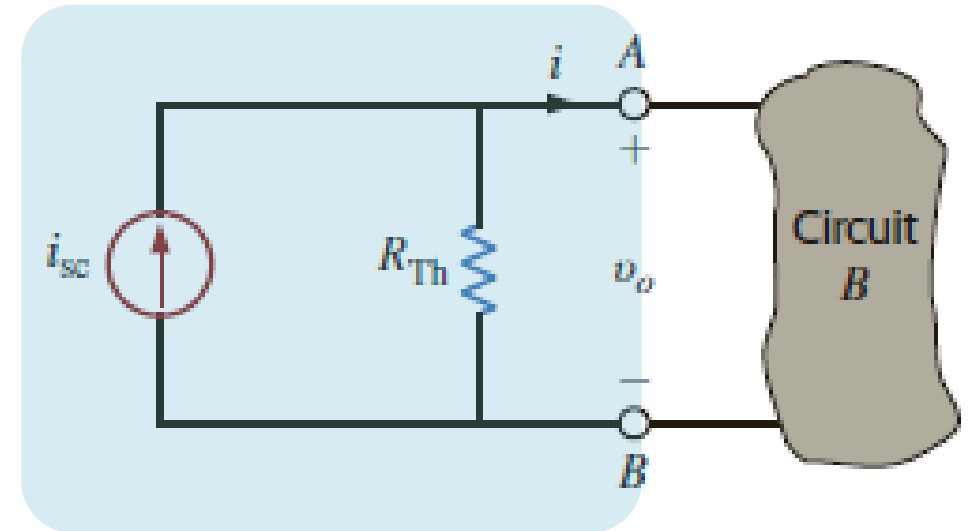

Thevenin and Norton Equivalent circuits are equivalent...
... hence source transformation is possible remembering

$$v_{oc} = R_{Th} \cdot i_{sc}$$

Learning Assessment → E5.13

10/2/2019

Use source transformation to find V_o in the network provided.

