

# Last Lecture → Thevenin & Norton

10/2/2019

## 1) Independent Sources Only

- Find either  $V_{oc}$  or  $I_{sc}$
- $R_{Th}$  can be extrapolated directly from the network

## 2) Dependent Sources Only

- The equivalent circuit is  $R_{Th}$  only
- Find  $R_{th}$  through ohms law by placing an voltage/current source and measuring the current/voltage


## 3) Independent and Dependent Sources

- Must calculate both the  $V_{OC}$  and  $I_{SC}$  to calculate  $R_{TH}$ .
- Must not split the dependent source an its controlling variable


# Last Lecture → Source Transformation

10/2/2019

- Thevenin

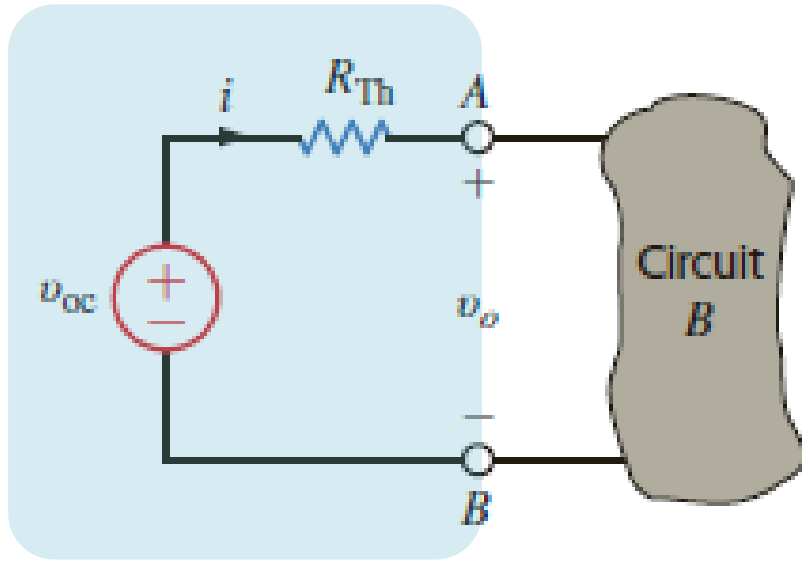

- Norton

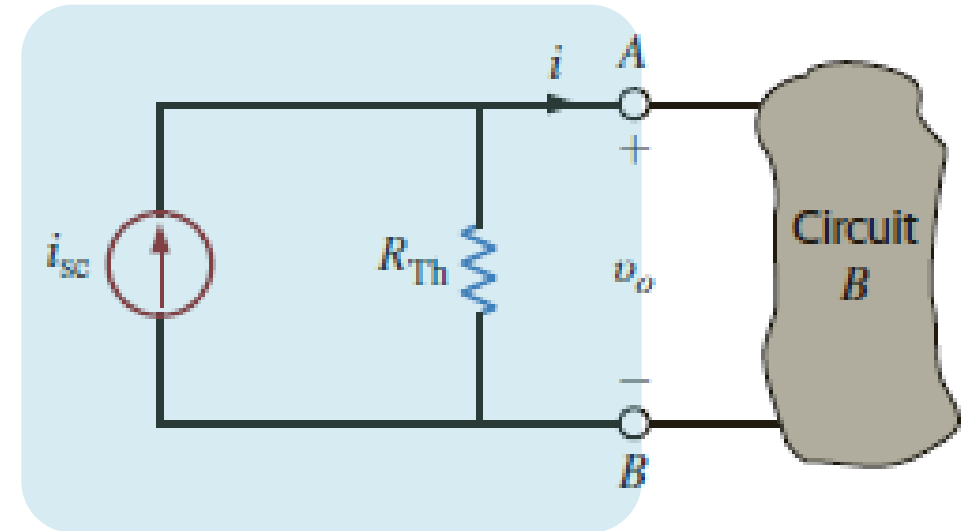


Thevenin and Norton Equivalent circuits are equivalent...  
... hence source transformation is possible remembering

$$v_{oc} = R_{Th} \cdot i_{sc}$$
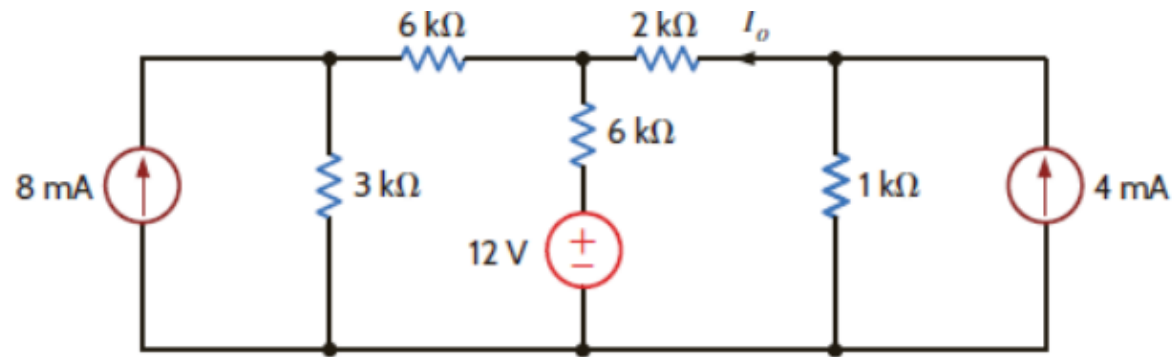
# Learning Assessment → E5.15

10/2/2019


For the given network find  $I_o$  using source transformation.


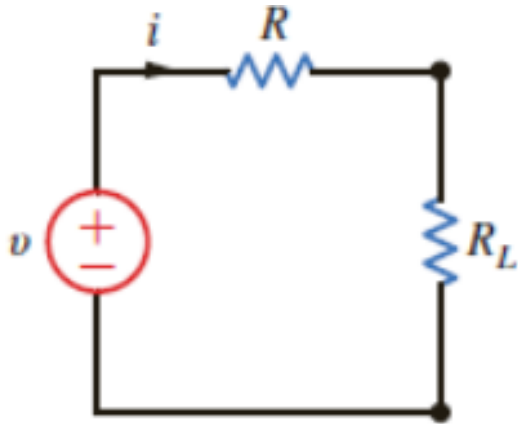
# Maximum Power Transfer

10/2/2019


Determine the value of  $R_L$  such that maximum power is transferred from the source to the load.



$$P_L = \frac{V_L^2}{R_L} = R_L \left[ \frac{v}{(R_L + R)} \right]^2$$

$$\frac{\delta P_L}{\delta R_L} = \left[ \frac{v}{(R_L + R)} \right]^2 - 2 \cdot R_L \left[ \frac{v}{(R_L + R)} \right]^2 \frac{1}{R_L + R} \quad \Rightarrow \quad \frac{\delta P_L}{\delta R_L} = 0 \quad \rightarrow \quad R_L = R$$

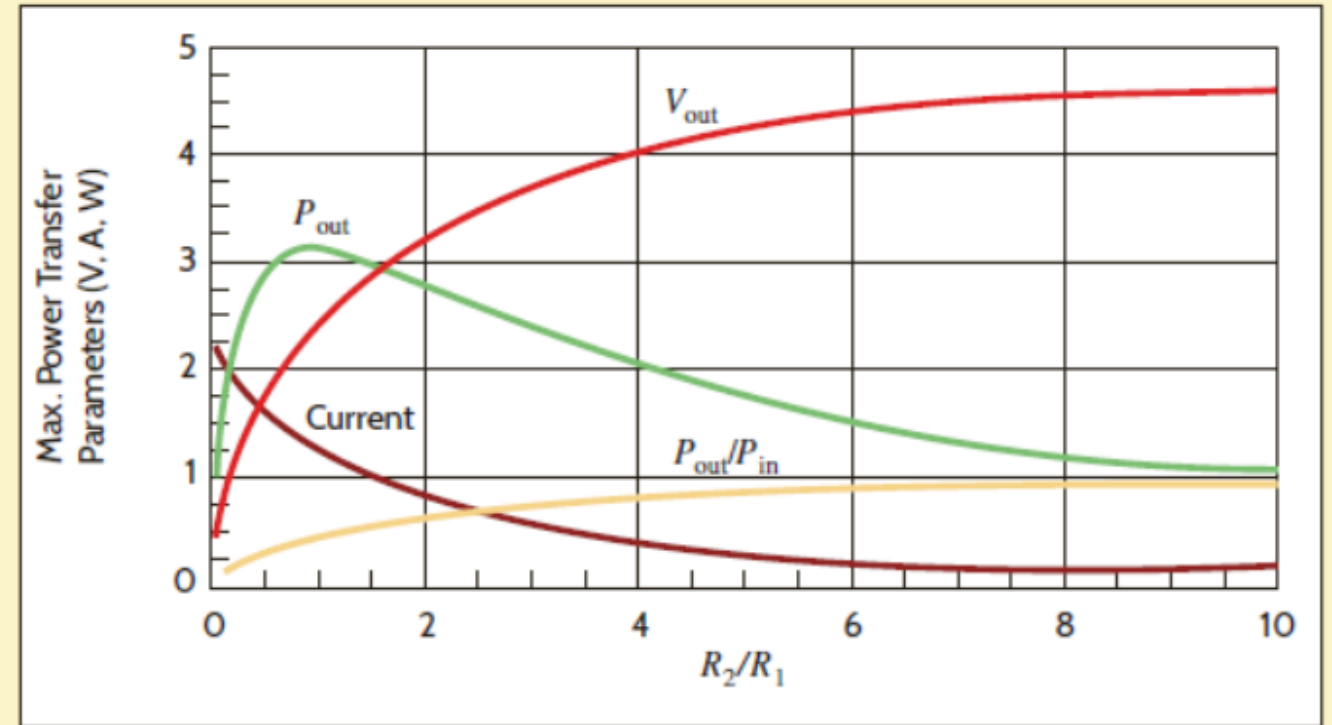
$$\eta = \frac{P_L}{P_{source}} = \frac{R_L}{R_L + R}$$


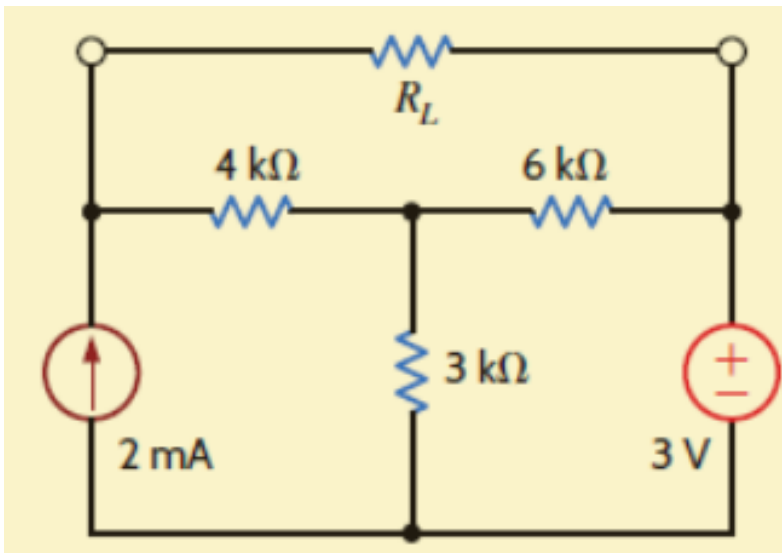
# Example → 5.15

10/2/2019


For the given network find the value of  $R_L$  for maximum power transfer and the maximum power that can be transferred to this load.



# Exam #1 → Grade Distribution

10/2/2019

INEL 4201 - 1er Ex. - 1er. 2019-2020

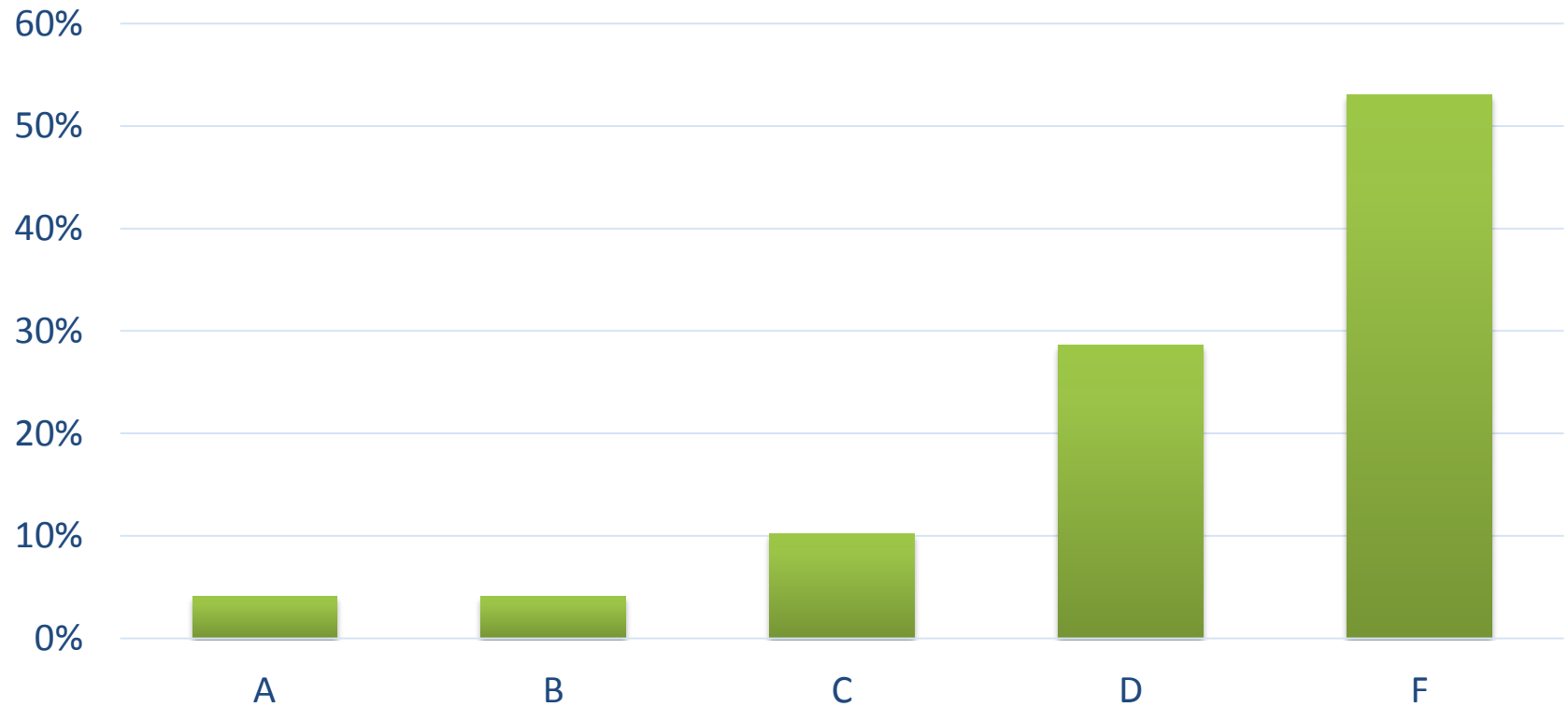

**49 Students**

**A – 2**

**B – 2**

**C – 5**