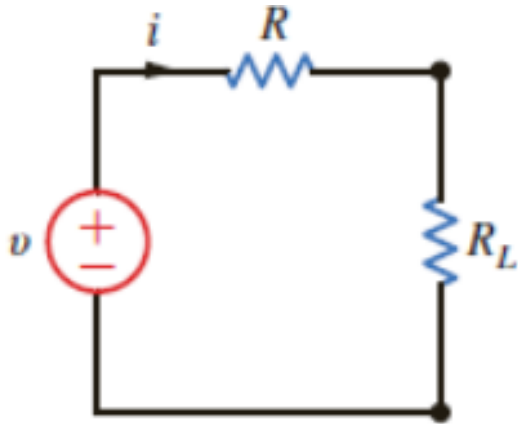


Last Lecture → Maximum Power Transfer

10/2/2019


Determine the value of R_L such that maximum power is transferred from the source to the load.



$$P_L = \frac{V_L^2}{R_L} = R_L \left[\frac{v}{(R_L + R)} \right]^2$$

$$\frac{\delta P_L}{\delta R_L} = \left[\frac{v}{(R_L + R)} \right]^2 - 2 \cdot R_L \left[\frac{v}{(R_L + R)} \right]^2 \frac{1}{R_L + R} \quad \Rightarrow \quad \frac{\delta P_L}{\delta R_L} = 0 \quad \rightarrow \quad R_L = R$$

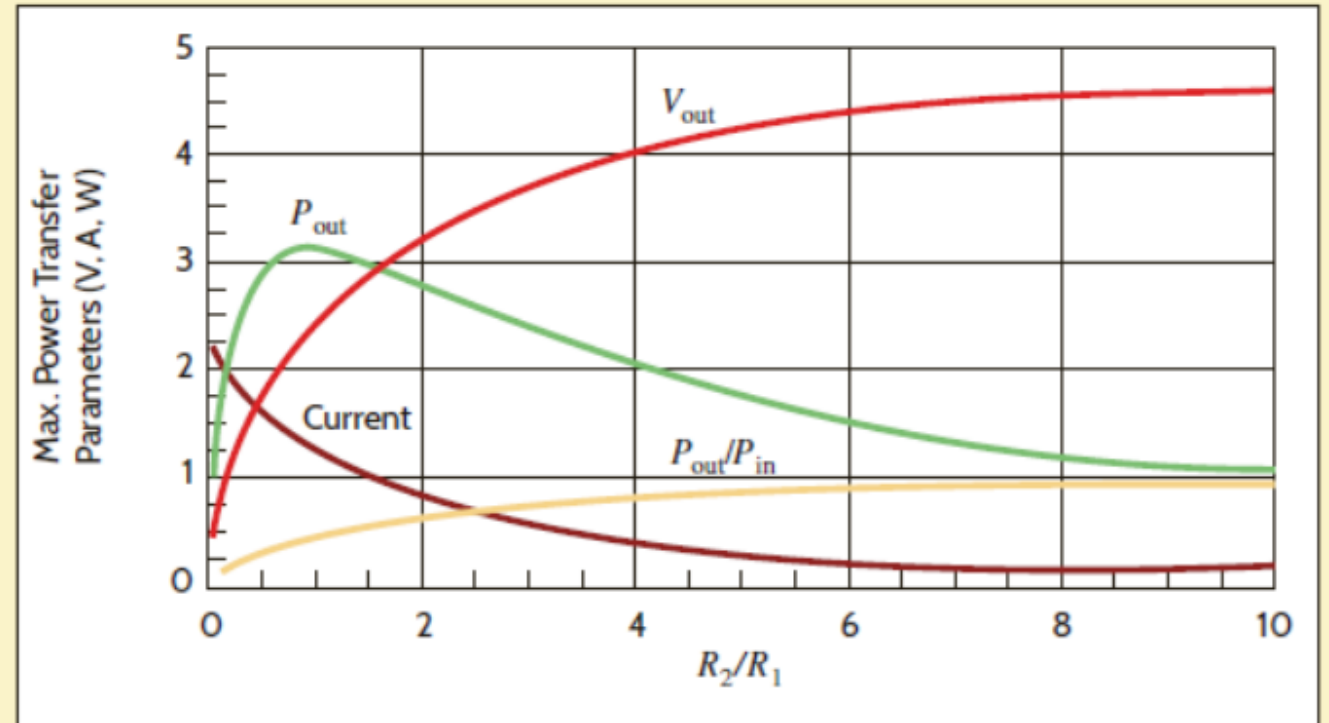
$$\eta = \frac{P_L}{P_{source}} = \frac{R_L}{R_L + R}$$




Operational Amplifiers → Chapter #4

10/2/2019

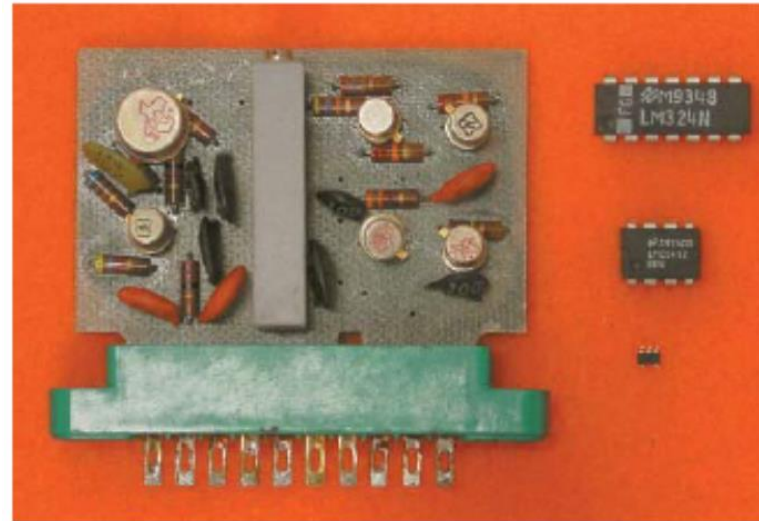- Amplifier Model
- Amplifier Based Circuit Analysis



(a)

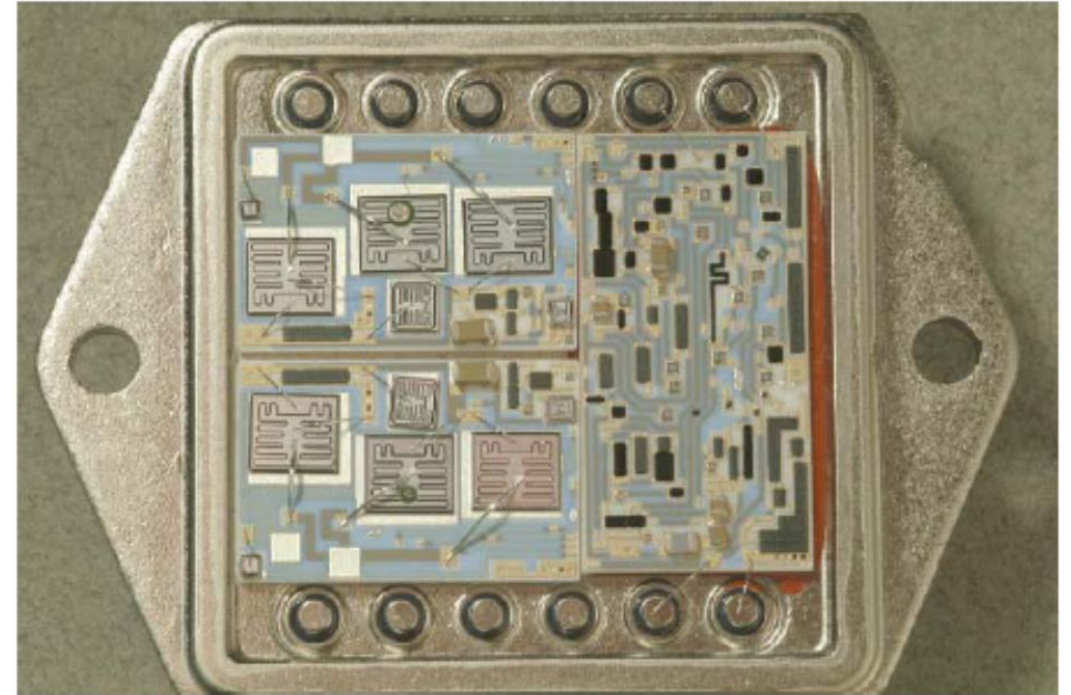

(b)

Op-amps


Op-Amp

- *Is the single most important integrated circuit for analog circuit design*
- *Is a versatile interconnection of transistors and resistors*
- *Is used in a wide range of applications, from engine control systems to cellular phones*
- *Was designed to perform mathematical operations*


Operational Amplifier

10/2/2019

- Internal Circuit Diagram

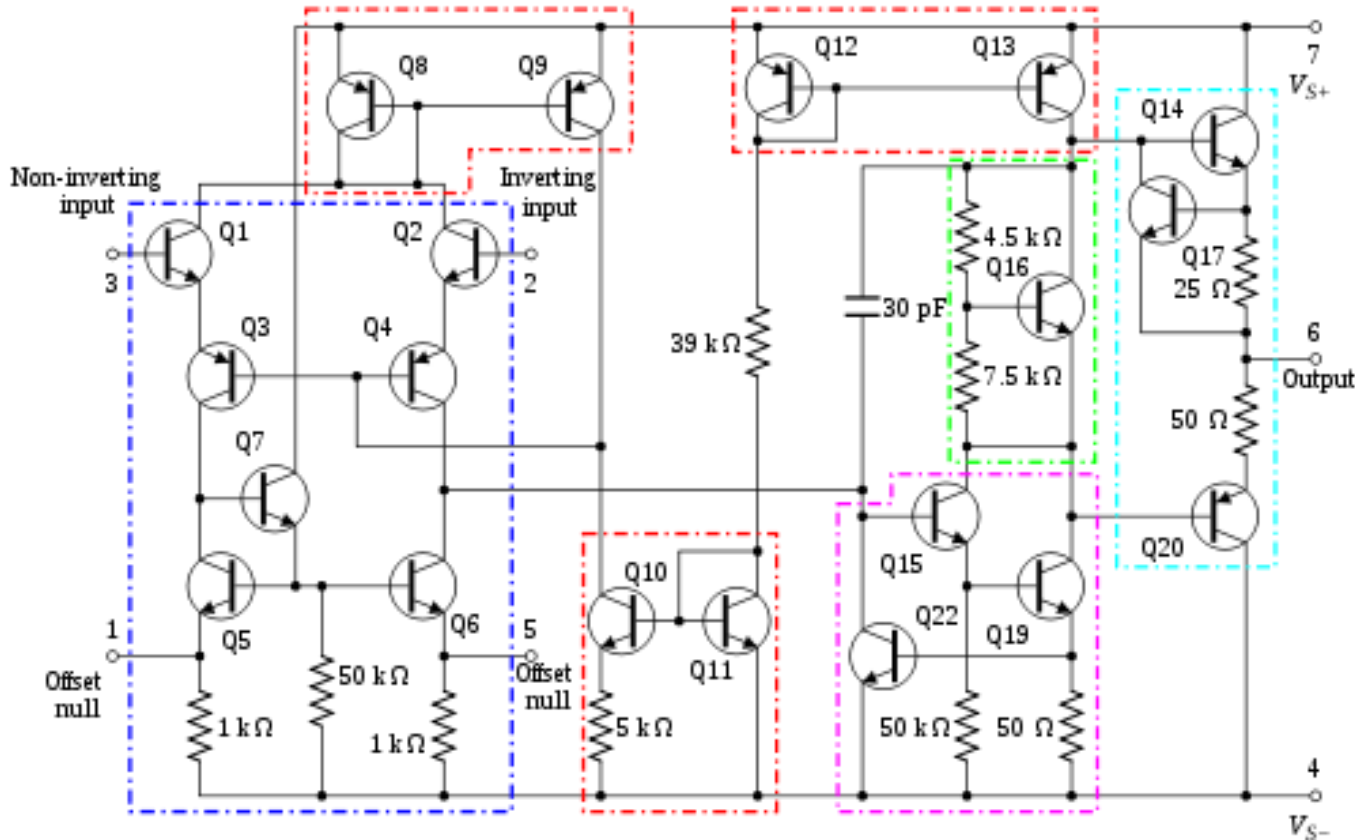

- Symbol / Equivalent Circuit


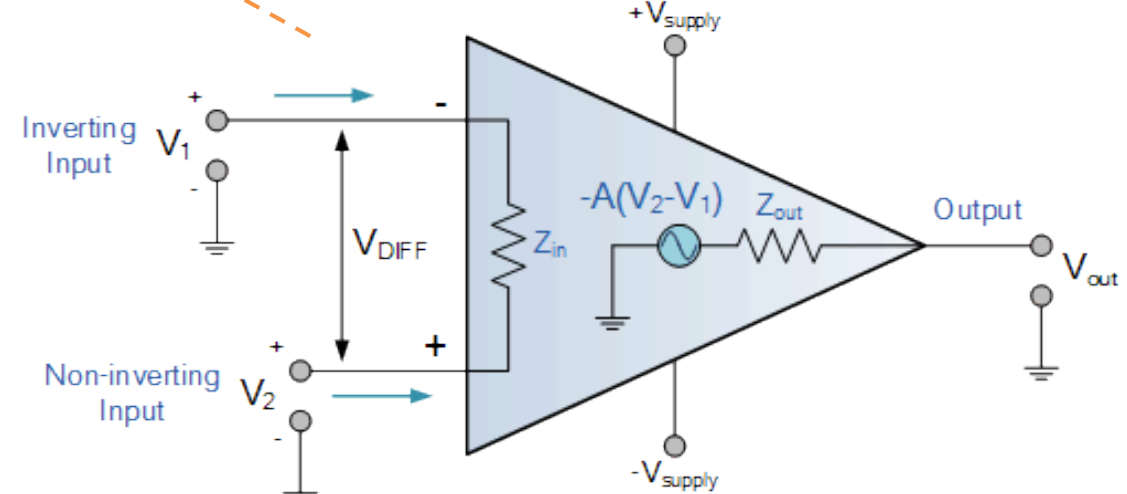


$$V_0 = A_0(IN_+ - IN_-)$$

Op-Amp Model

10/2/2019

LM324 – Dip Package - Pinout

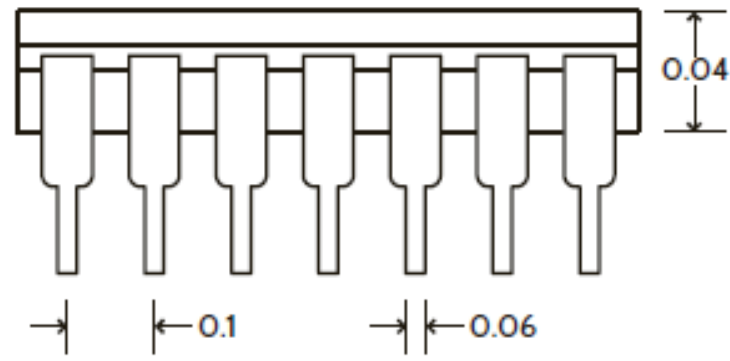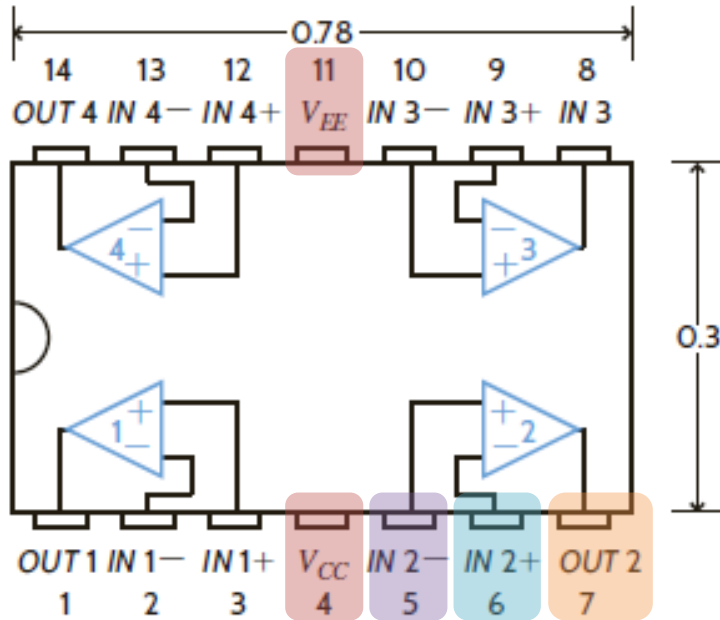


↓ Supply Voltage
↓ Inverting Input
↓ Non-inverting Input
↓ Output

$$V_0 = A_0(IN_+ - IN_-)$$

Gain of op-amp ~ (10,000 – 1,000,000)

Circuit Model

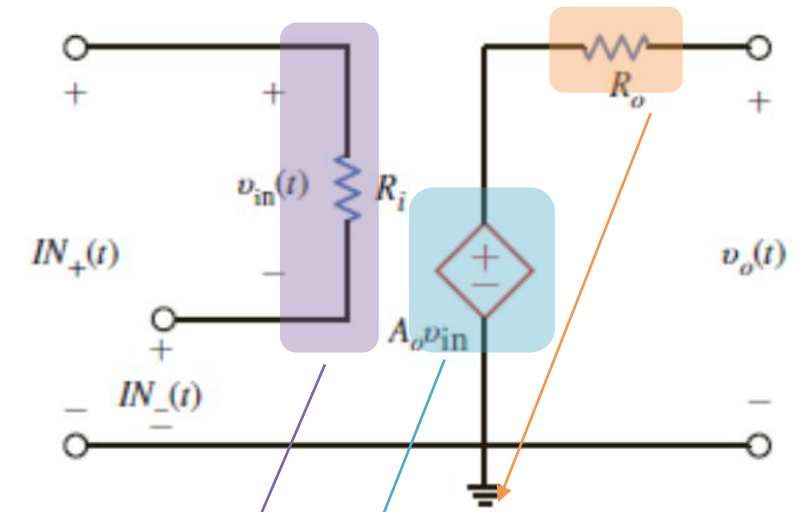


↖ Models I-V relationship at output
↖ Models op-amp gain
↖ Models I-V relationship at input

Circuits 1


Op-Amp Circuit

10/2/2019

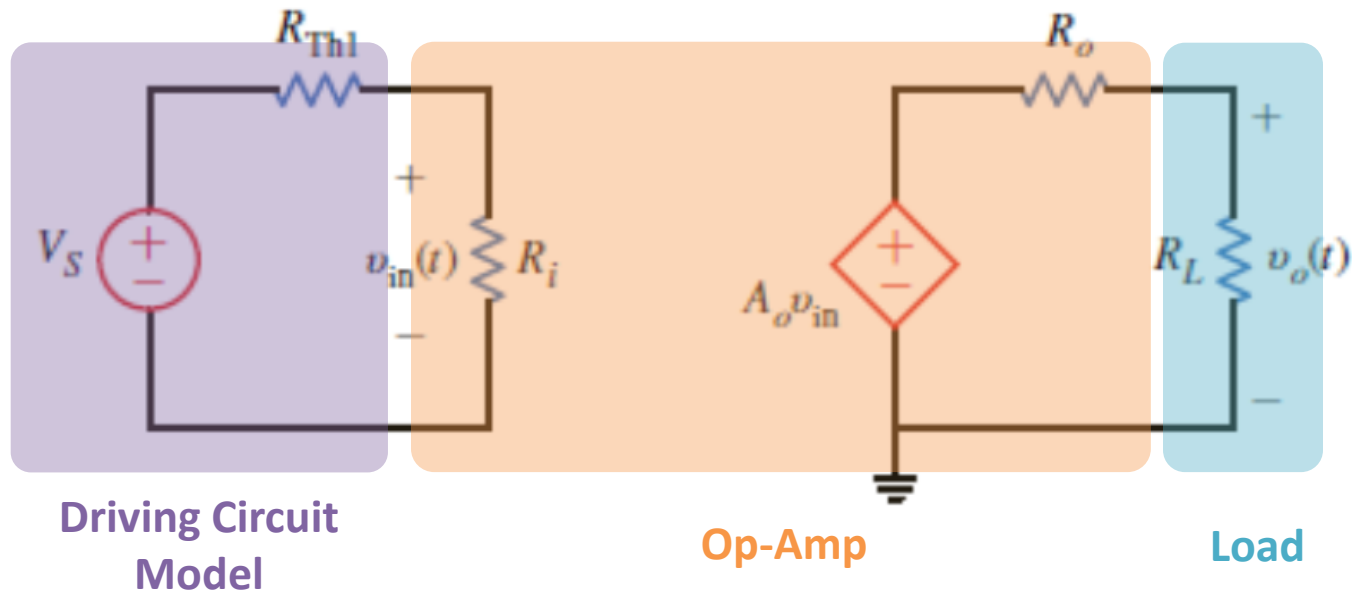

$$\frac{V_o}{V_s} = \left[\frac{R_i}{R_i + R_{TH1}} \right] [A_o] \left[\frac{R_L}{R_L + R_o} \right]$$

$$\text{for } R_i \rightarrow \infty, R_o \rightarrow 0 \quad \frac{V_o}{V_s} = A_o$$

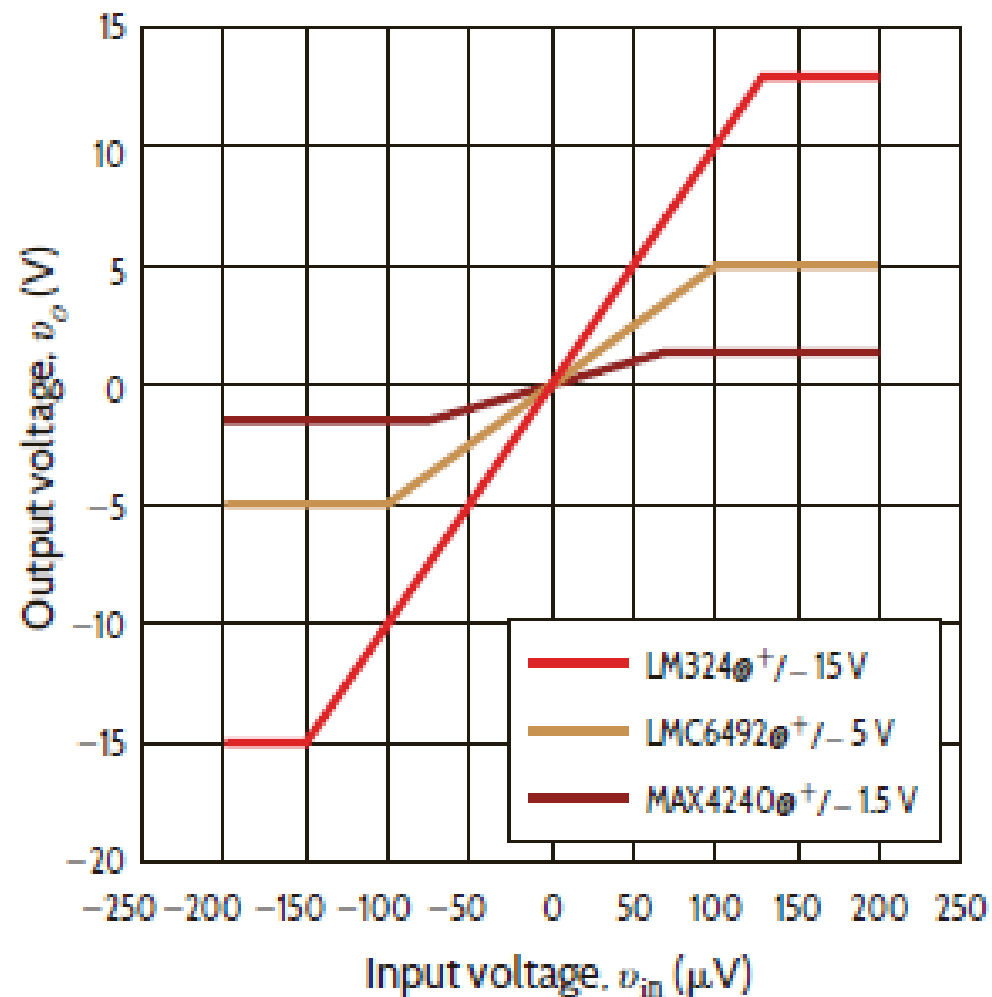

Example 4.1

10/2/2019


The input and output signals for an op-amp circuit are shown in figure below.

Determine:

- if the op-amp circuit is linear, and
- the circuit's gain

Op-amp saturates, therefore not linear

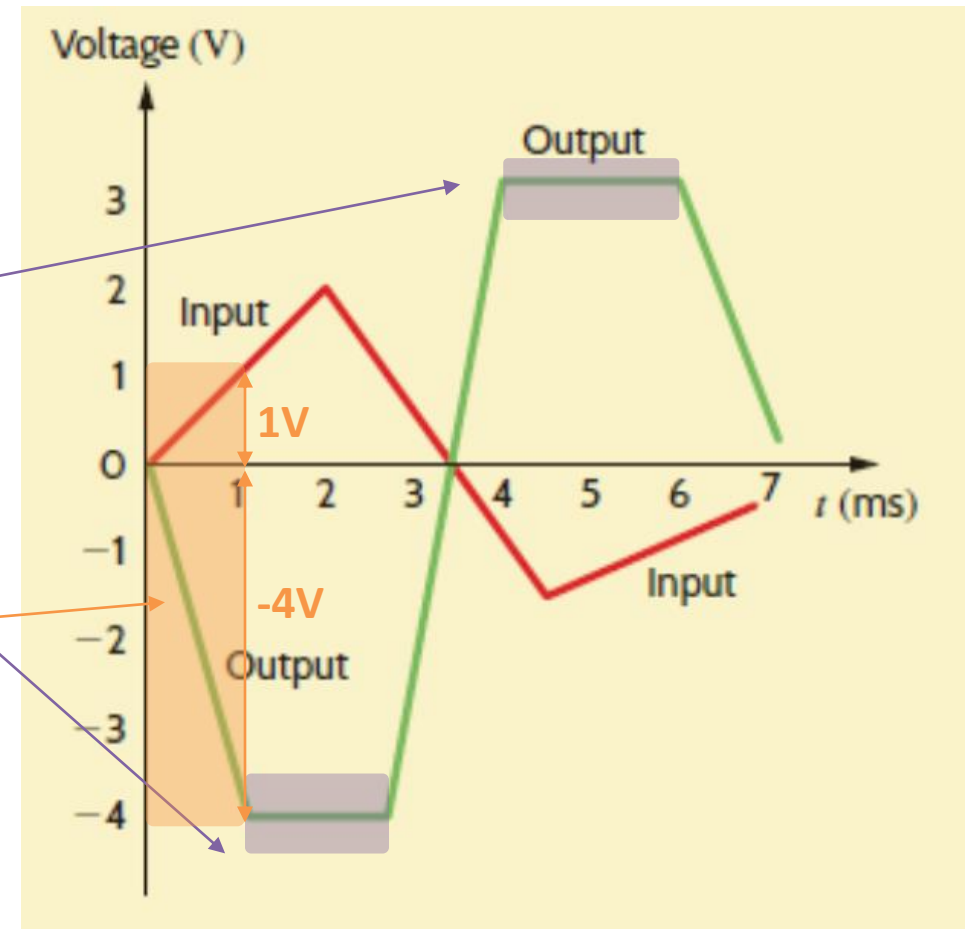
$$\frac{V_o}{V_s} = \frac{-4}{1} = -4V/V$$



Unity Gain Buffer

10/2/2019

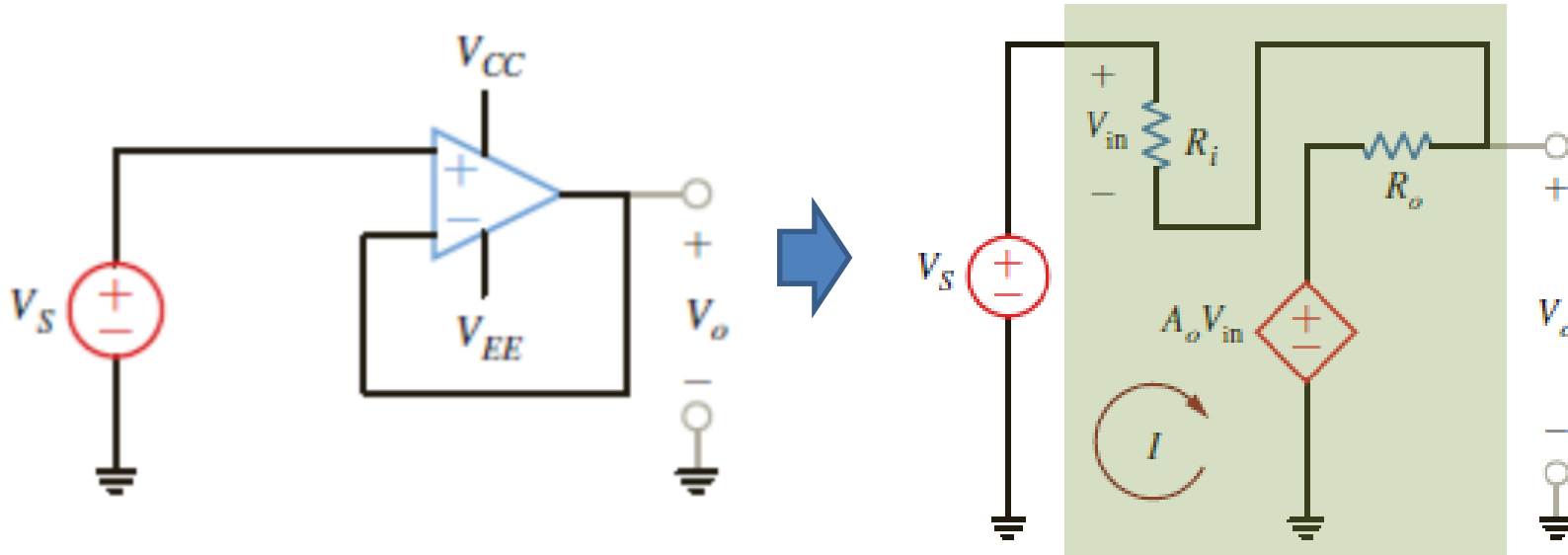Using the op-amp model find the expression for the transfer function V_o/V_s .



Op-Amp Ideal Behavior

- $R_i = \infty$
- $A_o = \infty$
- $R_o = 0$

$$i_{R_i} = \frac{V_{in}}{R_i} = 0$$

$$\therefore i_+ = i_- = 0$$

$$\frac{V_o}{V_s} = \frac{1}{1 + \frac{1}{A_o + \frac{R_o}{R_i}}} \approx \frac{1}{1 + \frac{1}{A_o}} \approx 1$$

$R_i = \infty, R_o = 0$ $A_o = \infty$

$$V_o = A_o(V_+ - V_-)$$

$$\hookrightarrow (V_+ - V_-) = \frac{V_o}{A_o} = 0 \quad \therefore V_+ = V_-$$

Ideal Op-Amp Circuit Analysis

10/2/2019

- Establish ideal op-amp conditions on the circuit schematic
- Write nodal equations at the op-amp input terminals
- Solve for the input/output relationship

MODEL ASSUMPTION

$A_o \rightarrow \infty$

$R_i \rightarrow \infty$


TERMINAL RESULT

input voltage $\rightarrow 0$ Vinput current $\rightarrow 0$ A


$V_+ = V_-$

$i_+ = i_- = 0$

Unity Gain Buffer - Revisited

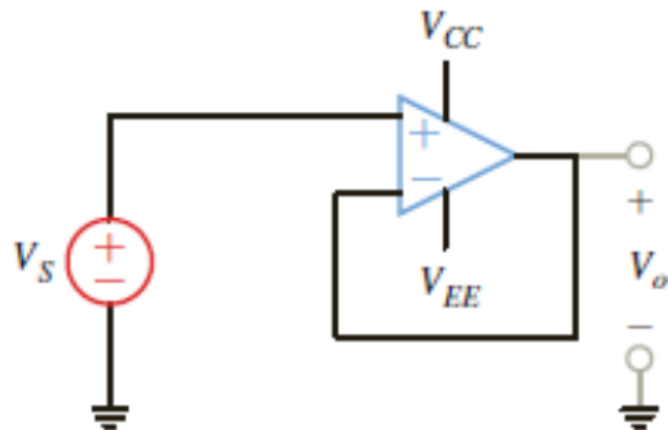


$$\therefore V_o = V_S$$

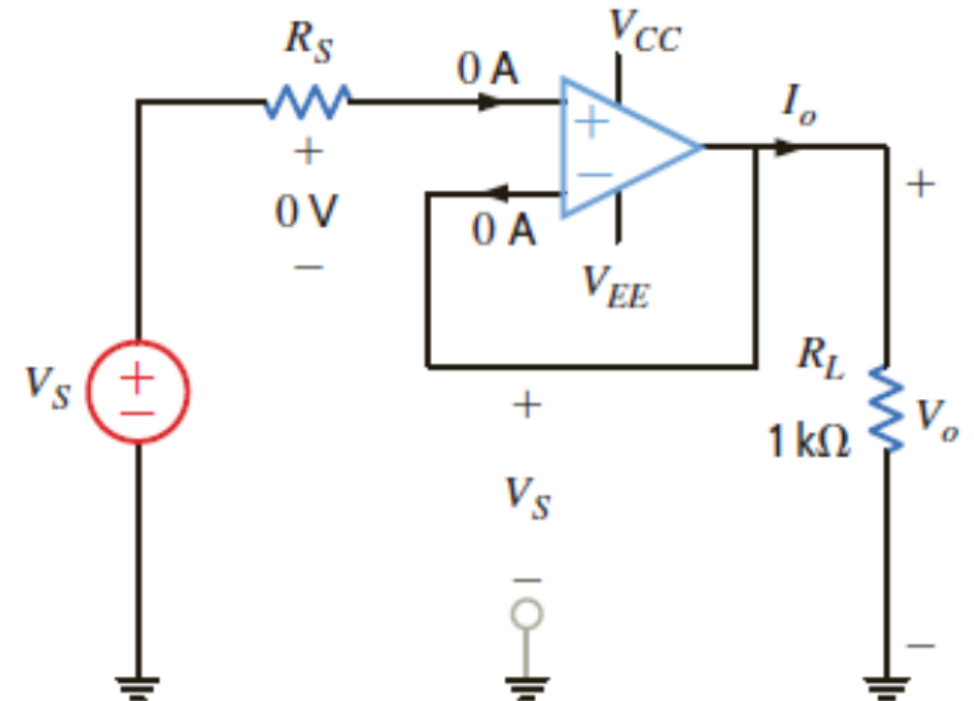

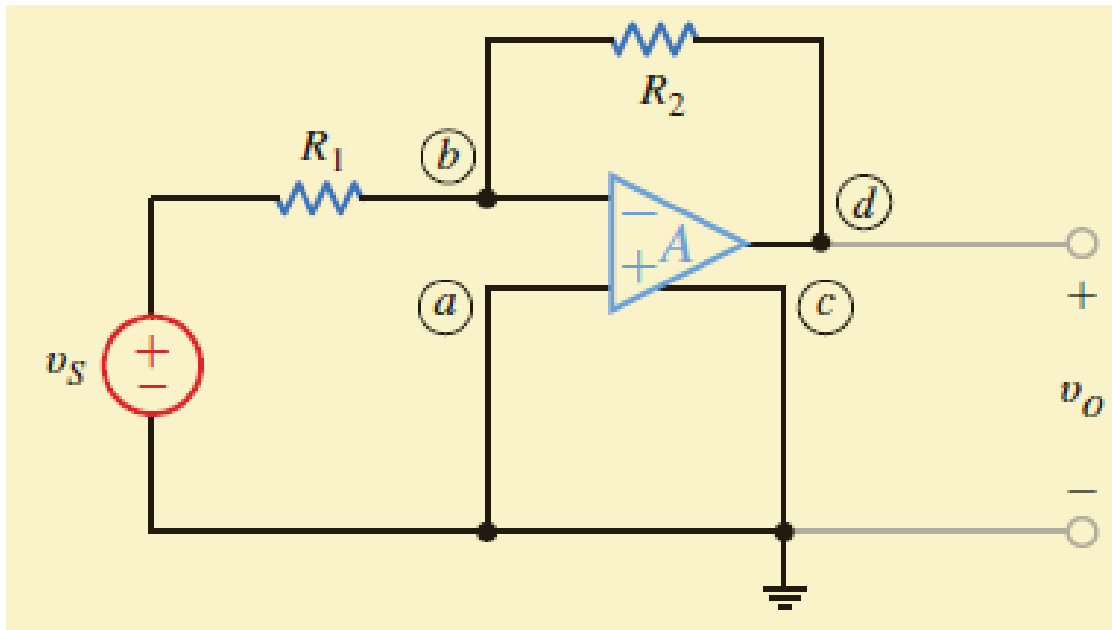Example 4.2

10/2/2019

Determine the gain v_o/v_s of the basic inverting op-amp configuration using both the non-ideal ($R_i=\infty$, $R_o=0$) and the ideal models.




$$\frac{V_o}{V_s} = -\frac{R_2}{R_1} \left[\frac{1}{1 + \frac{1}{A_0} \left(1 + \frac{R_2}{R_1} \right)} \right]$$

$$\text{for } A_0 = \infty \rightarrow \frac{V_o}{V_s} \approx -\frac{R_2}{R_1}$$

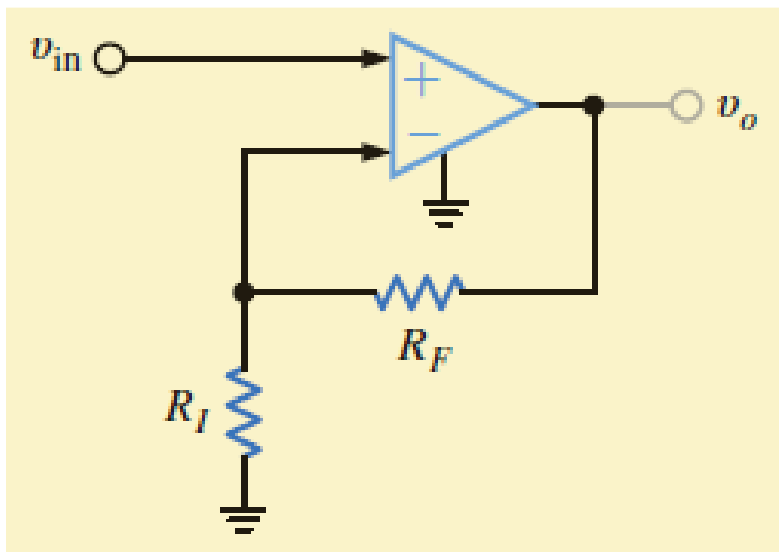Example 4.3

10/2/2019

Determine the gain v_o/v_s of the basic non-inverting op-amp configuration both the non-ideal ($R_i=\infty$, $R_o=0$) and the ideal models. Determine the expression for the gain error (GE).



$$\frac{V_o}{V_s} = \left[1 + \frac{R_F}{R_1} \right] \left[\frac{1}{1 + \frac{1}{A_0} \left(1 + \frac{R_F}{R_1} \right)} \right]$$

$$\text{for } A_0 = \infty \rightarrow \frac{V_o}{V_s} \approx 1 + \frac{R_F}{R_1}$$


$$GE = \left[\frac{A_{v_{ideal}} - A_v}{A_{v_{ideal}}} \right] \cdot 100 = \left[\frac{1}{1 + A_0 \left(\frac{R_1}{R_1 + R_F} \right)} \right] \cdot 100$$

$$\text{for } A_0 = \infty \rightarrow GE \approx 0$$

Op-Amp Basic Circuits


10/2/2019

- Unity – Gain Amp.

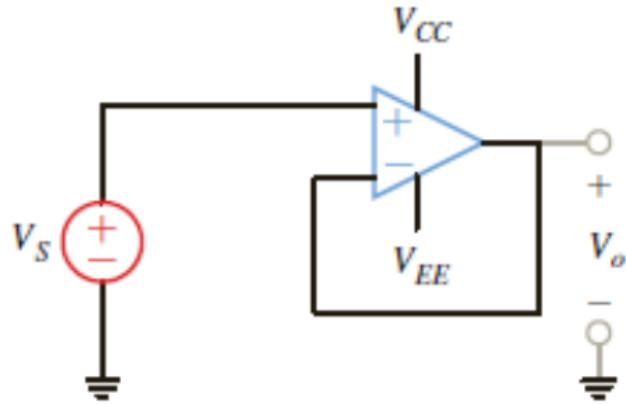


$$\frac{V_o}{V_s} \approx 1$$

- Non-Inverting Amp.

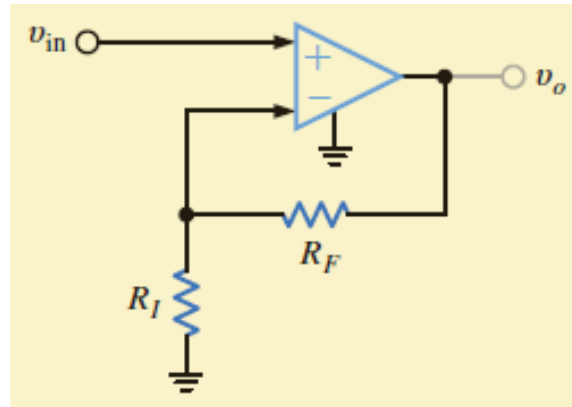

$$\frac{V_o}{V_s} \approx 1 + \frac{R_F}{R_I}$$

- Inverting Amp

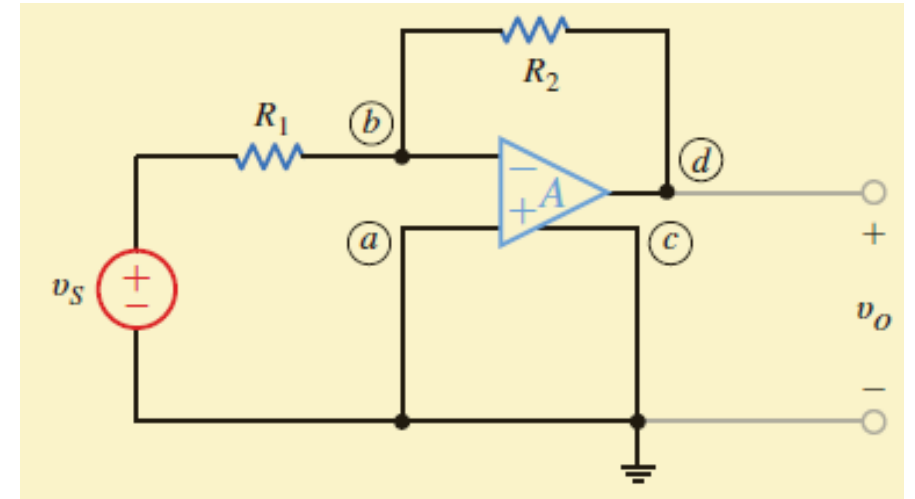


$$\frac{V_o}{V_s} \approx -\frac{R_2}{R_1}$$

Circuits 1

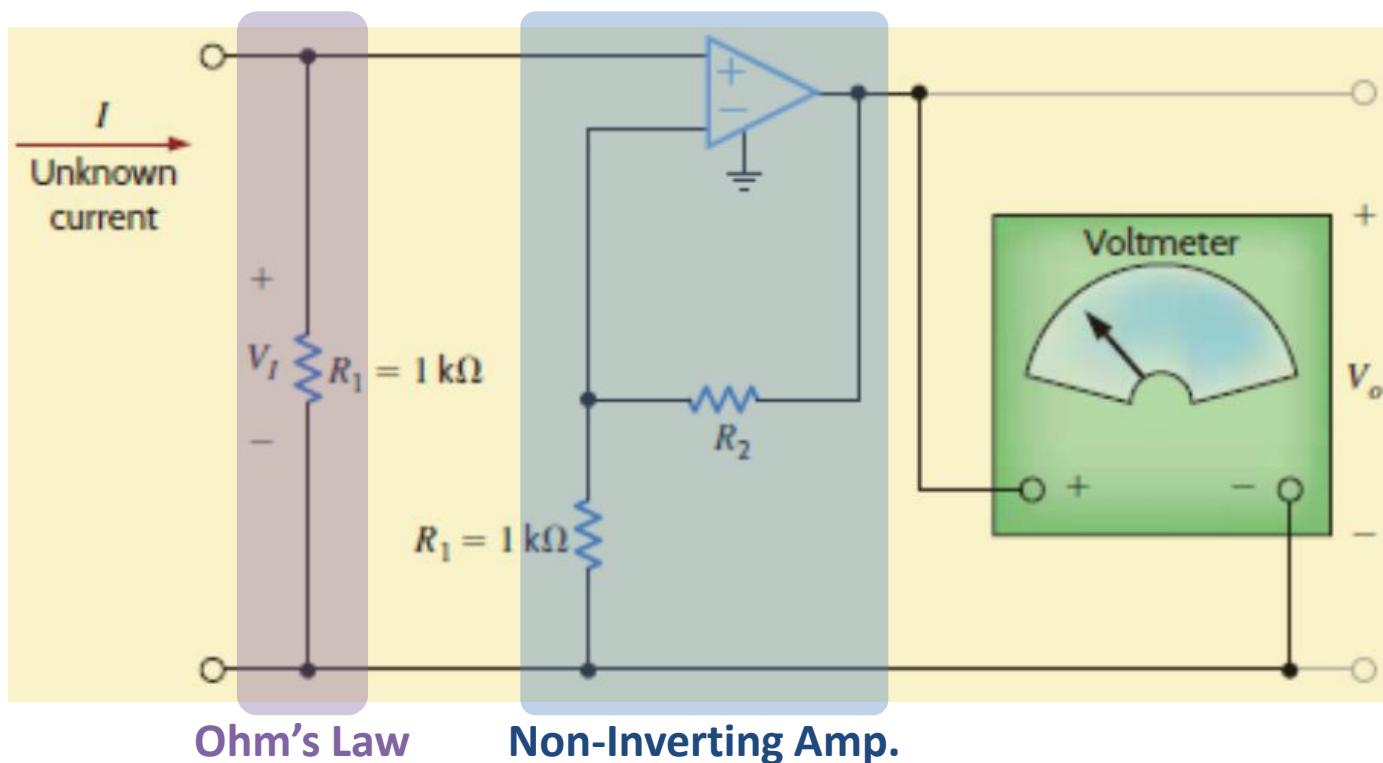Example 4.7

10/2/2019

The provided circuit is an electronic ammeter. It operates as follows: the unknown current, I , through R_1 produces a voltage, V_I . V_I is amplified by the op-amp to produce a voltage, V_o , which is proportional to I . The output voltage is measured with a simple voltmeter. Find the value of R_2 such that 10V appears at V_o for each milliamp of unknown current.



$$\frac{V_o}{I} = \frac{10}{1\text{m}} = 10\text{ k}\Omega$$

$$V_o = \left[1 + \frac{R_2}{1\text{k}} \right] V_I$$

$$V_I = [1\text{k}] \cdot I$$

$$\therefore V_o = [1\text{k} + R_2] \cdot I$$

$$\hookrightarrow \frac{V_o}{I} = [1\text{k} + R_2] = 10\text{ k}\Omega$$

$$\therefore R_2 = 9\text{ k}\Omega$$

Problem

10/2/2019

Determine v_o in the circuit provided.

