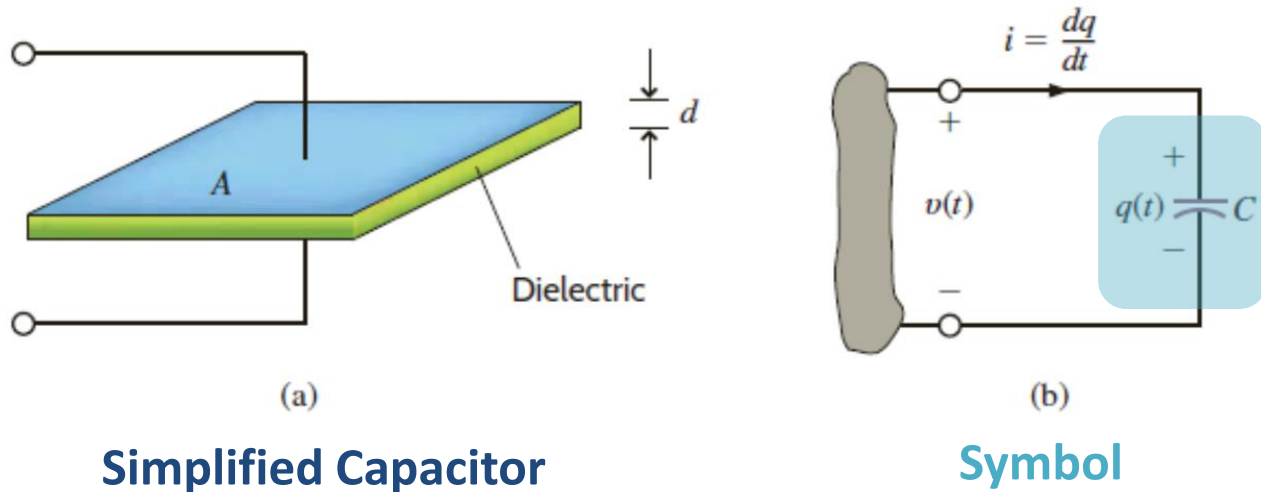


# Last Lecture → Capacitor

10/4/2019

... a circuit element that consists of two conducting surfaces separated by dielectric material



Capacitance (C) →  $C = \frac{\epsilon_0 A}{d}$

↓

permittivity of free space

Unit → farads (F) = coulombs per volts

$$q = C \cdot v \quad i = C \cdot \frac{dv}{dt}$$

$$v(t) = v(t_0) + \frac{1}{C} \cdot \int_{t_0}^t i(x) dx$$


$$p(t) = C \cdot v(t) \frac{dv(t)}{dt}$$

$$w_c(t) = \frac{1}{2} C \cdot v(t)^2$$

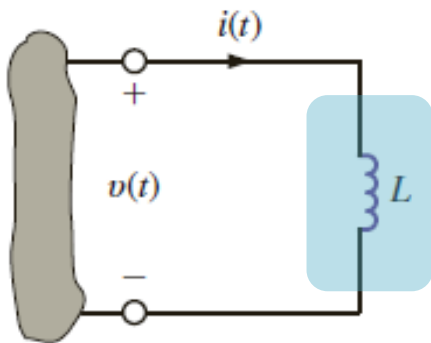
# Last Lecture → Inductor

10/4/2019

... a circuit element that consists of a conducting wire usually in the form of a coil.



Symbol

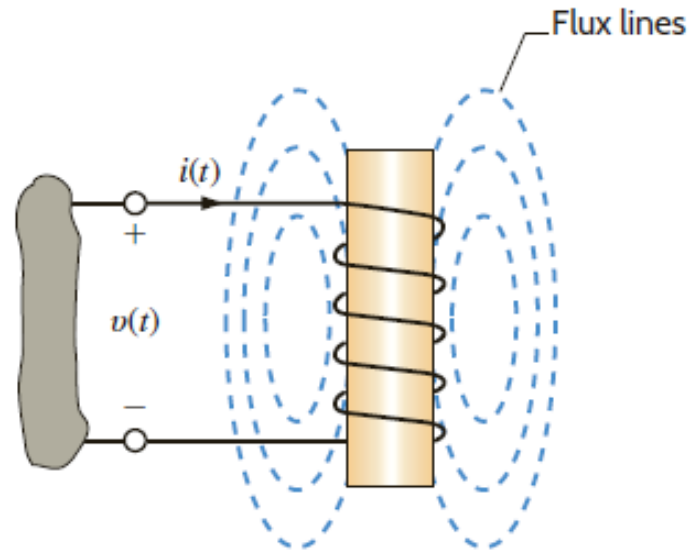

Simplified Inductor

Inductance (L)



Unit → Henry (H) = 1 volt-second per ampere

$$v = L \cdot \frac{di}{dt}$$

$$i(t) = i(t_0) + \frac{1}{L} \cdot \int_{t_0}^t v(x) dx$$


$$p(t) = L \cdot i(t) \frac{di(t)}{dt}$$

$$w_L(t) = \frac{1}{2} L \cdot i(t)^2$$
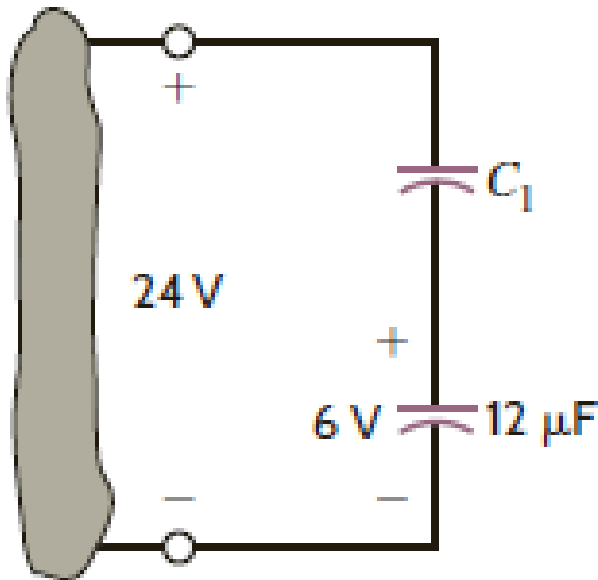
# Learning Assessment E6.11

10/4/2019


Two initially uncharged capacitors are connected as shown in the circuit below. After a period of time, the voltage reaches the value shown. Determine the value of  $C_1$ .



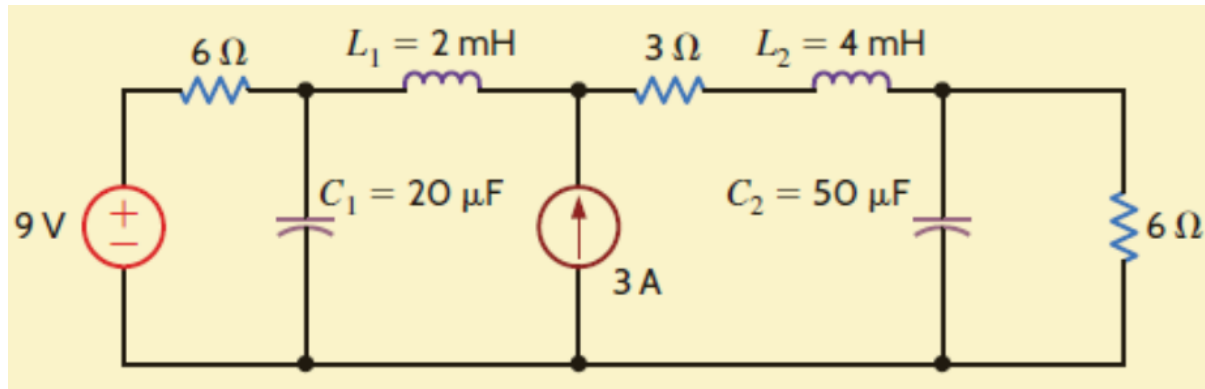
# DC Analysis → Example 6.5

10/4/2019

Find the total energy stored in the circuit provided.




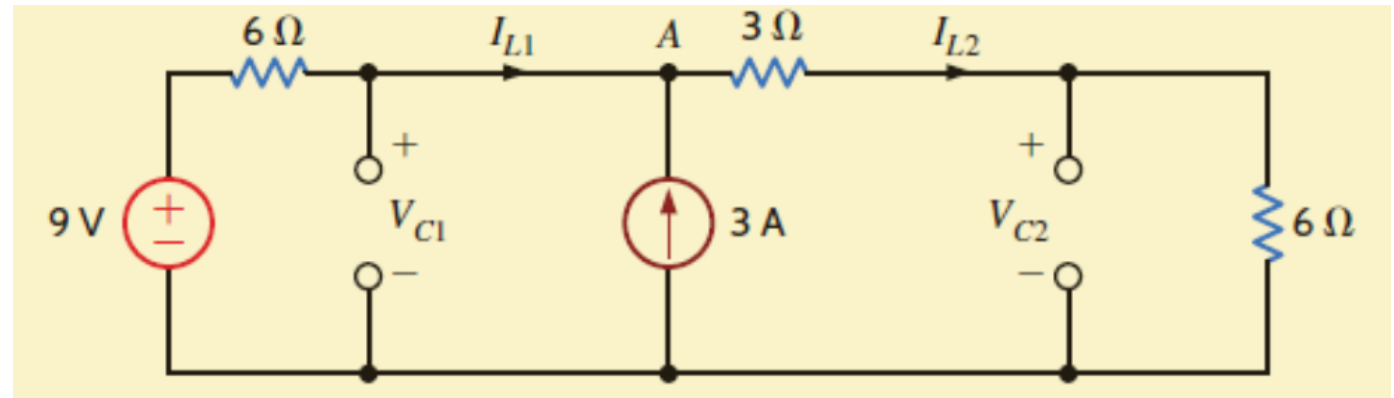@ DC  $V_L = 0$  &  $I_C = 0$   
 → L = short circuit  
 → C = open circuit




## Series \ Parallel Inductors


10/4/2019

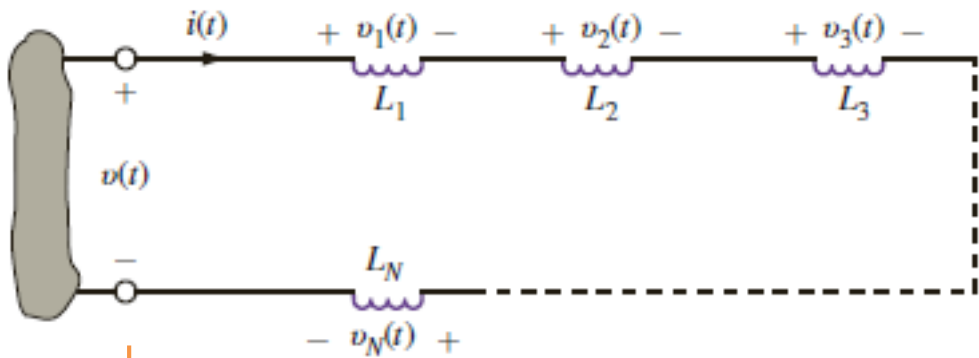

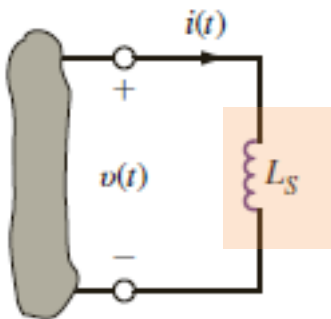
$$\begin{aligned} v(t) &= v_1(t) + v_2(t) + \dots + v_N(t) \\ &= L_1 \frac{di(t)}{dt} + L_2 \frac{di(t)}{dt} + \dots + L_N \frac{di(t)}{dt} \\ &= [L_1 + L_2 + \dots + L_N] \frac{di(t)}{dt} \end{aligned}$$



$$L_S = L_1 + L_2 + \dots + L_N$$

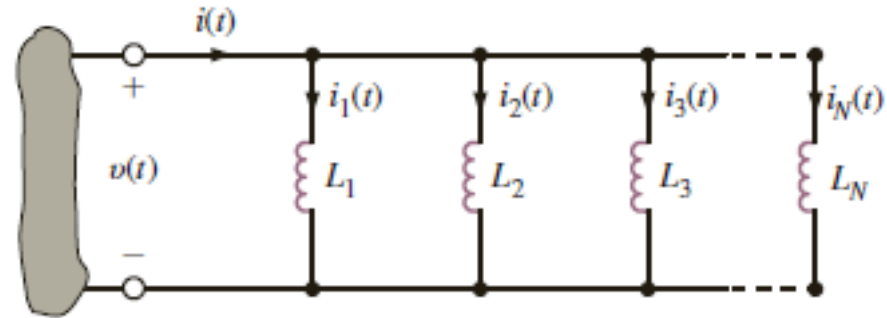

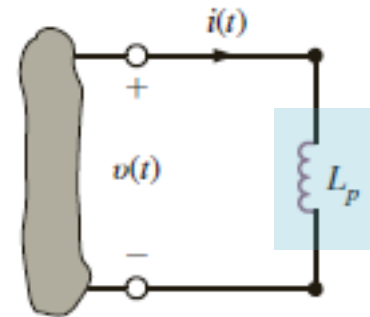
$$\begin{aligned} i(t) &= i_1(t) + i_2(t) + \dots + \\ &= \frac{1}{L_1} v(t) dt + \frac{1}{L_2} v(t) dt + \dots + \frac{1}{L_N} v(t) dt \\ &= \left[ \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right] v(t) dt \end{aligned}$$




$$\frac{1}{L_P} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

# Series \ Parallel Capacitors


10/4/2019

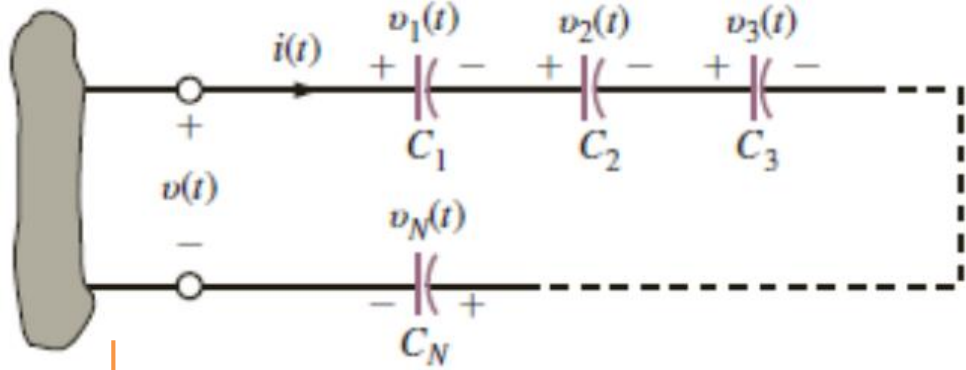

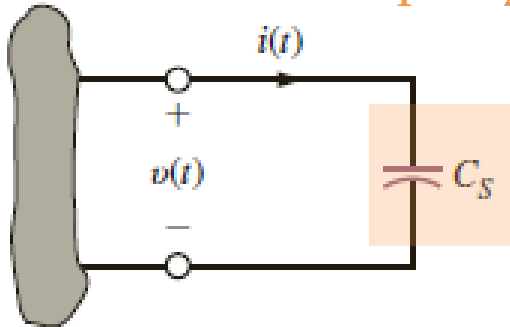
$$\begin{aligned}
 v(t) &= v_1(t) + v_2(t) + \dots + v_N(t) \\
 &= \frac{1}{C_1} i(t) dt + \frac{1}{C_2} i(t) dt + \dots + \frac{1}{C_N} i(t) dt \\
 &= \left[ \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right] i(t) dt
 \end{aligned}$$


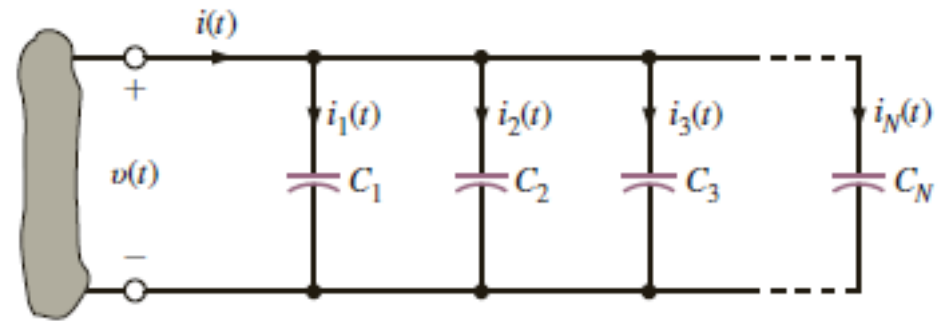
$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$


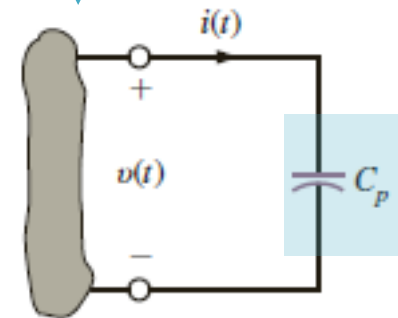
$$\begin{aligned}
 i(t) &= i_1(t) + i_2(t) + \dots + i_N(t) \\
 &= C_1 \frac{dv(t)}{dt} + C_2 \frac{dv(t)}{dt} + \dots + C_N \frac{dv(t)}{dt} \\
 &= [C_1 + C_2 + \dots + C_N] \frac{dv(t)}{dt}
 \end{aligned}$$




$$C_p = C_1 + C_2 + \dots + C_N$$
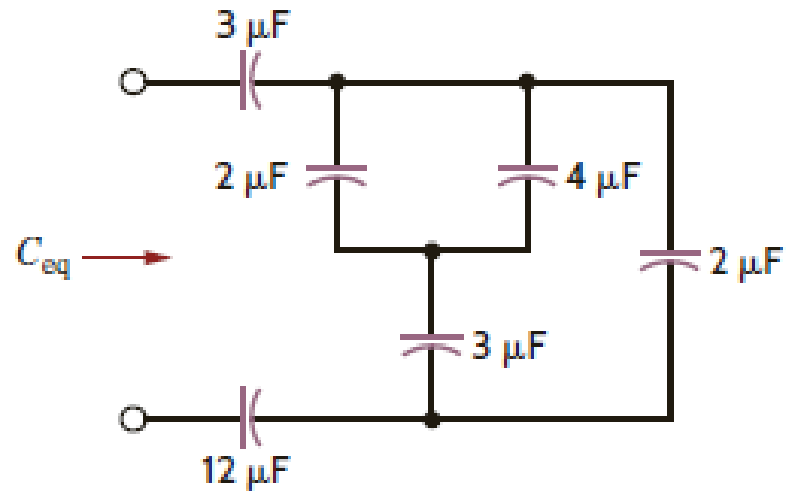
# Learning Assessment E6.12

10/4/2019


Compute the equivalent capacitance of the network provided.



# Learning Assessment E6.15

10/4/2019

Find  $L_T$  in the network provided.

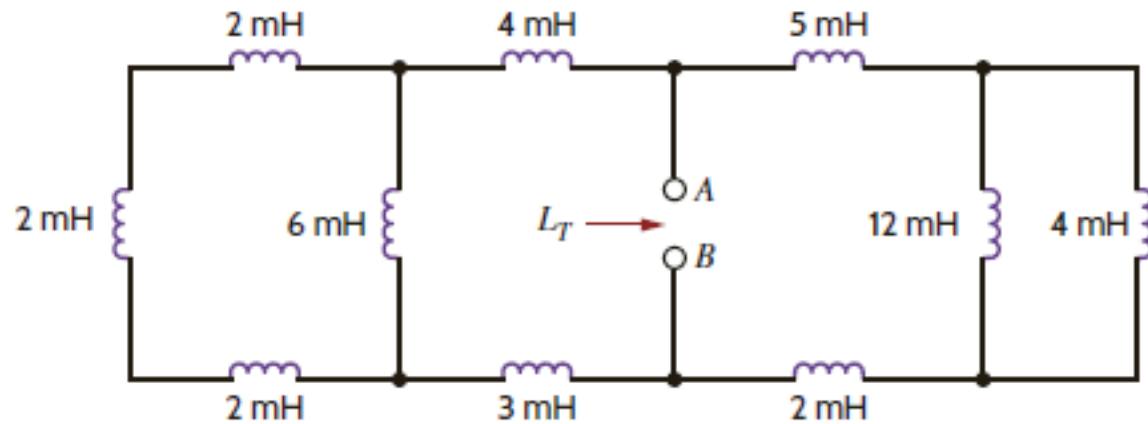



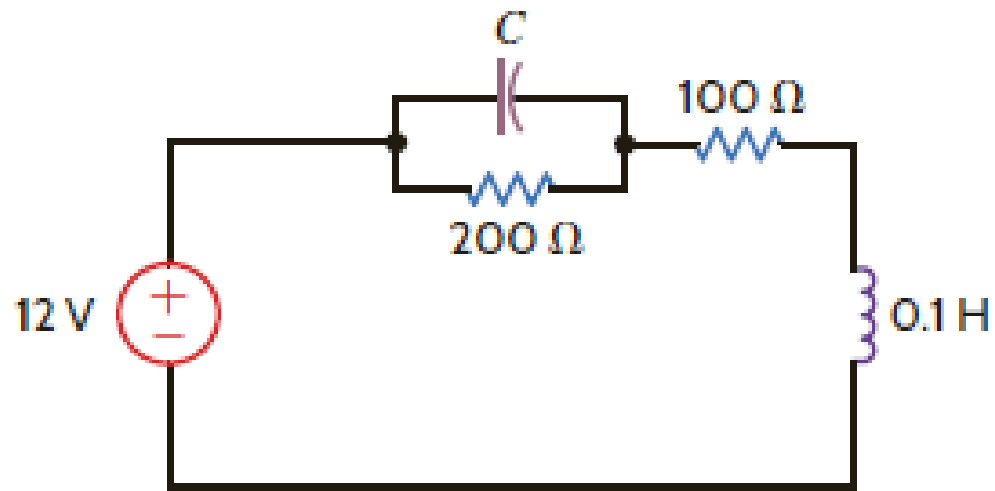
# Problem 6.38

10/4/2019


Find the value of  $C$  if the energy stored in the capacitor equals the energy stored in the inductor.


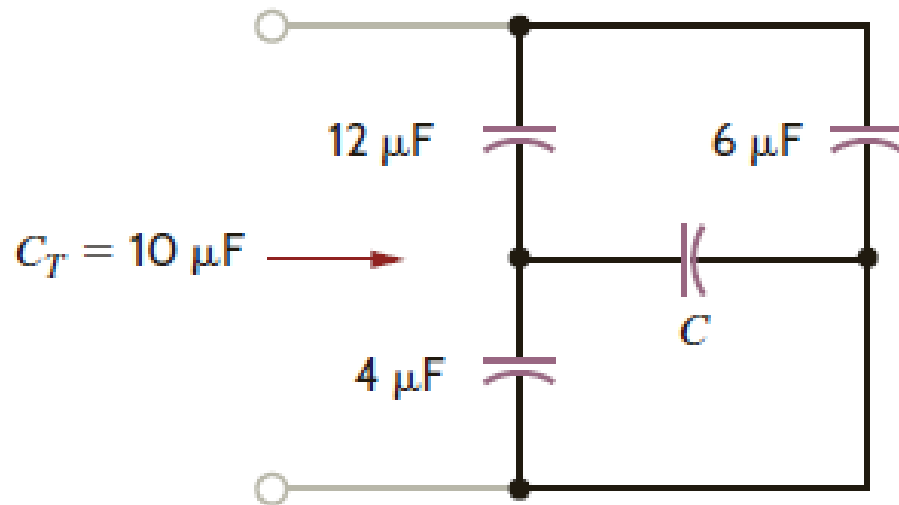
# Problem 6.57

10/4/2019


If the total capacitance of the provided network is  $10\mu\text{F}$ , find the value of  $C$ .


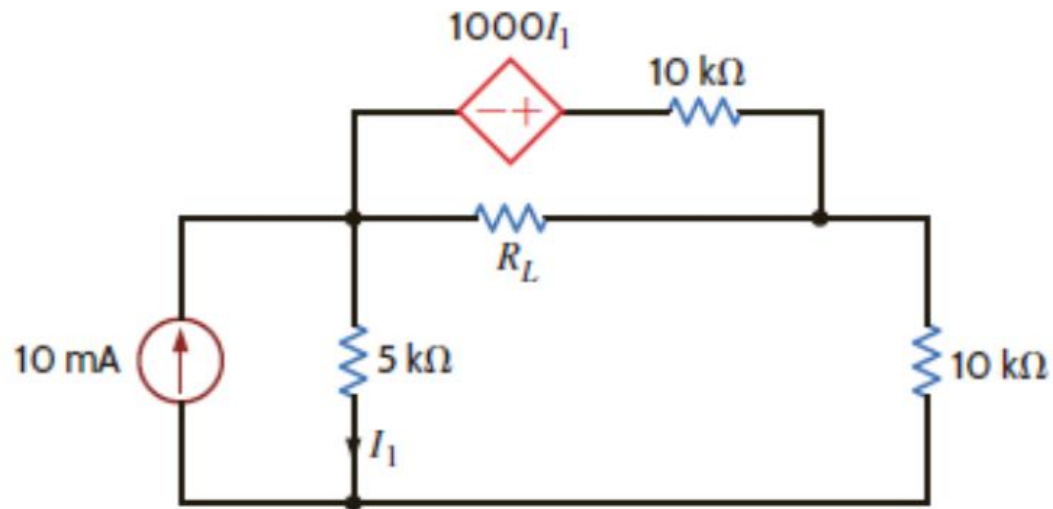
# Problem → P5.124

10/4/2019


For the given network find the value of  $R_L$  for maximum power transfer and the maximum power that can be transferred to this load.


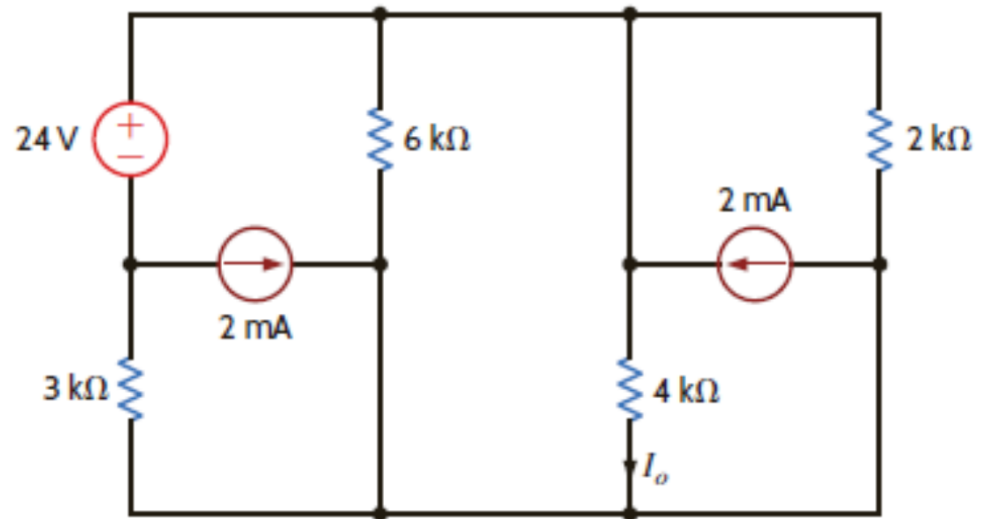
# Problem → P5.106

10/4/2019


Using source transformation, find  $I_o$  in the circuit provided.


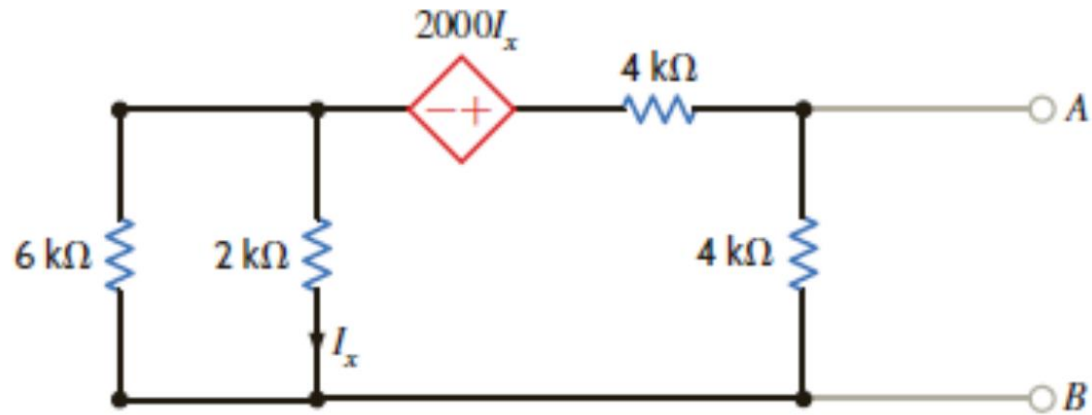
# Problem → P5.87

10/4/2019


Find the Thevenin's equivalent circuit of the provided network at terminals A-B.


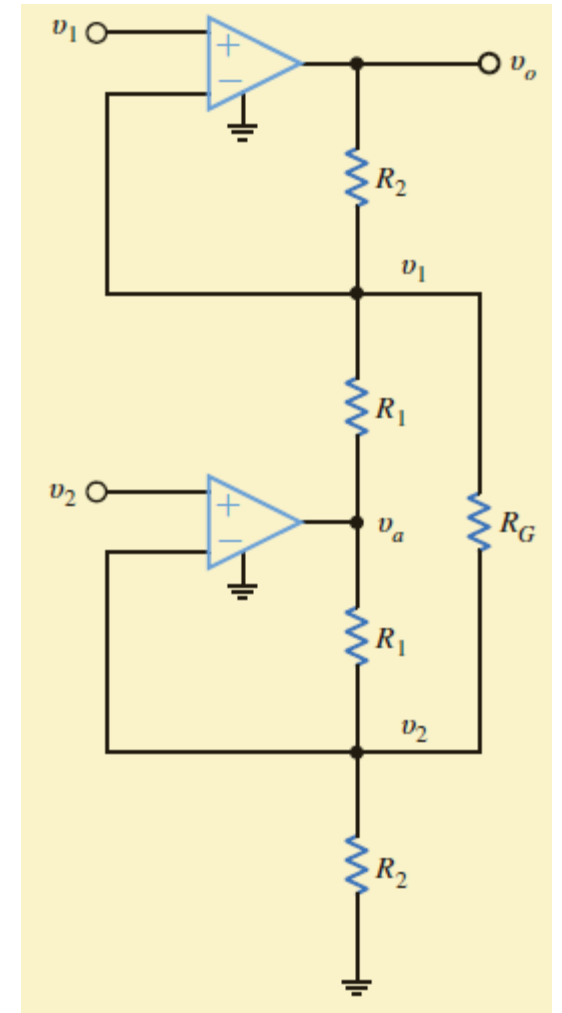
# Example 4.5

10/4/2019

The circuit shown is a precision differential voltage-gain device. It is used to provide a single-ended input for an analog-to-digital converter. Derive an expression for the output of the circuit in terms of the two inputs.




# Learning Assessment – E4.5

10/4/2019

Assuming ideal op-amp behavior find  $V_o$  in terms of  $V_1$  and  $V_2$ . If  $V_1=V_2=4$  find  $V_o$ . If the op-amp power supplies are  $\pm 15V$  and  $V_2=2V$ , what is the allowable range of  $V_1$ ?

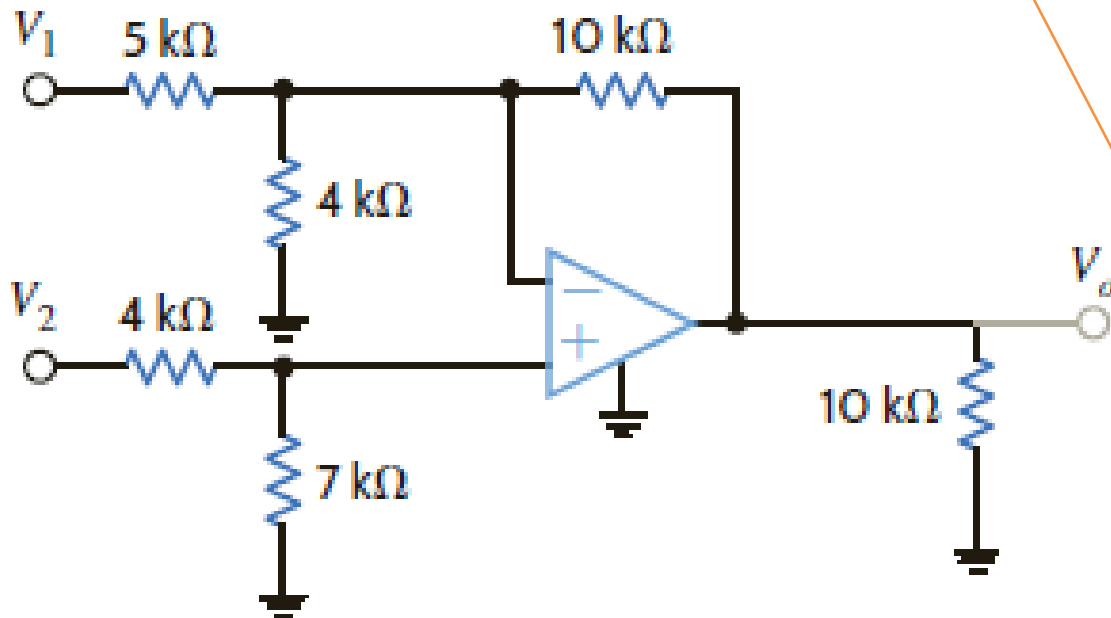→ Superposition: Inverting Amp. / Non-Inverting Amp.



$$V_o' = -V_1 \left[ \frac{10k}{5k} \right] = -2 \cdot V_1$$

$$V_o'' = V_2 \left[ \frac{7k}{11k} \right] \left[ 1 + \frac{10k}{4k//5k} \right] = 3.5 \cdot V_2$$

$$\therefore V_o = -2 \cdot V_1 + 3.5 \cdot V_2$$

$$-15V \leq V_o \leq 15V$$


$$\therefore V_o = -2 \cdot V_1 + 3.5 \cdot V_2 \leq 15$$

$$\therefore V_o = -2 \cdot V_1 + 3.5 \cdot V_2 \geq -15$$
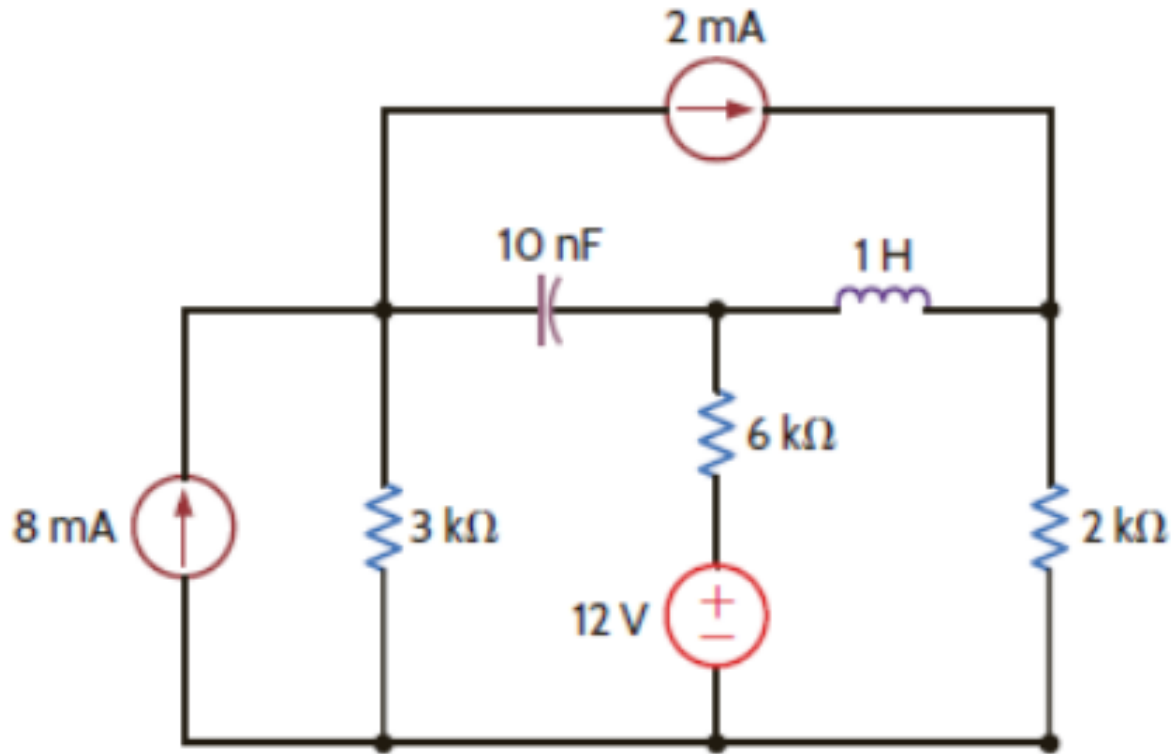
# Learning Assessment E6.10

10/4/2019

For the provided circuit find the energy stored in the capacitor and the inductor.





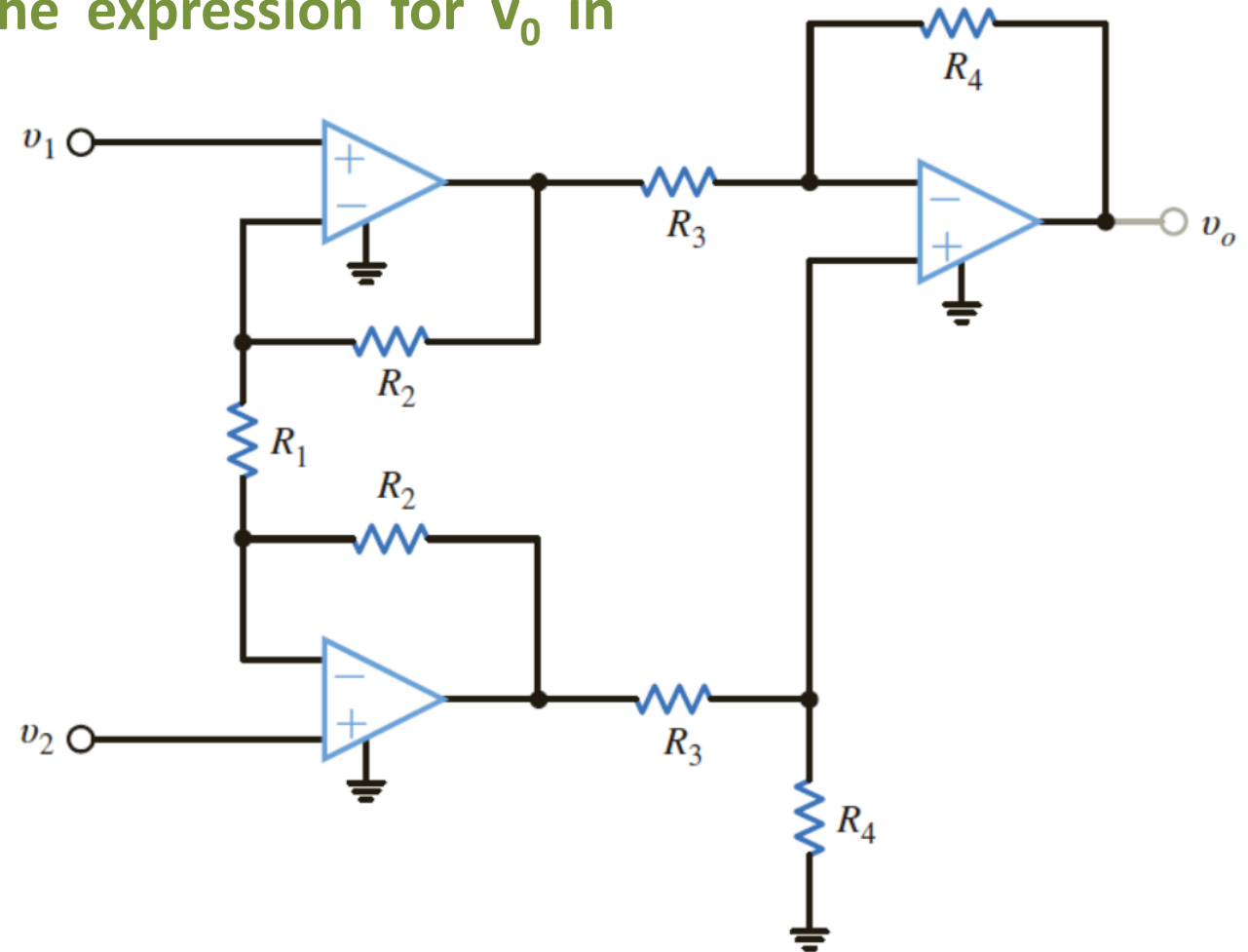
# Problem 4.43

10/4/2019

Assuming ideal op-amp behavior, find the expression for  $v_o$  in terms of  $(v_2 - v_1)$ .




# Learning Assessment – E4.6

10/4/2019

Assuming ideal op-amp behavior find  $V_0$  and  $V_3$  in the provided circuit.

Superposition:  
Voltage Divider

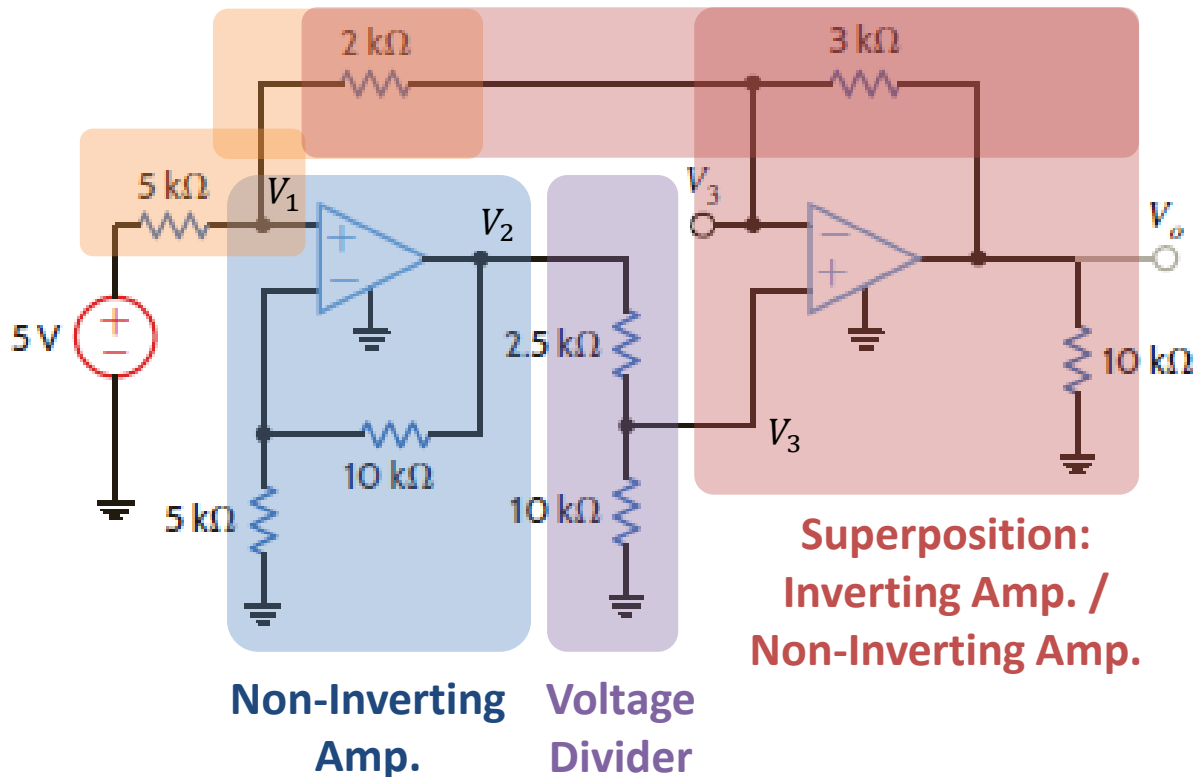

$$V_2 = \left[ 1 + \frac{10k}{5k} \right] V_1 = 3 \cdot V_1$$

$$V_3 = \left[ \frac{10k}{10k + 2.5k} \right] V_2 = \frac{4}{5} \cdot V_2 = \frac{12}{5} \cdot V_1$$

$$\begin{aligned} V_0 &= \left[ 1 + \frac{3k}{2k} \right] V_3 - \left[ \frac{3k}{2k} \right] V_1 \\ &= \frac{5}{2} \cdot V_3 - \frac{3}{2} \cdot V_1 = 6 \cdot V_1 - \frac{3}{2} \cdot V_1 = \frac{9}{2} \cdot V_1 \end{aligned}$$

$$V_1 = \left[ \frac{2k}{7k} \right] 5 + \left[ \frac{5k}{7k} \right] V_3 = \frac{10}{7} + \frac{12}{7} \cdot V_1$$

$$\therefore V_1 = -2V$$

$$\therefore V_0 = -9V$$

$$\therefore V_3 = -4.8V$$