

AC Steady State Analysis → Chapter #8

10/28/2019

- **Basic Characteristics of Sinusoidal Functions**
- **Phasor / Inverse Phasor Transformations & Diagrams**
- **Impedance and Admittance → R, L, C**
- **Equivalent Impedance / Equivalent Admittance**
- **Equivalent Circuit in Frequency Domain**
- **Apply Circuit Analysis Techniques to Frequency Domain Circuits**

Sinusoids



10/28/2019

$$x(t) = X_M \cdot \sin(\omega t + \theta)$$

- X_m → amplitude / maximum value
- ω → radian / angular frequency
- θ → phase angle

- T → period
- $f = \frac{1}{T}$ → # cycles per second

$$\omega = \frac{2\pi}{T} = 2\pi f$$

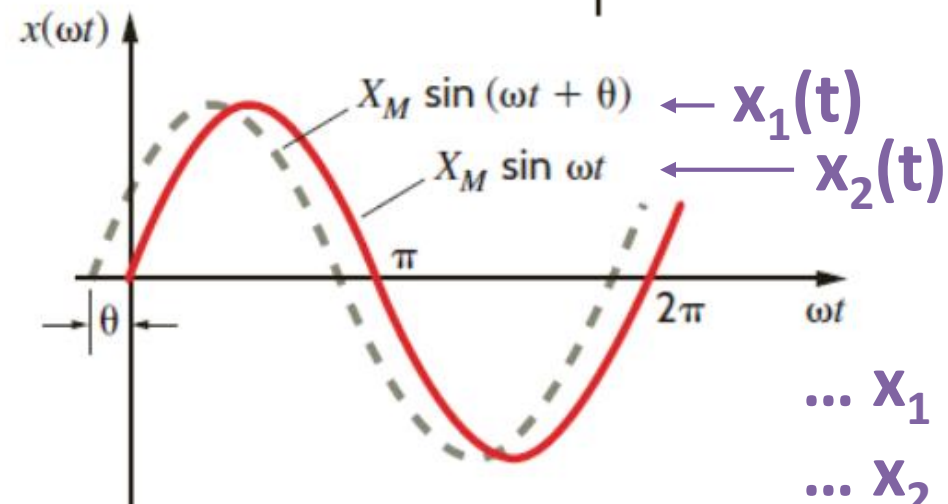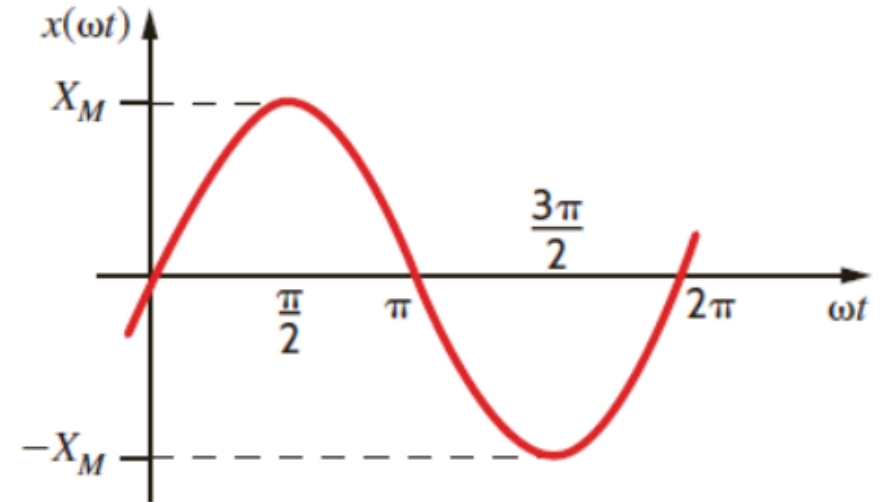

... x_1 leads x_2 by θ
 ... x_2 lags x_1 by θ

Trigonometric Identities

10/28/2019

$$-\cos(\omega t) = \cos(\omega t \mp 180^\circ)$$

$$-\sin(\omega t) = \sin(\omega t \mp 180^\circ)$$

$$\cos(\omega t) = \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$\sin(\omega t) = \cos\left(\omega t - \frac{\pi}{2}\right)$$

$$\sin(\alpha + \beta) = \sin(\alpha) \cos(\beta) + \cos(\alpha) \sin(\beta)$$

$$\cos(\alpha + \beta) = \cos(\alpha) \cos(\beta) - \sin(\alpha) \sin(\beta)$$

$$\sin(\alpha - \beta) = \sin(\alpha) \cos(\beta) - \cos(\alpha) \sin(\beta)$$

$$\cos(\alpha - \beta) = \cos(\alpha) \cos(\beta) + \sin(\alpha) \sin(\beta)$$

Example 8.2

10/28/2019

Determine the frequency and the phase angle between the two voltages:

- $v_1(t) = 12 \sin(1000 \cdot t + 60^\circ) \text{ V}$ and
- $v_2(t) = -6 \cos(1000 \cdot t + 30^\circ) \text{ V}$


Sinusoidal Forcing Functions

10/28/2019

Constant Forcing Function \rightarrow Linear Network
 \therefore Constant Steady State Response



Sinusoidal Forcing Function \rightarrow Linear Network
 \therefore Sinusoidal Steady State Response

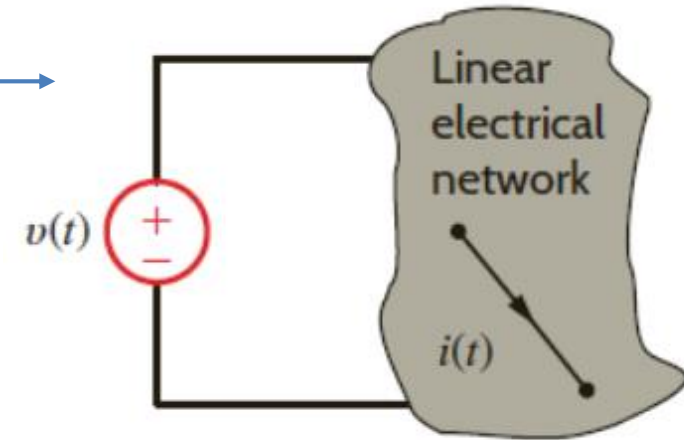


Example 8.3

Derive the expression for the current $i(t)$.

$$v(t) = R \cdot i(t) + L \frac{di(t)}{dt}$$

where $i(t) = I_M \cos(\omega t + \varphi)$

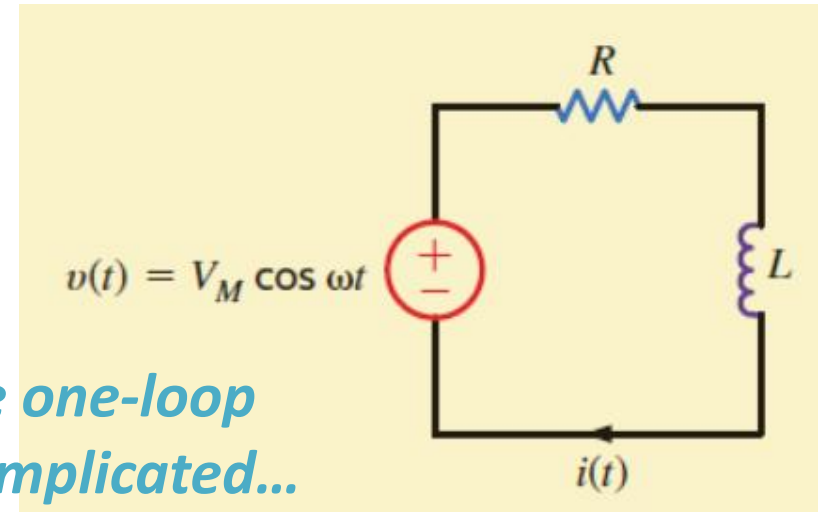Solution to the one-loop circuit is very complicated...



Sinusoidal Time Functions \leftrightarrow Complex Numbers

10/28/2019

This relationship leads to algebraic set of equations for currents and voltages in a network in which the coefficients of the variables are complex numbers.

Euler's Equation

$$e^{j\omega t} = \underbrace{\cos(\omega t)}_{\substack{\text{Re}(e^{j\omega t}) \\ \text{real part}}} + \underbrace{j \sin(\omega t)}_{\substack{\text{Im}(e^{j\omega t}) \\ \text{imaginary part}}}$$

$j = \sqrt{-1}$

Forcing Function

$$v(t) = V_M e^{j\omega t}$$



$$v(t) = V_M \cos(\omega t) + jV_M \sin(\omega t)$$

As a consequence of linearity, the principle of superposition applies, hence ...

$$i(t) = I_M \cos(\omega t + \varphi) + jI_M \sin(\omega t + \varphi)$$



$$i(t) = I_M e^{j(\omega t + \varphi)}$$

Example 8.4


10/28/2019

Derive the expression for the current $i(t)$ using the forcing function $v(t) = V_M e^{j\omega t}$ instead.

$$\begin{array}{l}
 \text{KVL} \\
 v(t) = R \cdot i(t) + L \frac{di(t)}{dt} \\
 \text{response} \\
 i(t) = I_M e^{j(\omega t + \varphi)}
 \end{array}
 \left. \vphantom{\begin{array}{l} \text{KVL} \\ v(t) = R \cdot i(t) + L \frac{di(t)}{dt} \\ \text{response} \\ i(t) = I_M e^{j(\omega t + \varphi)} \end{array}} \right\} \text{Differential Equation}$$

$$\Downarrow$$
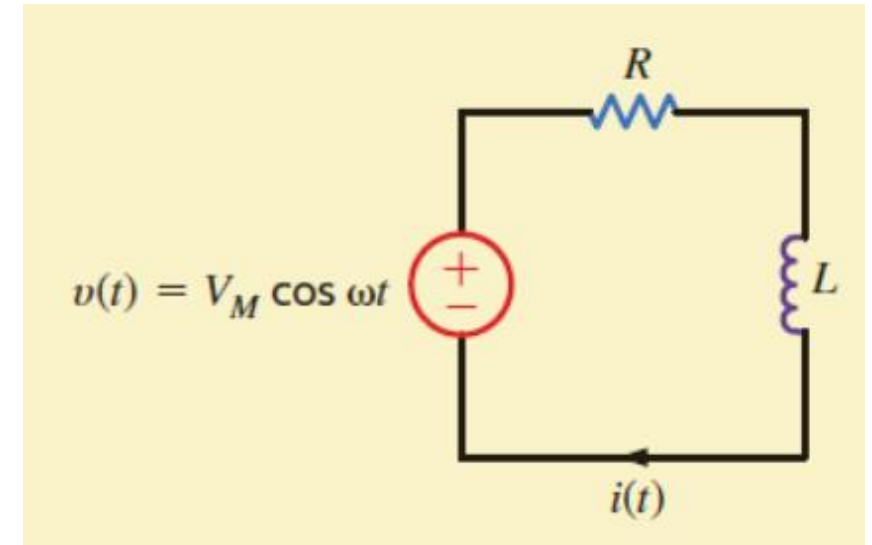
$$V_M e^{j\omega t} = R I_M e^{j(\omega t + \varphi)} + L \frac{d}{dt} (I_M e^{j(\omega t + \varphi)})$$



Solution

$$\therefore I_M = \frac{V_M}{\sqrt{R^2 + \omega^2 L^2}} \quad \therefore \varphi = -\tan^{-1} \left(\frac{\omega L}{R} \right)$$



$$i(t) = \frac{V_M}{\sqrt{R^2 + \omega^2 L^2}} \cos \left(\omega t - \tan^{-1} \left(\frac{\omega L}{R} \right) \right)$$

Phasors

10/28/2019

Representation of a complex number with just the magnitude and the phase angle.

- **Forcing Function**

$$v(t) = V_M e^{j(\omega t + \theta)} = V_M e^{j\omega t} e^{j\theta}$$

- **Steady State Response**

$$i(t) = I_M e^{j(\omega t + \varphi)} = I_M e^{j\omega t} e^{j\varphi}$$

$e^{j(\omega t)}$ → common to every term

Assuming...

$$v(t) = V_M \cos(\omega t + \theta) = \text{Re}[V_M e^{j(\omega t + \theta)}]$$

$$i(t) = I_M \cos(\omega t + \varphi) = \text{Re}[I_M e^{j(\omega t + \varphi)}]$$

$$V = \text{Re}[V_M \langle \theta e^{j\omega t} \rangle] = V_M \langle \theta$$

phasor

$$I = \text{Re}[I_M \langle \varphi e^{j\omega t} \rangle] = I_M \langle \varphi$$

TABLE 8.1 Phasor representation

TIME DOMAIN	FREQUENCY DOMAIN
$A \cos(\omega t \pm \theta)$	$A \angle \pm \theta$
$A \sin(\omega t \pm \theta)$	$A \angle \pm \theta - 90^\circ$

Learning Assessment

10/28/2019

E8.3 – Convert the following voltage functions to phasors

- $v_1(t) = 12 \cos(377t - 425^\circ) V$
- $v_2(t) = 18 \sin(2513t + 4.2^\circ) V$


E8.4 – Convert the following phasor to the time domain if the frequency is 400Hz.

- $V_3 = 10 \angle 20^\circ V$
- $V_4 = 12 \angle -60^\circ V$

Phasor Relationships → Resistor

10/28/2019

• Time Domain

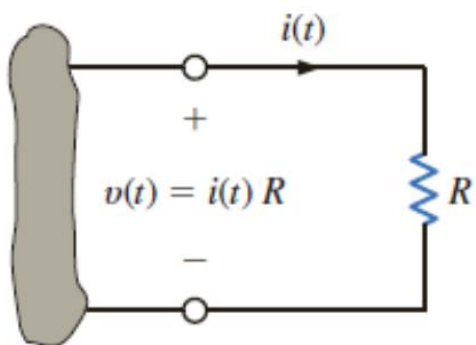


$$v(t) = R \cdot i(t)$$



$$V_M e^{j(\omega t + \theta_v)} = R \cdot I_M e^{j(\omega t + \theta_i)}$$


• Frequency Domain

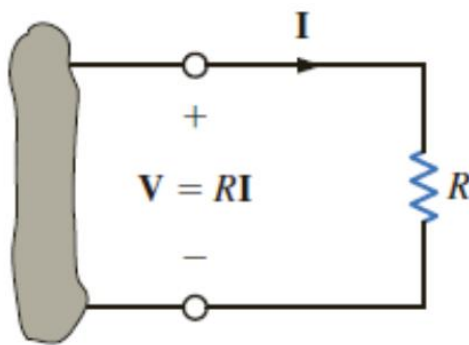


$$\therefore V_M e^{j\theta_v} = R \cdot I_M e^{j\theta_i}$$

$$\hookrightarrow V_M \angle \theta_v = R \cdot I_M \angle \theta_i$$
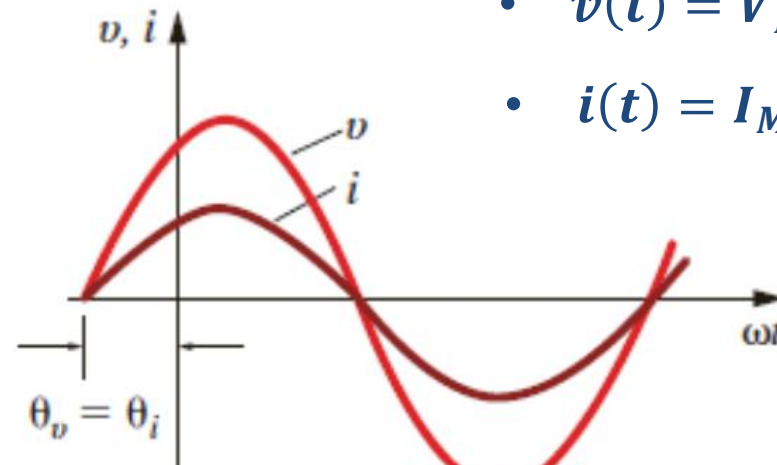
$$\therefore \theta_v = \theta_i \rightarrow v(t) \text{ and } i(t) \text{ are in phase}$$



- $v(t) = V_M e^{j(\omega t + \theta_v)}$
- $i(t) = I_M e^{j(\omega t + \theta_i)}$

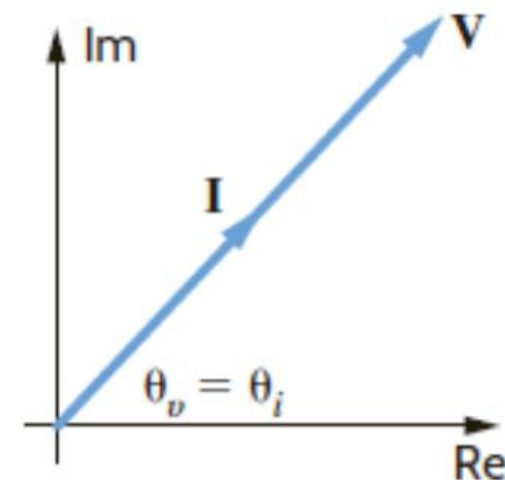

Example 8.6


10/28/2019

If the voltage $v(t) = 24 \cos(377t + 75^\circ)$ V is applied to a 6- Ω resistor, find the resultant current.

Phasor Relationships → Inductor

10/28/2019


• Time Domain

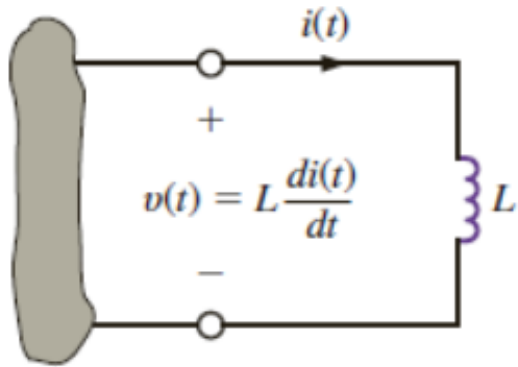

$$v(t) = L \cdot \frac{di(t)}{dt}$$

$$V_M e^{j(\omega t + \theta_v)} = L \cdot \frac{d}{dt} I_M e^{j(\omega t + \theta_i)}$$


• Frequency Domain

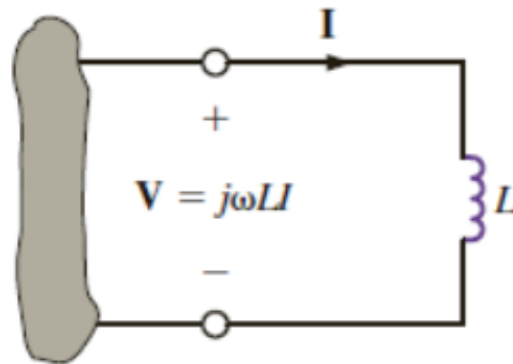

$$\therefore V_M e^{j\theta_v} = j\omega L \cdot I_M e^{j\theta_i}$$


$$\hookrightarrow V_M \angle \theta_v = j\omega L \cdot I_M \angle \theta_i$$
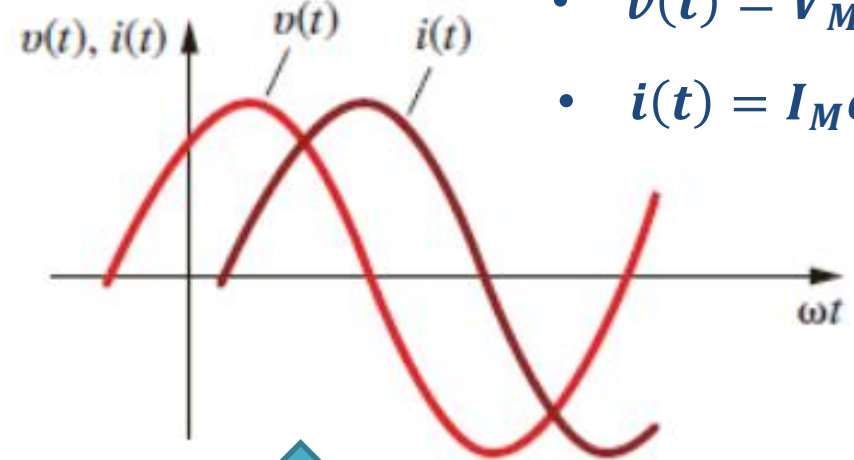
$$\therefore \theta_v = \theta_i + 90^\circ \rightarrow v(t) \text{ lead } i(t) \text{ by } 90^\circ$$



$$\bullet v(t) = V_M e^{j(\omega t + \theta_v)}$$

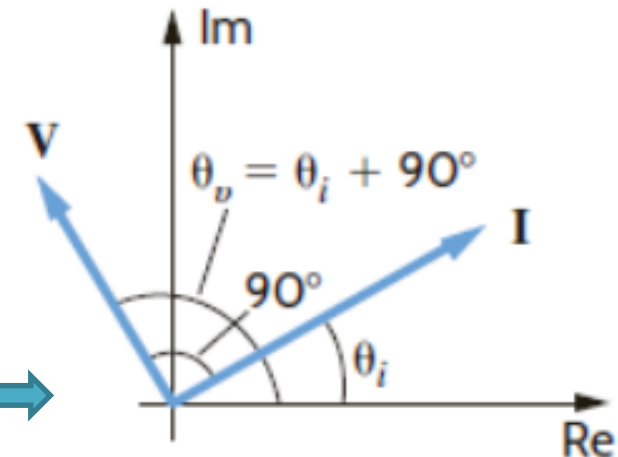
$$\bullet i(t) = I_M e^{j(\omega t + \theta_i)}$$



Phasor Relationships → Capacitance

10/28/2019


• **Time Domain**

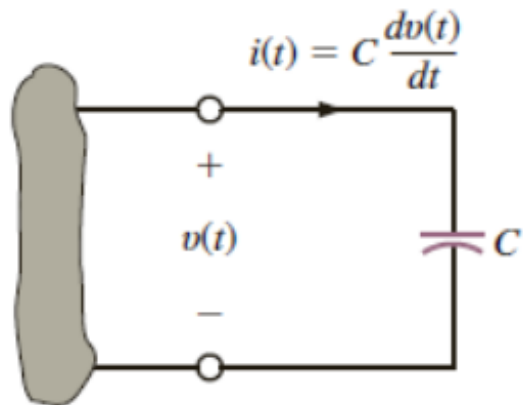

$$i(t) = C \cdot \frac{dv(t)}{dt}$$

$$I_M e^{j(\omega t + \theta_i)} = C \cdot \frac{d}{dt} V_M e^{j(\omega t + \theta_v)}$$


• **Frequency Domain**

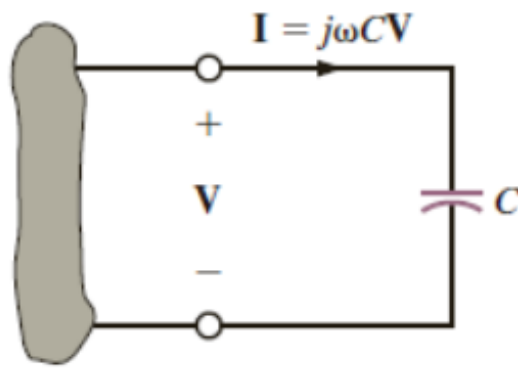


$$\therefore I_M e^{j\theta_i} = j\omega C \cdot V_M e^{j\theta_v}$$

$$\hookrightarrow I_M \angle \theta_i = j\omega C \cdot V_M \angle \theta_v$$
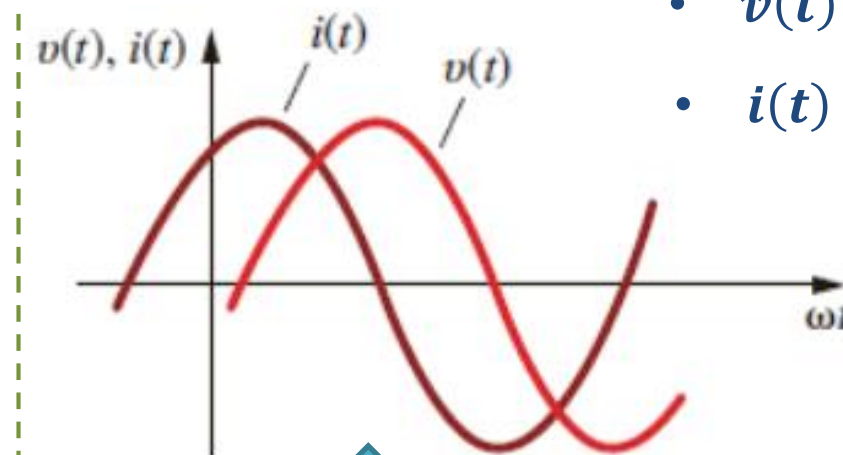
$$\therefore \theta_v = \theta_i - 90^\circ \rightarrow v(t) \text{ lags } i(t) \text{ by } 90^\circ$$



- $v(t) = V_M e^{j(\omega t + \theta_v)}$
- $i(t) = I_M e^{j(\omega t + \theta_i)}$

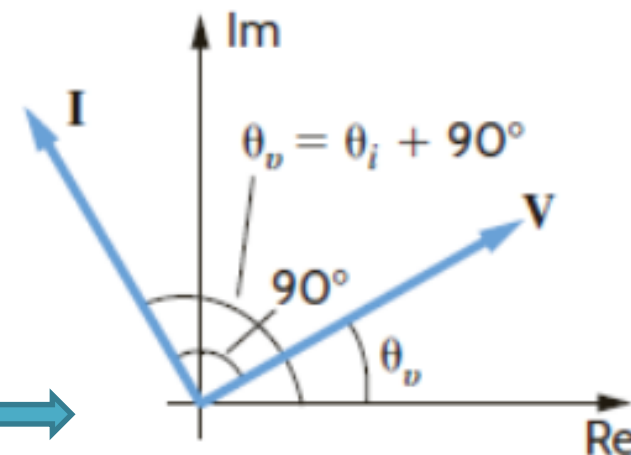

Example 8.8

10/28/2019

If the voltage $v(t) = 100 \cos(314t + 15^\circ)$ V is applied to a 100- μ F capacitor, find the resultant current.