

Last Lecture → Solving Circuits in Time Domain

11/4/2019

Derive the expression for the current $i(t)$ using the forcing function $v(t) = V_M e^{j\omega t}$ instead.

response

$$i(t) = I_M e^{j(\omega t + \varphi)}$$


KVL

$$v(t) = R \cdot i(t) + L \frac{di(t)}{dt}$$

Differential Equation


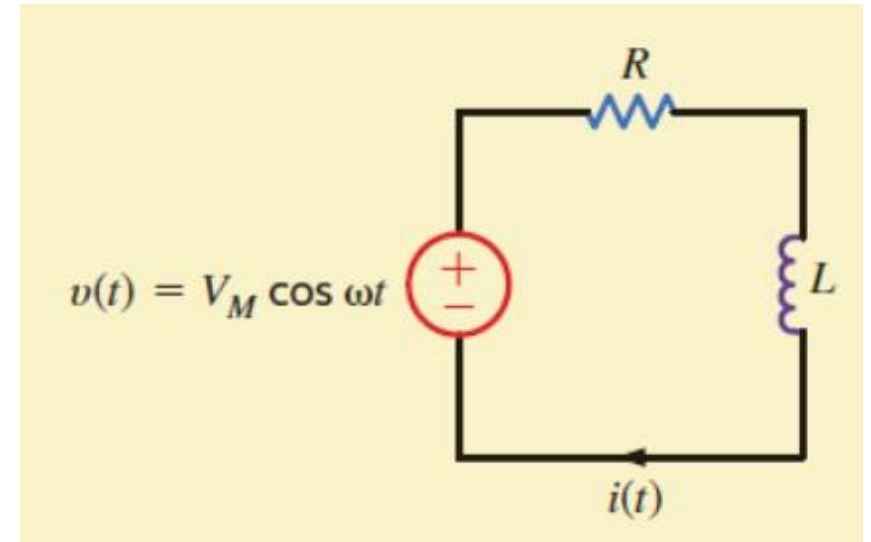
$$V_M e^{j\omega t} = R I_M e^{j(\omega t + \varphi)} + L \frac{d}{dt} (I_M e^{j(\omega t + \varphi)})$$



Solution

$$\therefore I_M = \frac{V_M}{\sqrt{R^2 + \omega^2 L^2}} \quad \therefore \varphi = -\tan^{-1} \left(\frac{\omega L}{R} \right)$$



$$i(t) = \frac{V_M}{\sqrt{R^2 + \omega^2 L^2}} \cos \left(\omega t - \tan^{-1} \left(\frac{\omega L}{R} \right) \right)$$

Last Lecture → Phasors

11/4/2019

Representation of a complex number with just the magnitude and the phase angle.

- **Forcing Function**

$$v(t) = V_M e^{j(\omega t + \theta)}$$



- **Steady State Response**

$$i(t) = I_M e^{j(\omega t + \varphi)}$$

$$v(t) = V_M \cos(\omega t + \theta) = \text{Re}[V_M e^{j(\omega t + \theta)}]$$

$$e^{j(\omega t)}$$

common to every term


$$V = \text{Re}[V_M \angle \theta e^{j\omega t}] = V_M \angle \theta$$

phasor

Phasor Relationships → Resistor

11/4/2019

• Time Domain

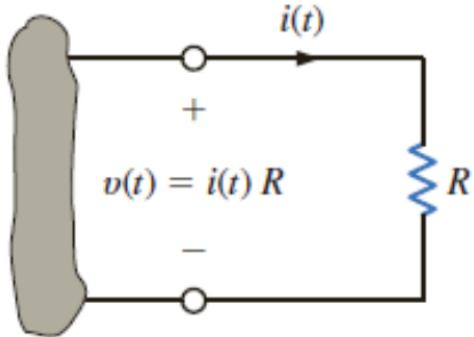


$$v(t) = R \cdot i(t)$$



$$V_M e^{j(\omega t + \theta_v)} = R \cdot I_M e^{j(\omega t + \theta_i)}$$

• Frequency Domain

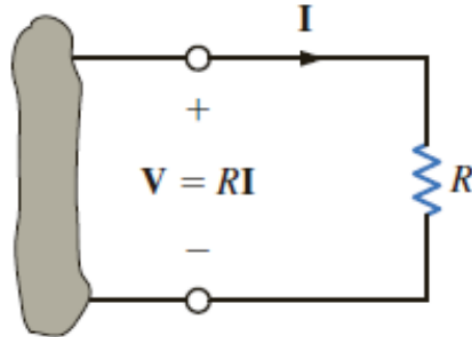

$$\therefore V_M e^{j\theta_v} = R \cdot I_M e^{j\theta_i}$$

$$\hookrightarrow V_M \angle \theta_v = R \cdot I_M \angle \theta_i$$

$$\frac{V_M \angle \theta_v}{I_M \angle \theta_i} = R$$

$$\therefore \theta_v = \theta_i$$

→ $v(t)$ and $i(t)$ are in phase


- $v(t) = V_M e^{j(\omega t + \theta_v)}$
- $i(t) = I_M e^{j(\omega t + \theta_i)}$

Phasor Relationships → Inductor

11/4/2019

- $v(t) = V_M e^{j(\omega t + \theta_v)}$
- $i(t) = I_M e^{j(\omega t + \theta_i)}$

• Time Domain

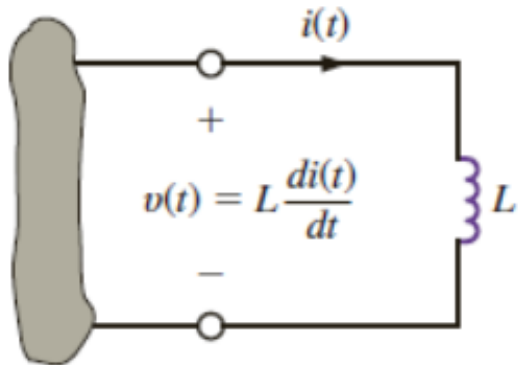


$$v(t) = L \cdot \frac{di(t)}{dt}$$



$$V_M e^{j(\omega t + \theta_v)} = L \cdot \frac{d}{dt} I_M e^{j(\omega t + \theta_i)}$$

• Frequency Domain

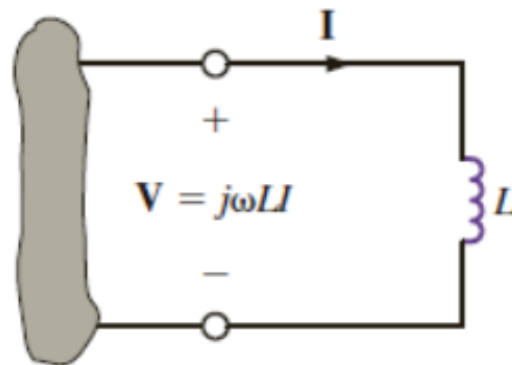

$$\therefore V_M e^{j\theta_v} = j\omega L \cdot I_M e^{j\theta_i}$$

$$\hookrightarrow V_M \angle \theta_v = j\omega L \cdot I_M \angle \theta_i$$

$$\frac{V_M \angle \theta_v}{I_M \angle \theta_i} = j\omega L$$

$$\therefore \theta_v = \theta_i + 90^\circ$$



→ $v(t)$ leads $i(t)$ by 90°

Phasor Relationships → Capacitance

11/4/2019

• Time Domain

• Frequency Domain

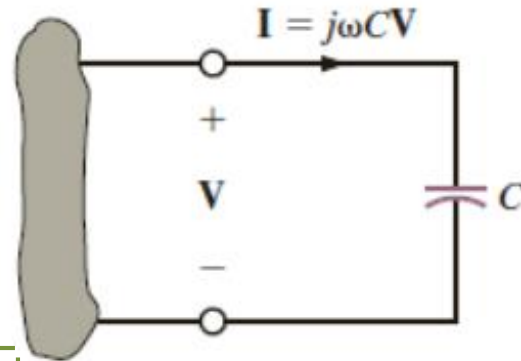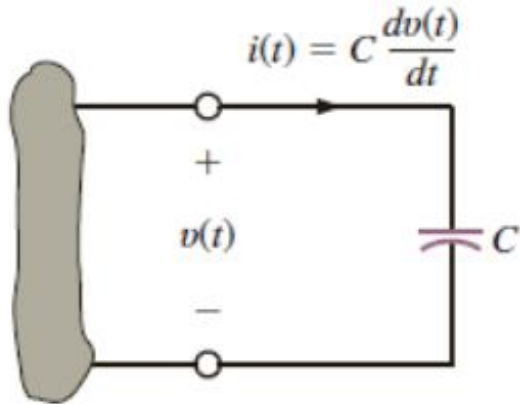

$$i(t) = C \cdot \frac{dv(t)}{dt}$$

$$I_M e^{j(\omega t + \theta_i)} = C \cdot \frac{d}{dt} V_M e^{j(\omega t + \theta_v)}$$

$$\therefore I_M e^{j\theta_i} = j\omega C \cdot V_M e^{j\theta_v}$$

$$\hookrightarrow I_M \angle \theta_i = j\omega C \cdot V_M \angle \theta_v$$

$$\bullet v(t) = V_M e^{j(\omega t + \theta_v)}$$

$$\bullet i(t) = I_M e^{j(\omega t + \theta_i)}$$

$$\frac{V_M \angle \theta_v}{I_M \angle \theta_i} = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

$$\therefore \theta_v = \theta_i - 90^\circ$$

→ $v(t)$ lags $i(t)$ by 90°


Impedance

11/4/2019

The ratio of the phasor voltage V to the phasor current I .

$$Z = \frac{V}{I} \text{ [Ohms]}$$
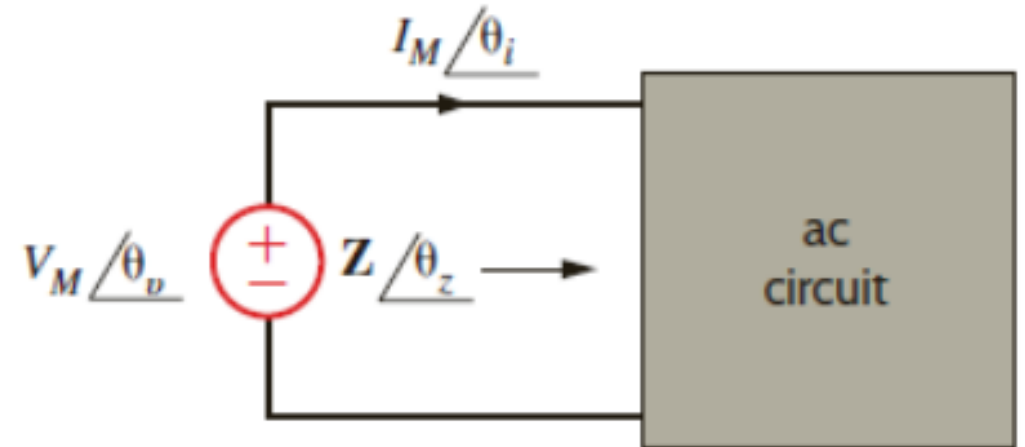
$$= \frac{V_M \angle \theta_v}{I_M \angle \theta_i} = \frac{V_M}{I_M} \angle (\theta_v - \theta_i) = Z \angle \theta_z$$



$$Z \angle \theta_z = R + jX$$

\downarrow \downarrow
Resistance **Reactance**

Polar Coordinates


$$Z = \sqrt{R^2 + X^2}$$

$$\angle \theta_z = \tan^{-1} \left(\frac{X}{R} \right)$$

Rectangular Coordinates

$$R = Z \cos \theta_z$$

$$X = Z \sin \theta_z$$

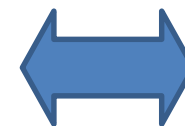

Impedance

11/4/2019

The ratio of the phasor voltage V to the phasor current I .

Series → Equivalent Impedance

$$Z_s = Z_1 + Z_2 + \dots + Z_n$$

Parallel → Equivalent Impedance

$$\frac{1}{Z_p} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}$$


PASSIVE ELEMENT	IMPEDANCE
R	$Z = R$
L	$Z = j\omega L = jX_L, X_L = \omega L$
C	$Z = \frac{1}{j\omega C} = -\frac{j}{\omega C} = -jX_C, X_C = \frac{1}{\omega C}$

KVL & KCL are valid in the frequency domain!

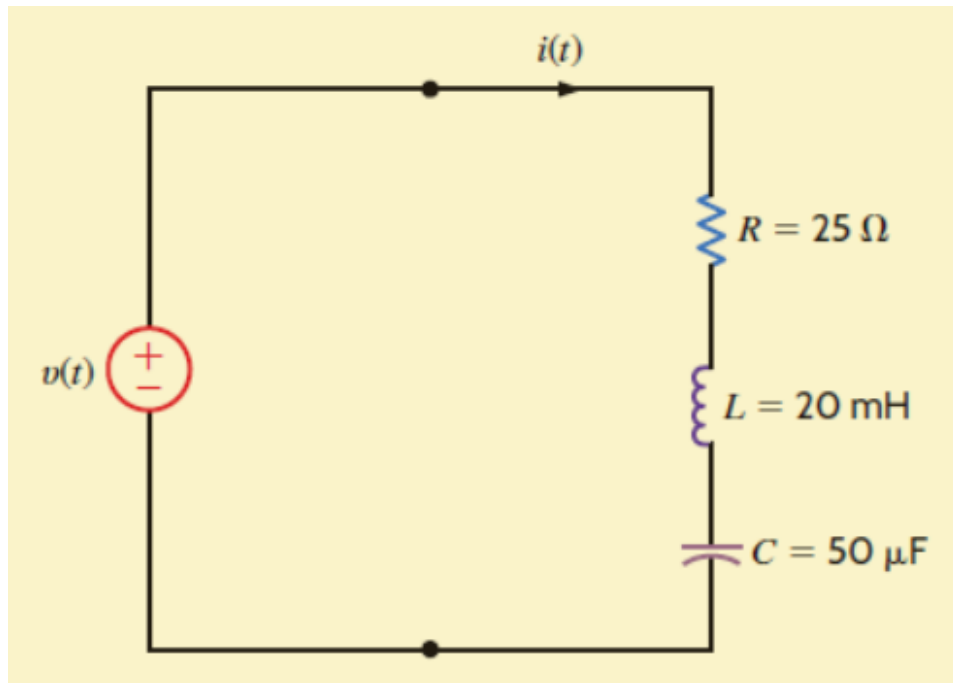Example 8.9

11/4/2019

Determine the equivalent impedance of the network provided if the frequency is $f=60\text{Hz}$. Then compute the current $i(t)$ if the voltage source is $v(t) = 50 \cos(\omega t + 30^\circ) \text{ V}$.



Admittance

11/4/2019

The ratio of the phasor current I to the phasor voltage V .

$$Y = \frac{I}{V} = \frac{1}{Z} \text{ [Siemens]}$$

$$Y \angle \theta_y = G + jB$$

Conductance

Susceptance

Parallel → Equivalent Admittance

$$Y_p = Y_1 + Y_2 + \dots + Y_n$$


Series → Equivalent Admittance

$$\frac{1}{Y_s} = \frac{1}{Y_1} + \frac{1}{Y_2} + \dots + \frac{1}{Y_n}$$

Example 8.10

11/4/2019



Calculate the equivalent admittance Y_p for the network provided and use it to determine the current I if $V_s = 60\angle 45^\circ$.

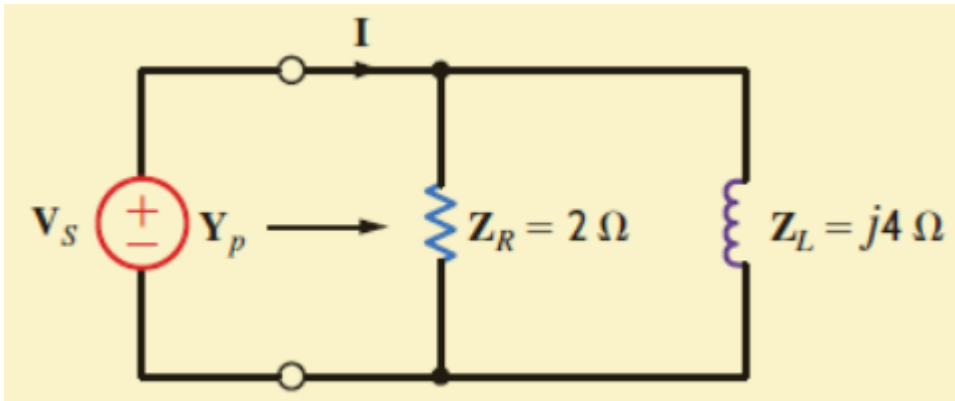

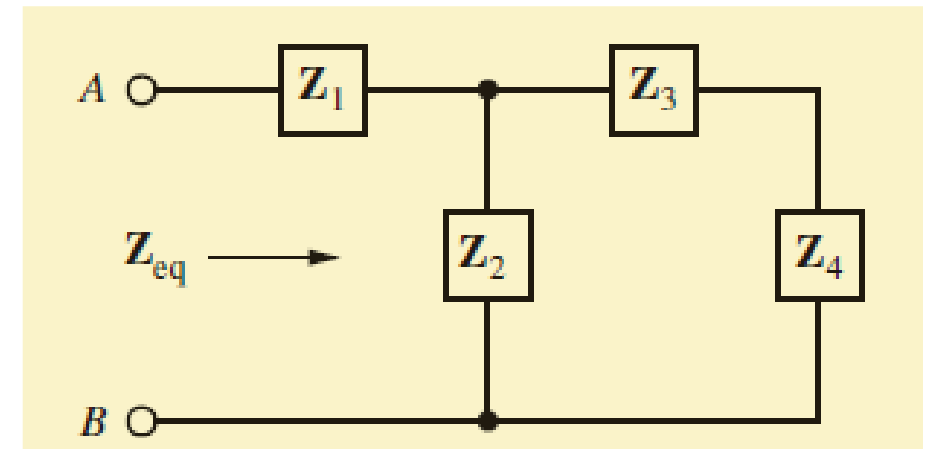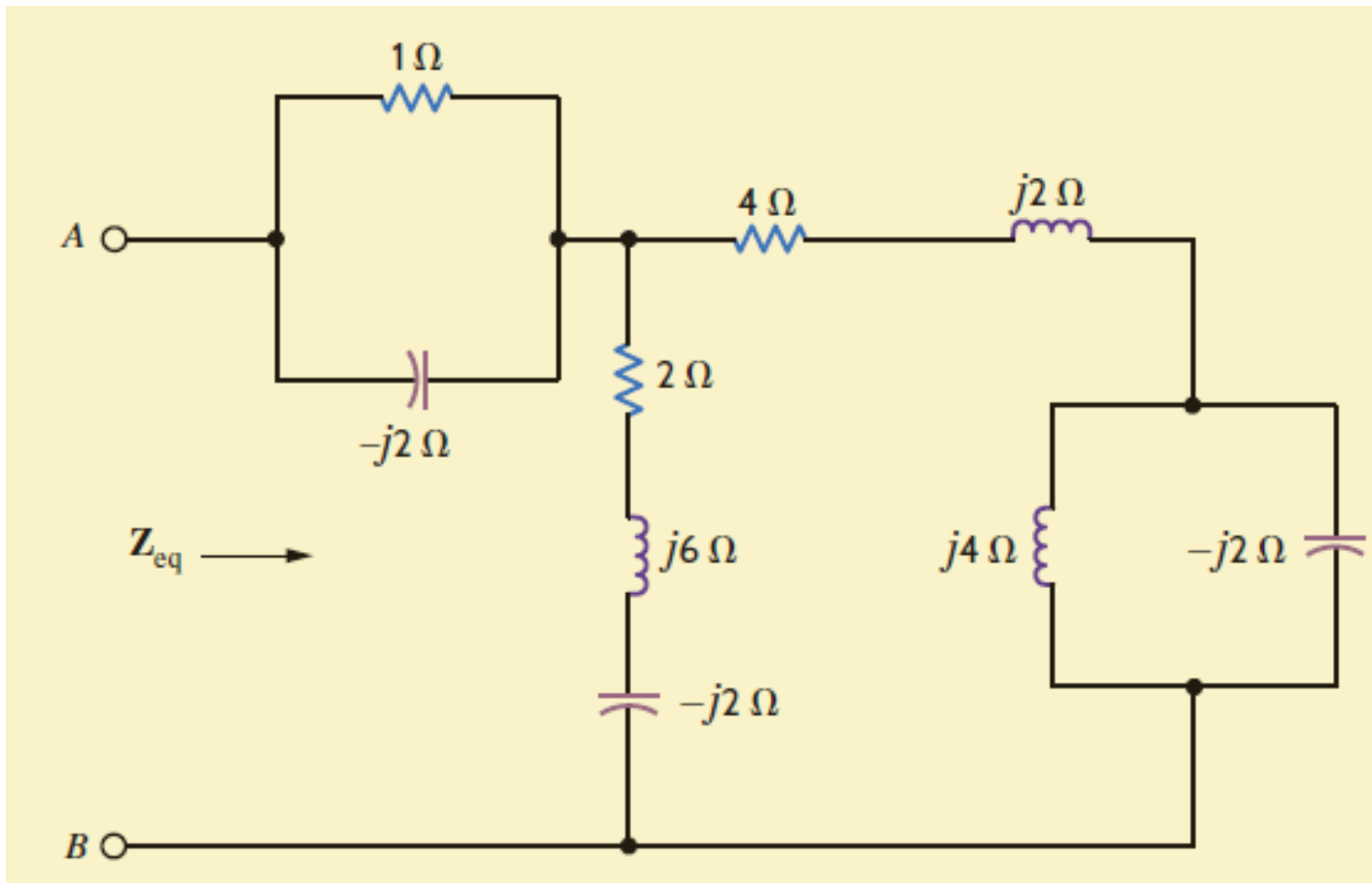Example 8.11

11/4/2019

For the given circuit calculate the equivalent impedance Z_{eq} at terminals A-B.





Technique for taking the reciprocal...

$$\frac{1}{R + jX} = \frac{R - jX}{R^2 + X^2}$$

Learning Assessment E8.12

11/4/2019

Draw the phasor diagram to illustrate all currents and voltages for the network provided.

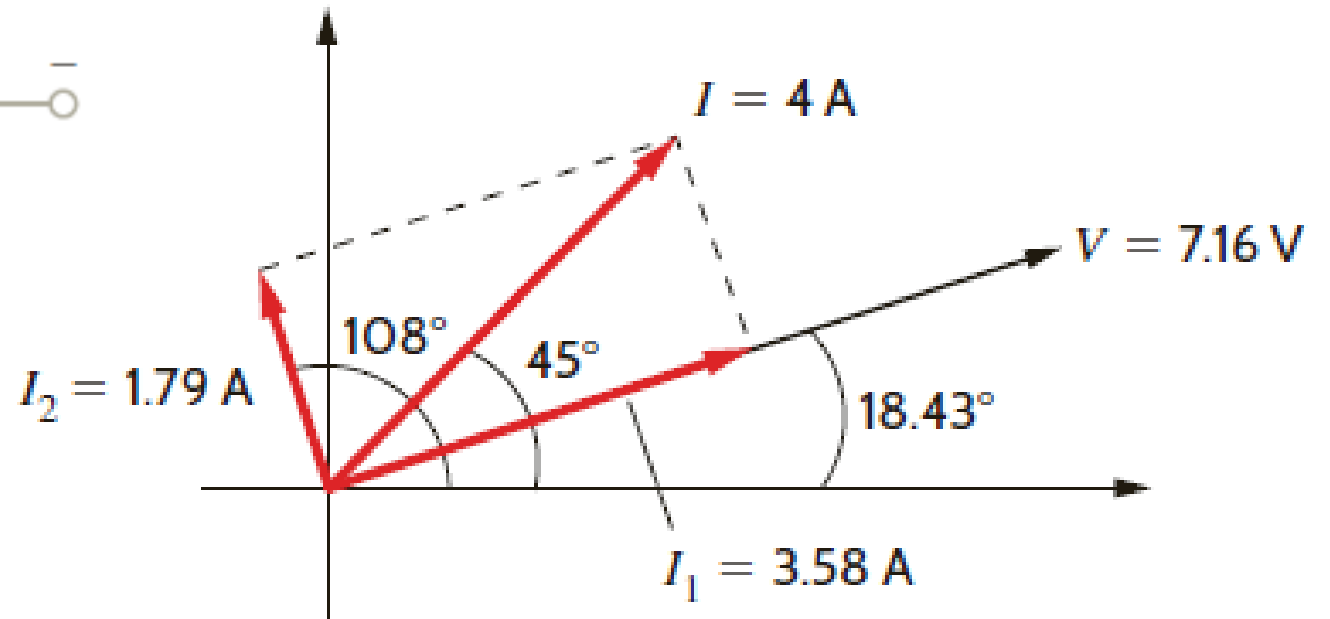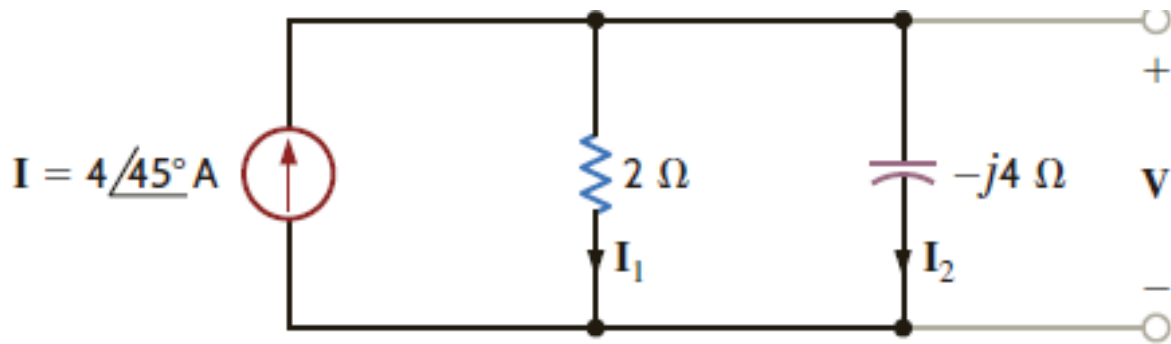

Problem 8.25

11/4/2019

The admittance of the box in the figure provided is $0.1 + j0.2 \text{ S}$ at 500 rad/s . What is the impedance at 300 rad/s ?

