


Magnetically Coupled Networks → Chapter #10

11/12/2019

-
- **Mutual Inductance / Coefficient of Coupling / Turns Ratio**
 - **Circuit Analysis with Mutual Inductance**
 - **Circuit Analysis with Ideal Transformers**

Single Coil Behavior

11/12/2019

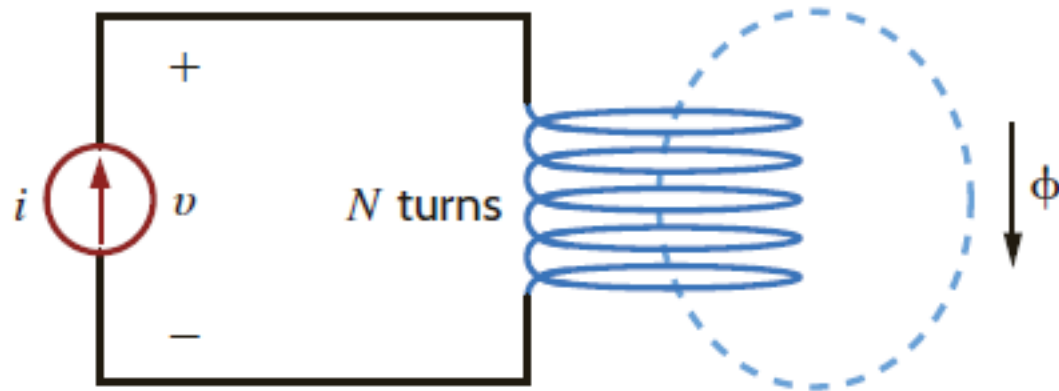

Flux Linkage $\rightarrow \lambda$

$$\lambda = N \cdot \phi$$

coil turns \rightarrow N
magnetic flux \rightarrow ϕ

$$\lambda = L \cdot i$$

$$\phi = \frac{L}{N} i$$


Faraday's Law $\rightarrow v = f(\lambda)$

$$v = \frac{d\lambda}{dt}$$

$$= L \frac{di}{dt} + i \frac{dL}{dt}$$


$$L \neq f(t)$$

$$v = L \frac{di}{dt}$$

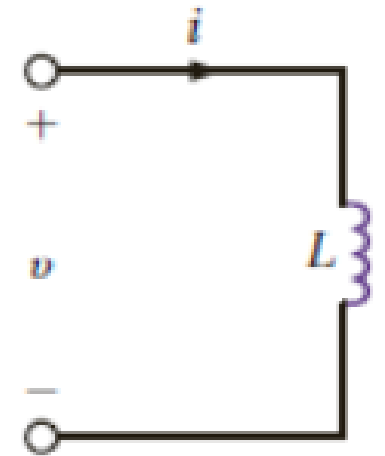

Two Coils → Magnetically Coupled

11/12/2019

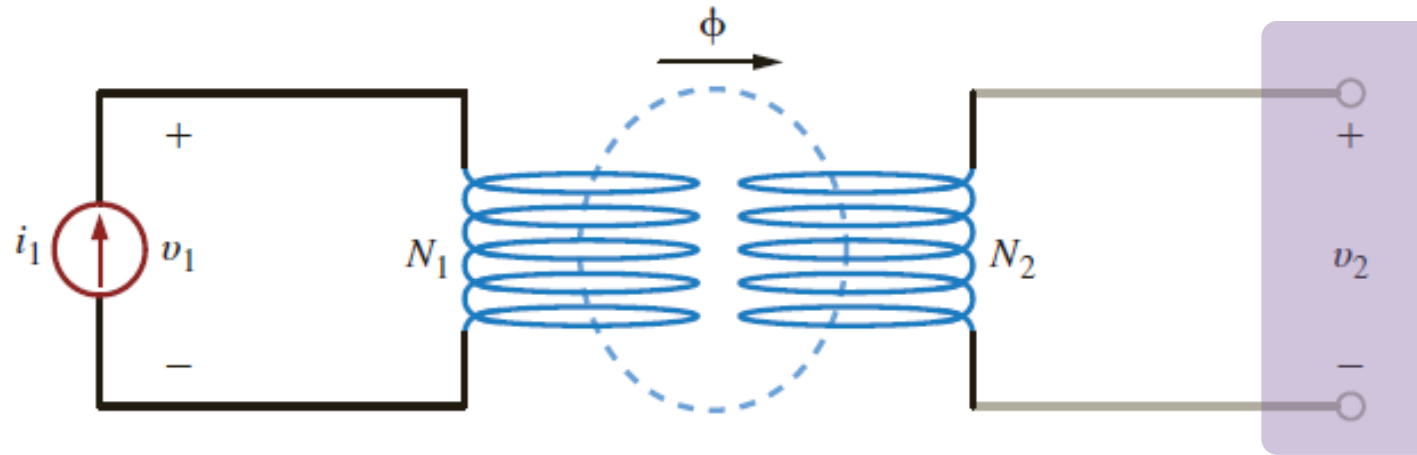

No Load!
→ $i_2 = 0$

$$\lambda_1 = N_1 \cdot \phi = L_1 \cdot i_1$$

$$\lambda_2 = N_2 \cdot \phi$$

$$v_1 = \frac{d\lambda_1}{dt}$$

$$v_2 = \frac{d\lambda_2}{dt}$$


L_{21} → Mutual Inductance

$$v_2 = \frac{d\lambda_2}{dt} = \frac{d}{dt}(N_2 \cdot \phi) = \frac{d}{dt}\left(\frac{N_2}{N_1} \cdot \lambda_1\right) = \frac{d}{dt}\left(\frac{N_2}{N_1} \cdot L_1 \cdot i_1\right) = \frac{N_2}{N_1} L_1 \frac{di_1}{dt}$$

Induced Voltage

Magnetically Coupled Coils

11/12/2019

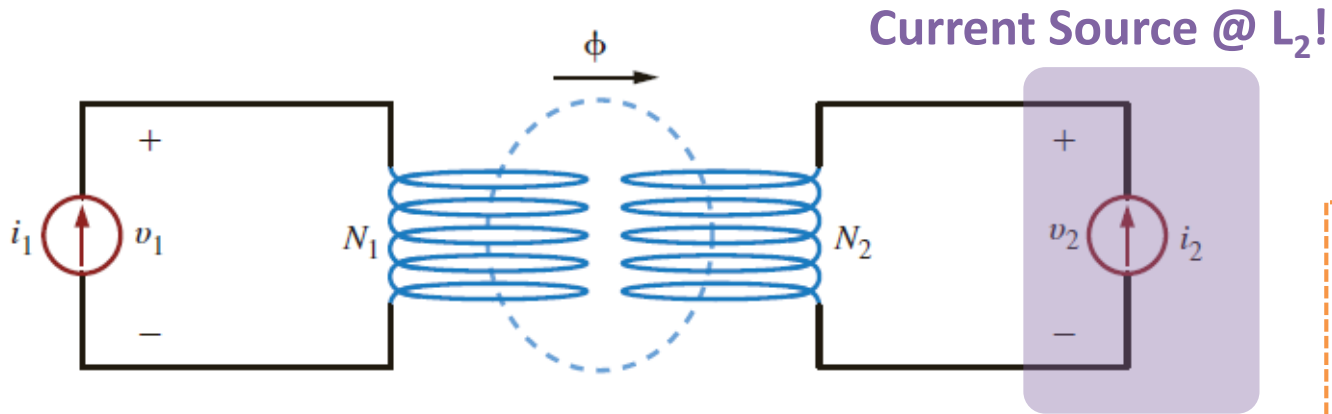

$$v_1 = L_1 \frac{di_1}{dt} + L_{12} \frac{di_2}{dt}$$


$$v_2 = L_2 \frac{di_2}{dt} + L_{21} \frac{di_1}{dt}$$

$L_{12} = L_{21} = M$

Self Term Mutual Term

Using Superposition

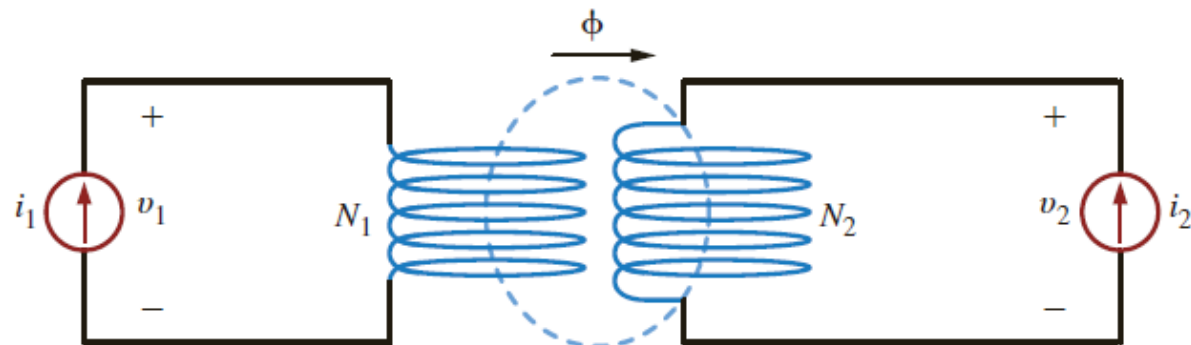
$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$




$$v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} \quad v_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

Magnetically Coupled Coils → Circuit Diagram

11/12/2019

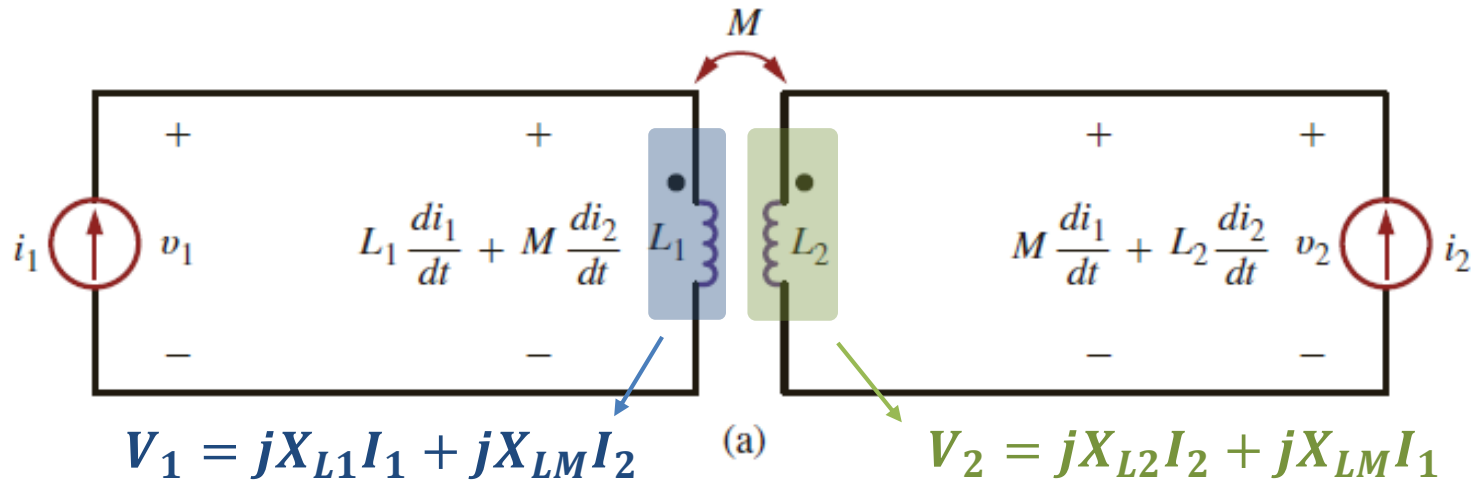

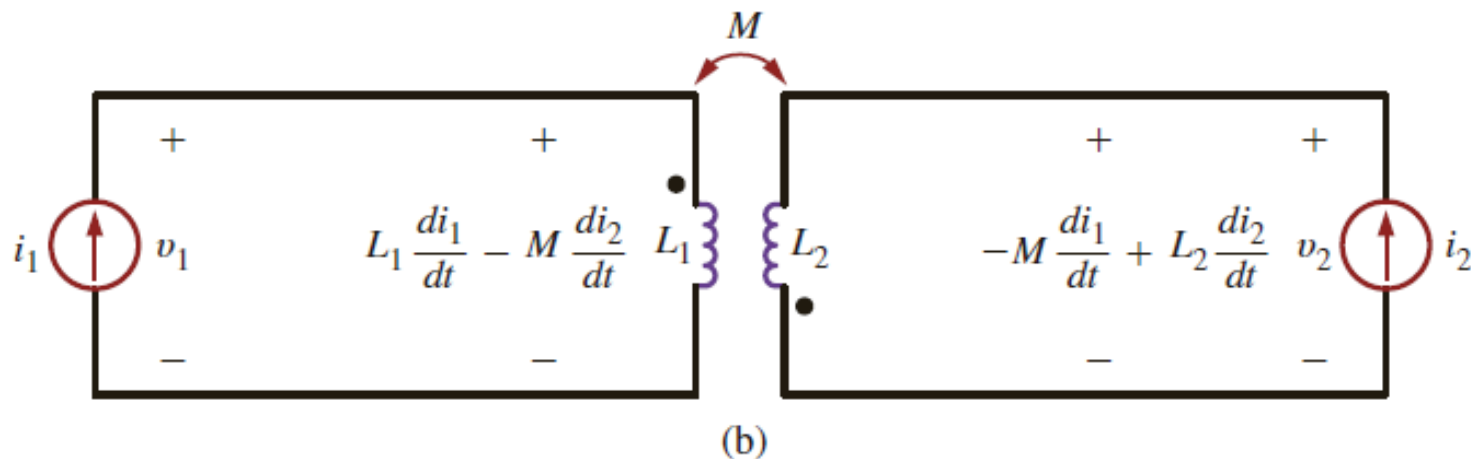- Current enters the dotted terminal → voltage at coupled coil is positive at the dotted terminal




- Current enters the undotted terminal → voltage at coupled coil is positive at the undotted terminal

Example 10.4


11/12/2019

Determine V_o for the given circuit.

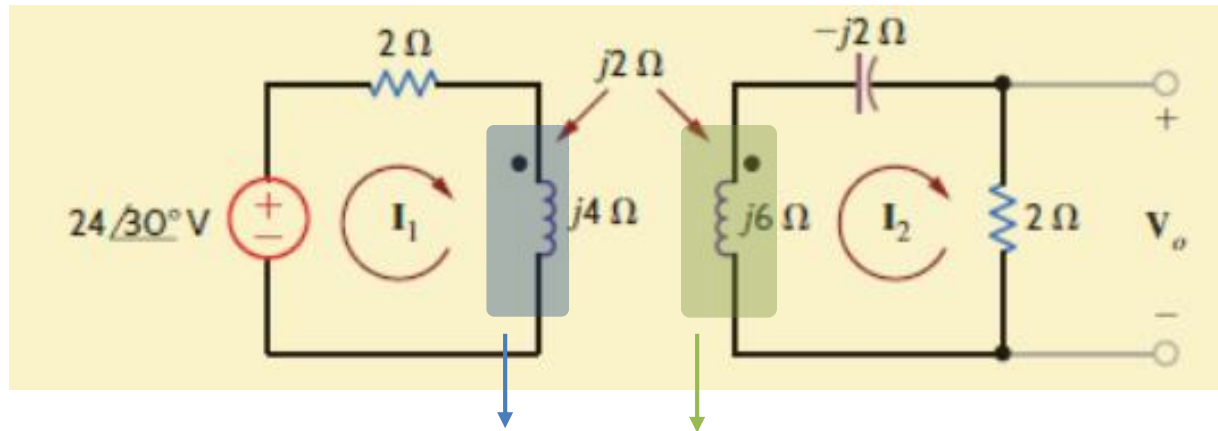

$$V_1 = jX_{L1}I_1 - jX_{LM}I_2 \quad V_2 = jX_{L2}I_2 - jX_{LM}I_1$$

Find V_x in the provided circuit.

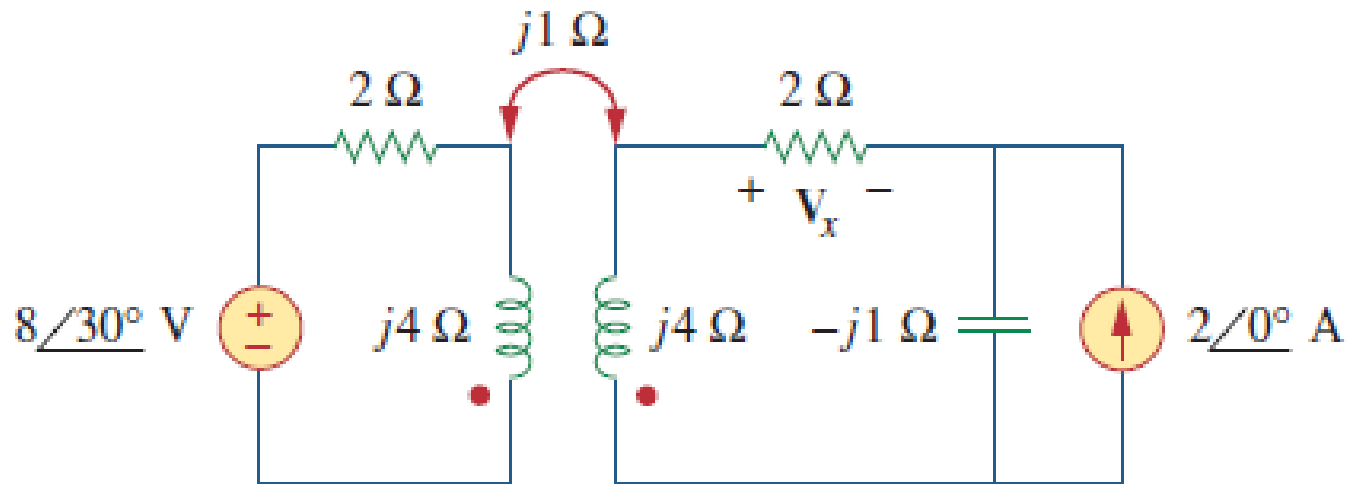

Problem

11/12/2019

Determine the equivalent inductance L_{eq} of the circuit.

