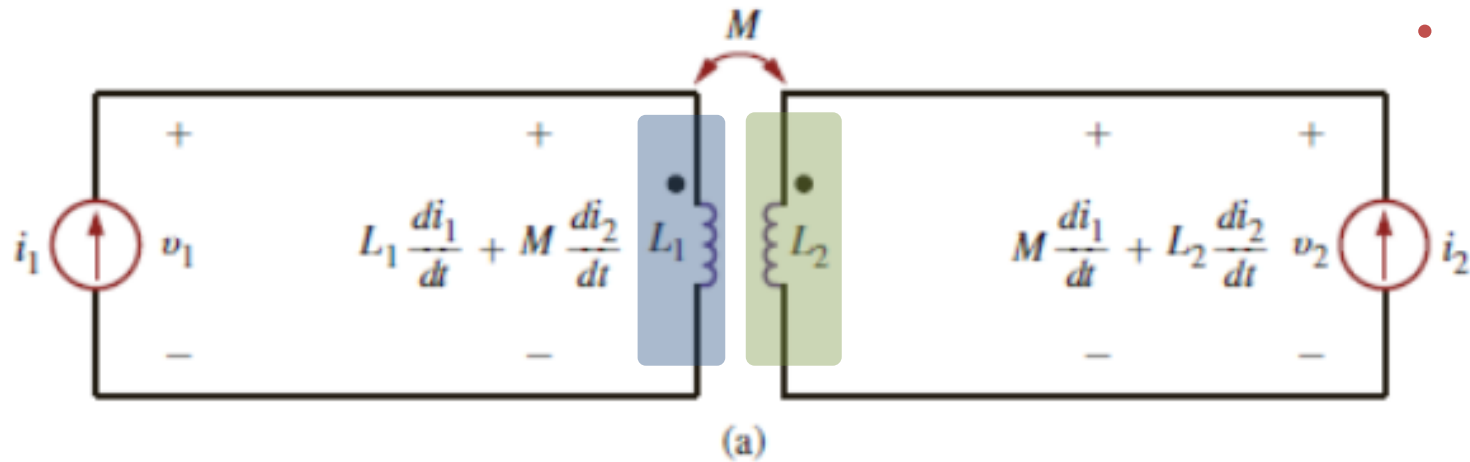


# Last Lecture → Magnetically Coupled Coils


11/12/2019



- Current enters the dotted terminal → voltage at coupled coil is positive at the dotted terminal

$$V_1 = jX_{L1}I_1 + jX_{LM}I_2$$

$$V_2 = jX_{L2}I_2 + jX_{LM}I_1$$

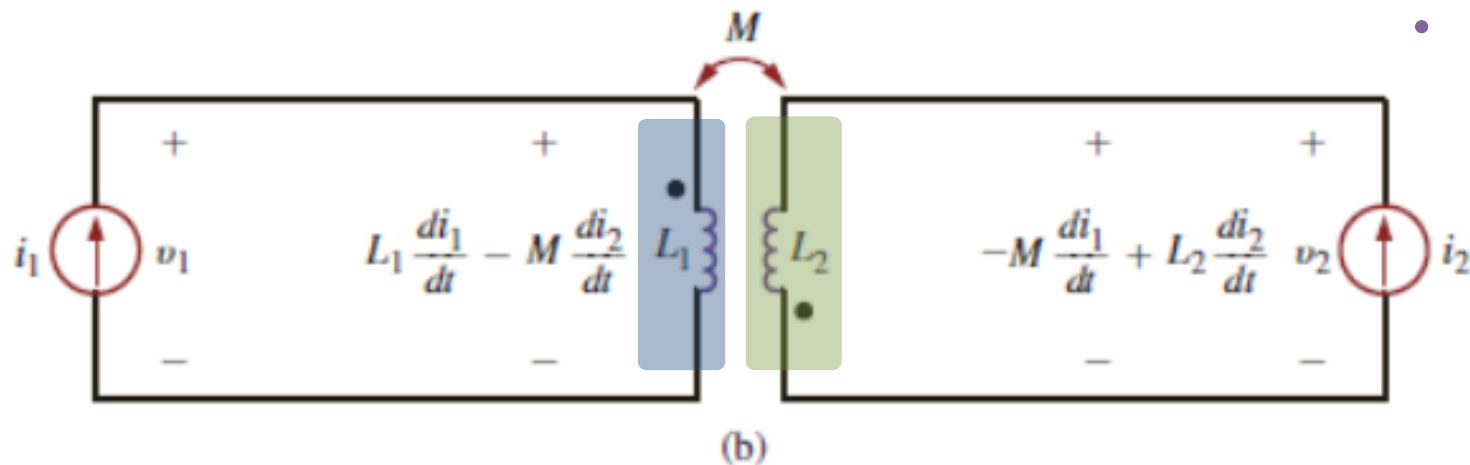

- Current enters the undotted terminal → voltage at coupled coil is positive at the undotted terminal


$$V_1 = jX_{L1}I_1 - jX_{LM}I_2$$

$$V_2 = jX_{L2}I_2 - jX_{LM}I_1$$
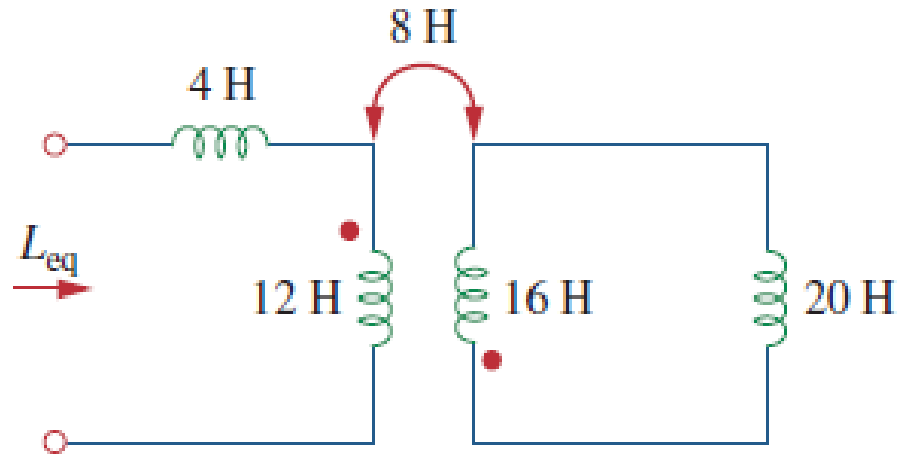
# Problem


11/12/2019

Determine the equivalent inductance  $L_{eq}$  of the circuit.



# Magnetically Coupled Coils → Energy

11/12/2019

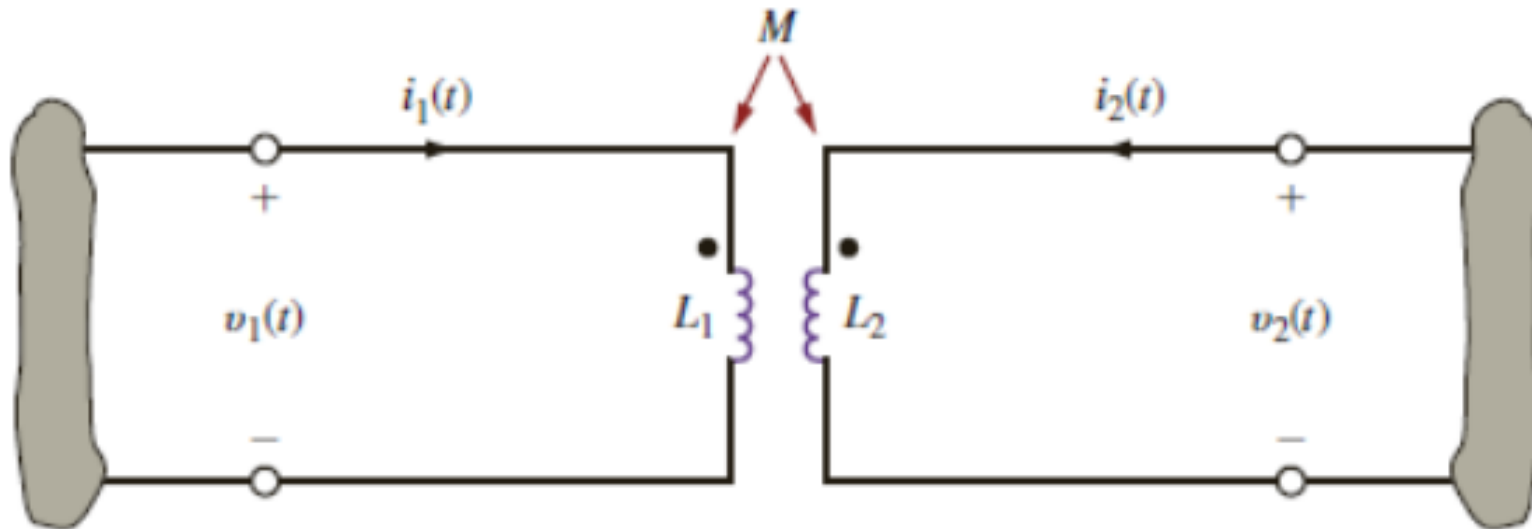


$$w(t) = \frac{1}{2}L_1[i_1(t)]^2 + \frac{1}{2}L_2[i_2(t)]^2 \pm Mi_1(t)i_2(t)$$

Coefficient of Coupling  $k = \frac{M}{\sqrt{L_1L_2}} \quad 0 \leq k \leq 1$
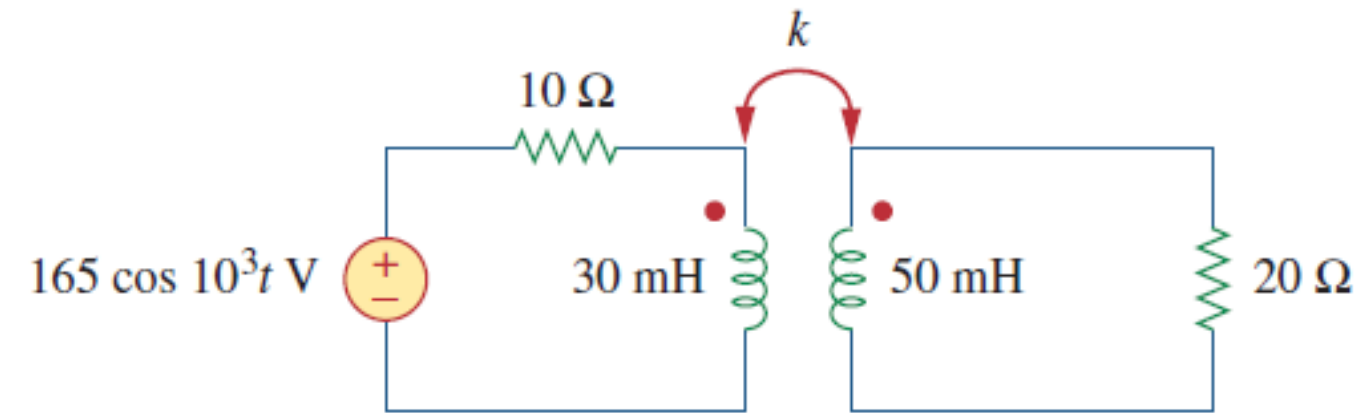
# Problem


11/12/2019

Find the value of the coupling coefficient  $k$  that will make the  $10\ \Omega$  resistor dissipate  $320\text{W}$ . For this value of  $k$ , find the energy stored in the coupled coils at  $t = 1.5\text{s}$ .



# The Ideal Transformer

11/12/2019

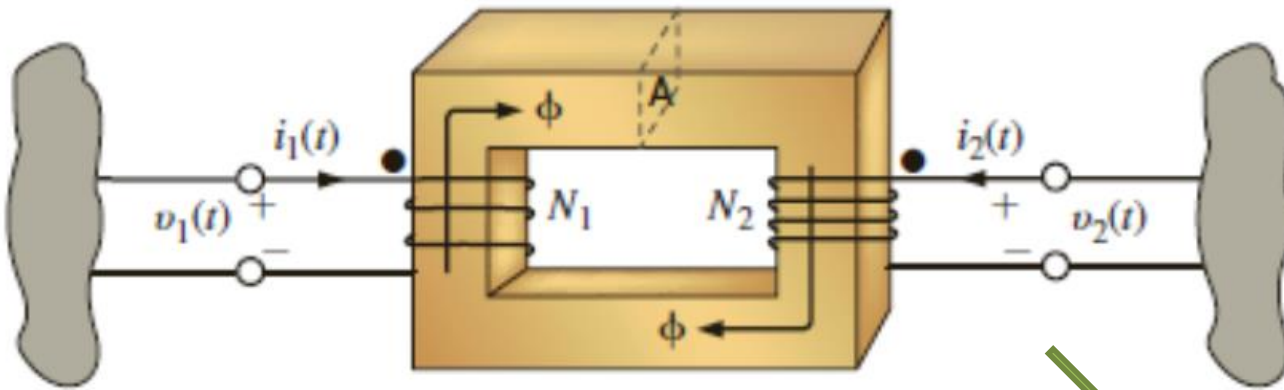

$$\lambda_1 = N_1 \cdot \phi$$

$$\lambda_2 = N_2 \cdot \phi$$


$$v_1 = \frac{d\lambda_1}{dt} = N_1 \frac{d\phi}{dt}$$

$$v_2 = \frac{d\lambda_2}{dt} = N_2 \frac{d\phi}{dt}$$

$$\therefore \frac{v_2}{v_1} = \frac{N_2}{N_1}$$

Assuming an ideal magnetic core with infinite permeability...
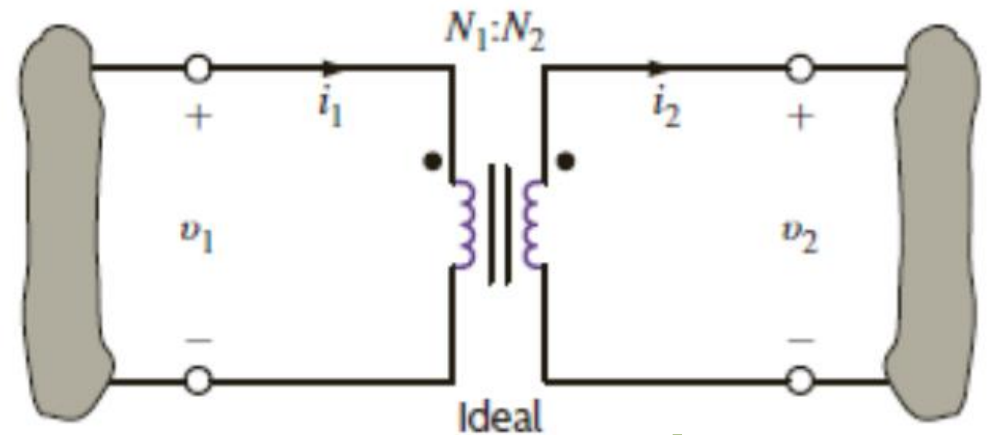
$$\left. \begin{array}{l} P_1 + P_2 = 0 \\ v_1 \cdot i_1 + v_1 \cdot \frac{N_2}{N_1} \cdot i_2 = 0 \end{array} \right\} \therefore \frac{i_2}{i_1} = -\frac{N_1}{N_2}$$



$$\frac{v_2}{v_1} = \frac{N_2}{N_1}$$

$$\frac{i_2}{i_1} = \frac{N_1}{N_2}$$




# Problem

11/12/2019

Ten bulbs in parallel are supplied by a 7,200/120 V transformer as shown, where the bulbs are modeled by the  $144 \Omega$  resistors. Find:

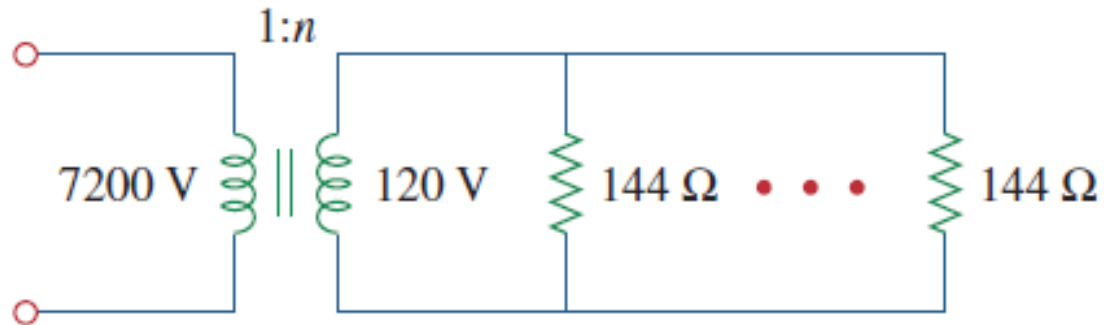
- the turns ratio  $n$ ,
- the current through the primary winding.


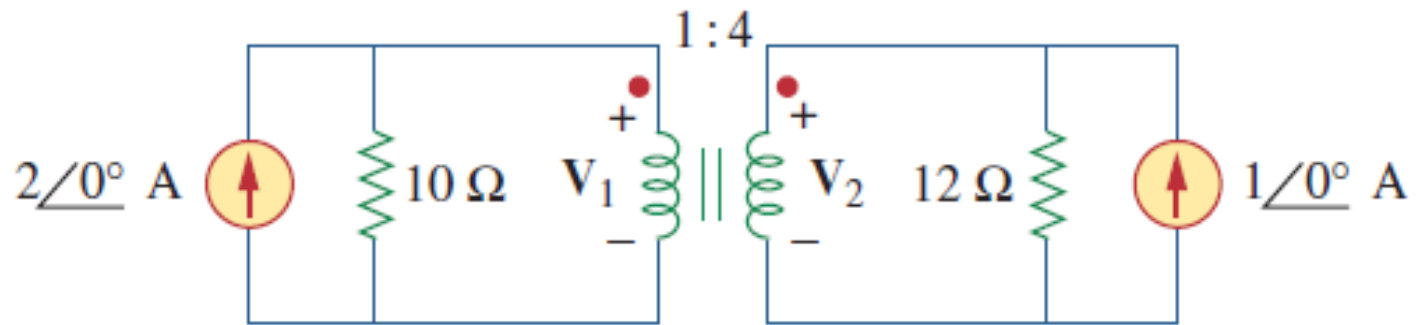
# Problem

11/12/2019

Obtain  $V_1$  and  $V_2$  in the ideal transformer circuit provided.






# Problem

11/12/2019

A transformer is used to match an amplifier with an  $8\Omega$  load as shown in the figure provided. The Thevenin equivalent of the amplifier is:  $V_{th} = 10V$ ,  $Z_{th} = 128\Omega$ .

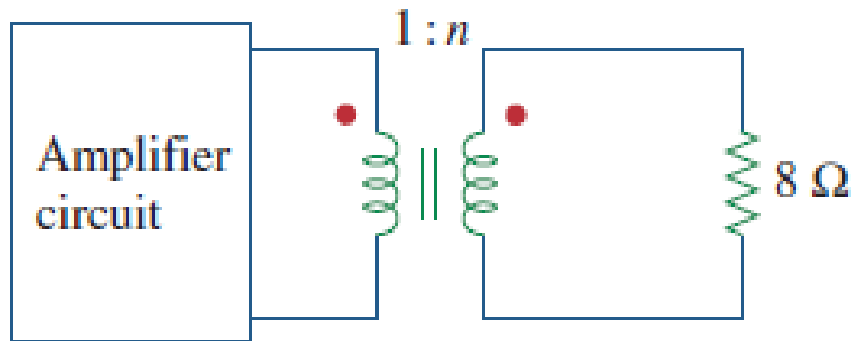- Find the required turns ratio  $n$  for maximum energy power transfer
- Determine the primary and secondary currents
- Determine the primary and secondary voltages



# Problem

11/12/2019

Find the Thevenin equivalent for the circuit provided at terminals a-b.

