

Steady State Power Analysis → Chapter #9

12/11/2019


-
- **Instantaneous and Average Power (AC Circuits)**
 - **Maximum Average Power Transfer (AC Circuits)**
 - **Effective / RMS Value (periodic waveform)**
 - **Real Power, Reactive Power, Complex Power, & Power Factor**
 - **Power Factor Correction**

Instantaneous Power

12/11/2019

The steady-state voltage and current in the network can be written as:
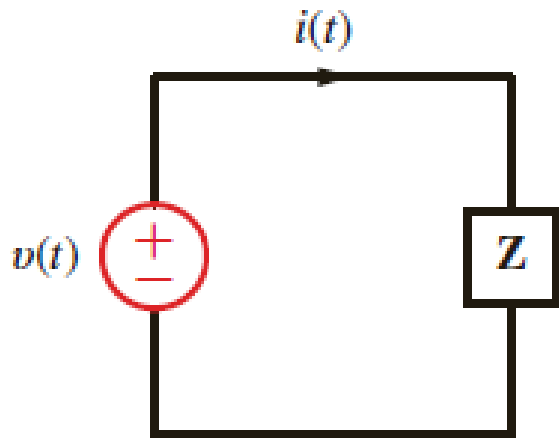
$$\left. \begin{aligned} \bullet \quad v(t) &= V_M \cos(\omega t + \theta_v) \\ \bullet \quad i(t) &= I_M \cos(\omega t + \theta_i) \end{aligned} \right\} p(t) = V_M I_M \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$



$$p(t) = \frac{V_M I_M}{2} \left[\underbrace{\cos(\theta_v - \theta_i)}_{\text{constant}} + \underbrace{\cos(2\omega t + \theta_v + \theta_i)}_{\text{Freq} = 2\omega} \right]$$

Trigonometric Identity

$$\cos(\phi_1) \cos(\phi_2) = \frac{1}{2} \cos(\phi_1 - \phi_2) + \frac{1}{2} \cos(\phi_1 + \phi_2)$$

Average Power

12/11/2019

The average value of any waveform can be computed by integrating the function over a complete period and dividing this result by the period:

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) dt$$

$$= \frac{1}{T} \int_{t_0}^{t_0+T} \frac{V_M I_M}{2} [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)] dt$$


$$\therefore P = \frac{1}{2} V_M I_M \cos(\theta_v - \theta_i)$$

- $P_{resistive} = \frac{1}{2} V_M I_M$
- $P_{reactive} = \frac{1}{2} V_M I_M \cos(\pm 90^\circ) = 0$

Learning Assessment E9.2

12/11/2019

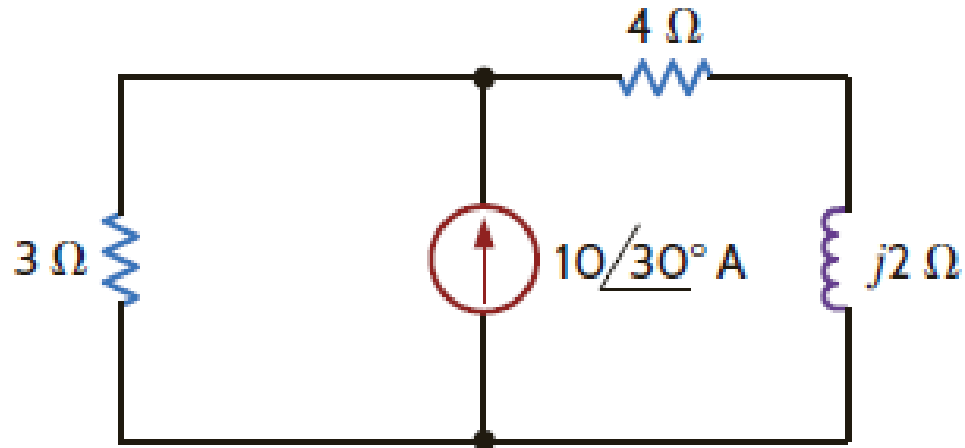Find the average power absorbed by each passive circuit element and the total average power supplied by the current source.




Maximum Power Transfer

12/11/2019

Reexamining the maximum power transfer for AC sources.../

$$Z_{th} = R_{th} + jX_{th}$$
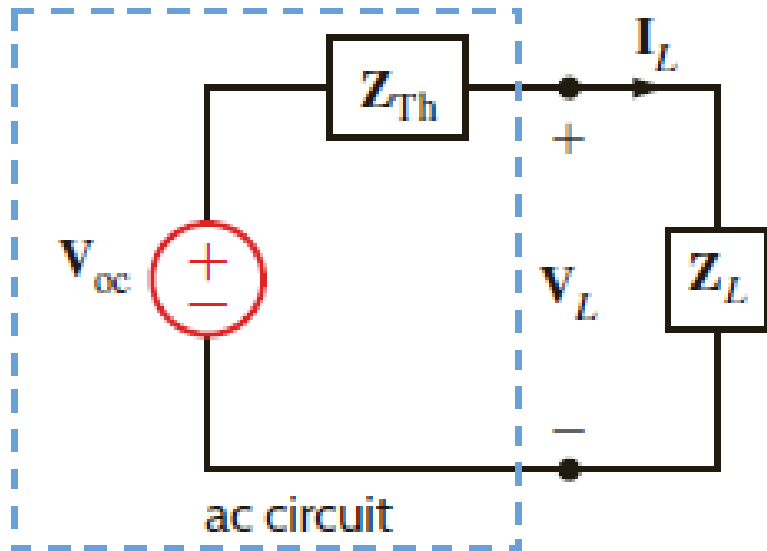
$$V_L = V_{oc} \frac{Z_L}{Z_{Th} + Z_L} \quad I_L = \frac{V_{oc}}{Z_{Th} + Z_L}$$



$$P_L = \frac{1}{2} \frac{V_{oc}^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$


$$Z_L = R_L + jX_L$$

$$\left. \begin{array}{l} \therefore X_L = -X_{th} \\ \therefore R_L = R_{th} \end{array} \right\} Z_L = R_{th} - jX_{th}$$

Learning Assessment E9.8

12/11/2019

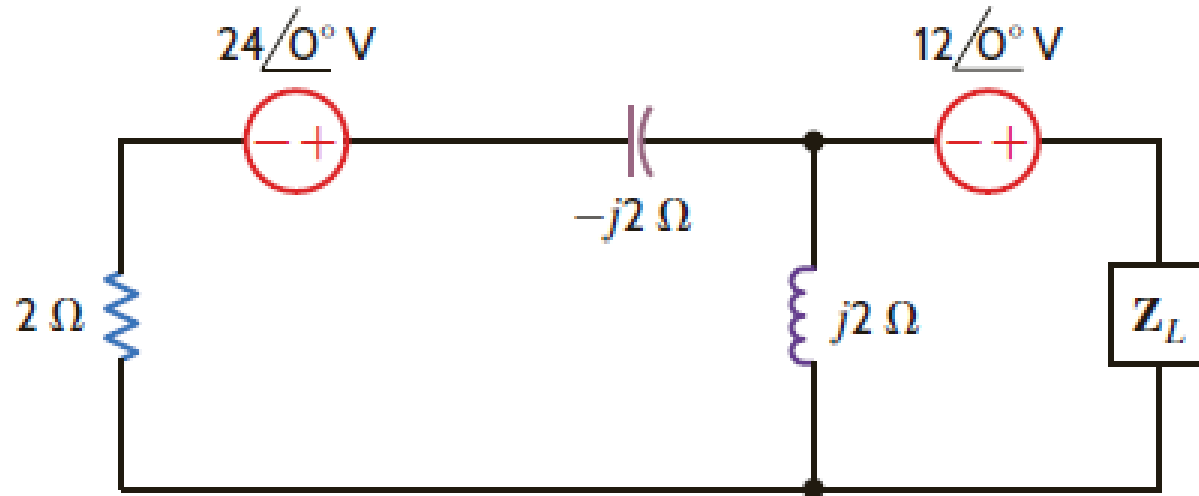Find Z_L for maximum average power transfer and the maximum average power transferred to the load.



Effective or RMS Values

12/11/2019

- There are many types of periodic waveforms in circuit analysis
- An RMS value allows for effective comparison of different sources

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) R dt$$

$$P = I_{rms}^2 R$$

$$\therefore I_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt}$$

rms = root mean square

RMS Value of a Sinusoid

12/11/2019

- $i(t) = I_M \cos(\omega t - \theta)$
- $T = 2\pi/\omega$

$$I_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T I_M^2 \cos^2(\omega t - \theta) dt}$$

Trigonometric Identity

$$\cos(\phi_1) \cos(\phi_2) = \frac{1}{2} \cos(\phi_1 - \phi_2) + \frac{1}{2} \cos(\phi_1 + \phi_2)$$

$$= I_M \sqrt{\frac{1}{T} \int_0^T \left[\frac{1}{2} + \frac{1}{2} \cos(2\omega t - 2\theta) \right] dt}$$

$$= I_M \sqrt{\frac{1}{T} \int_0^T \frac{1}{2} dt} = \frac{I_M}{\sqrt{2}}$$

$$P = \frac{1}{2} V_M I_M \cos(\theta_v - \theta_i)$$

$$\therefore P = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

Example E9.8

12/11/2019

Determine the rms value of the current waveform provided and use this value to compute the average power delivered to a $2\ \Omega$ resistor through which this current is flowing.

