

Steady State Power Analysis → Chapter #9

12/11/2019

-
- ✓ **Instantaneous and Average Power (AC Circuits)**
 - ✓ **Maximum Average Power Transfer (AC Circuits)**
 - ✓ **Effective / RMS Value (periodic waveform)**
 - **Real Power, Reactive Power, Complex Power, & Power Factor**
 - **Power Factor Correction**

Last Lecture → Average Power

12/11/2019

The average value of any waveform can be computed by integrating the function over a complete period and dividing this result by the period:

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) dt$$

$$\therefore P = \frac{1}{2} V_M I_M \cos(\theta_v - \theta_i)$$

- $P_{resistive} = \frac{1}{2} V_M I_M = \frac{1}{2} R I_M^2 = \frac{1}{2} \frac{V_M^2}{R}$
- $P_{reactive} = \frac{1}{2} V_M I_M \cos(\pm 90^\circ) = 0$

$$= \frac{1}{T} \int_{t_0}^{t_0+T} \frac{V_M I_M}{2} [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)] dt$$


Last Lecture → Maximum Power Transfer

12/11/2019

Reexamining the maximum power transfer for AC sources.../

$$Z_{th} = R_{th} + jX_{th}$$
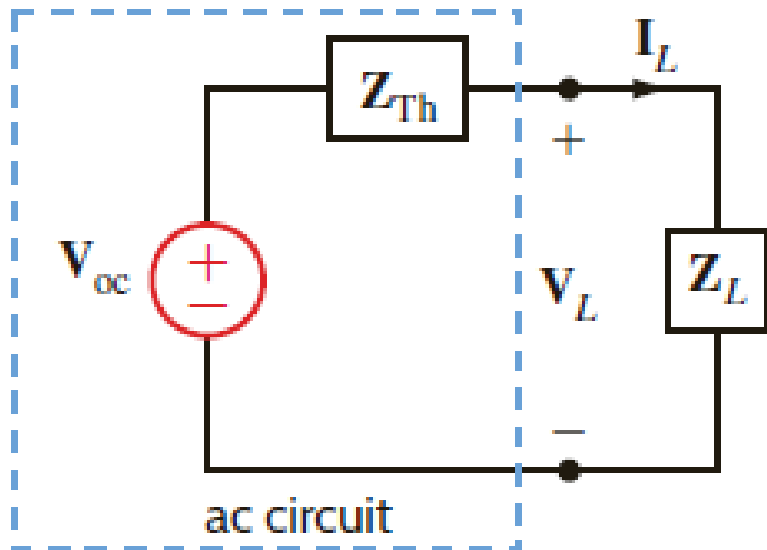
$$V_L = V_{oc} \frac{Z_L}{Z_{Th} + Z_L} \quad I_L = \frac{V_{oc}}{Z_{Th} + Z_L}$$



$$P_L = \frac{1}{2} \frac{V_{oc}^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

$$Z_L = R_L + jX_L$$

$$\left. \begin{array}{l} \therefore X_L = -X_{th} \\ \therefore R_L = R_{th} \end{array} \right\} Z_L = R_{th} - jX_{th}$$

Last Lecture → RMS Value (Sinosoid)

12/11/2019

- $i(t) = I_M \cos(\omega t - \theta)$
- $T = 2\pi/\omega$

$$I_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T I_M^2 \cos^2(\omega t - \theta) dt}$$

$$= I_M \sqrt{\frac{1}{T} \int_0^T \left[\frac{1}{2} + \frac{1}{2} \cos(2\omega t - 2\theta) \right] dt}$$

$$= I_M \sqrt{\frac{1}{T} \int_0^T \frac{1}{2} dt} = \frac{I_M}{\sqrt{2}}$$


$$\therefore P = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$\therefore P_R = R I_{rms}^2 = \frac{V_{rms}^2}{R}$$

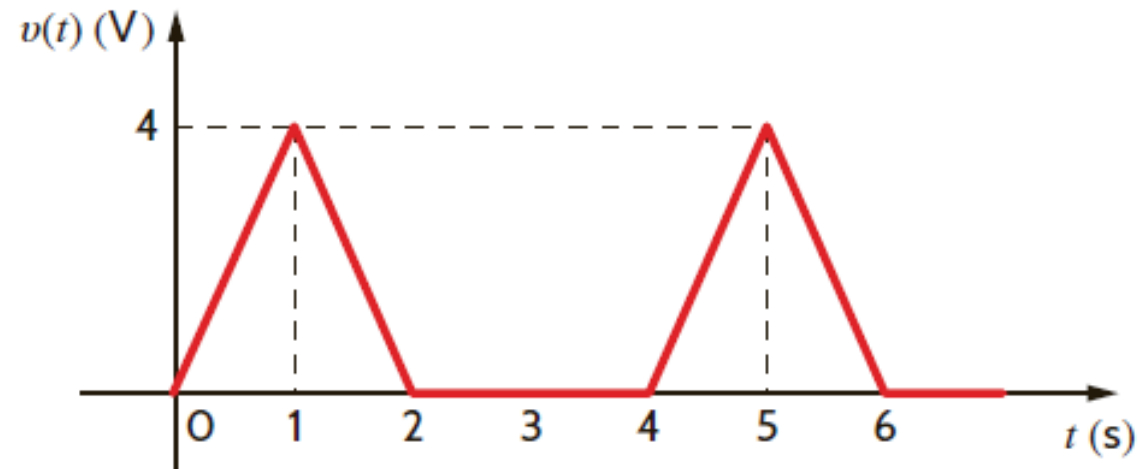Example E9.8

12/11/2019

Calculate the rms value of the provided waveform.



Power Factor

12/11/2019

- $P = V_{rms}I_{rms} \cos(\theta_v - \theta_i) \rightarrow$ *average power (W)*
- $V_{rms}I_{rms} \rightarrow$ *apparent power (VA)*

$$pf = \frac{P}{V_{rms}I_{rms}} = \cos(\theta_v - \theta_i) \rightarrow \text{power factor (VA)}$$

$pf = 1 \rightarrow$ *purely resistive load*

$pf = 0 \rightarrow$ *purely reactive load*

Phase of the current with respect to the voltage


- **leading = $\theta_v - \theta_i < 0$**
- **lagging = $\theta_v - \theta_i > 0$**

Example 9.10

12/11/2019

An industrial load consumes 88kW at a pf of 0.707 lagging from a 480 V_{rms} line. The transmission line resistance from the power company's transformer to the plant is 0.08 Ω. Determine the power that must be supplied by the power company

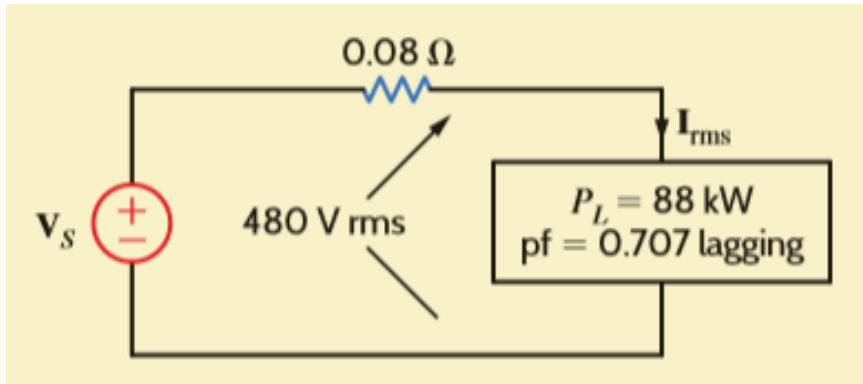- under present conditions and
- if the pf is somehow change to 0.90 lagging.



Complex Power

12/11/2019

$$\mathbf{S} = V_{rms} I_{rms}^* \quad (I_{rms}^* \rightarrow \text{complex conjugate of } I_{rms})$$

$$= V_{rms} I_{rms} \langle \theta_v - \theta_i$$

$$= \underbrace{V_{rms} I_{rms} \cos(\theta_v - \theta_i)}_{\mathbf{P}} + \underbrace{j V_{rms} I_{rms} \sin(\theta_v - \theta_i)}_{\mathbf{Q}}$$

P → Real/Average Power


Q → Reactive Power

$$\mathbf{S} = P + jQ \quad \tan(\theta_v - \theta_i) = \frac{Q}{P}$$

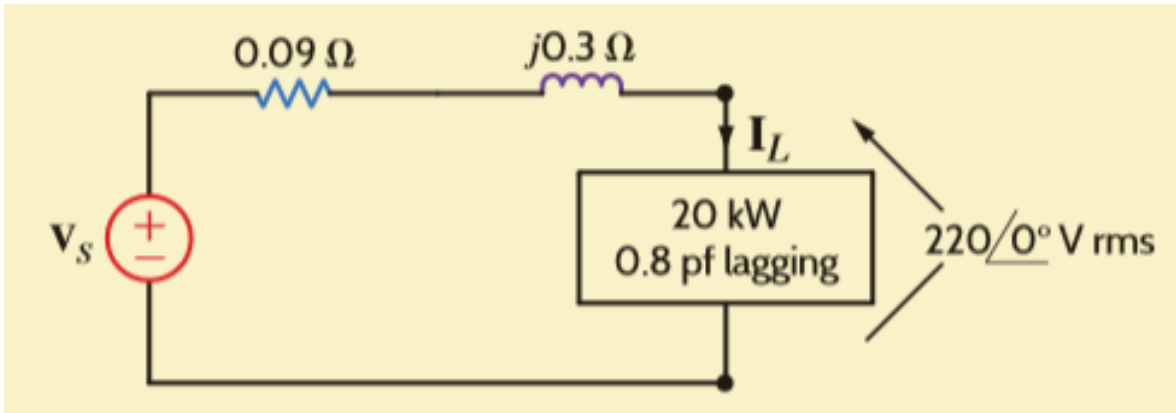Example 9.11

12/11/2019

A load operates at 20 kW, 0.8 pf lagging. The load voltage is $220 \text{ V}_{\text{rms}}$ at 60 Hz. The impedance of the line is $0.09 + j0.3 \Omega$. Determine the voltage and the power factor at the input to the line.





Power Factor Correction

12/11/2019

PF can be increased by decreasing the reactive power through a capacitor bank!

$$S_{new} = S_{old} + S_{cap}$$

$$S_{cap} = -j\omega CV_{rms}^2$$

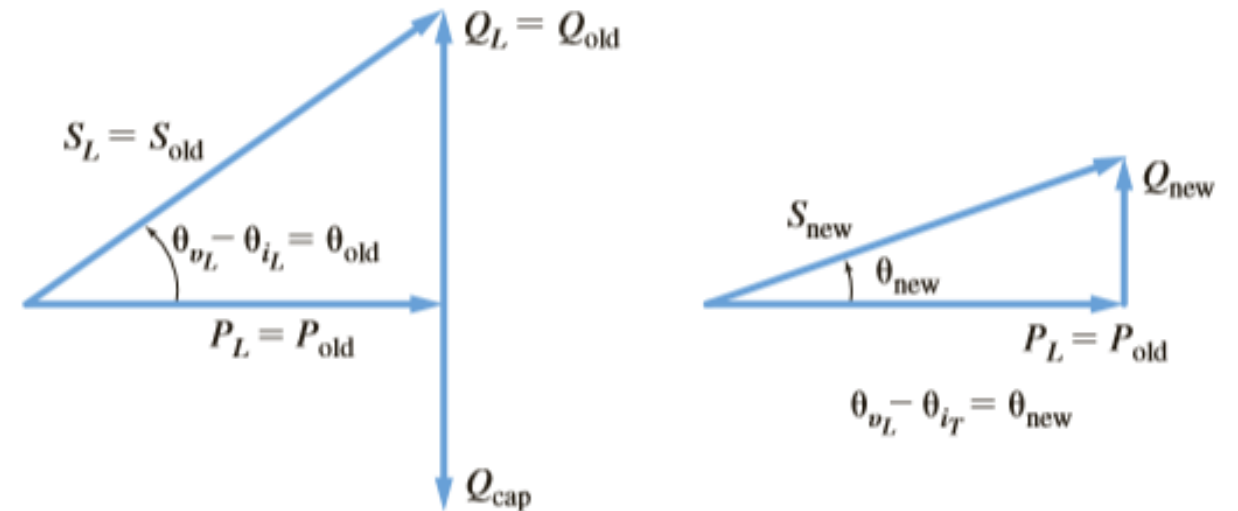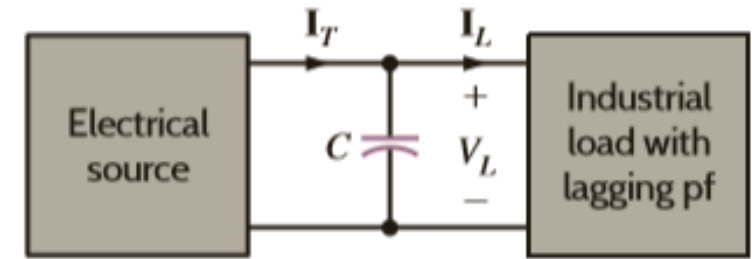

Example 9.14

12/11/2019

Plastic kayaks are manufactured using a process called roto-molding. Molten plastic is injected into a mold, which is then spun on the long axis of the kayak until the plastic cools, resulting in a hollow one-piece craft. Suppose that the induction motors used to spin the molds consume 50kW at a pf of 0.8 lagging from a 220 V_{rms}, 60 Hz line. What would be the capacitor bank size to be placed in parallel to raise the pf to 0.95 lagging?

