

Exam #1 → ~~Thursday January 31~~

→ Tuesday February 5

Concepts Chapter #1:

- Current/Charge Relationship
- Power/Energy/Current/Voltage Relationships
- Conservation of Energy


Concepts Chapter #2:

- Ohm's Law (passive sign convention)
- Kirchhoff's Current Law (KCL)
- Kirchhoff's Voltage Law (KVL)
- Voltage/Current Divider
- Equivalent Resistance
- Wye/Delta Transformations
- Solving Circuits


*** "Bate": bring your own set of equations (no problems, photocopies, solutions, etc)... subject to approval by the professor

Last Lecture → Ohm's Law

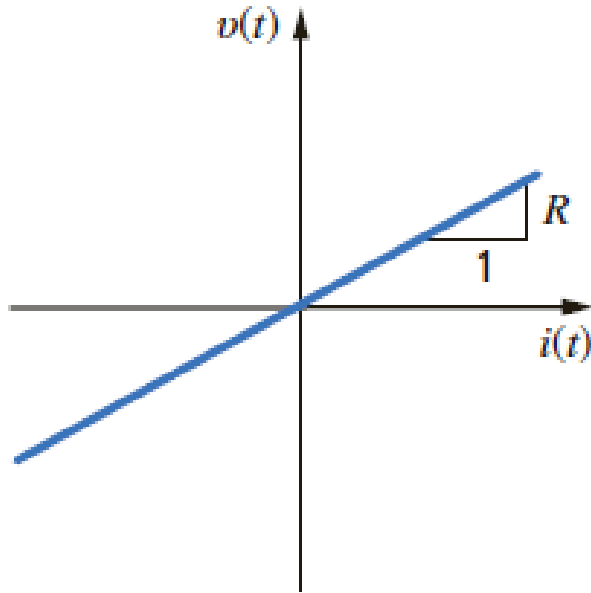States that the voltage across a resistance is directly proportional to the current flowing through it.



$$v(t) = R \cdot i(t)$$

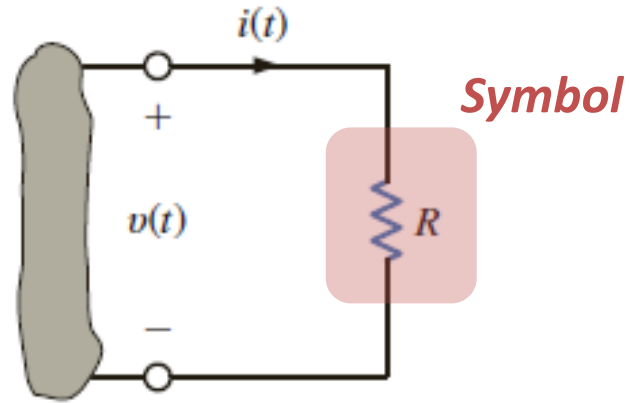

- **Resistance** [$\Omega = V/A$]

$$R = \frac{v(t)}{i(t)}$$

- **Conductance** [$S = A/V$]

$$G = \frac{1}{R} = \frac{i(t)}{v(t)}$$

- **Power Dissipation** [W]

$$\begin{aligned} p(t) &= v(t) \cdot i(t) = R \cdot i(t)^2 = \frac{v(t)^2}{R} \\ &= \frac{i(t)^2}{G} = G \cdot v(t)^2 \end{aligned}$$

Last Lecture → Kirchhoff's Laws


KCL- the algebraic sum of the all the currents entering any node is zero

$$\sum_{h=1}^K i_h^{in}(t) = 0 \quad \longrightarrow \quad \sum_{j=1}^N i_j^{in}(t) = \sum_{i=1}^M i_i^{out}(t)$$

KVL- the algebraic sum of the voltages around any loop is zero

$$\sum_{h=1}^K v_h(t) = 0 \quad \longrightarrow \quad \sum_{j=1}^N v_j^{\uparrow}(t) = \sum_{i=1}^M v_i^{\downarrow}(t)$$

Single Loop Circuits → Voltage Division

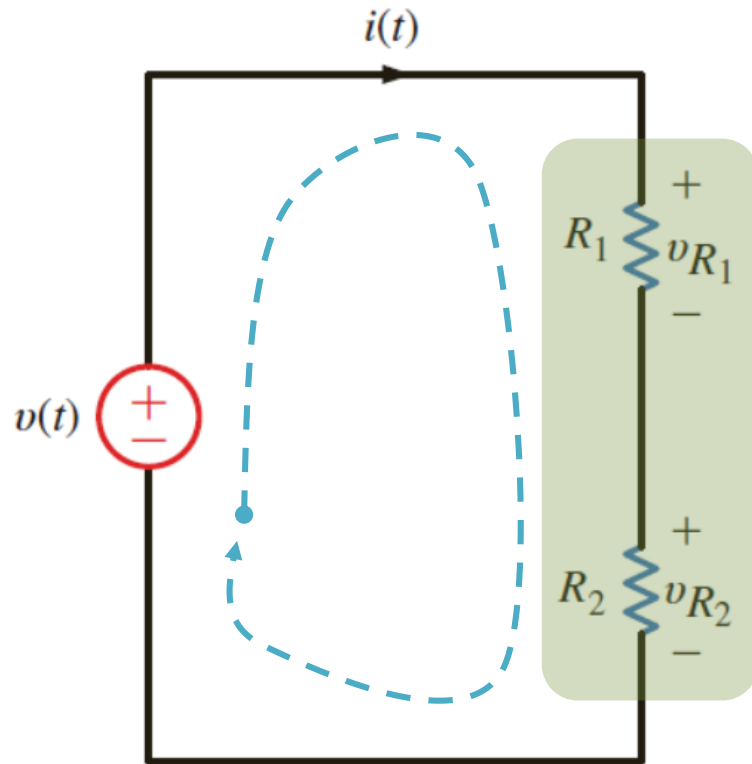

* $I_{R1} = I_{R2} = i(t)$
 $\therefore R_1$ and R_2 are in series


$$\begin{aligned}
 & \bullet \text{ KVL: } v(t) = v_{R_1} + v_{R_2} \\
 & \bullet \text{ Ohm's: } v_{R_1} = R_1 \cdot i(t) \\
 & \quad \quad \quad v_{R_2} = R_2 \cdot i(t)
 \end{aligned}
 \left. \vphantom{\begin{aligned} & \bullet \text{ KVL: } v(t) = v_{R_1} + v_{R_2} \\ & \bullet \text{ Ohm's: } v_{R_1} = R_1 \cdot i(t) \\ & \quad \quad \quad v_{R_2} = R_2 \cdot i(t) \end{aligned}} \right\} \therefore i(t) = \frac{v(t)}{R_1 + R_2}$$

$$\begin{aligned}
 \therefore v_{R1} &= \frac{R_1}{R_1 + R_2} \cdot v(t) \\
 v_{R2} &= \frac{R_2}{R_1 + R_2} \cdot v(t)
 \end{aligned}$$

The source voltage $v(t)$ is divided between the resistors R_1 and R_2 in direct proportion to their resistances.

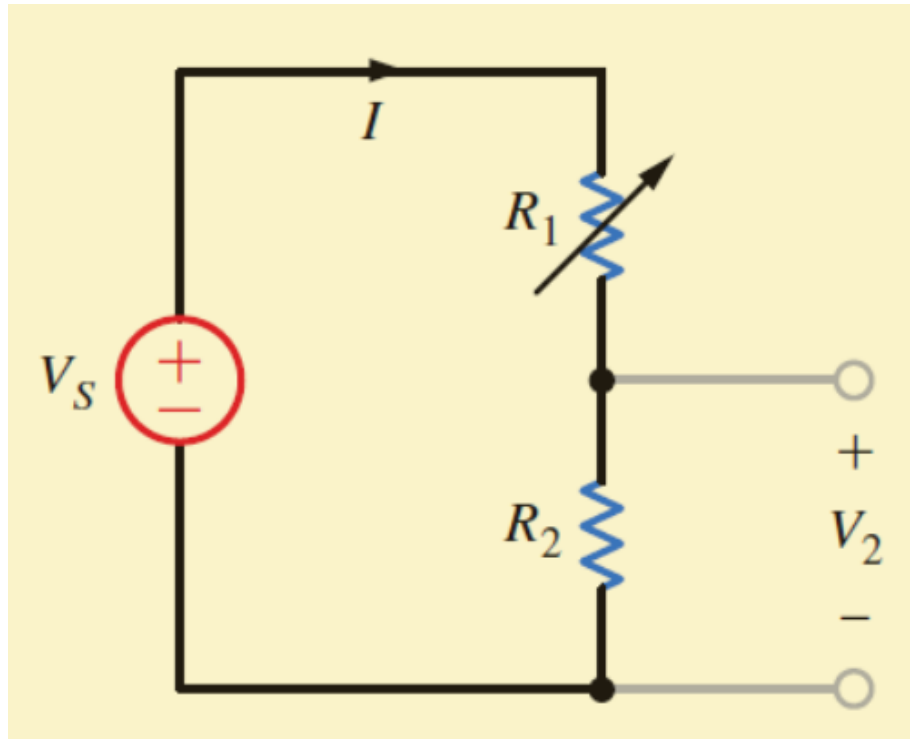
Example 2.13

Assuming $V_s=9V$, $R_1=90k\Omega$, and $R_2=30k\Omega$, examine the change in both the voltage across R_2 and the power absorbed in the resistor as R_1 is changed from $90k\Omega$ to $15k\Omega$.



Single Loop Circuits → Multiple Source/Resistor Networks

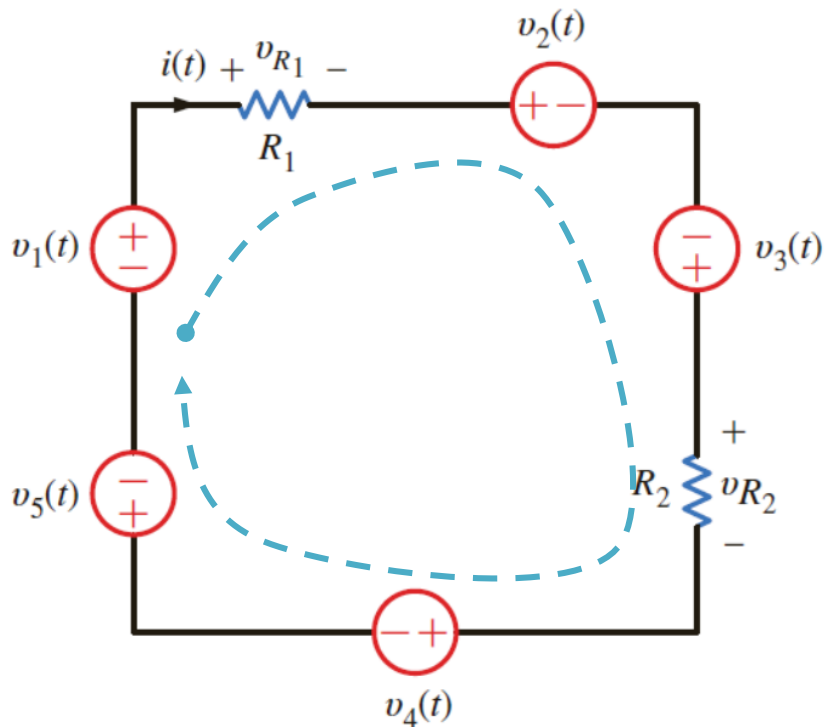- KVL: $v_1(t) - v_{R1} - v_2(t) + v_3(t) - v_{R2} - v_4(t) - v_5(t) = 0$




$$v_1(t) - v_2(t) + v_3(t) - v_4(t) - v_5(t) = v_{R1} + v_{R2}$$

$$v_1(t) - v_2(t) + v_3(t) - v_4(t) - v_5(t) = i(t) \cdot [R_1 + R_2]$$




Equivalent Circuit

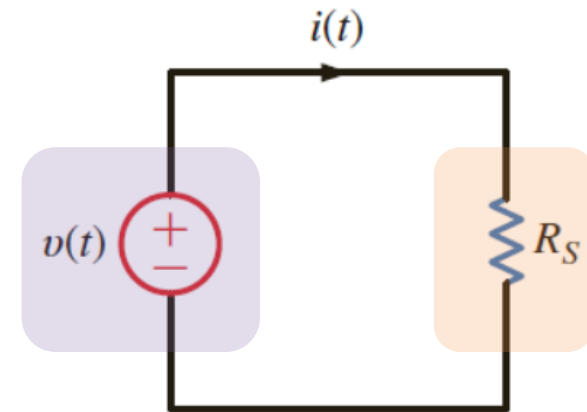


Single Loop Circuits → Multiple Source/Resistor Networks

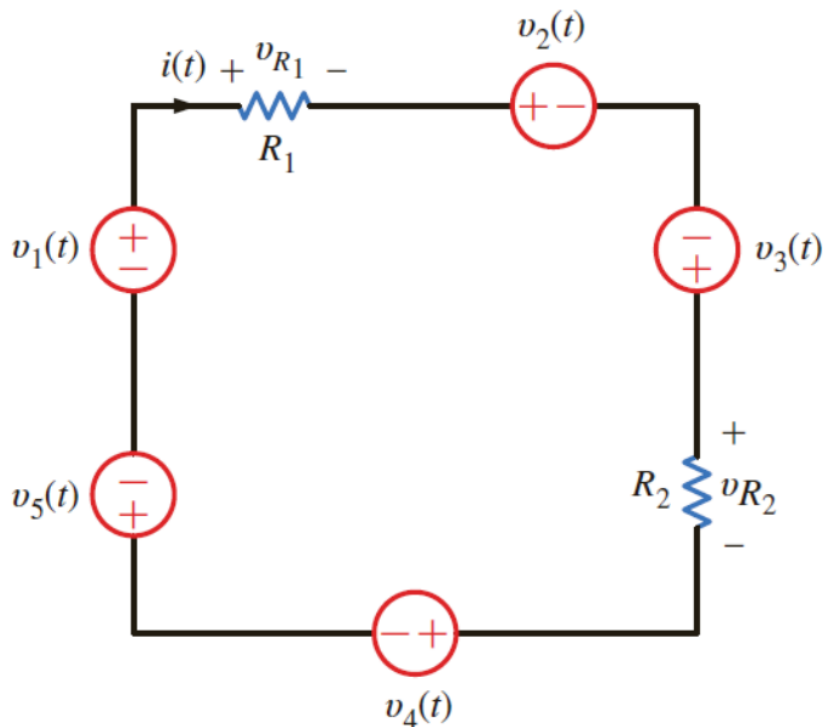- ∴ The sum of several voltage source in series can be replaced by one source whose value is the algebraic sum of the individual source
- ∴ The equivalent resistance of N resistors in series is simply the sum of the individual resistances.




$$R_S = \sum R_1 + R_2 + \dots + R_N$$

→ *Equivalent Circuit*

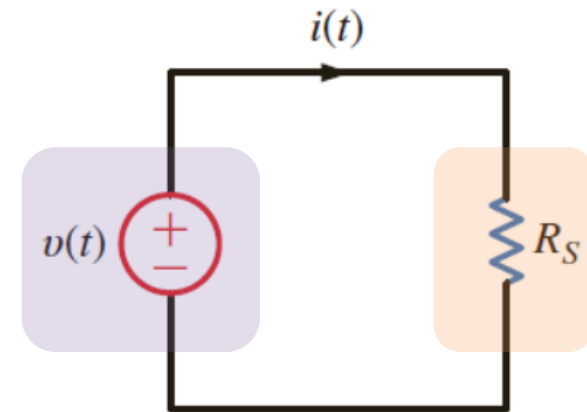


Learning Assessment E2.11

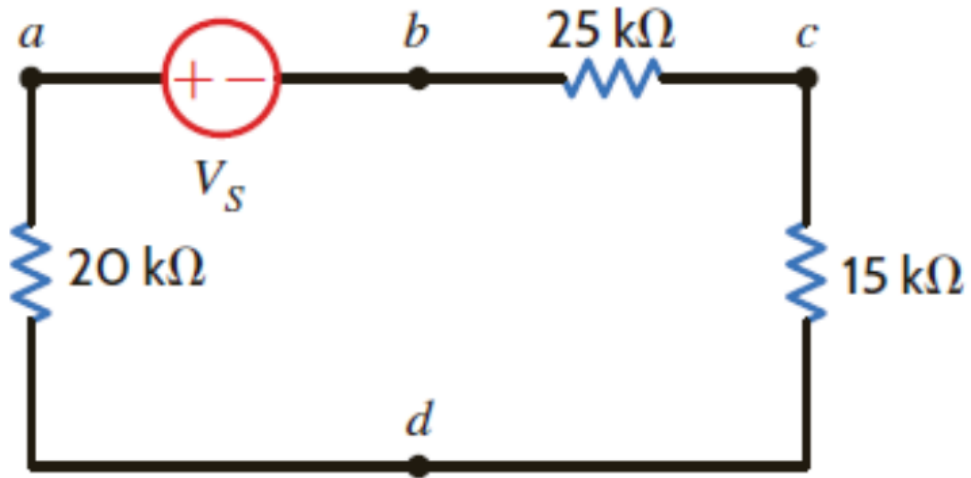In the network provided, if V_{ad} is 3V, find V_s .



Current Division

$i_1 = ?$ $i_2 = ?$

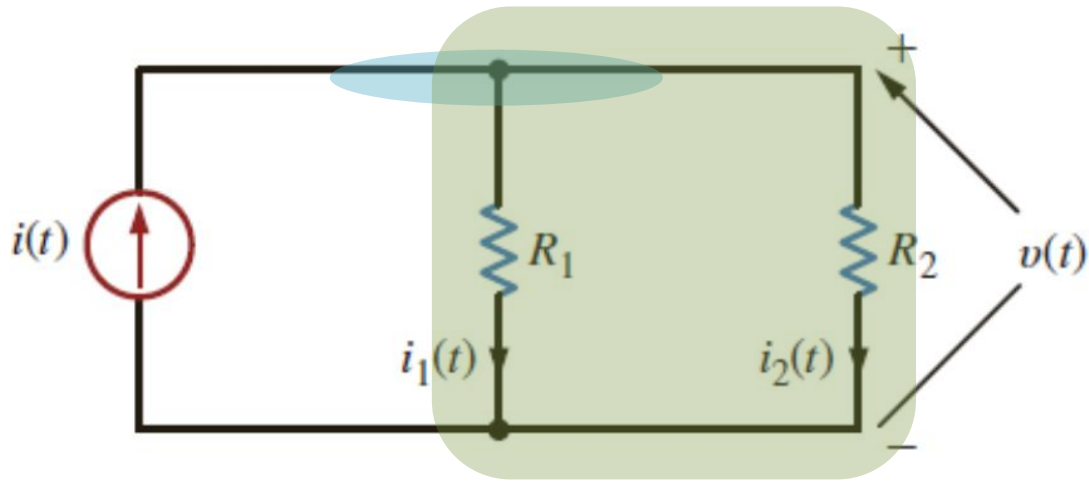

- KCL: $i(t) = i_1(t) + i_2(t)$
- Ohm's: $i_1(t) = \frac{v(t)}{R_1}$
- $i_2(t) = \frac{v(t)}{R_2}$

$\therefore v(t) = i(t) \cdot \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$

$\therefore i_1(t) = \frac{R_2}{R_1 + R_2} \cdot i(t)$

$i_2(t) = \frac{R_1}{R_1 + R_2} \cdot i(t)$

* $V_{R1} = V_{R2} = v(t)$
 $\therefore R_1$ and R_2 are in parallel

Single Loop Circuits → Multiple Source/Resistor Networks


- KCL: $i_1(t) - i_2(t) - i_3(t) + i_4(t) - i_5(t) - i_6(t) = 0$

$$\hookrightarrow i_1(t) - i_3(t) + i_4(t) - i_6(t) = i_2(t) + i_5(t)$$

$$i_1(t) - i_3(t) + i_4(t) - i_6(t) = v(t) \cdot \left[\frac{1}{R_1} + \frac{1}{R_2} \right]$$

$$i_0(t)$$

$$1/R_p$$

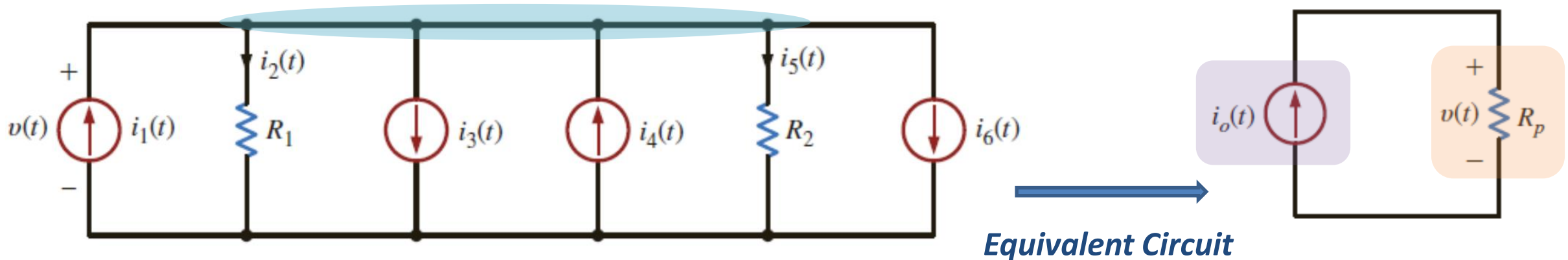


Single Loop Circuits → Multiple Source/Resistor Networks

- ∴ The sum of several current sources in series can be replaced by one source whose value is the algebraic sum of the individual source
- ∴ The reciprocal of the equivalent resistance of N resistors in parallel is equal to the sum of the reciprocal of the individual resistances.

$$\frac{1}{R_p} = \sum \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$


For 2 resistances in parallel R_p can be expressed as...

$$R_p = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

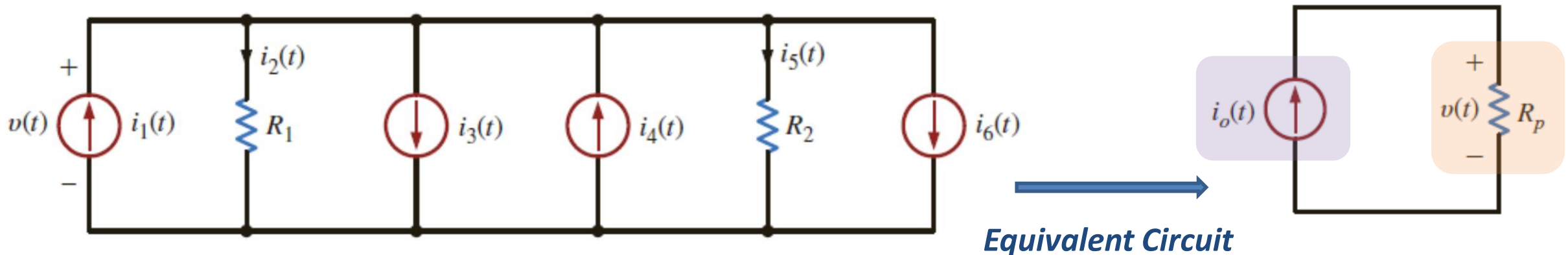

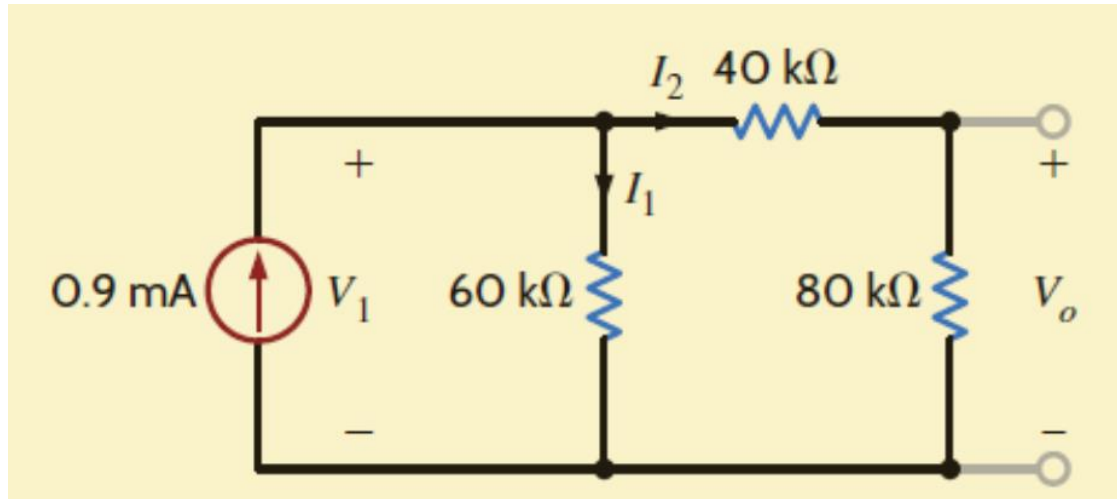
Example 2.17

For the given network find I_1 , I_2 , and V_o .



Series/Parallel Resistor Combinations

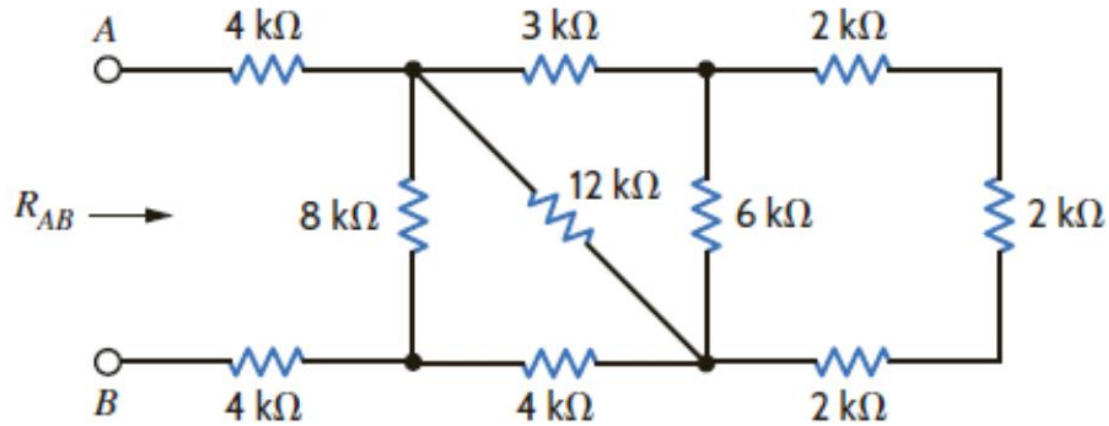E2.16: Find R_{AB} in the provided network.



- **Series:** $R_S = R_1 + R_2 + \dots + R_N$
- **Parallel:** $\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$

Learning Assessment E2.22

Find V_0 , V_1 , and V_2 in the network provided.

