

# Exam #1 → Tuesday February 5, 2018 @ 3:30pm

## Concepts Chapter #1:


- Current/Charge Relationship
- Power/Energy/Current/Voltage Relationships
- Conservation of Energy

## Concepts Chapter #2:

- Ohm's Law (passive sign convention)
- Kirchhoff's Current Law (KCL)
- Kirchhoff's Voltage Law (KVL)
- Voltage/Current Divider
- Equivalent Resistance
- Wye/Delta Transformations
- Solving Circuits

\*\*\* "Bate": bring your own set of equations (no problems, photocopies, solutions, etc)... subject to approval by the professor
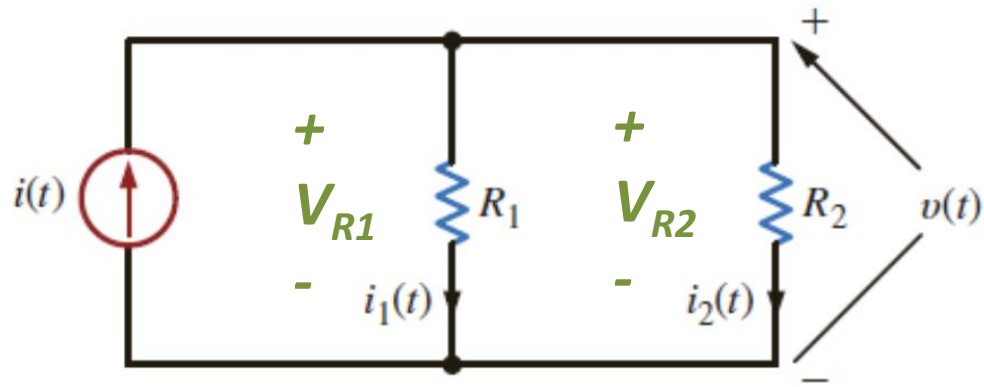
# Last Lecture → Current / Voltage Division




$$* V_{R1} = V_{R2} = v(t)$$

$$\therefore R_1 \text{ and } R_2 \text{ are in parallel}$$

$$\therefore i_1(t) = \frac{R_2}{R_1 + R_2} \cdot i(t)$$
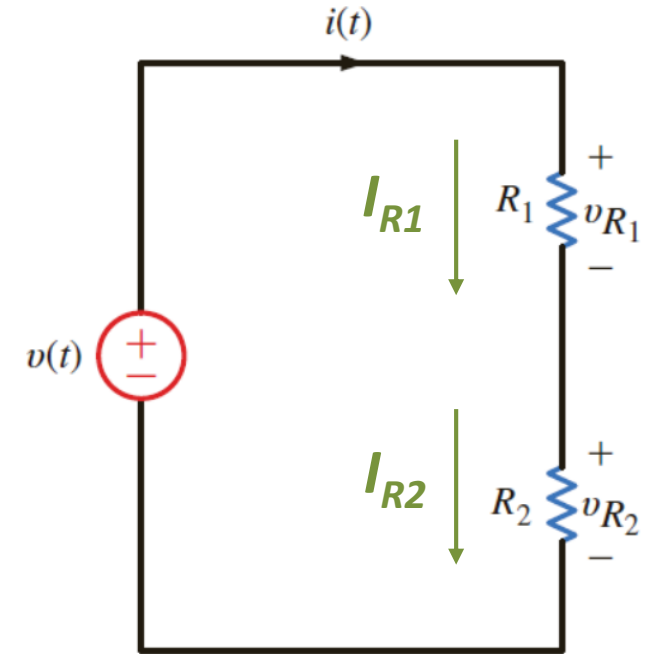
$$i_2(t) = \frac{R_1}{R_1 + R_2} \cdot i(t)$$



$$* I_{R1} = I_{R2} = i(t)$$

$$\therefore R_1 \text{ and } R_2 \text{ are in series}$$

$$\therefore v_{R1} = \frac{R_1}{R_1 + R_2} \cdot v(t)$$

$$v_{R2} = \frac{R_2}{R_1 + R_2} \cdot v(t)$$

## Last Lecture → Multiple Source/Resistor Networks

- Series

The sum of several voltage source in series can be replaced by one source whose value is the algebraic sum of the individual source

The equivalent resistance of N resistors in series is simply the sum of the individual resistances.

$$R_s = R_1 + R_2 + \dots + R_N$$

---

- Parallel




The sum of several current source in series can be replaced by one source whose value is the algebraic sum of the individual source

The reciprocal of the equivalent resistance of N resistors in parallel is equal to the sum of the reciprocal of the individual resistances.

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

# Series/Parallel Resistor Combinations

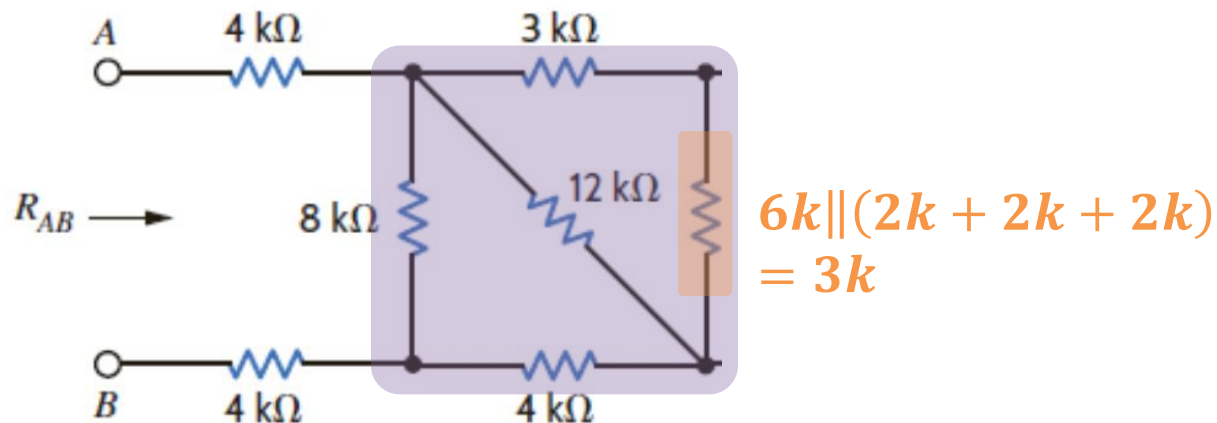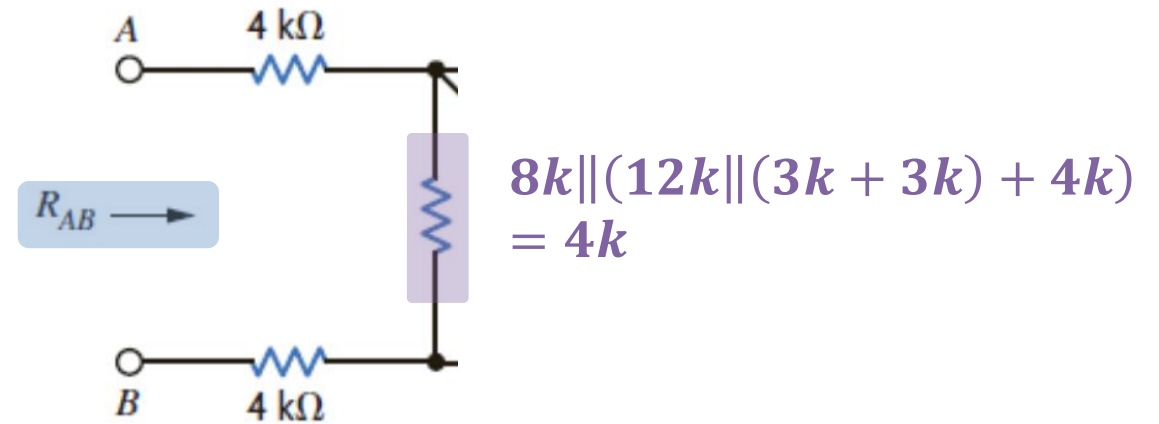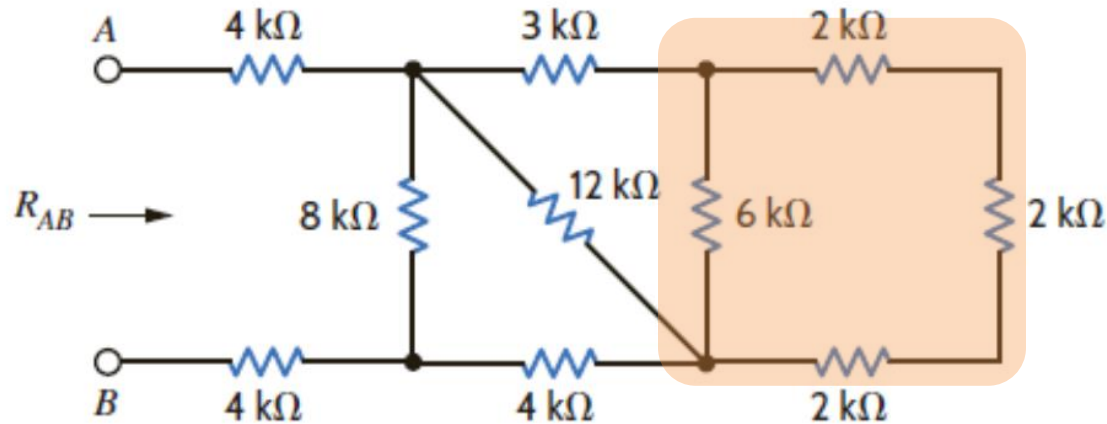
**E2.16: Find  $R_{AB}$  in the provided network.**



$$\therefore R_{AB} = 4k + 4k + 4k$$

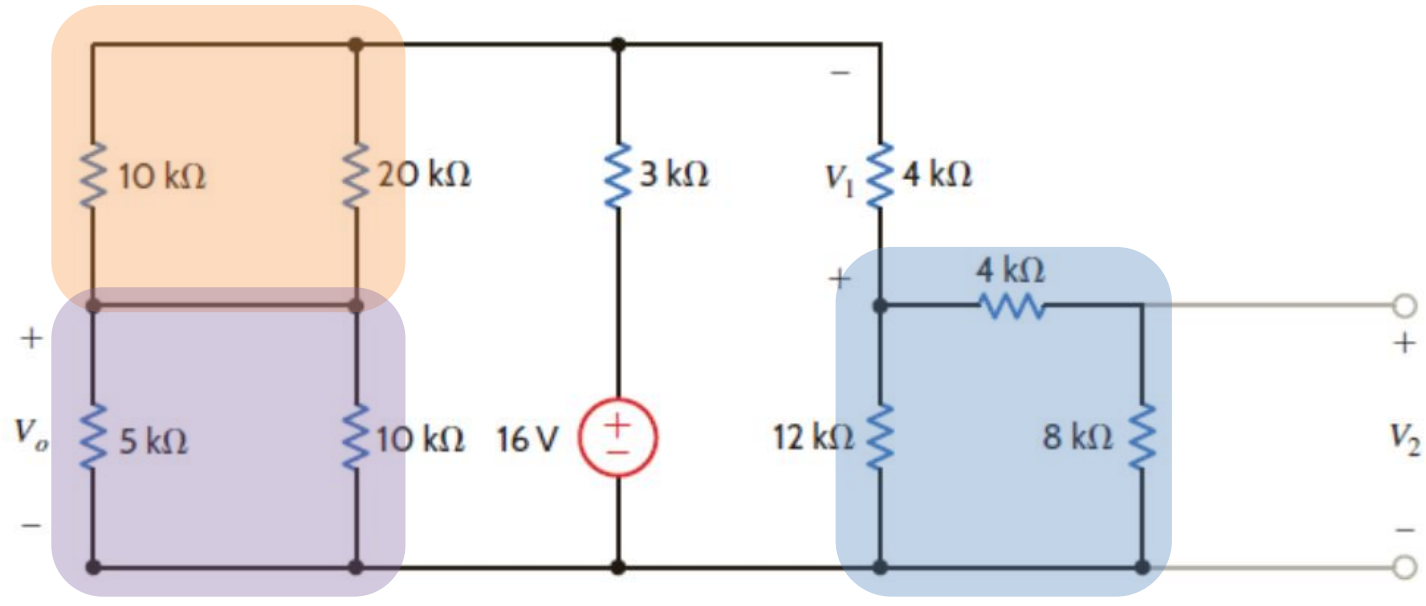
# Learning Assessment E2.22

Find  $V_0$ ,  $V_1$ , and  $V_2$  in the network provided.



$$V_0 = V_x \left[ \frac{3.3k}{6.7k + 3.3k} \right] = 1.24V$$
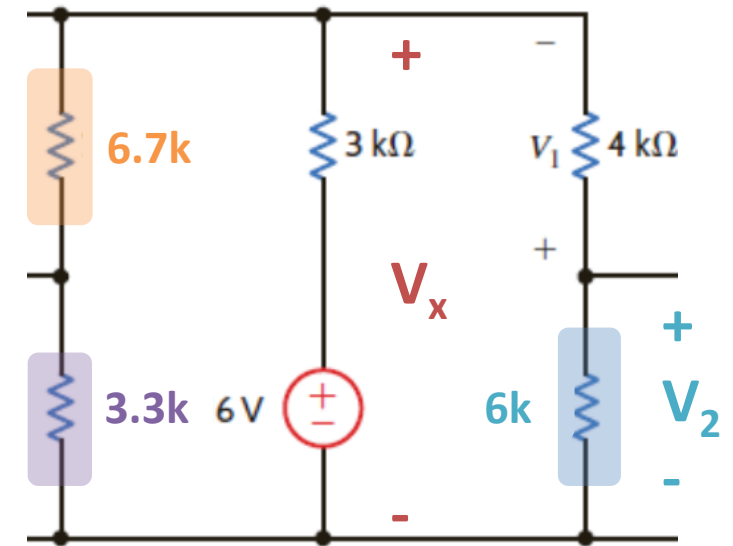
$$V_0 = 4.5 \left[ \frac{8k}{4k + 8k} \right] = 3V$$



$$V_x = 6 \left[ \frac{10k \parallel 10k}{3k + 10k \parallel 10k} \right] = 3.75V$$

$$V_1 = -V_x \left[ \frac{4k}{6k + 4k} \right] = -1.5V$$

$$V_2 = 6 + V_1 = 4.5V$$

# Wye $\Leftrightarrow$ Delta Transformations


For the two networks to be equivalent at each corresponding pair of terminals, it is necessary that the resistance at the corresponding terminals be equal (e.g., the resistance at terminals a and b with c open-circuited must be the same for both networks).

$\Delta \leftarrow Y$


$$R_1 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_c}$$
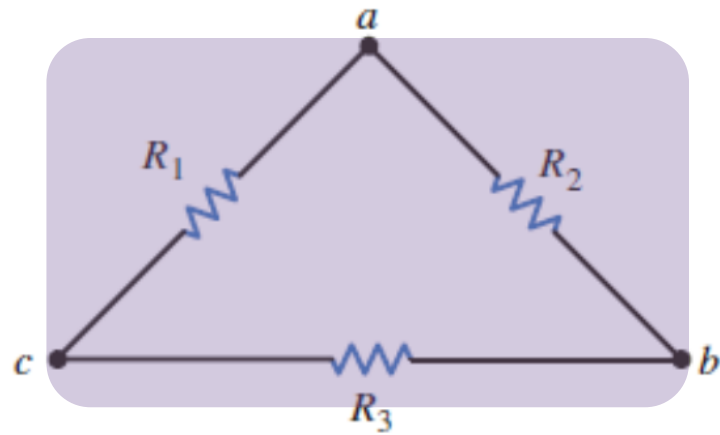
$$R_3 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_a}$$



(a)

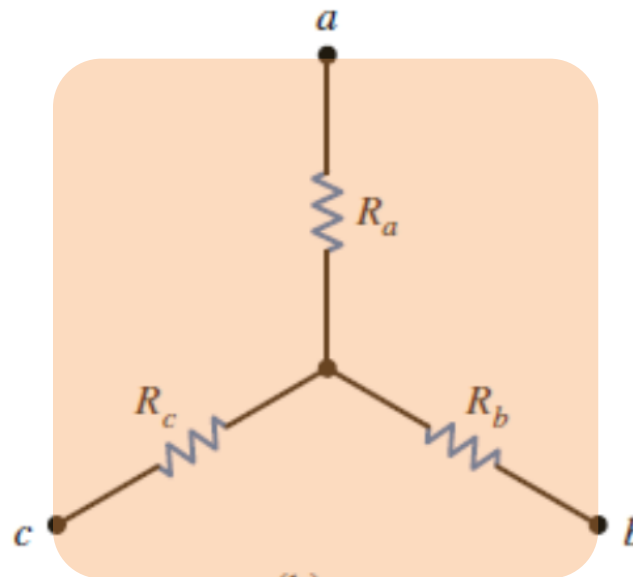

(b)

$Y \leftarrow \Delta$



$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$
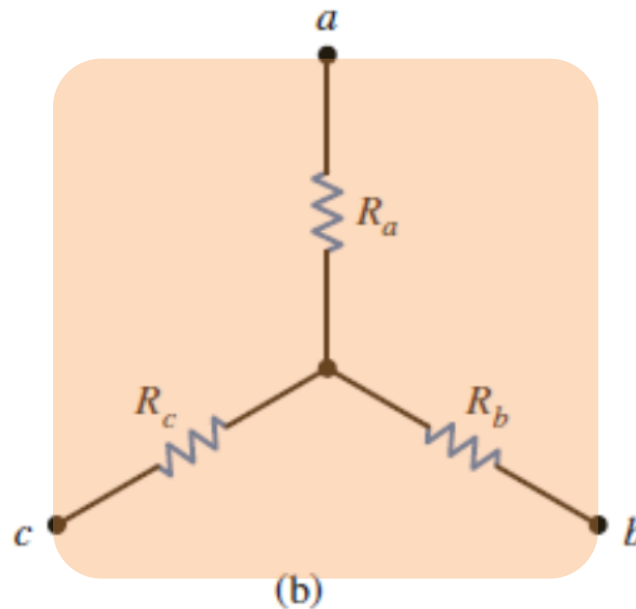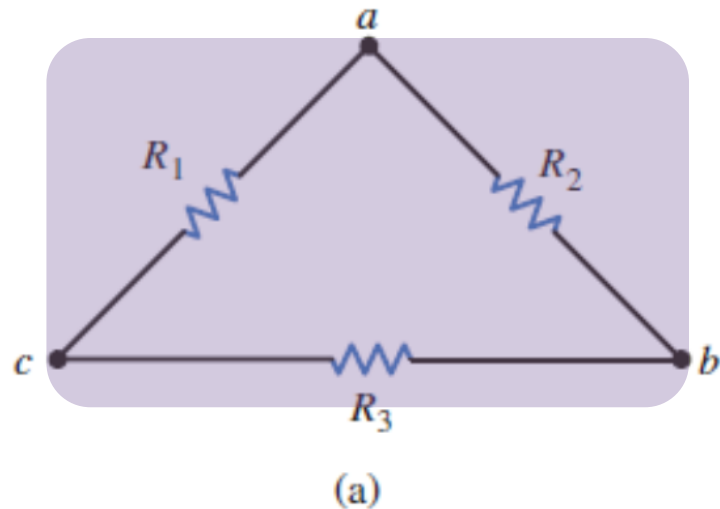
# Wye $\Leftrightarrow$ Delta Transformations

For the two networks to be equivalent at each corresponding pair of terminals, it is necessary that the resistance at the corresponding terminals be equal (e.g., the resistance at terminals a and b with c open-circuited must be the same for both networks).



$$\dots \text{ for } R_a = R_b = R_c = R_Y$$


$$R_1 = R_2 = R_3 = R_\Delta$$

$$\Delta \leftarrow Y \quad \left\{ R_\Delta = 3R_Y \right.$$

$$Y \leftarrow \Delta \quad \left\{ R_Y = \frac{1}{3}R_\Delta \right.$$

# Learning Assessment E2.26

Find  $I_1$  in the network provided.

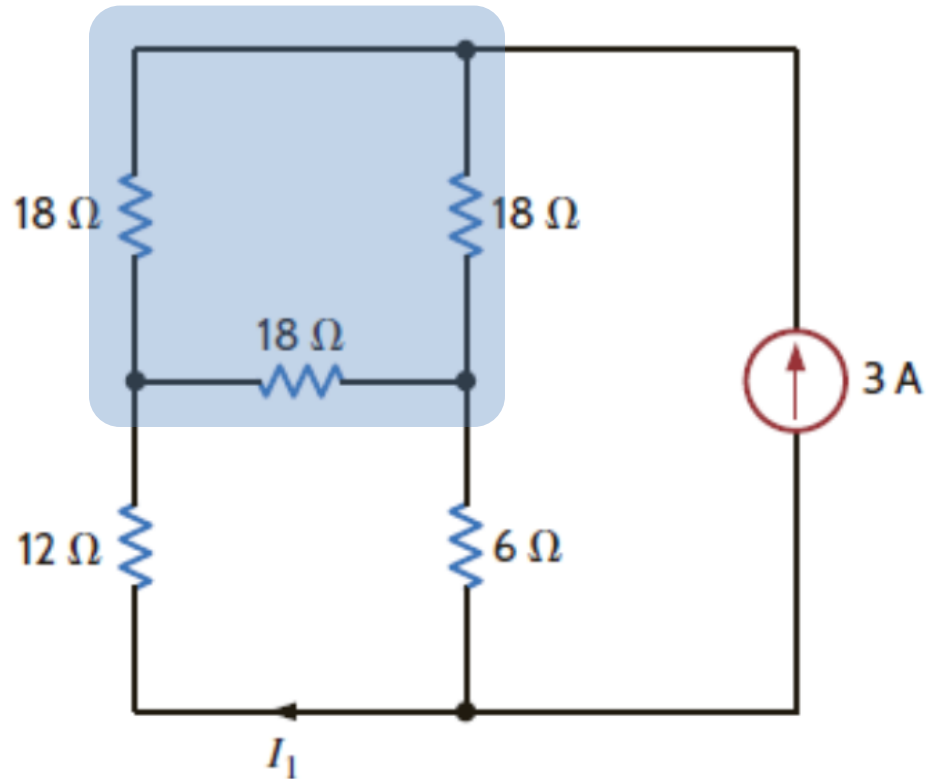




# Circuits with Dependent Sources

- 1) Write KVL and/or KCL equations for the network  
→ treat the dependent CS as an independent CS
- 2) Write the equation that specifies the relationship of the dependent source to the controlling parameter.
- 3) Solve the equations for the unknowns.  
→ Be sure the number of linearly independent equations matches the number of unknowns.

# Learning Assessment E2.29

Find  $V_A$  in the network provided.

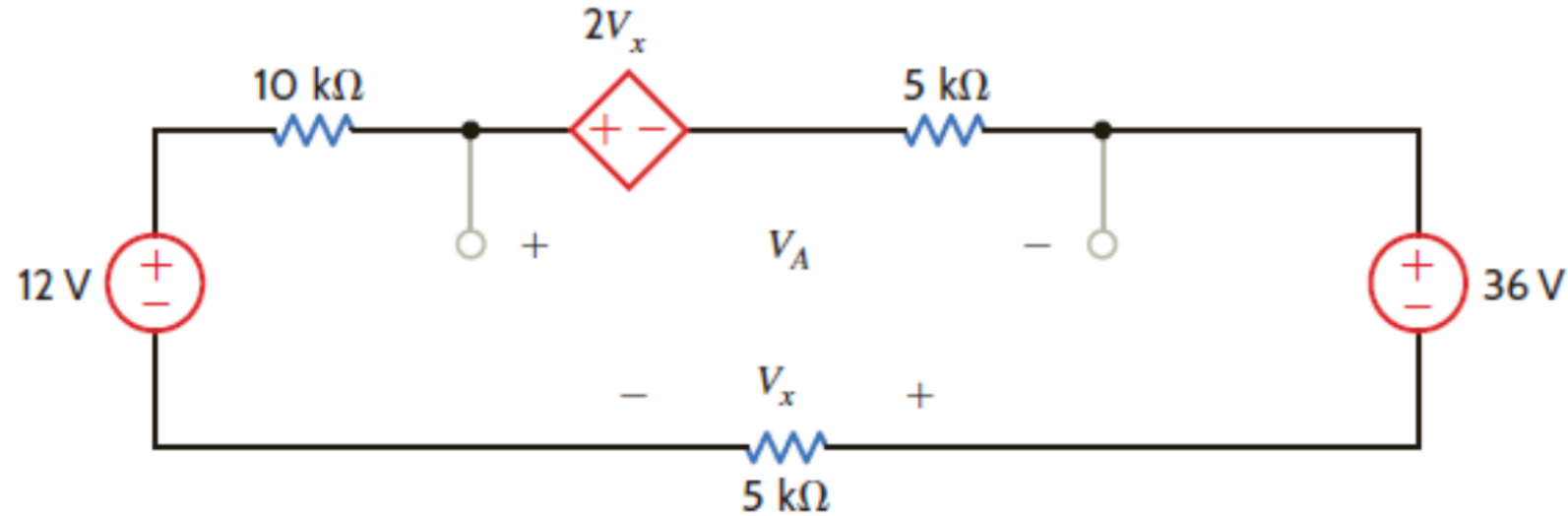

## Problem 2.35

Find the power absorbed by the dependent source in the circuit provided.

