
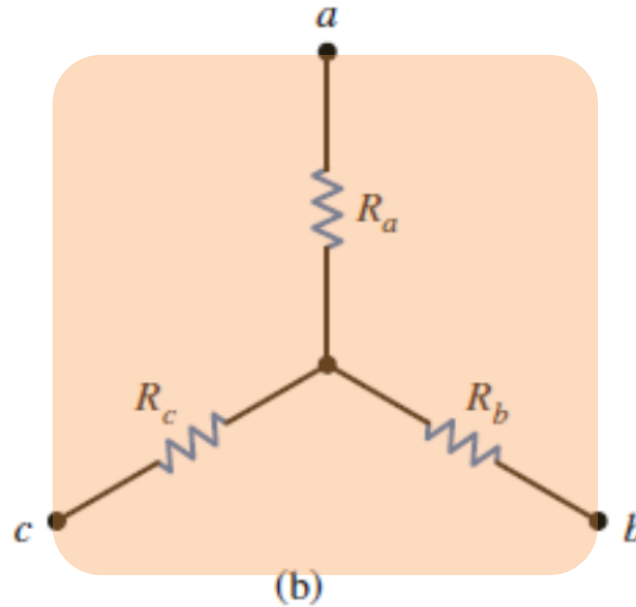


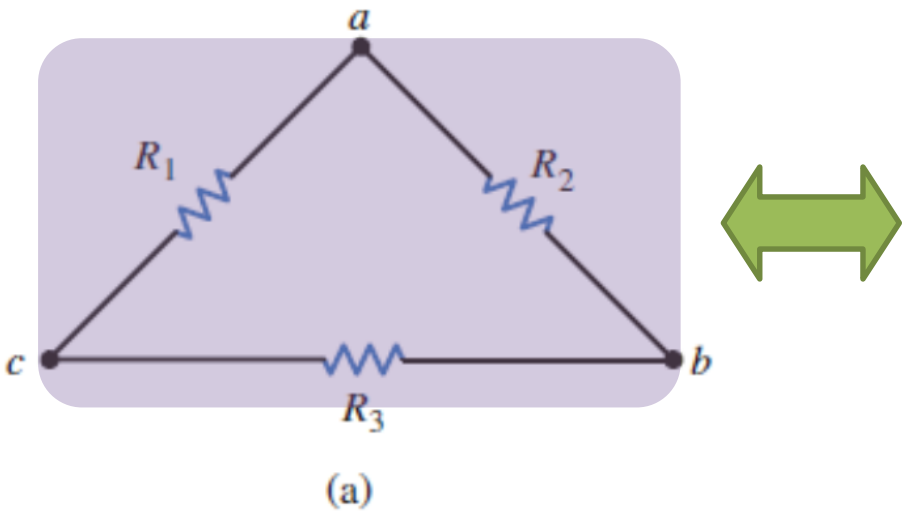Last Lecture → Wye ⇌ Delta Transformation



$\Delta \leftarrow Y$

$$R_1 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_a}$$

$Y \leftarrow \Delta$

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

assuming $R_a = R_b = R_c = R_Y$

$R_1 = R_2 = R_3 = R_\Delta$

$$R_\Delta = 3R_Y \quad R_Y = \frac{1}{3}R_\Delta$$

Nodal and Loop Analysis → Chapter #3

- **Solve circuits with multiple nodes using nodal analysis**
- **Solve circuits with multiple loops using loop analysis**
- **Identify the most appropriate analysis technique that should be utilized to solve a particular problem**


Nodal Analysis

- One node is selected as the reference node
- KCL is applied to the remaining $N-1$ nodes

Ohm's Law:

$$i = \frac{v_m - v_n}{R}$$

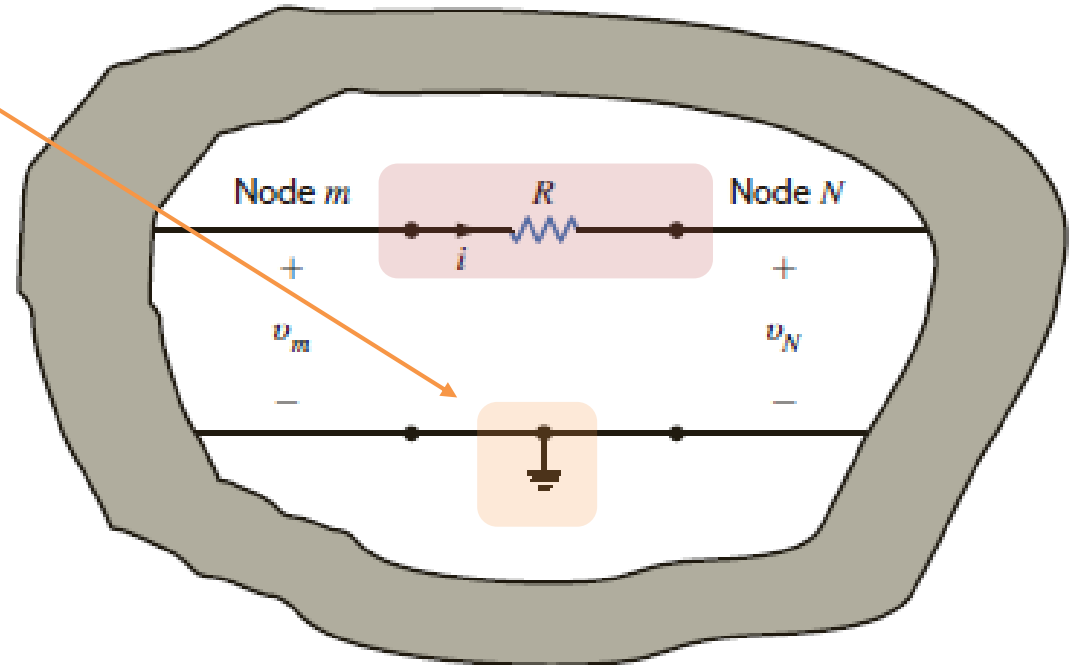
- Current defined by Ohm's law
- Variables are node voltages
- Voltages are defined with respect to a common point (the reference)



N-1 independent simultaneous equations!

Nodal Analysis → known node voltages

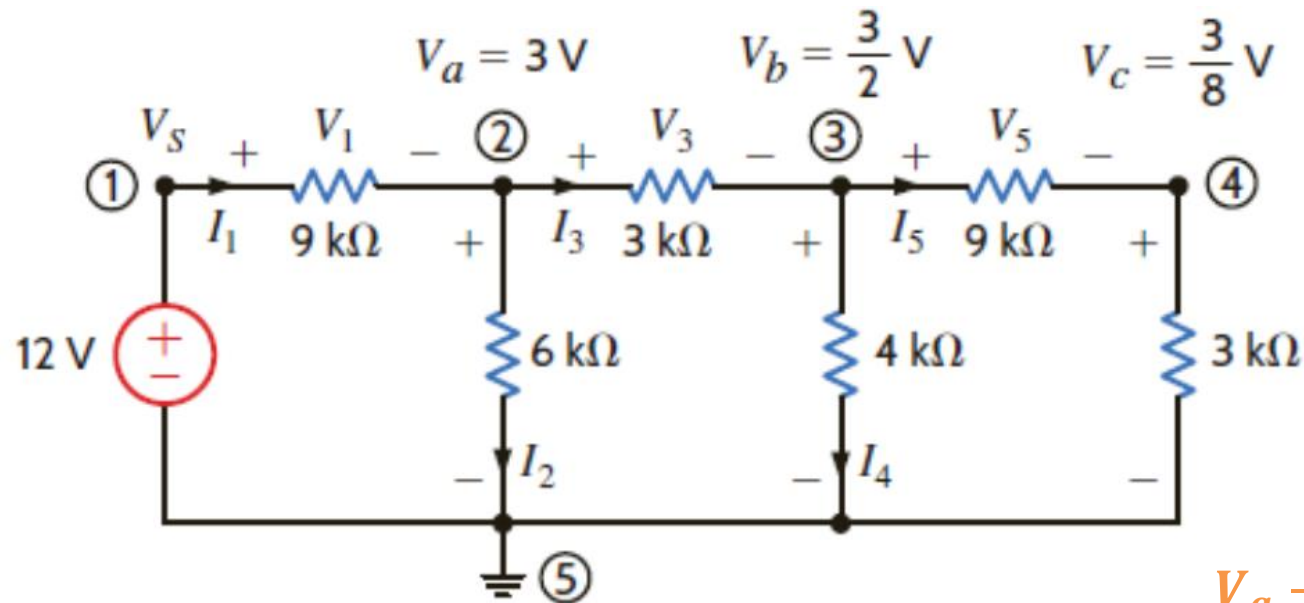- Define node voltages to be positive with respect to the reference node
- Define currents with respect to node voltages



- Voltage across resistors

$$V_1 = V_S - V_a = 9V$$

$$V_3 = V_a - V_b = \frac{3}{2}V$$

$$V_5 = V_b - V_c = \frac{9}{8}V$$

- Current in resistors

$$I_1 = \frac{V_1}{9k} = \frac{V_S - V_a}{9k} = 1mA$$

$$I_3 = \frac{V_3}{3k} = \frac{V_a - V_b}{3k} = \frac{1}{2}mA$$

$$I_5 = \frac{V_5}{9k} = \frac{V_b - V_c}{9k} = \frac{1}{8}mA$$


$$I_2 = \frac{V_a - 0}{6k} = \frac{1}{2}mA$$

$$I_4 = \frac{V_b - 0}{4k} = \frac{3}{8}mA$$

Nodal Analysis → with Independent Current Sources

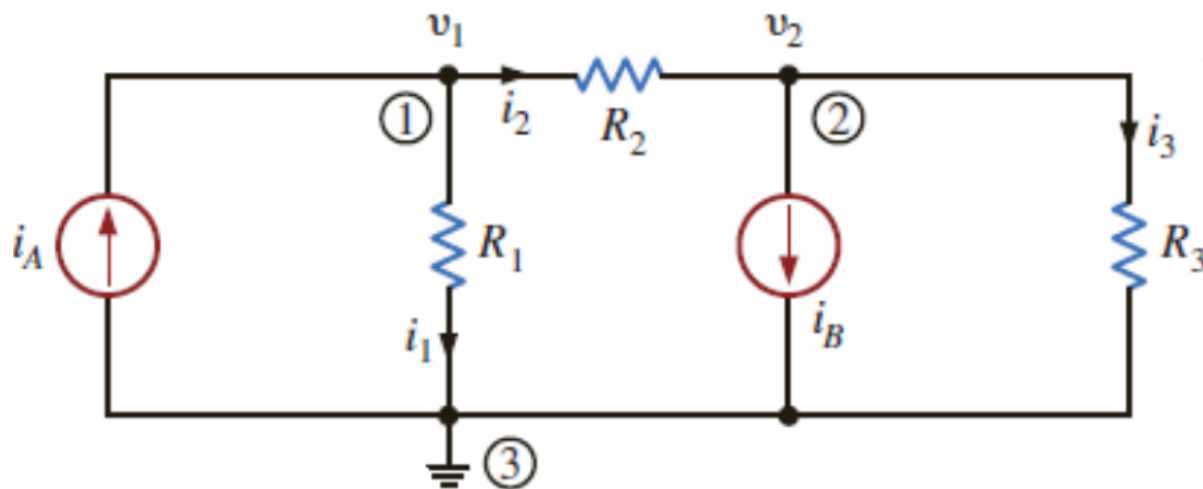- 1) Identify #of nodes: 3 node circuit
- 2) Select reference node: bottom node, 3
- 3) Label other node voltages: v_1, v_2
- 4) Identify branch currents: i_1, i_2, i_3
- 5) Apply KCL to nodes: 1, 2 → 2 independent equations

assume: $I_A = 1mA$ $R_1 = 12k\Omega$
 $I_B = 4mA$ $R_2 = 6k\Omega$
 $R_3 = 6k\Omega$



KCLs: $I_A = I_1 + I_2 = \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} = V_1 \left[\frac{1}{R_1} + \frac{1}{R_2} \right] - V_2 \left[\frac{1}{R_2} \right]$

$I_B = I_2 + I_3 = \frac{V_1 - V_2}{R_2} - \frac{V_2}{R_3} = V_1 \left[\frac{1}{R_2} \right] - V_2 \left[\frac{1}{R_2} + \frac{1}{R_3} \right]$


matrix eq.

$$\begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} \frac{1}{R_1 \parallel R_2} & -\frac{1}{R_2} \\ \frac{1}{R_2} & -\frac{1}{R_2 \parallel R_3} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

Nodal Analysis → Example 3.2

Write the equations in matrix form for the provided circuit.
Assume $R_1=R_2=2\text{k}\Omega$, $R_3=R_4=4\text{k}\Omega$, $R_5=1\text{k}\Omega$, $i_A=4\text{mA}$, and $i_B=2\text{mA}$.

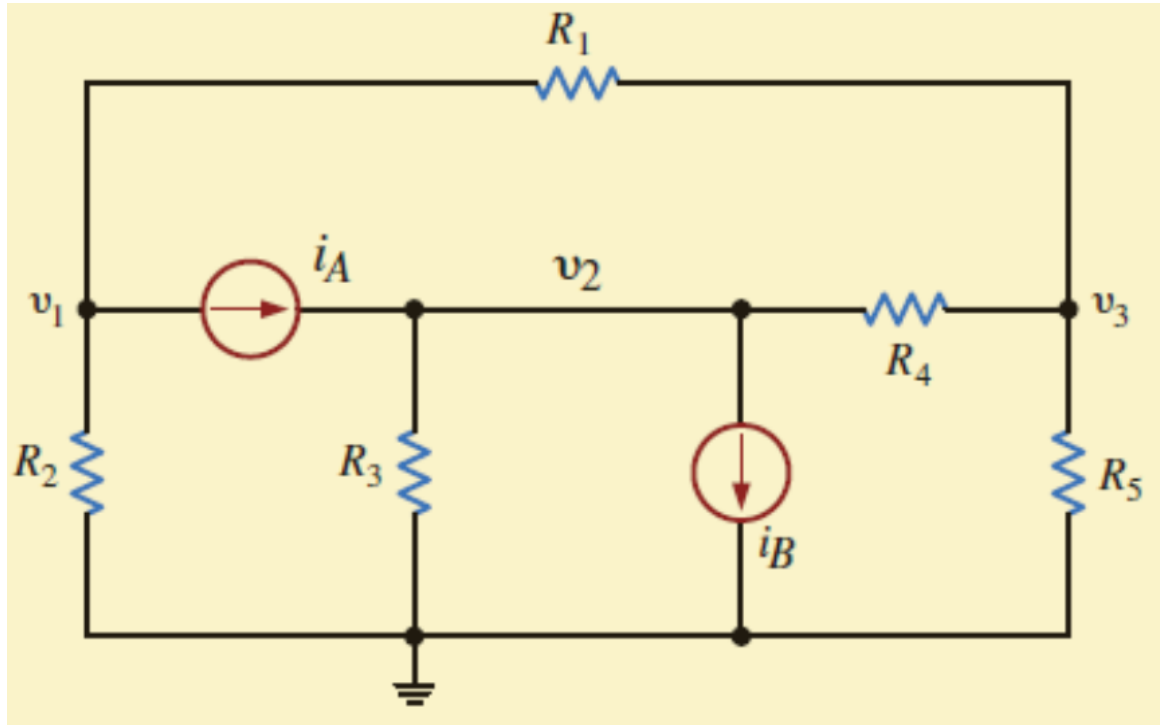- 1) Identify #of nodes
- 2) Select reference node
- 3) Label other node voltages
- 4) Identify branch currents
- 5) Apply KCL to nodes



matrix eq.

$$\begin{bmatrix} I_A \\ I_A \\ 0 \end{bmatrix} = \begin{bmatrix} -\frac{1}{R_1 \parallel R_2} & 0 & \frac{1}{R_1} \\ 0 & \frac{1}{R_3 \parallel R_4} & -\frac{1}{R_4} \\ \frac{1}{R_1} & \frac{1}{R_4} & -\frac{1}{R_1 \parallel R_4 \parallel R_5} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

Exam #1 → Tuesday February 5, 2018 @ 3:30pm

Concepts Chapter #1:

- Current/Charge Relationship
- Power/Energy/Current/Voltage Relationships
- Conservation of Energy


Concepts Chapter #2:

- Ohm's Law (passive sign convention)
- Kirchhoff's Current Law (KCL)
- Kirchhoff's Voltage Law (KVL)
- Voltage/Current Divider
- Equivalent Resistance
- Wye/Delta Transformations
- Solving Circuits

*** "Bate": bring your own set of equations (no problems, photocopies, solutions, etc)... subject to approval by the professor


Problem 2.65

Find R_{AB} in the circuit provided.

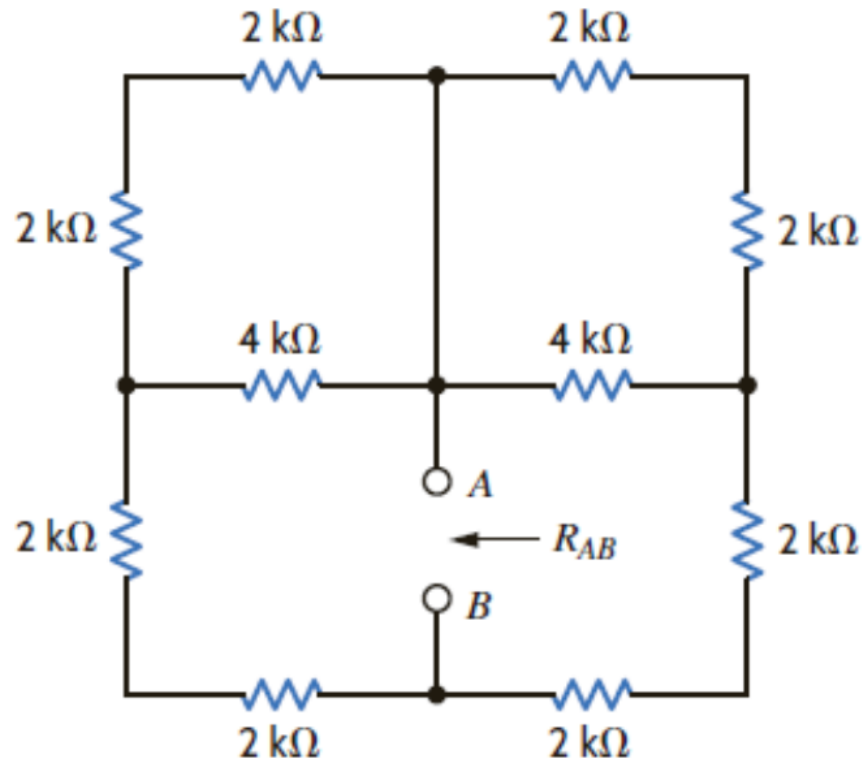

Learning Assessment E2.33

If the power supplied by the 3A current source is 12W, find V_s and the power supplied by the 10V source.

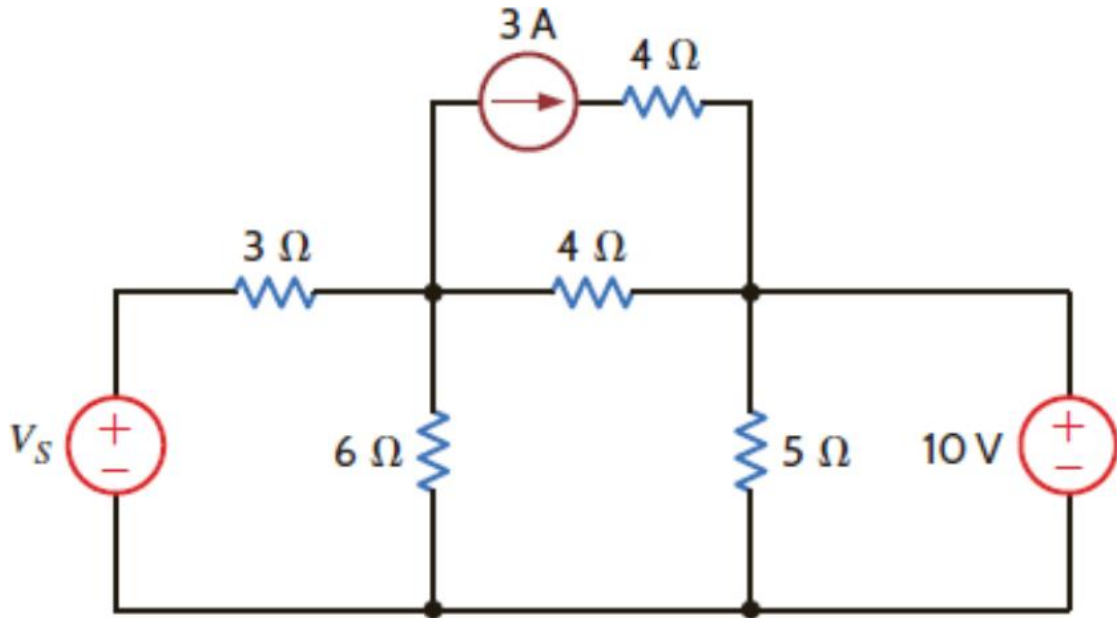

Problem 2.121

Find V_o in the provided network.

