

# Exam #2 → ~~Thursday, February 14~~

## Concepts Chapter #3:

→ Tuesday, February 21

### 1) Nodal Analysis

- Select node as reference
- # of Eq. = # of nodes – 1
- variables → voltages
- KCL → equations
- voltage source → constraint eq. (express in terms of variables)
- voltage source between 2 non-reference nodes → supernode

\*\*\* “Bate”: bring your own set of equations (no problems, photocopies, solutions, etc)... subject to approval by the professor


### 2) Loop Analysis

- # of Eq. = # of independent loops
- variables → currents (assign a loop current to each independent loop)
- KVL → equations
- current source → constraint eq. (express in terms of variables)

# Last Lecture → Nodal Analysis

## Analysis Procedure

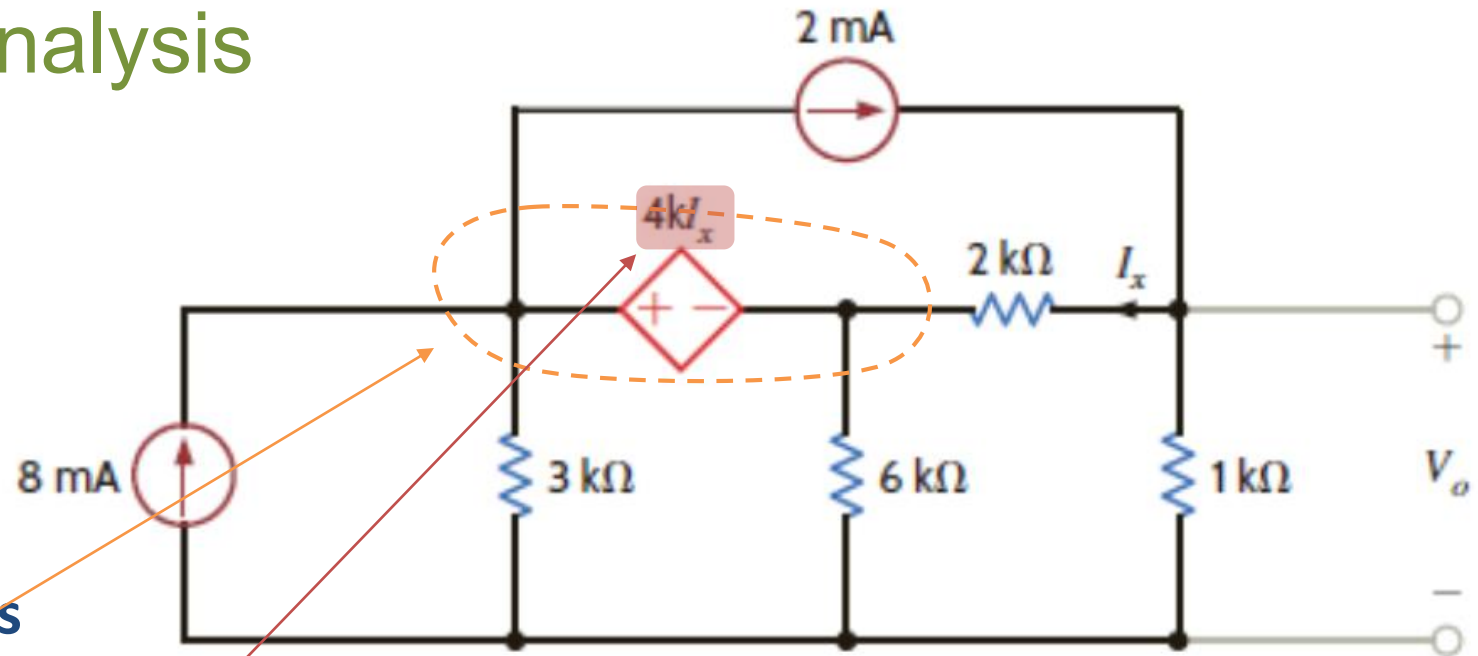- 1) Identify #of nodes
- 2) Select reference node
- 3) Label other node voltages
- 4) Identify branch currents
- 5) Identify **supernode** / **dependent sources**
- 6) Apply KCL to nodes and supernodes
- 7) Write constraint equation - **supernodes**
- 8) Write controlling equation – **dependent sources**
- 9) Solve equation system



$$V_1 - V_2 = 4k \cdot I_x$$

$$I_x = \frac{V_0 - V_2}{2k}$$

# Mesh Analysis

## Alternative # 1

- $B \rightarrow$  # of branches
- $N \rightarrow$  # of nodes
- $B - N + 1 \rightarrow$  # independent simultaneous equations

## Alternative # 2

- $M \rightarrow$  # of independent loops in a planar circuit
- $M \rightarrow$  # independent simultaneous equations



$$B = 8 \quad M = 4$$

$$N = 5$$

$$\# \text{ Eq.} = 4$$

Establish the currents  
around the loops




$$i_A(t) = i_1(t)$$

$$v_1 = V_{R_1} + V_{R_2}$$

$$-v_2 = V_{R_3} + V_{R_4}$$

$$v_2 - v_1 = V_5$$

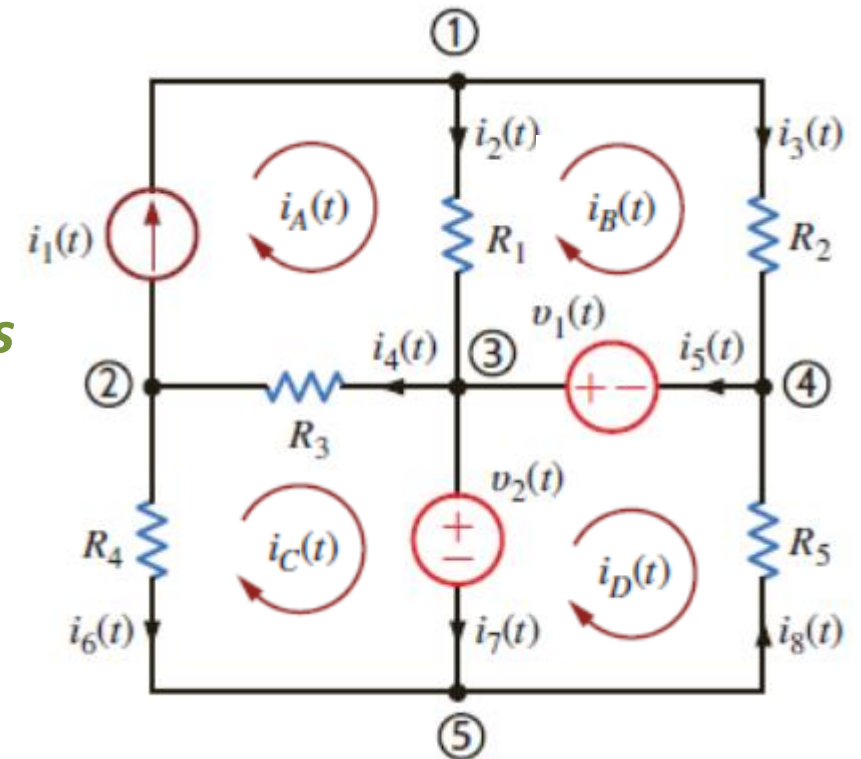


Express voltages in terms  
of currents:  $i_A(t)$ ,  $i_B(t)$ ,  $i_C(t)$ ,  
and  $i_D(t)$

KVLs according to the current around the loop
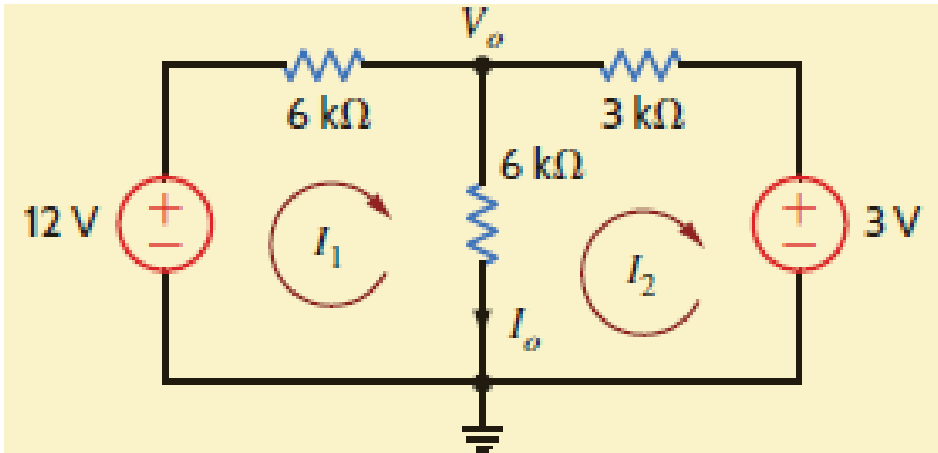
# Loop Analysis → with Independent Voltage Sources

\*\*\*Use passive sign convention with respect the loop currents




$M = 2$   
# Eq. = 2

- KVLs in terms of  $I_1$  and  $I_2$

$$12 = 6k \cdot I_1 + 6k \cdot (I_1 - I_2)$$

$$-3 = 6k \cdot (I_2 - I_1) + 3k \cdot I_2$$

using the outer loop...

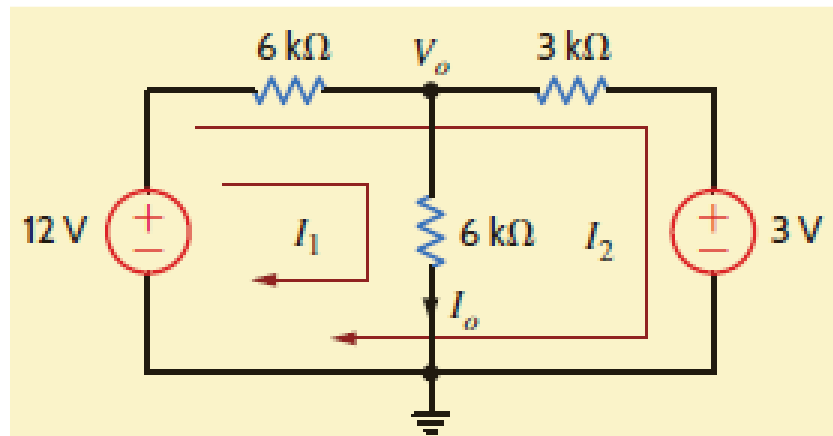


$$I_1 = \frac{1}{25} \text{ mA}$$

$$I_2 = \frac{1}{4} \text{ mA}$$
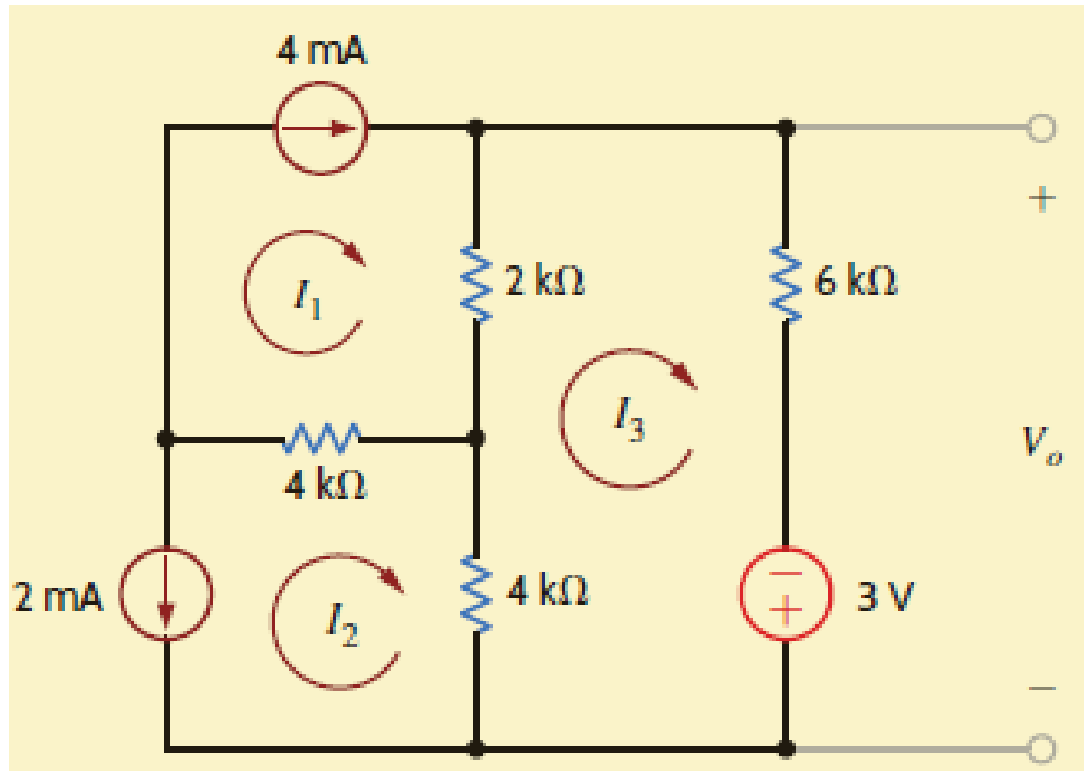
# Loop Analysis → with Independent Current Sources

\*\*\* The current source will determine loop current



$M = 3$   
# Eq. = 3

- Independent CS

$$I_1 = 4mA$$

$$I_2 = -2mA$$


- KVLs in terms of  $I_1$ ,  $I_2$ , and  $I_3$

$$3 = 4k \cdot (I_3 - I_2) + 2k \cdot (I_3 - I_1) + 6k \cdot I_3$$

$$\hookrightarrow I_1 = \frac{1}{4}mA$$
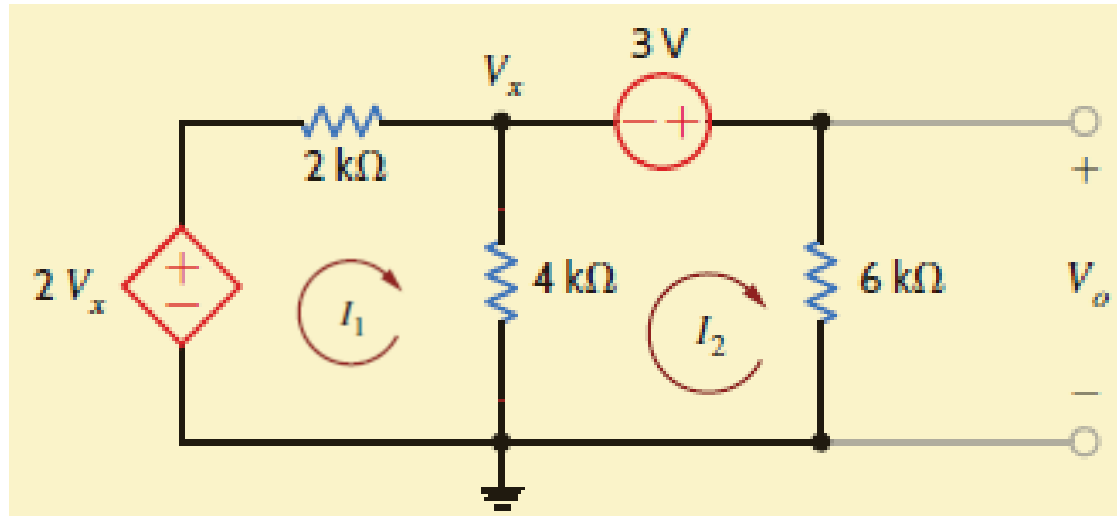
# Loop Analysis → with Dependent Voltage Sources

\*\*\* After the KVLs, write the controlling equation for the dependent sources



$$I_1 = 3 \text{ mA}$$

$$I_2 = \frac{3}{2} \text{ mA}$$

$$V_o = 9 \text{ V}$$

$M = 2$   
# Eq. = 2

- KVLs in terms of  $I_1$  and  $I_2$

$$2V_x = 2k \cdot I_1 + 4k \cdot (I_1 - I_2)$$


$$3 = 6k \cdot I_2 + 4k \cdot (I_2 - I_1)$$

- Controlling Eq.

$$V_x = 4k \cdot [I_1 - I_2]$$

# Loop Analysis → Super-mesh
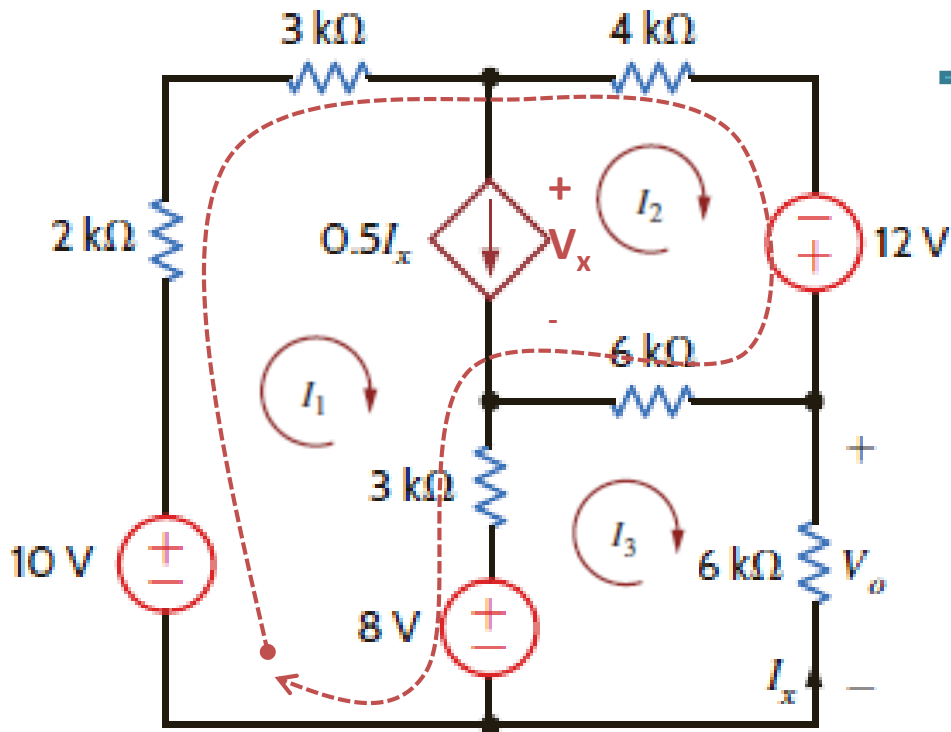
## Learning Assessment – E3.23: Find $V_o$ .



$M = 3$   
# Eq. = 3

- KVLs in terms of  $I_1$ , and  $I_2$

$$10 - 5k \cdot I_1 - V_x - 3k \cdot (I_1 - I_3) - 8 = 0$$

$$12 - 6k \cdot (I_2 - I_3) + V_x - 4k \cdot I_2 = 0$$




- KVLs @ Super-mesh

$$10 - 5k \cdot I_1 - 4k \cdot I_2 + 12 - 6k \cdot (I_2 - I_3) - 3k \cdot (I_1 - I_3) - 8 = 0$$

# Loop Analysis → Super-mesh
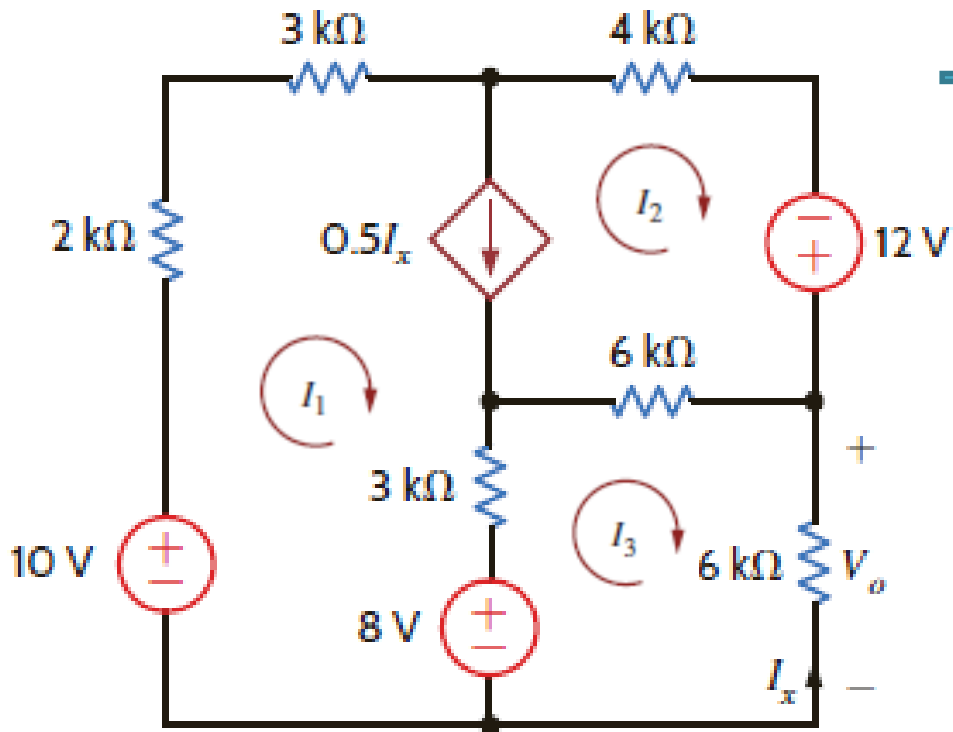
## Learning Assessment – E3.23: Find $V_o$ .



$M = 3$   
# Eq. = 3

- KVLs in terms of  $I_1, I_2$  and  $I_3$

$$14 = 8k \cdot I_1 + 10k \cdot I_2 - 9k \cdot I_3$$

$$8 = -3k \cdot I_1 - 6k \cdot I_2 + 15k \cdot I_3$$

- Controlling Eq.

$$I_x = -I_3$$

- Dependent CS

$$I_1 - I_2 = \frac{1}{2} I_x$$

$$I_1 = \frac{10}{9} \text{ mA}$$

$$I_3 = \frac{3}{2} \text{ mA}$$

$$V_o = 9\text{V}$$