

Last Lecture → Superposition

In any linear circuit containing multiple independent sources, the current or voltage at any point in the network may be calculated as the algebraic sum of the individual contributions of each source acting alone.


$$i_1(t) = i_1'(t) + i_1''(t)$$

Analysis:


Each independent source can be applied independently with the remaining source turned off:

- *Turn off a voltage source* → short circuit
- *Turn off a current source* → open circuit

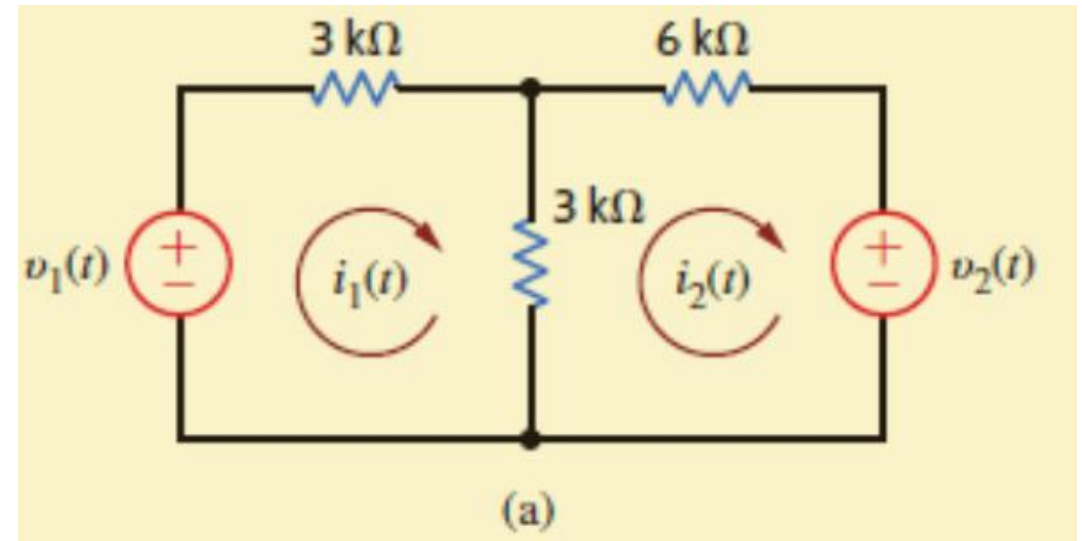
The final solution is the algebraic sum of the independent results!.



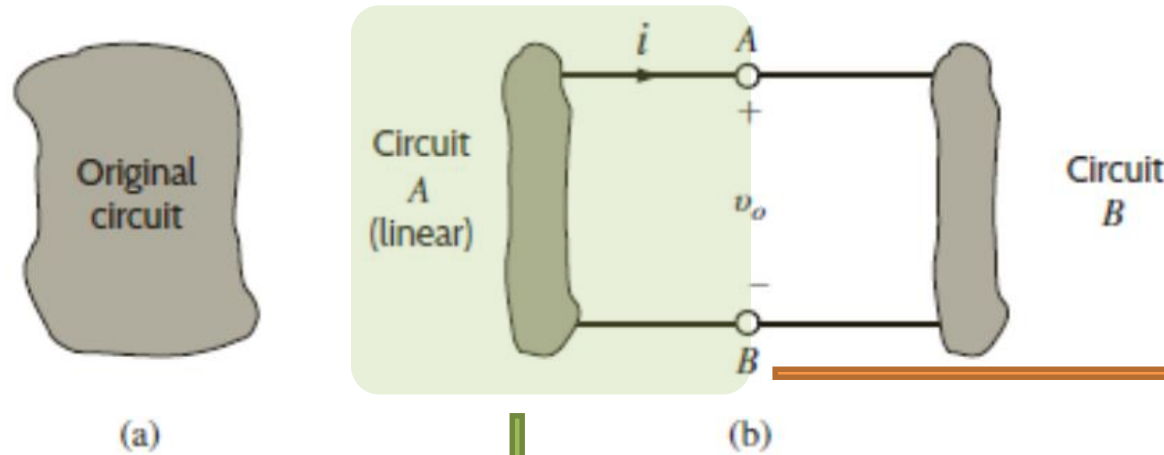Last Lecture → Thevenin's & Norton's Theorem




- Thevenin

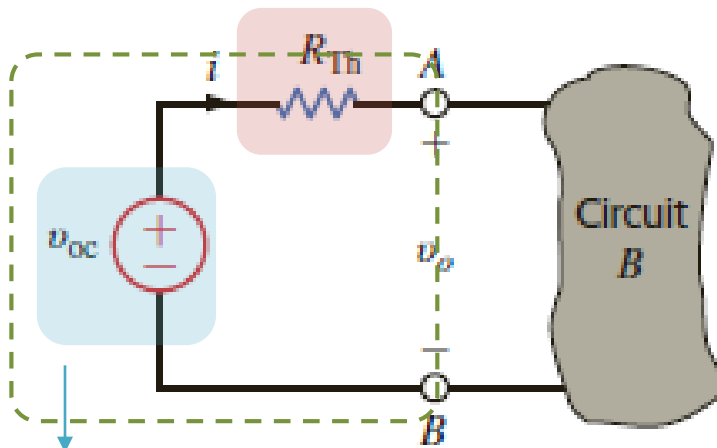

V_{oc} : Open circuit voltage from circuit A measured at A-B

- Norton

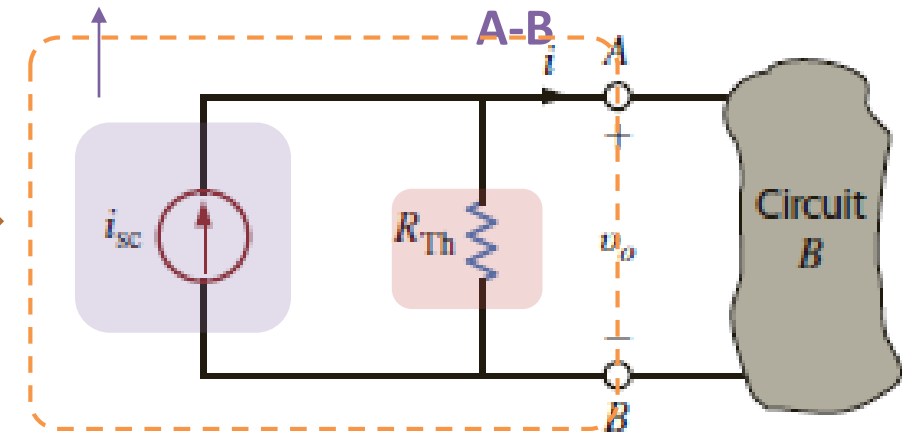I_{sc} : Short circuit current from circuit A measured at




R_{th} : Equivalent resistance looking back into circuit A from A-B with all independent sources in circuit A made zero

$$v_{oc} = R_{Th} \cdot i_{sc}$$

Learning Assessment → E5.6

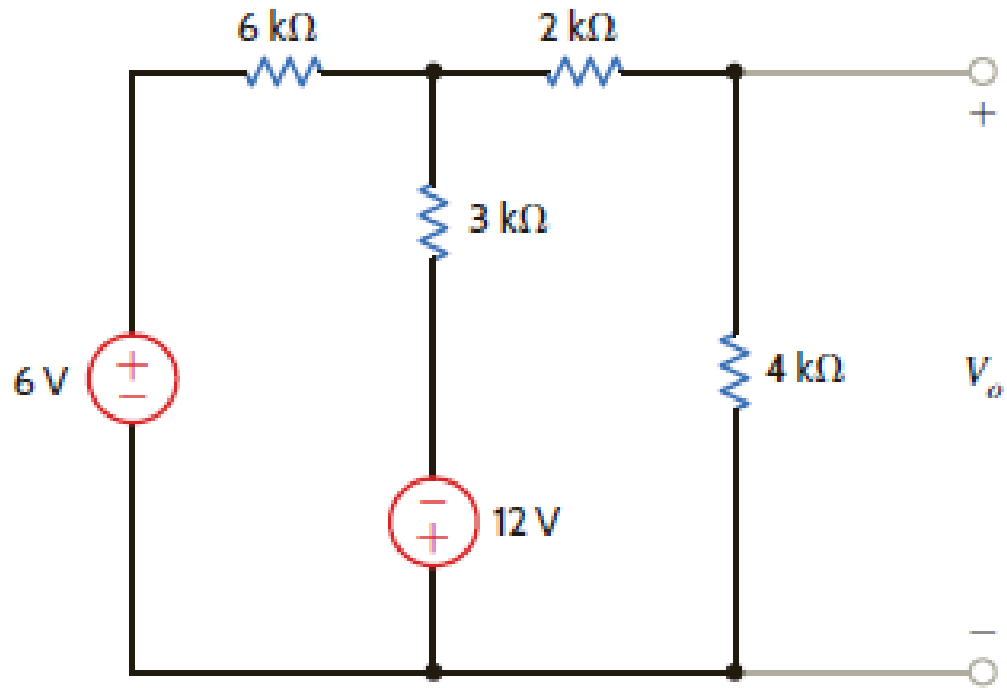Use Thevenin's Theorem to find V_o in the network provided.



Thevenin and Norton Equivalent Circuits

1) Independent Sources Only

- Find either V_{oc} or I_{sc}
- R_{Th} can be extrapolated directly from the network

2) Dependent Sources Only

- The equivalent circuit is R_{Th} only
- Find R_{th} through ohms law by placing an voltage/current source and measuring the current/voltage

3) Independent and Dependent Sources



- Must calculate both the V_{oc} and I_{sc} to calculate R_{Th} .
- Must not split the dependent source an its controlling variable

Thevenin's Norton's Theorem → Dependent Sources Only

The Thevenin /Norton equivalent of a network containing only dependent sources is R_{th} !

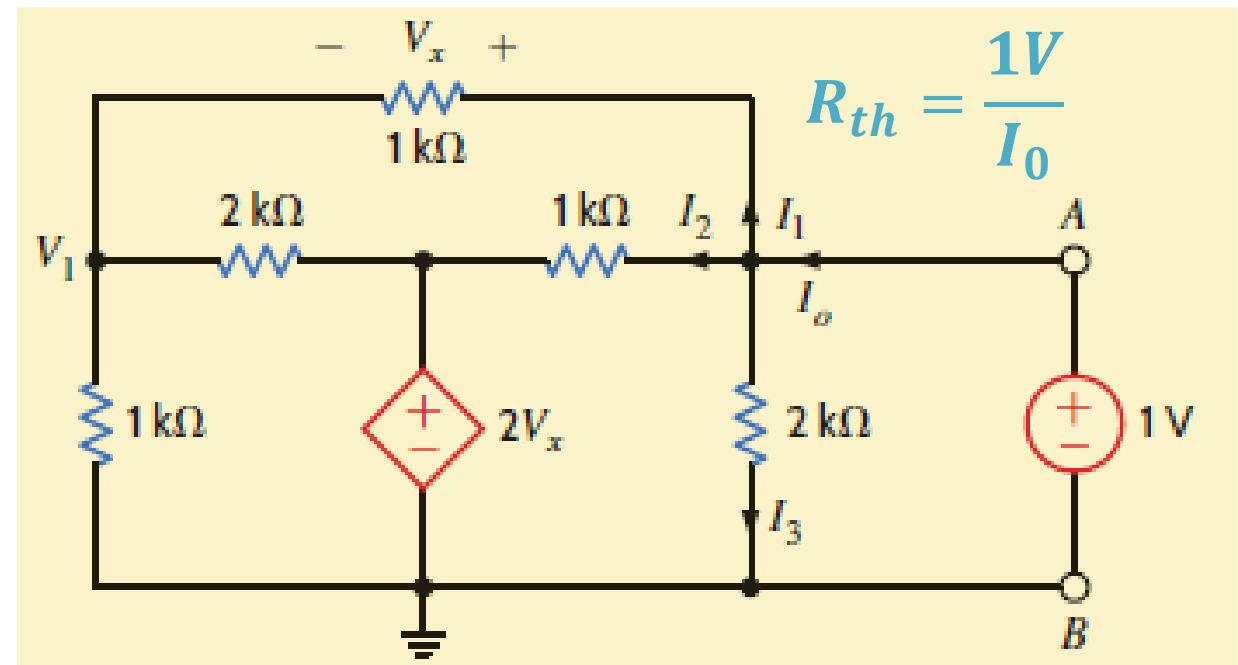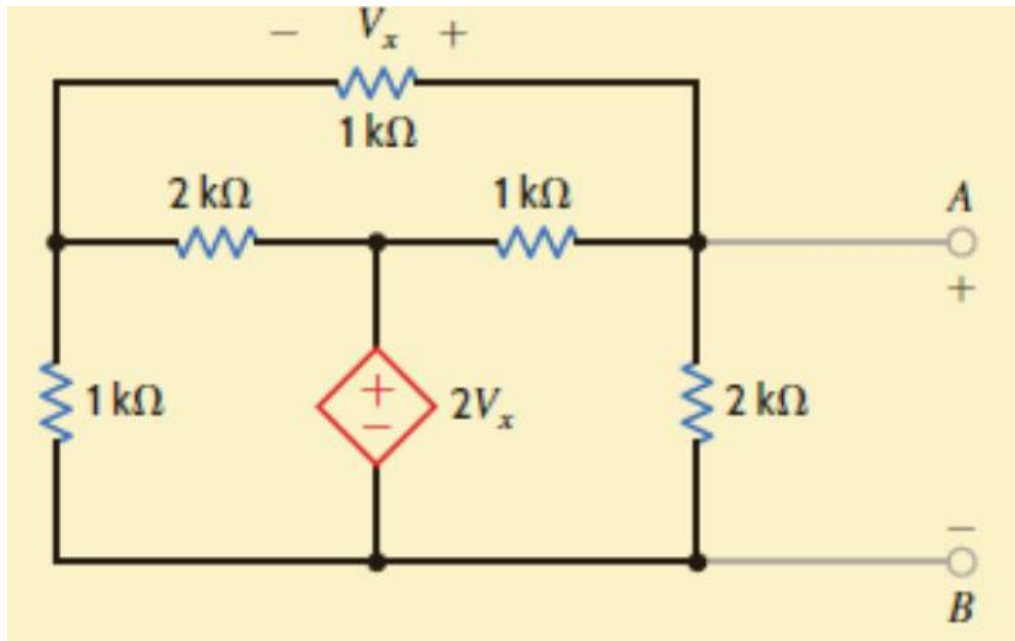Example 5.8:

Determine the Thevenin equivalent of the network provided at terminals A-B.




Thevenin's Norton's Theorem → Independent & Dep. Sources


- *Must calculate both the V_{OC} and I_{SC} to calculate R_{TH} .*
- *Must not split the dependent source an its controlling variable*

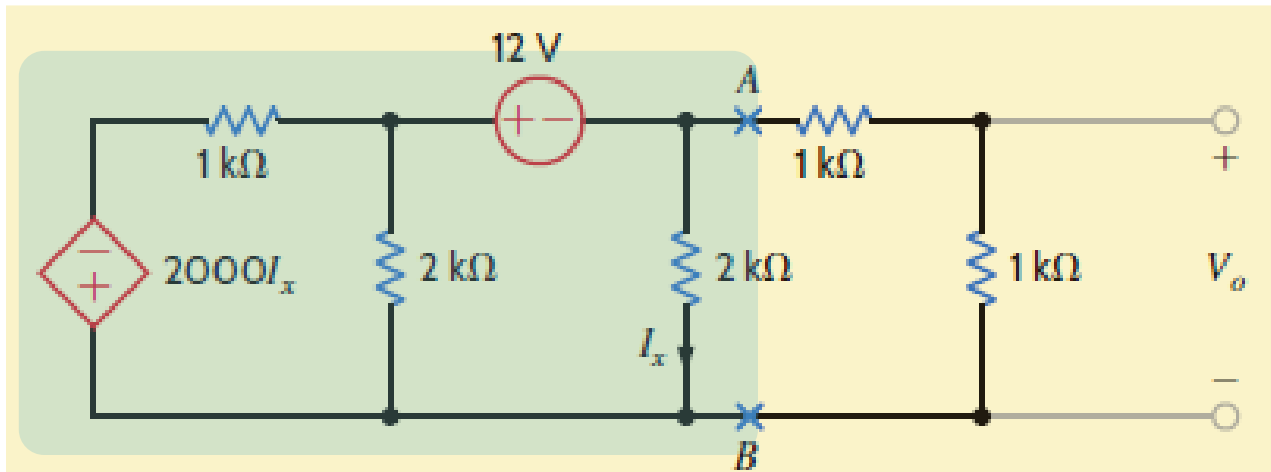Example 5.10:

Use Thevenin's theorem to find V_o in the network provided..


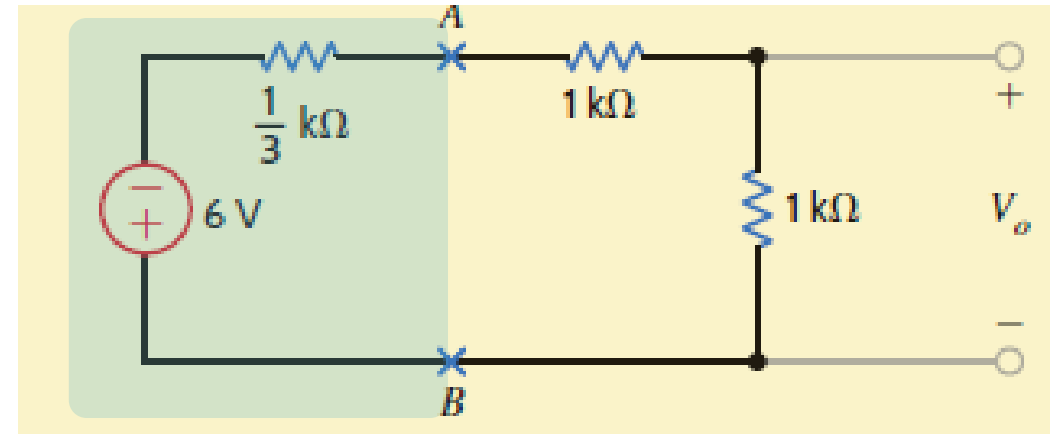
$$\left. \begin{aligned} I_{SC} &= -18 \text{ mA} \\ V_{OC} &= -6 \text{ V} \\ \therefore R_{th} &= \frac{1}{3} \text{ k}\Omega \end{aligned} \right\} V_o = -\frac{18}{7} \text{ V}$$



Learning Assessment → E5.13

Find the Thevenin equivalent of the network at terminals A-B.

