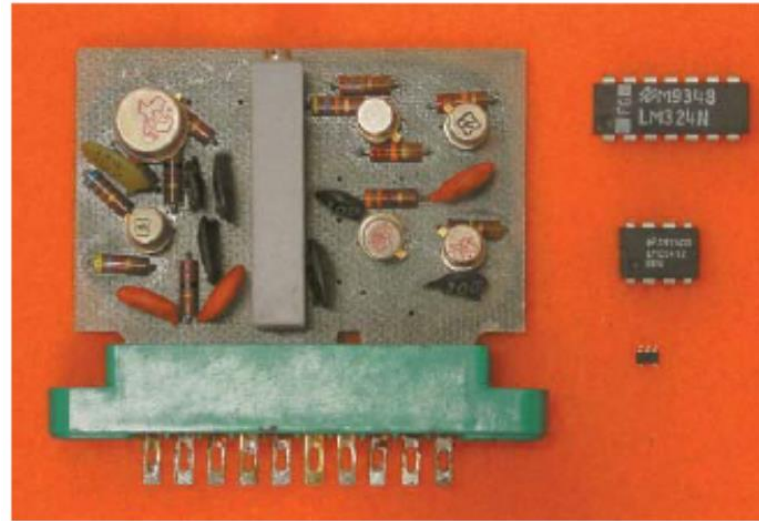



# Operational Amplifiers → Chapter #4

## Op-amps

- Amplifier Model
- Amplifier Based Circuit Analysis



(a)

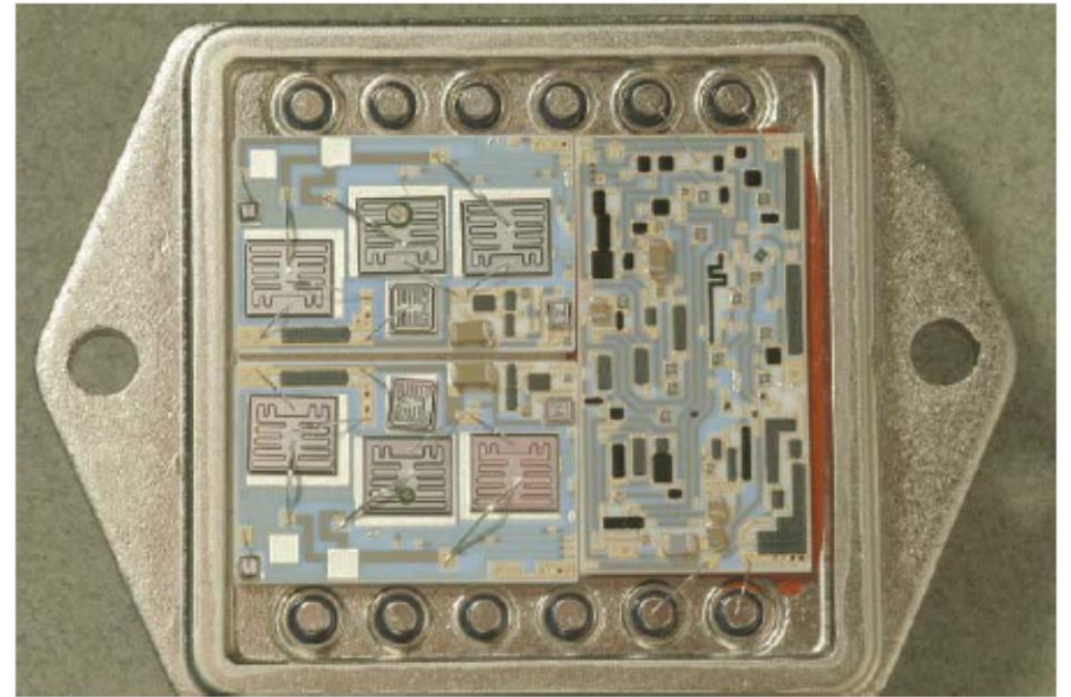



(b)

### Op-Amp

- *Is the single most important integrated circuit for analog circuit design*
- *Is a versatile interconnection of transistors and resistors*
- *Is used in a wide range of applications, from engine control systems to cellular phones*
- *Was designed to perform mathematical operations*

# Op-Amp Model

- LM324 – Dip Package - Pinout**

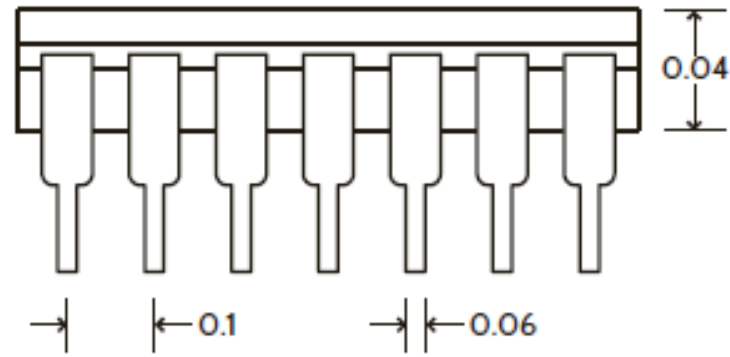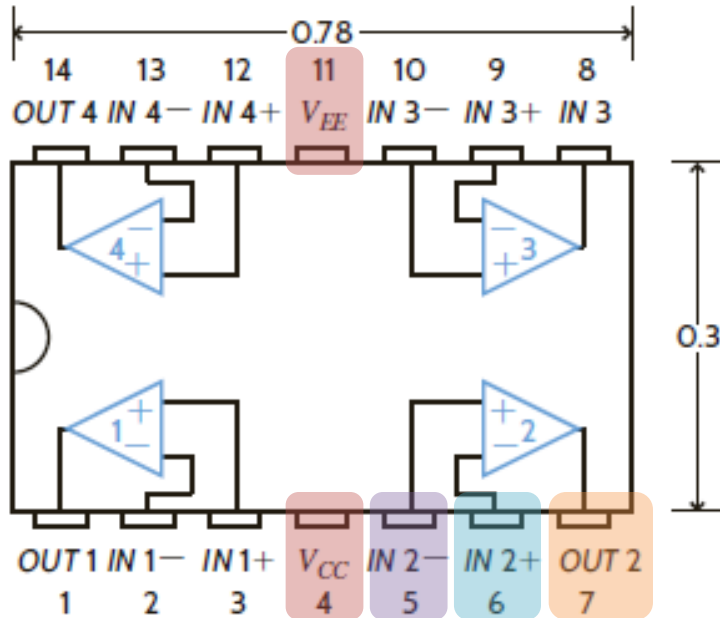


(a)   
 Negative / Positive Supply   
 Inverting Input   
 Non-inverting Input   
 Output

(b)   

$$V_o = A_o(IN_+ - IN_-)$$


Gain of op-amp ~ (10,000 – 1,000,000)

- Circuit Model**

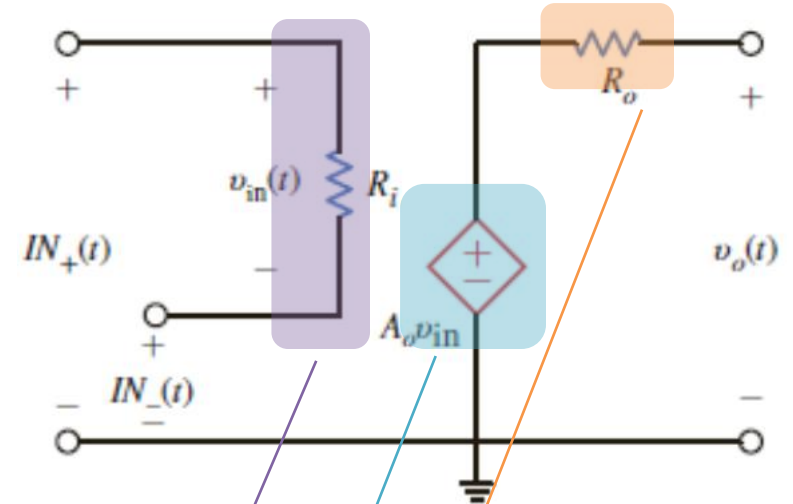


Models I-V relationship at output   
 Models op-amp gain   
 Models I-V relationship at input

# Op-Amp Circuit

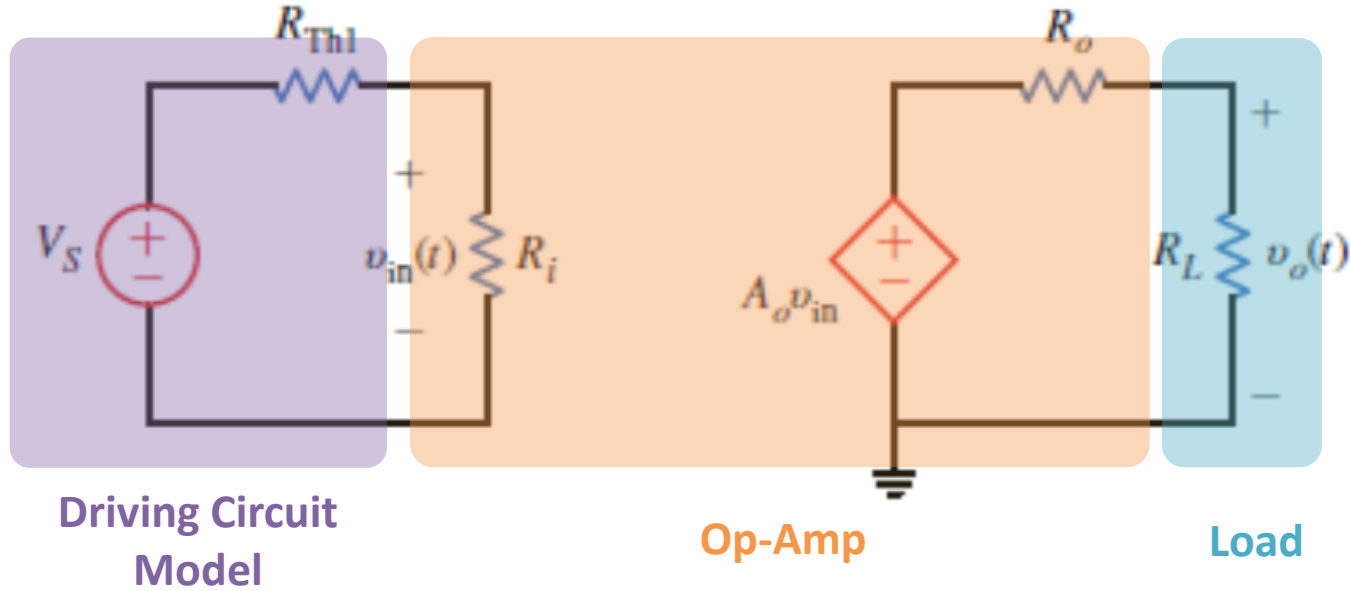

$$\frac{V_o}{V_s} = \left[ \frac{R_i}{R_i + R_{TH1}} \right] [A_o] \left[ \frac{R_L}{R_L + R_o} \right]$$

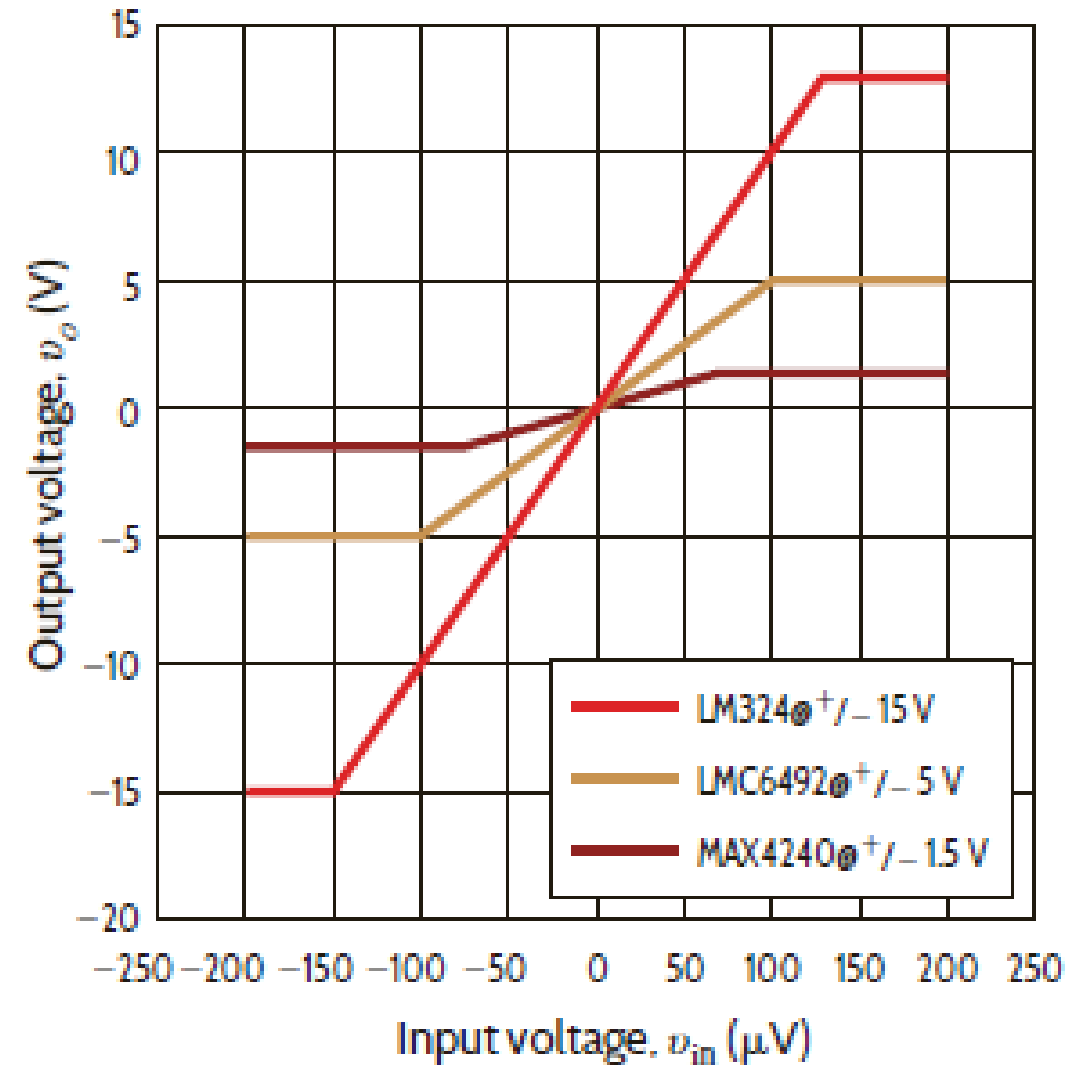for  $R_i \rightarrow \infty, R_o \rightarrow 0$        $\frac{V_o}{V_s} = A_o$



## Example 4.1


The input and output signals for an op-amp circuit are shown in figure below.

Determine:

- if the op-amp circuit is linear, and
- the circuit's gain


Op-amp saturates, therefore not linear
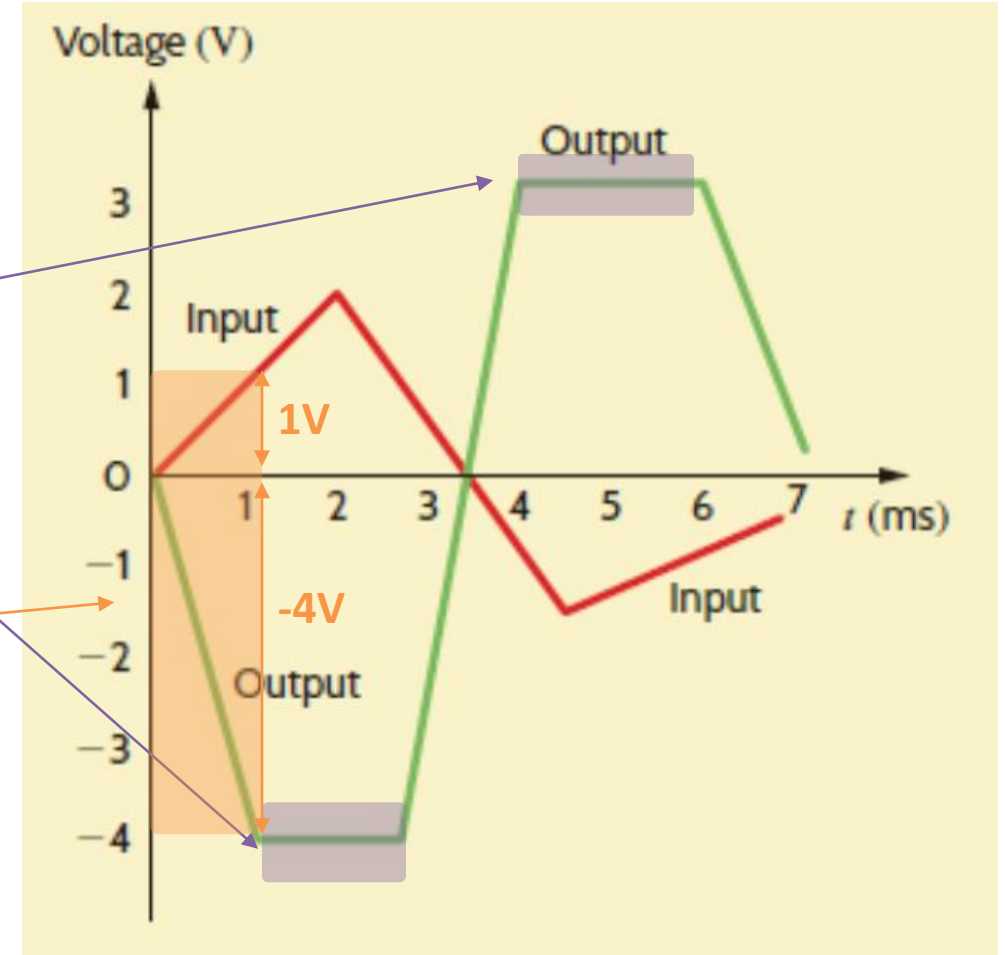
$$\frac{V_o}{V_s} = \frac{-4}{1} = -4V/V$$


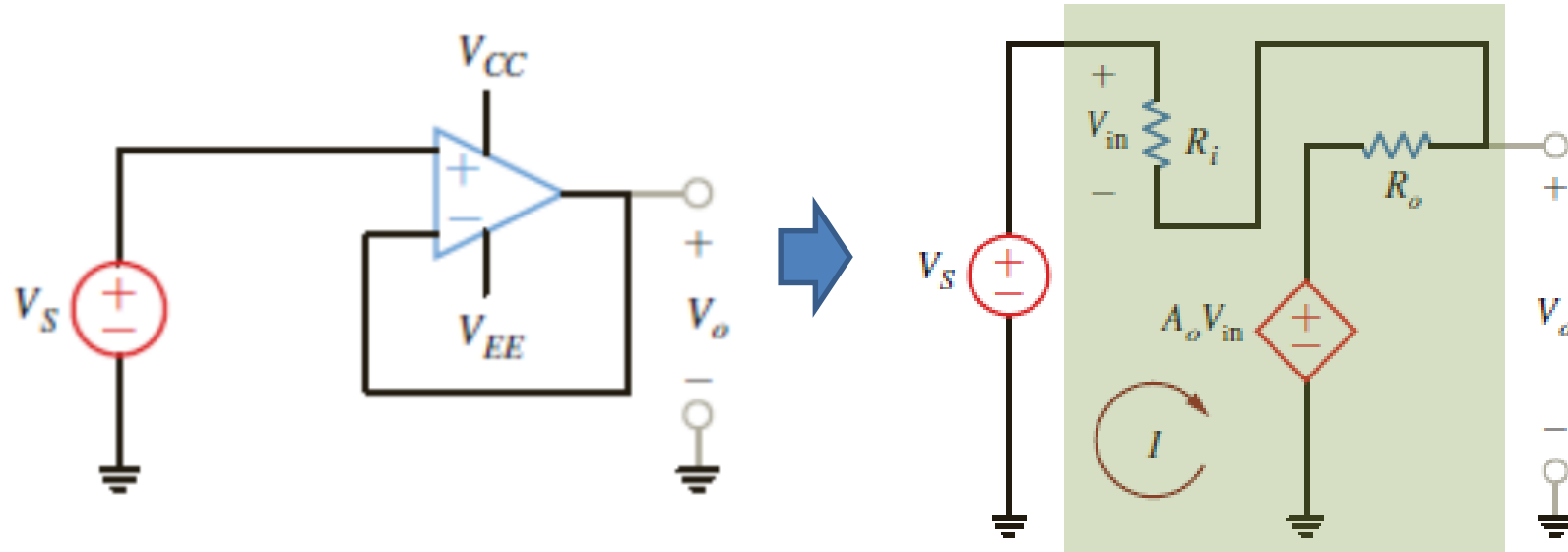
# Unity Gain Buffer

Using the op-amp model find the expression for the transfer function  $V_o/V_s$ .



## Op-Amp Ideal Behavior

- $R_i = \infty$
- $A_0 = \infty$
- $R_o = 0$

$$i_{R_i} = \frac{V_{in}}{R_i} = 0$$

$$\therefore i_+ = i_- = 0$$

$$\frac{V_o}{V_s} = \frac{1}{1 + \frac{1}{A_0 + \frac{R_o}{R_i}}} \approx \frac{1}{1 + \frac{1}{A_0}} \approx 1$$

$R_i = \infty, R_o = 0$

$A_0 = \infty$

$$V_o = A_0(V_+ - V_-)$$

$$\hookrightarrow (V_+ - V_-) = \frac{V_o}{A_0} = 0 \quad \therefore V_+ = V_-$$