
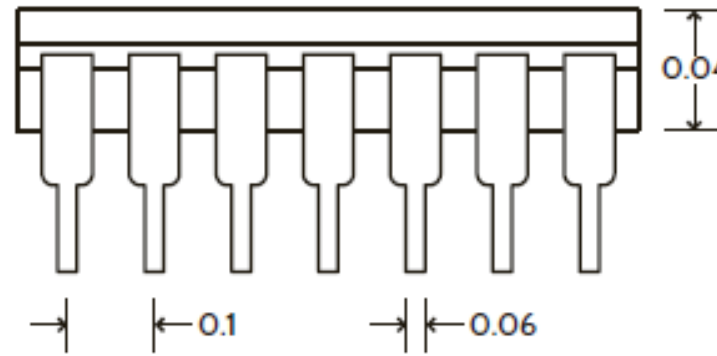


Last Lecture → Op-Amp

• LM324 – Dip Package - Pinout

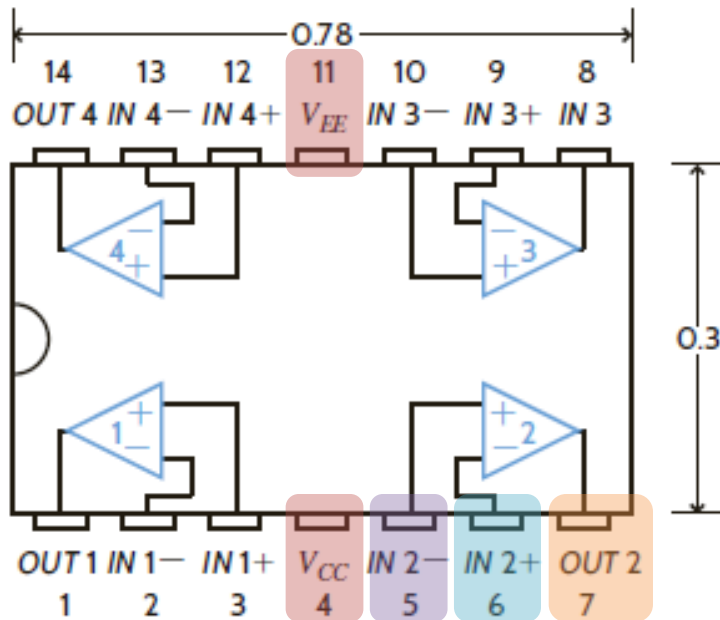


(a)
 Negative / Positive Supply
 Inverting Input
 Non-inverting Input
 Output

$$V_o = A_o(IN_+ - IN_-)$$

Gain of op-amp ~ (10,000 – 1,000,000)

• Circuit Model


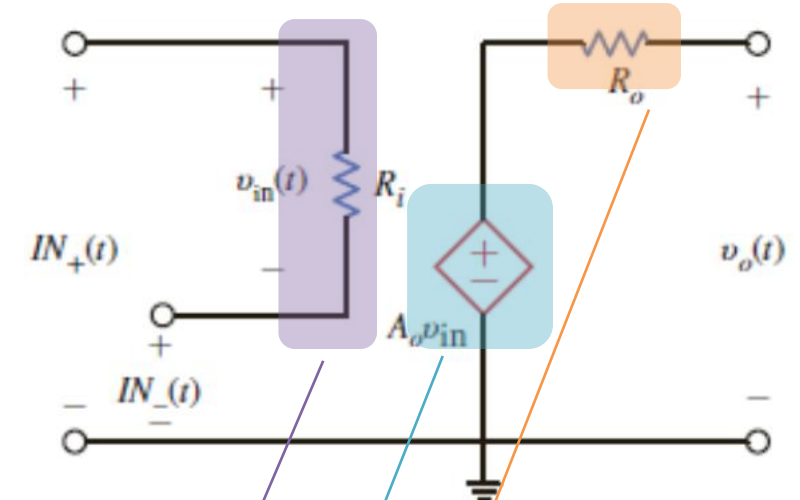


Models I-V relationship at output
 Models op-amp gain
 Models I-V relationship at input

Operational Amplifier

- Internal Circuit Diagram**


- Symbol / Equivalent Circuit**

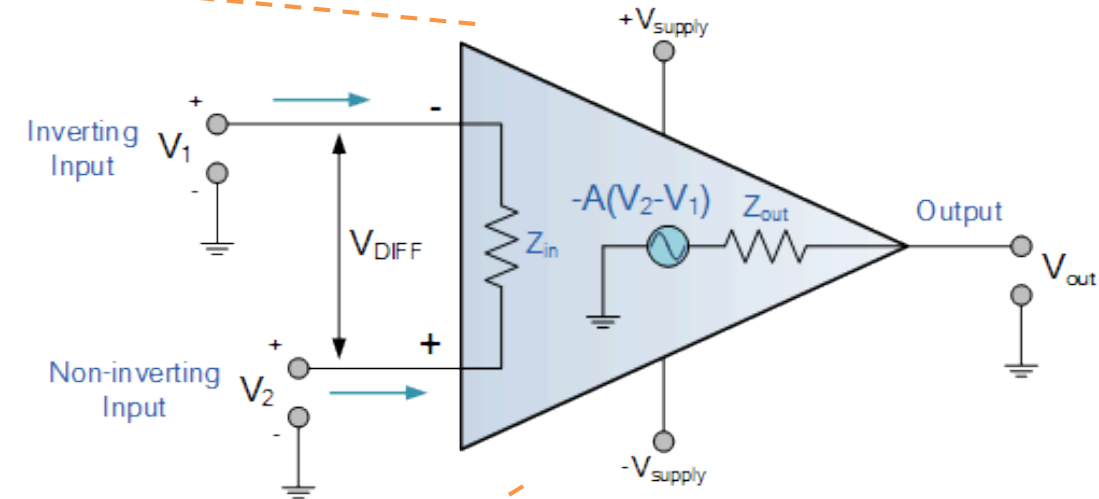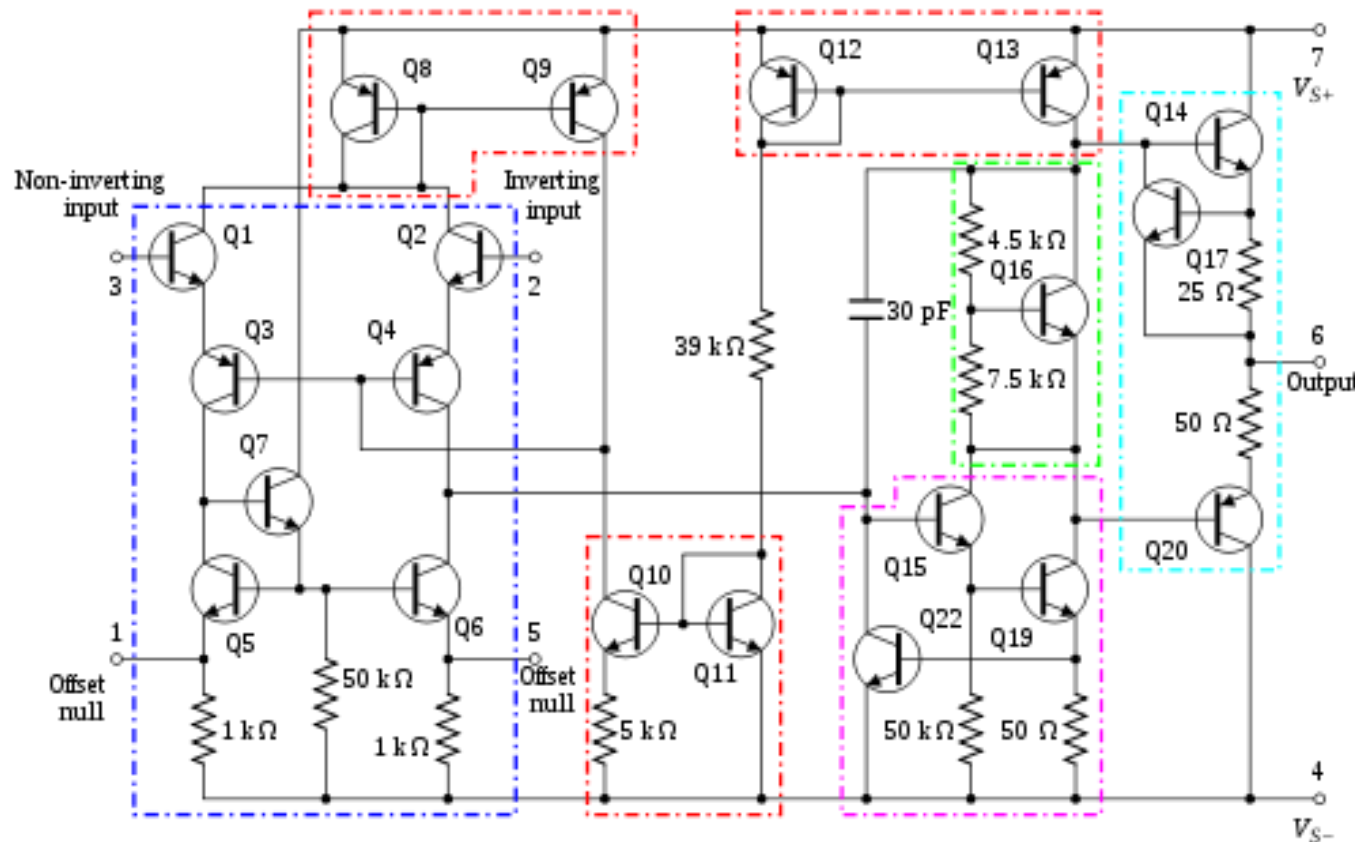

$$V_0 = A_0(IN_+ - IN_-)$$

Unity Gain Buffer

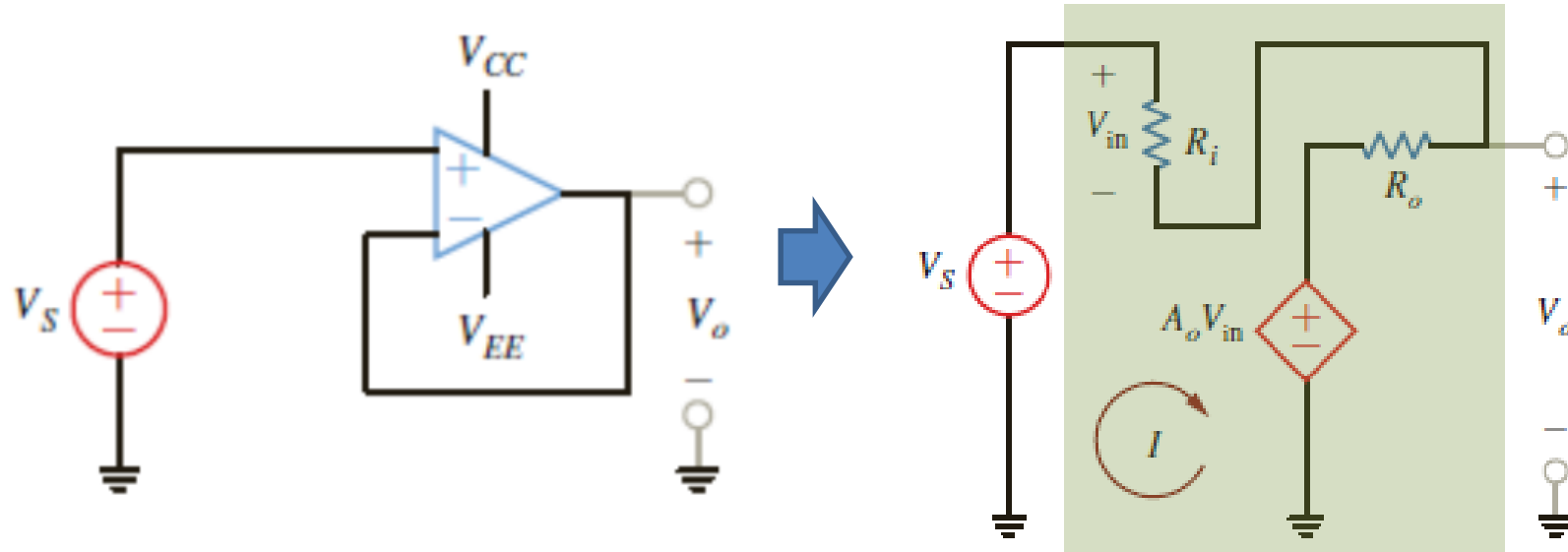Using the op-amp model find the expression for the transfer function V_o/V_s .



Op-Amp Ideal Behavior

- $R_i = \infty$
- $A_o = \infty$
- $R_o = 0$

$$i_{R_i} = \frac{V_{in}}{R_i} = 0$$

$$\therefore i_+ = i_- = 0$$

$$\frac{V_o}{V_s} = \frac{1}{1 + \frac{1}{A_o + \frac{R_o}{R_i}}} \approx \frac{1}{1 + \frac{1}{A_o}} \approx 1$$

$R_i = \infty, R_o = 0$

$A_o = \infty$

$$V_o = A_o(V_+ - V_-)$$

$$\hookrightarrow (V_+ - V_-) = \frac{V_o}{A_o} = 0 \quad \therefore V_+ = V_-$$

Ideal Op-Amp Circuit Analysis

- Establish ideal op-amp conditions on the circuit schematic
 - 1) $i_+ = i_- = 0$
 - 2) $v_+ = v_-$
- Write nodal equations at the op-amp input terminals
- Solve for the input/output relationship


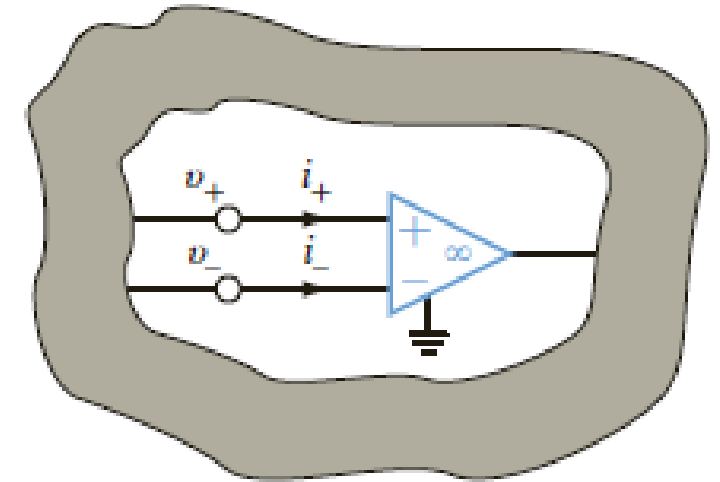


Figure 4.9

Ideal model for an operational amplifier. Model parameters:
 $i_+ = i_- = 0$, $v_+ = v_-$.

Unity Gain Buffer - Revisited

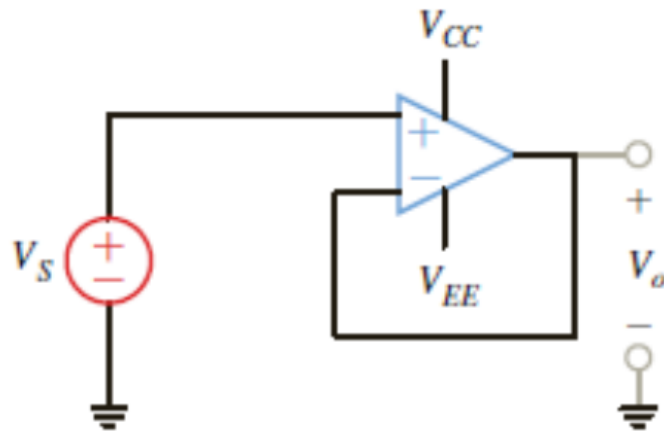

MODEL ASSUMPTION

$$A_o \rightarrow \infty$$

$$R_i \rightarrow \infty$$

TERMINAL RESULT



input voltage $\rightarrow 0$ V

input current $\rightarrow 0$ A

Ideal Op-Amp Circuit Analysis

- Establish ideal op-amp conditions on the circuit schematic
 - 1) $i_+ = i_- = 0$
 - 2) $v_+ = v_-$
- Write nodal equations at the op-amp input terminals
- Solve for the input/output relationship

Unity Gain Buffer - Revisited

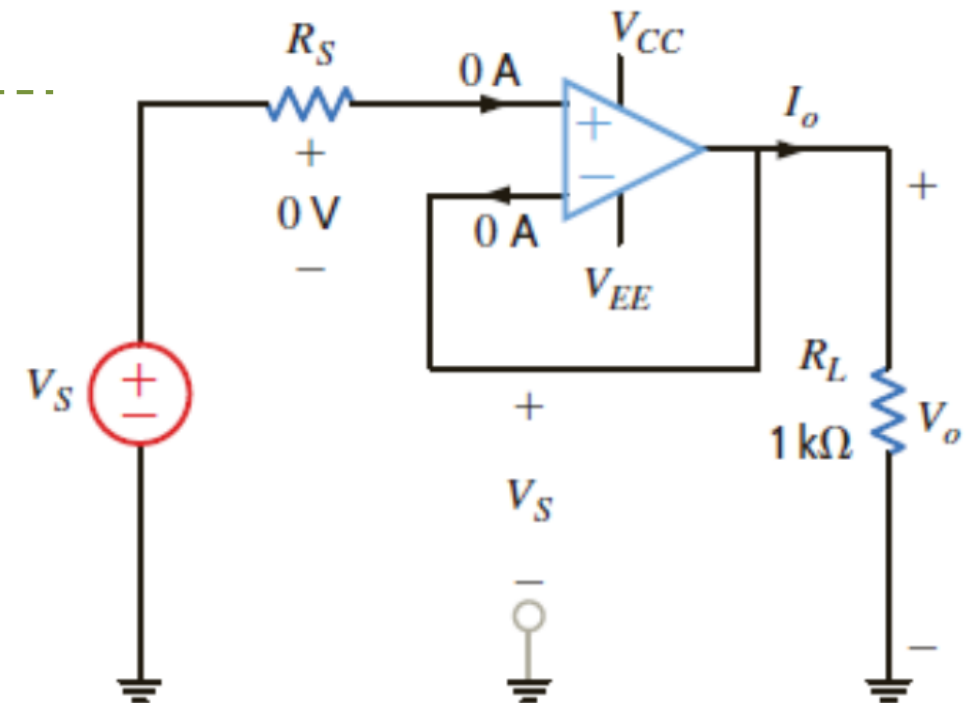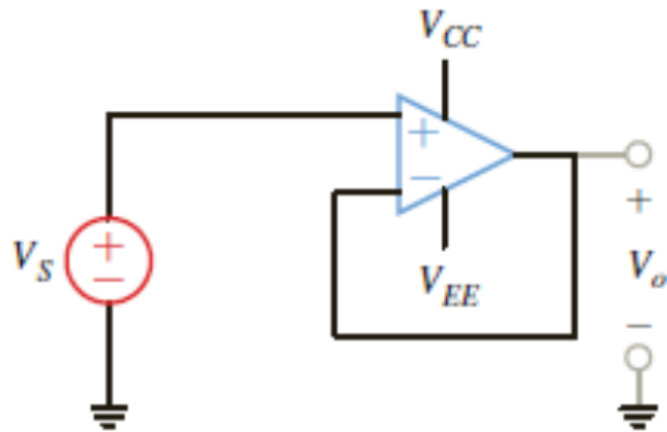


Exam #3 → Tuesday, March 12

Concepts Chapter #5:

- 1) Superposition
- 2) Thevenin's & Norton's Theorem
- 3) Source Transformation
- 4) Maximum Power Transfer

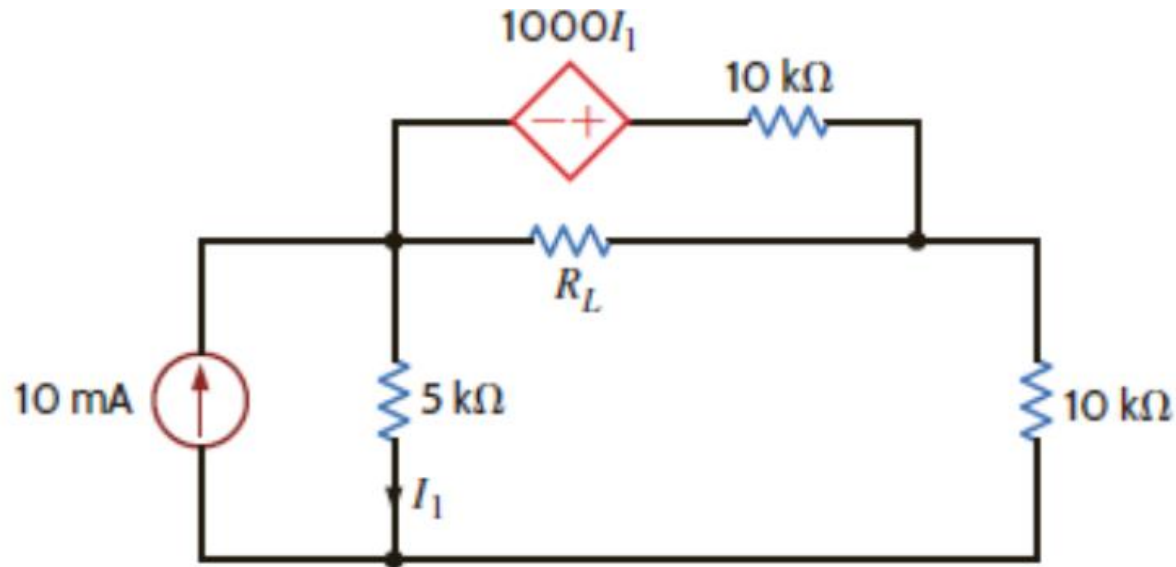
Problem → P5.124

For the given network find the value of R_L for maximum power transfer and the maximum power that can be transferred to this load.



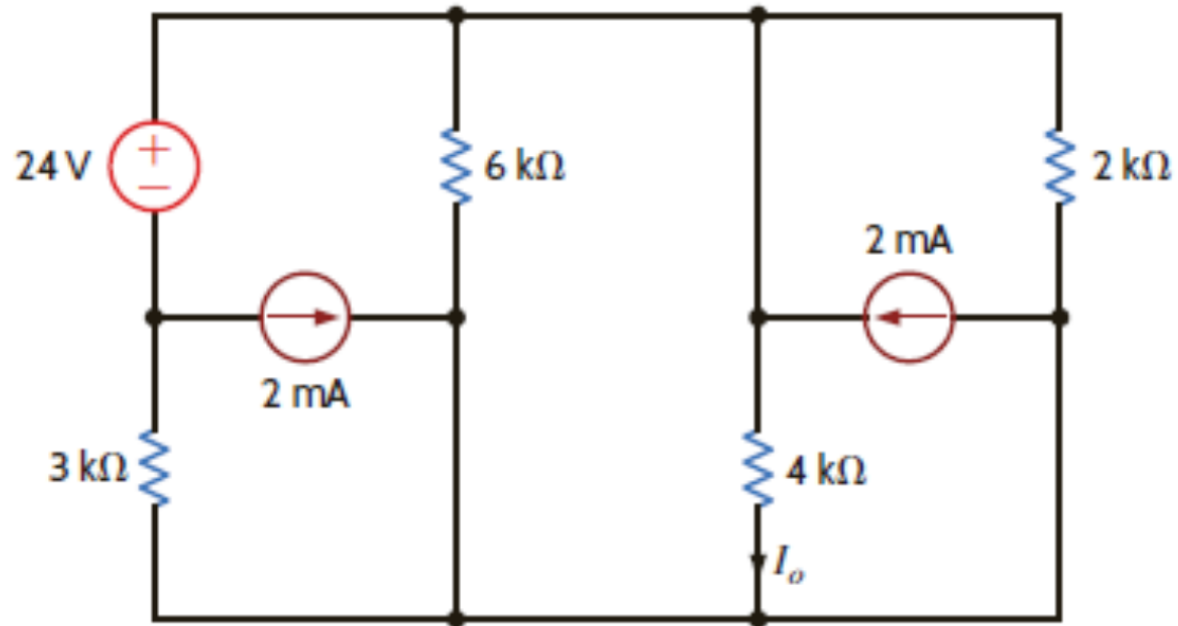Problem → P5.106

Using source transformation, find I_o in the circuit provided.



Problem → P5.87

Find the Thevenin equivalent circuit of the provided network at terminals A-B.

