

Exam #4 → ~~Thursday, March 21~~

→ Tuesday, March 26
→ Thursday, March 28

Concepts Chapter #4 & #6:

1) Op-Amp

- Model
- Circuit Analysis
 - Ideal behavior
 - Non-ideal behavior


2) Capacitor / Inductor

- Model / Behavior
- DC Analysis
- Series / Parallel Combination

*** “Bate”: bring your own set of equations (no problems, photocopies, solutions, etc)... subject to approval by the professor


Last Lecture → Op-Amp Amplifiers

- Unity – Gain Amp.

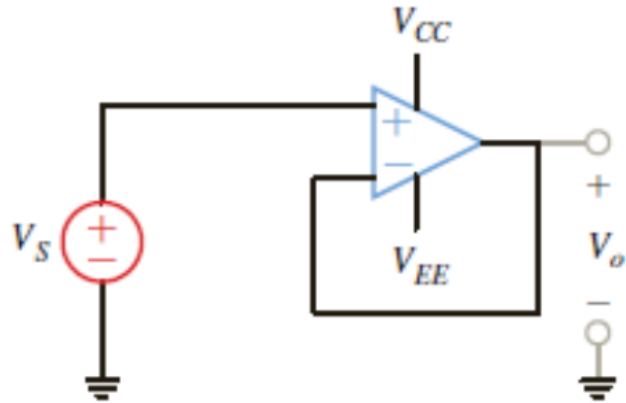


$$\frac{V_o}{V_s} \approx 1$$

- Non-Inverting Amp.

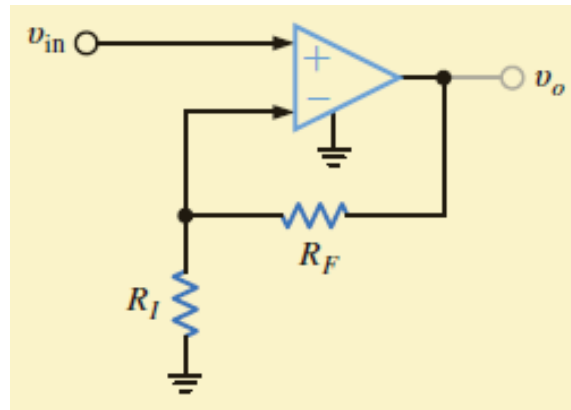

$$\frac{V_o}{V_s} \approx 1 + \frac{R_F}{R_I}$$


- Inverting Amp

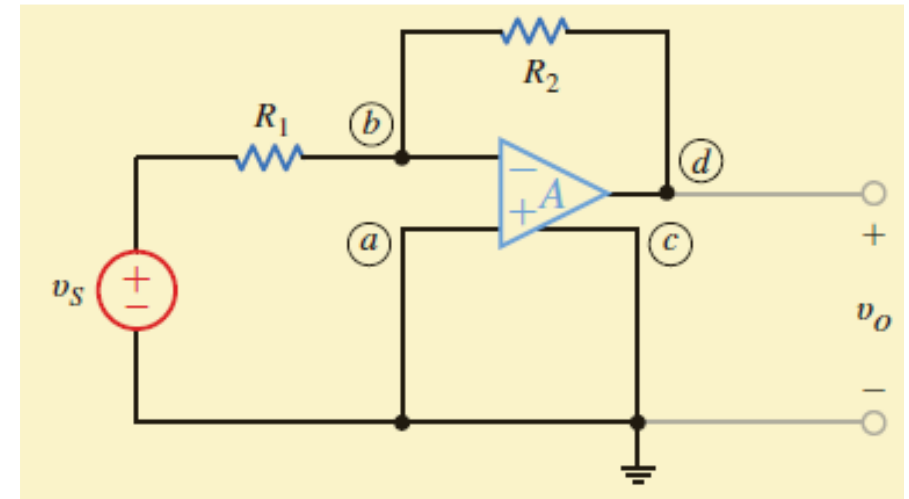

$$\frac{V_o}{V_s} \approx -\frac{R_2}{R_1}$$

Last Lecture → Capacitor

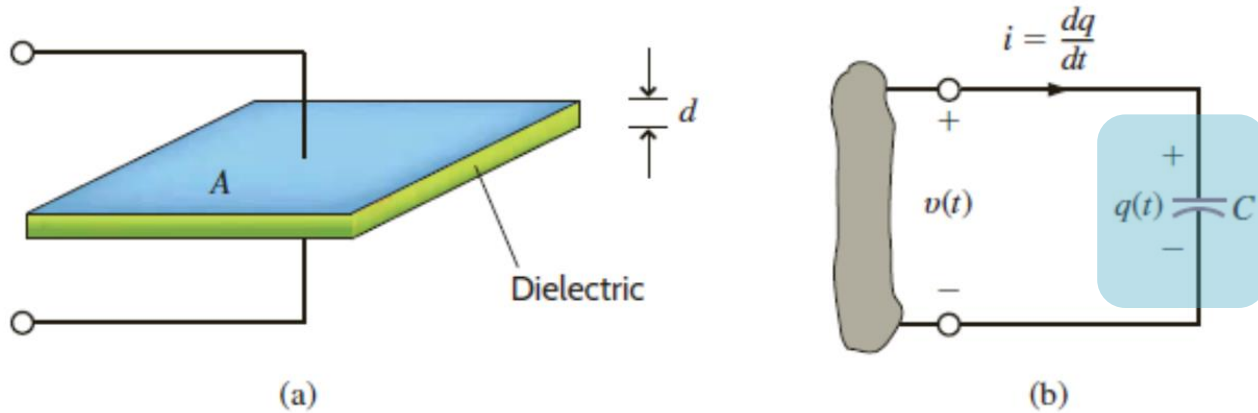... a circuit element that consists of two conducting surfaces separated by dielectric material



Simplified Capacitor

Symbol

Capacitance (C) → $C = \frac{\epsilon_0 A}{d}$

↓

Unit → farads (F) = coulombs per volts

ϵ_0 ← permittivity of free space

Typical Capacitors



$$q = C \cdot v \quad i = C \cdot \frac{dv}{dt}$$

$$v(t) = v(t_0) + \frac{1}{C} \cdot \int_{t_0}^t i(x) dx$$

$$p(t) = C \cdot v(t) \frac{dv(t)}{dt}$$

$$w_c(t) = \frac{1}{2} C \cdot v(t)^2$$

Example 6.1

If the charge accumulated on two parallel conductors charge to 12V is 600 pC, what is the capacitance of the parallel conductors?

Example 6.1

If the charge accumulated on two parallel conductors charge to 12V is 600 pC, what is the capacitance of the parallel conductors?

$$v = 12V$$

$$q = 600 \text{ pC}$$


$$q = C \cdot v$$



$$C = \frac{q}{v} = \frac{600 \text{ p}}{12} = 50 \text{ pF}$$

Example 6.2

If voltage across a 5- μF capacitor has the waveform shown below, determine the current waveform?

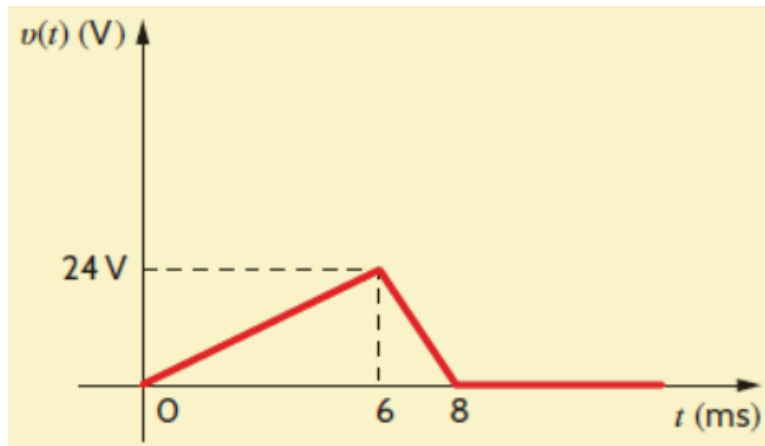

Example 6.1

If the charge accumulated on two parallel conductors charge to 12V is 600 pC, what is the capacitance of the parallel conductors?

$$v = 12V$$

$$q = 600 \text{ pC}$$


$$q = C \cdot v$$




$$C = \frac{q}{v} = \frac{600 \text{ p}}{12} = 50 \text{ pF}$$

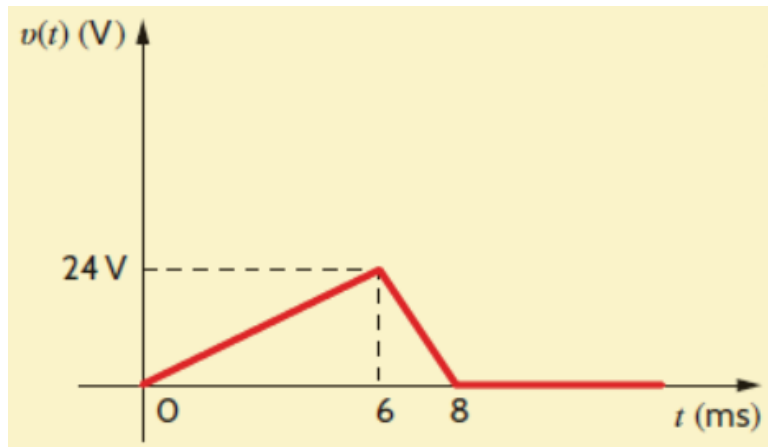Example 6.2

If voltage across a 5- μF capacitor has the waveform shown below, determine the current waveform?



$$i = C \cdot \frac{dv}{dt} = ?$$

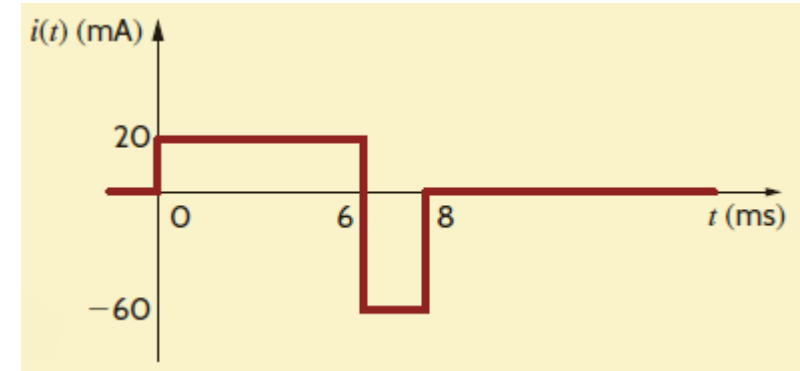


$$v(t) = 4k \cdot t \rightarrow t = [0: 6]$$

$$24 - 12k \cdot (t - 6m) \rightarrow t = [6: 8]$$

$$0 \rightarrow t = [8: \infty]$$


Learning Assessment E6.2-E6.3

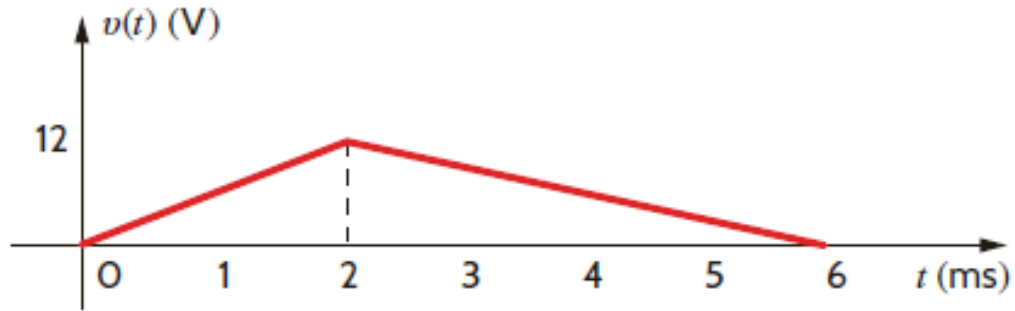The voltage across a 2- μF capacitor is provided below. Determine the waveforms for the current, power, and energy and compute the energy stored in the electric field of the capacitor at $t=2\text{ms}$.



Learning Assessment E6.2-E6.3

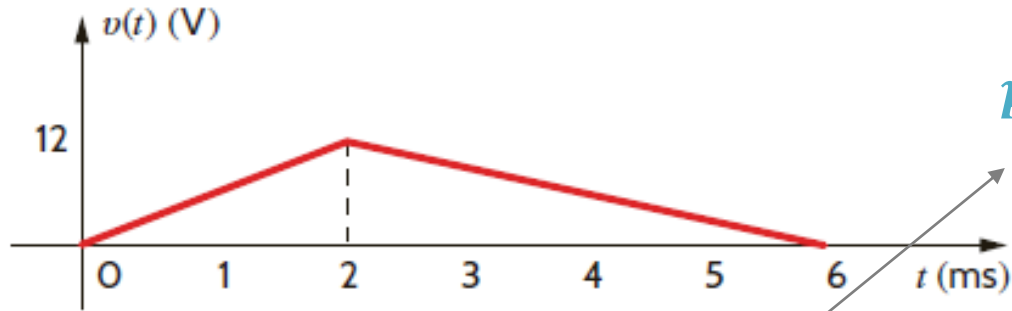The voltage across a 2- μ F capacitor is provided below. Determine the waveforms for the current, power, and energy and compute the energy stored in the electric field of the capacitor at $t=2$ ms.



$$p(t) = C \cdot v(t) \frac{dv(t)}{dt} =$$

$$w_c(t) = \frac{1}{2} C \cdot v(t)^2 =$$


$$v(t) =$$

$$i = C \cdot \frac{dv}{dt} =$$

$$w_c(t = 2m) =$$

Learning Assessment E6.2-E6.3

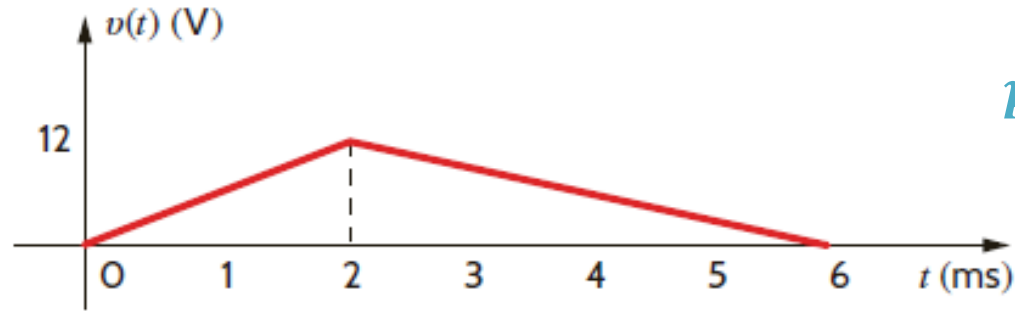The voltage across a 2- μ F capacitor is provided below. Determine the waveforms for the current, power, and energy and compute the energy stored in the electric field of the capacitor at $t=2$ ms.



$$p(t) = C \cdot v(t) \frac{dv(t)}{dt} = 72 \cdot t \text{ W} \rightarrow t = [0:2]$$

$$-72 + 18 \cdot (t - 2\text{m}) \text{ W} \rightarrow t = [2:6]$$

$$v(t) = 6k \cdot t \rightarrow t = [0:2]$$


$$12 - 3k \cdot (t - 2\text{m}) \rightarrow t = [2:6]$$

$$i = C \cdot \frac{dv}{dt} = 12 \text{ mA} \rightarrow t = [0:2]$$

$$-6 \text{ mA} \rightarrow t = [2:6]$$

$$w_c(t) = \frac{1}{2} C \cdot v(t)^2 = 36 \cdot t^2 \text{ J} \rightarrow t = [0:2]$$

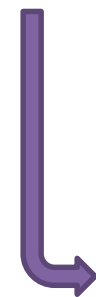
$$[17 - 3k \cdot t]^2 \text{ uJ} \rightarrow t = [2:6]$$




$$w_c(t = 2\text{m}) = 144 \text{ uJ}$$

Inductor

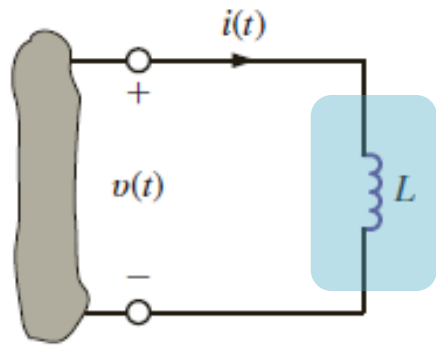... a circuit element that consists of a conducting wire usually in the form of a coil.




Symbol

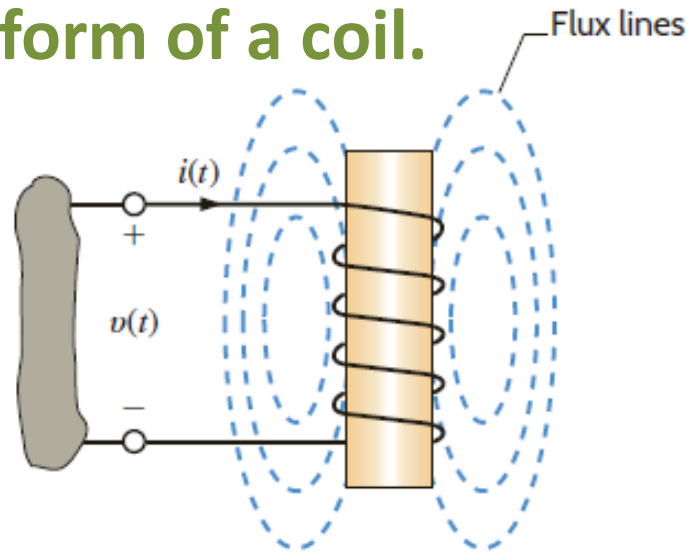

Simplified Inductor

Typical Inductors

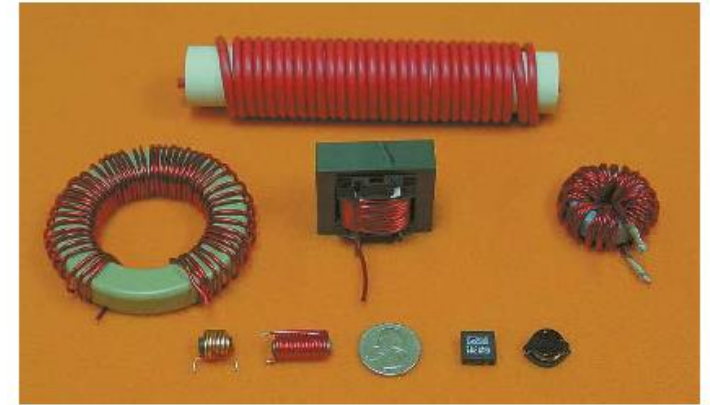


Inductance (L)




Unit \rightarrow Henry (H) = 1 volt-second per ampere

Inductor

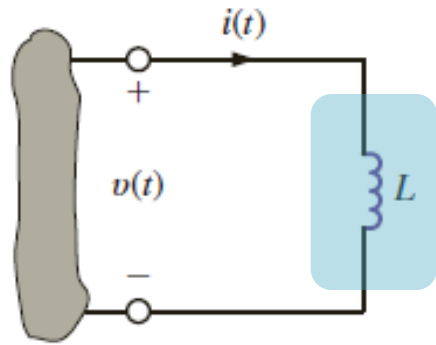... a circuit element that consists of a conducting wire usually in the form of a coil.




Symbol

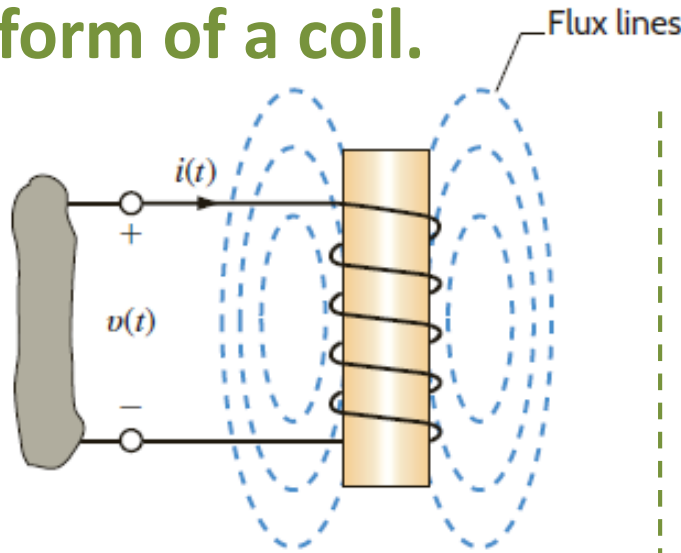

Simplified Inductor

Flux lines

Typical Inductors

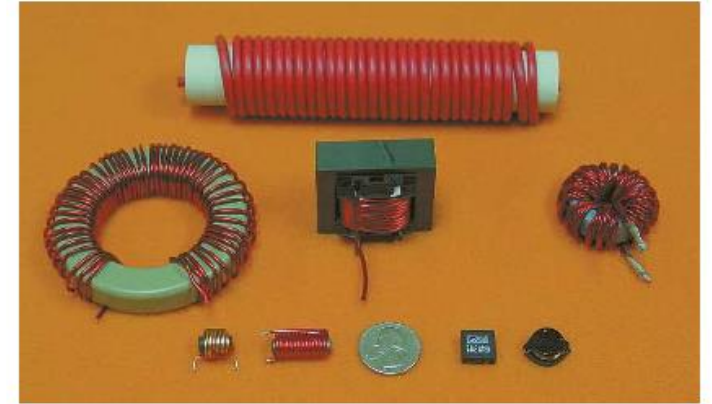

Inductance (L)



Unit → Henry (H) = 1 volt-second per ampere

$$v = L \cdot \frac{di}{dt}$$


$$i(t) = i(t_0) + \frac{1}{L} \cdot \int_{t_0}^t v(x) dx$$

$$p(t) = L \cdot i(t) \frac{di(t)}{dt}$$

$$w_L(t) = \frac{1}{2} L \cdot i(t)^2$$


Learning Assessment E6.6-E6.7

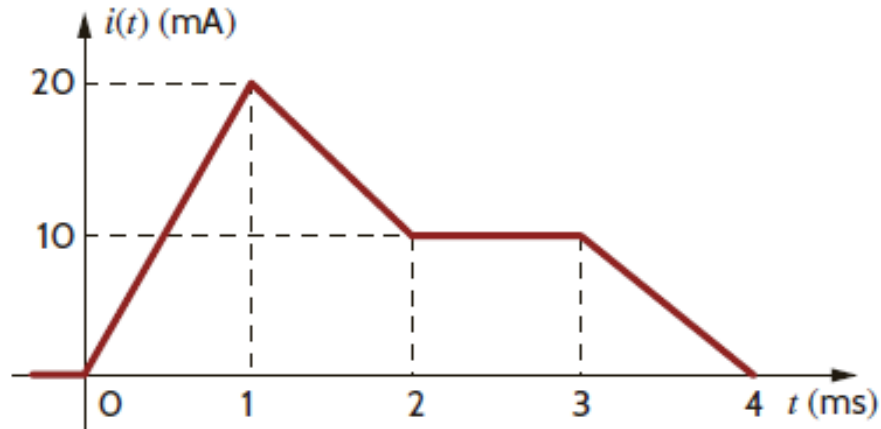The current across a 5-mH inductor is provided below. Determine the waveforms for the voltage, power, and energy and compute the energy stored in the magnetic field of the inductor at $t=1.5\text{ms}$.



Learning Assessment E6.6-E6.7

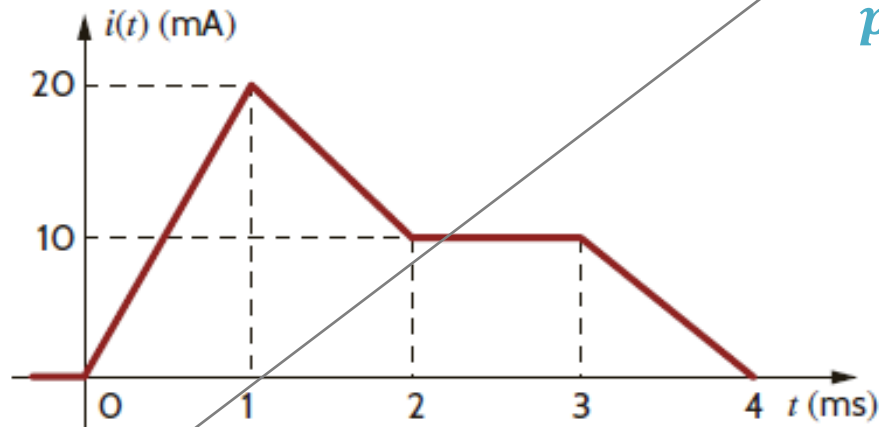The current across a 5-mH inductor is provided below. Determine the waveforms for the voltage, power, and energy and compute the energy stored in the magnetic field of the inductor at $t=1.5\text{ms}$.



$i(t) =$

$$v = L \cdot \frac{di}{dt} =$$


$$p(t) = L \cdot i(t) \frac{di(t)}{dt} =$$

$$w_L(t) = \frac{1}{2} L \cdot i(t)^2 =$$

$$w_L(t = 1.5\text{m}) =$$

Learning Assessment E6.6-E6.7

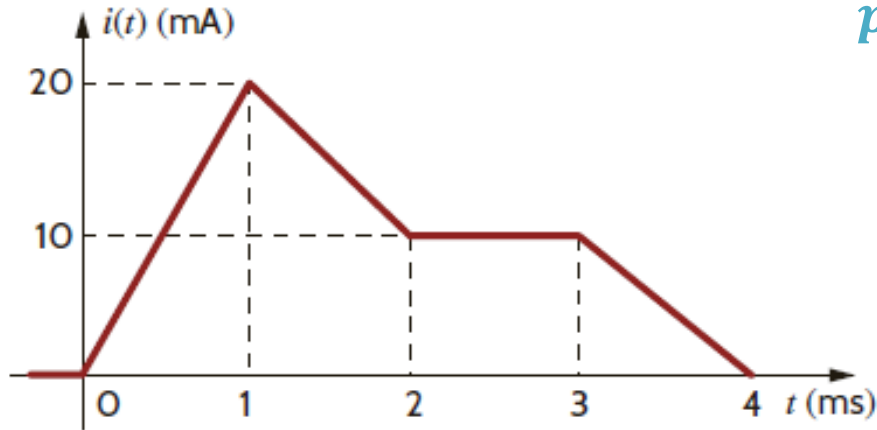The current across a 5-mH inductor is provided below. Determine the waveforms for the voltage, power, and energy and compute the energy stored in the magnetic field of the inductor at $t=1.5\text{ms}$.



$$i(t) = \begin{cases} 20 \cdot t \text{ A} & \rightarrow t = [0: 1] \\ 20\text{m} - 10 \cdot (t - 1\text{m}) \text{ A} & \rightarrow t = [1: 2] \\ 10 \text{ mA} & \rightarrow t = [2: 3] \\ 10\text{m} - 10 \cdot (t - 3\text{m}) \text{ A} & \rightarrow t = [3: 4] \end{cases}$$

$$v = L \cdot \frac{di}{dt} = \begin{cases} 100 \text{ mV} & \rightarrow t = [0: 1] \\ -50 \text{ mV} & \rightarrow t = [1: 2] \\ 0 & \rightarrow t = [2: 3] \\ -50 \text{ mV} & \rightarrow t = [3: 4] \end{cases}$$


$$p(t) = L \cdot i(t) \frac{di(t)}{dt} = \begin{cases} 2 \cdot t \text{ W} & \rightarrow t = [0: 1] \\ -1\text{m} + 0.5 \cdot (t - 1\text{m}) \text{ W} & \rightarrow t = [1: 2] \\ 0 & \rightarrow t = [2: 3] \\ -0.5\text{m} + 0.5 \cdot (t - 3\text{m}) \text{ W} & \rightarrow t = [3: 4] \end{cases}$$

$$w_L(t) = \frac{1}{2} L \cdot i(t)^2 = \begin{cases} t^2 \text{ J} & \rightarrow t = [0: 1] \\ 2.5 \cdot [30\text{m} - 10 \cdot t]^2 \text{ mJ} & \rightarrow t = [1: 2] \\ 250 \text{ nJ} & \rightarrow t = [2: 3] \\ 2.5 \cdot [40\text{m} - 10 \cdot t]^2 \text{ mJ} & \rightarrow t = [3: 4] \end{cases}$$

\downarrow
 $w_L(t = 1.5\text{m}) = 562 \text{ nJ}$


Example 6.5

Find the total energy stored in the circuit provided.

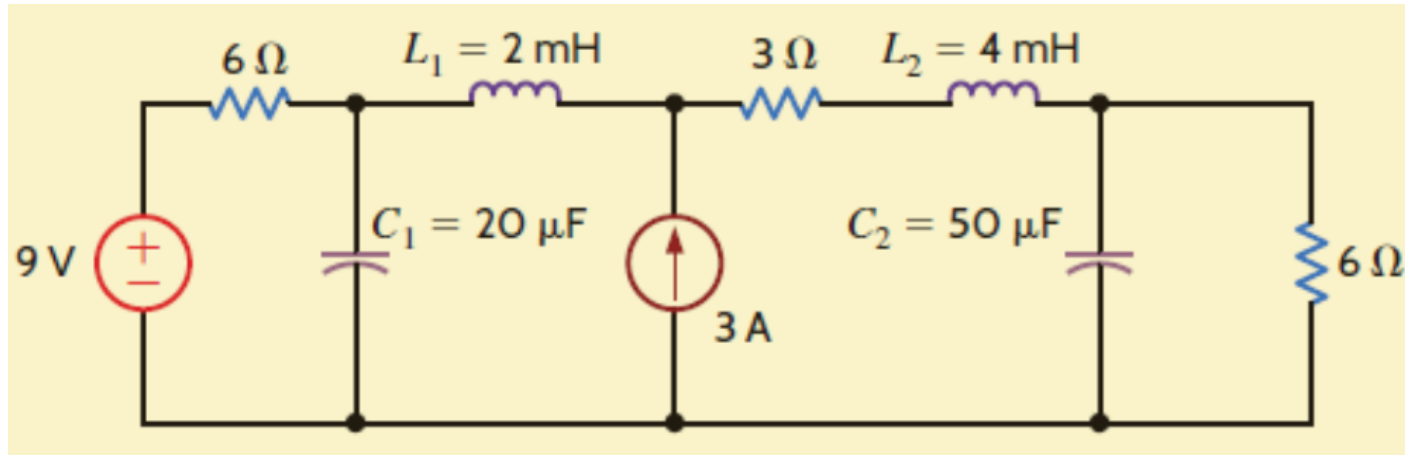


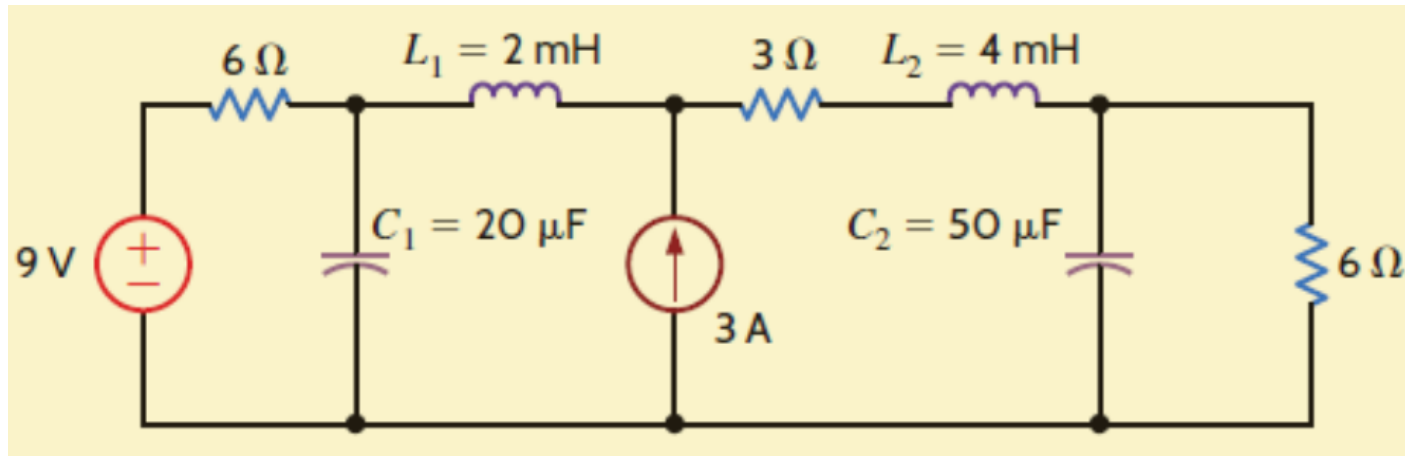Example 6.5



Find the total energy stored in the circuit provided.



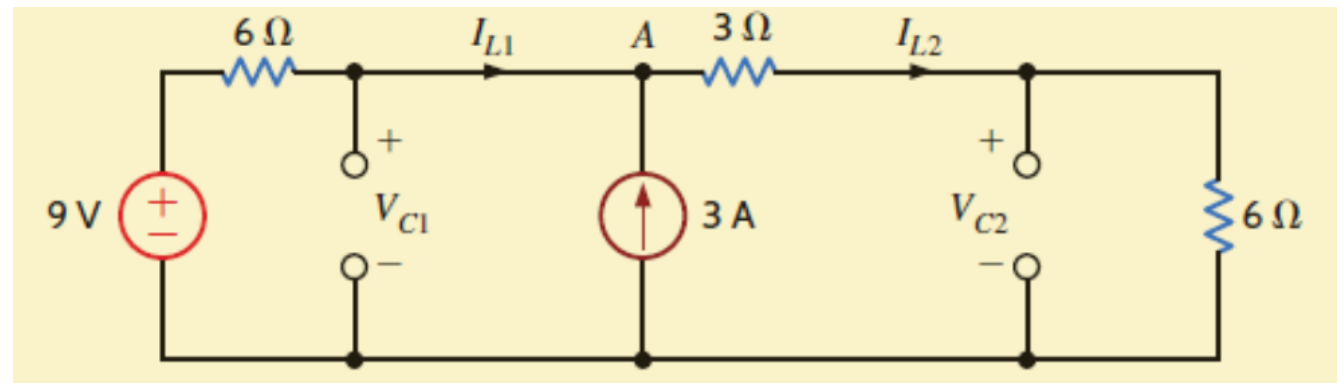
@ DC $V_L = 0$ & $I_C = 0$
 → L = short circuit
 → C = open circuit




Series \ Parallel Inductors

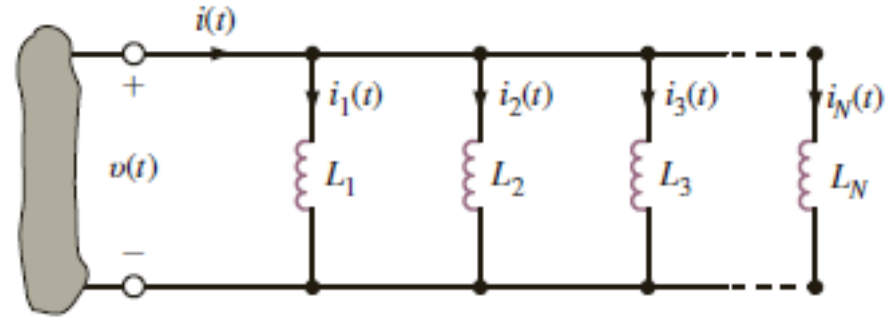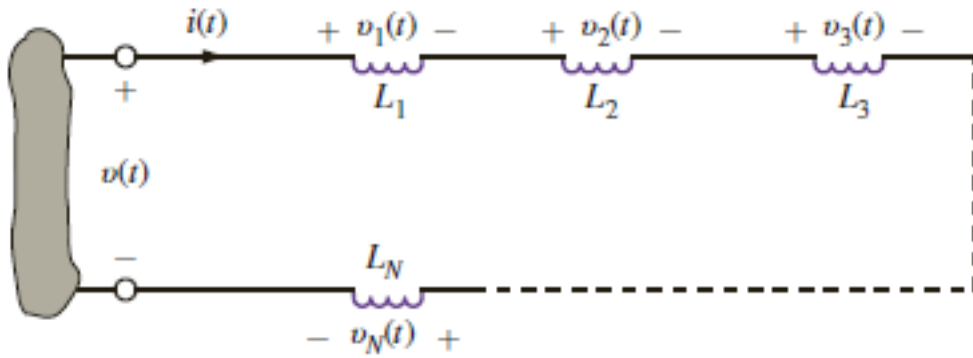

Series \ Parallel Inductors

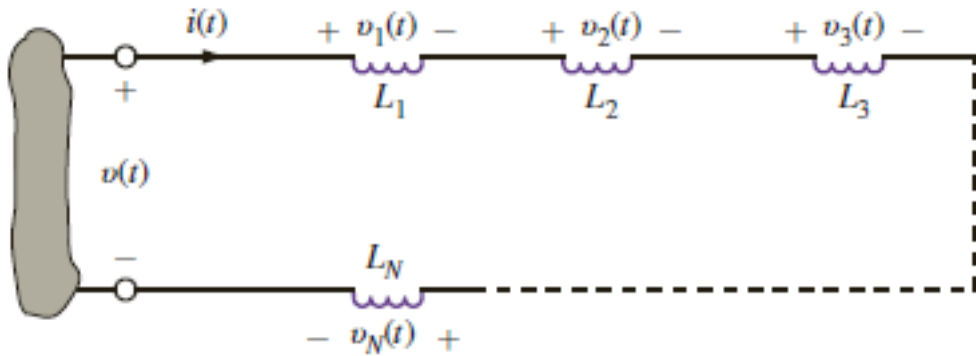

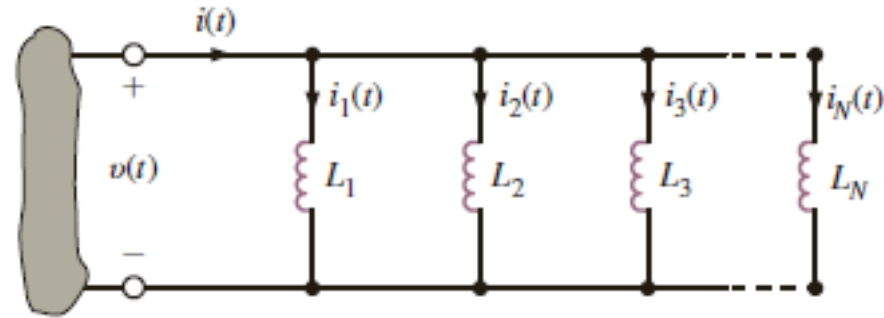
$$\begin{aligned}
 v(t) &= v_1(t) + v_2(t) + \dots + v_N(t) \\
 &= L_1 \frac{di(t)}{dt} + L_2 \frac{di(t)}{dt} + \dots + L_N \frac{di(t)}{dt} \\
 &= [L_1 + L_2 + \dots + L_N] \frac{di(t)}{dt}
 \end{aligned}$$




$$\begin{aligned}
 i(t) &= i_1(t) + i_2(t) + \dots + \\
 &= \frac{1}{L_1} v(t) dt + \frac{1}{L_2} v(t) dt + \dots + \frac{1}{L_N} v(t) dt \\
 &= \left[\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right] v(t) dt
 \end{aligned}$$


Series \ Parallel Inductors

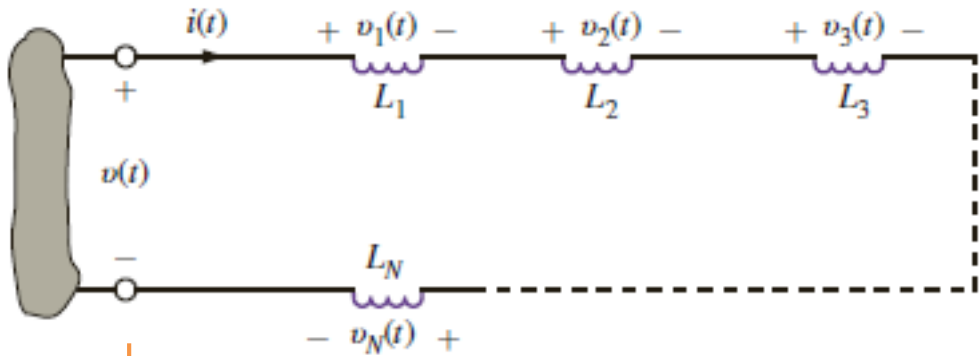

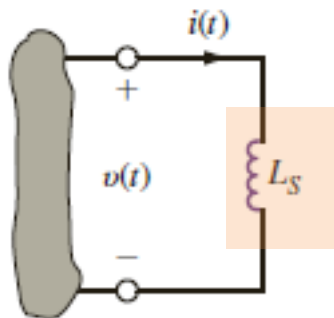
$$\begin{aligned} v(t) &= v_1(t) + v_2(t) + \dots + v_N(t) \\ &= L_1 \frac{di(t)}{dt} + L_2 \frac{di(t)}{dt} + \dots + L_N \frac{di(t)}{dt} \\ &= [L_1 + L_2 + \dots + L_N] \frac{di(t)}{dt} \end{aligned}$$



$$L_S = L_1 + L_2 + \dots + L_N$$


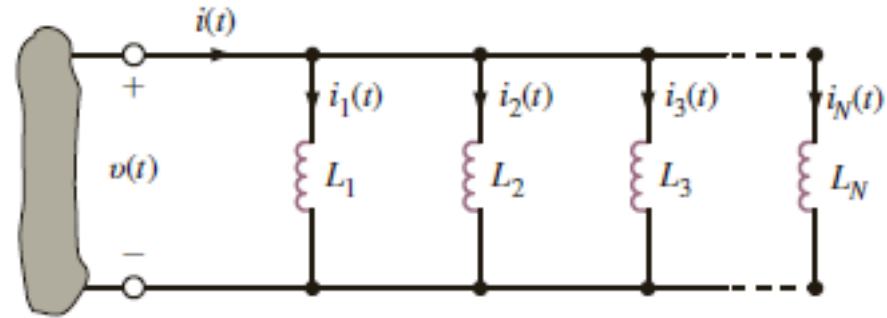

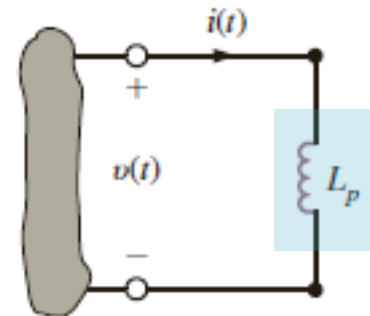
$$\begin{aligned} i(t) &= i_1(t) + i_2(t) + \dots + \\ &= \frac{1}{L_1} v(t) dt + \frac{1}{L_2} v(t) dt + \dots + \frac{1}{L_N} v(t) dt \\ &= \left[\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right] v(t) dt \end{aligned}$$




$$\frac{1}{L_P} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$


Series \ Parallel Capacitors

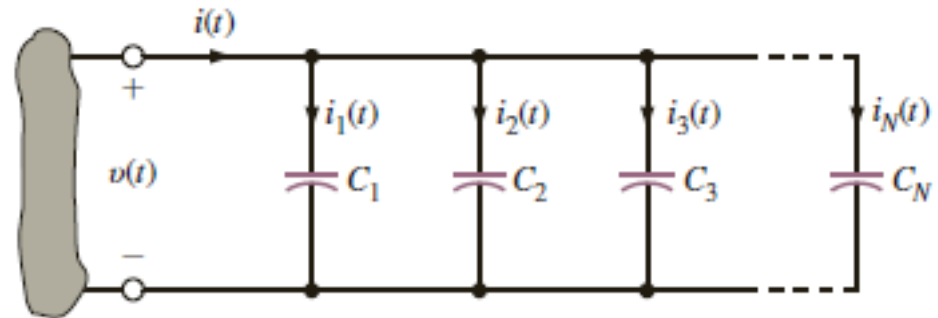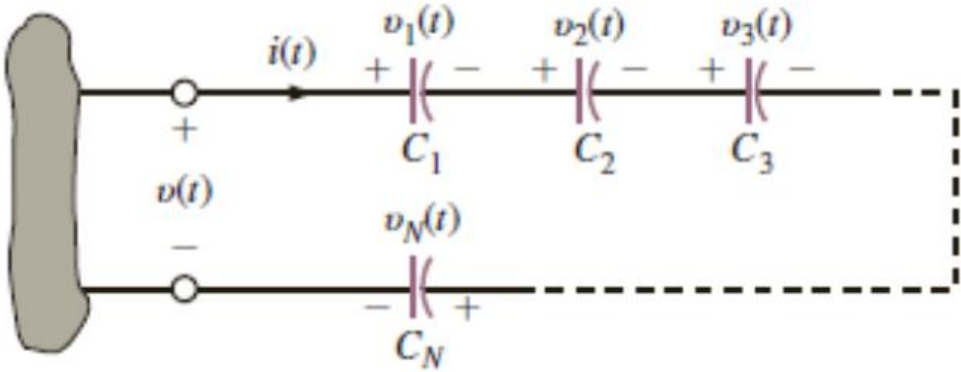

Series \ Parallel Capacitors

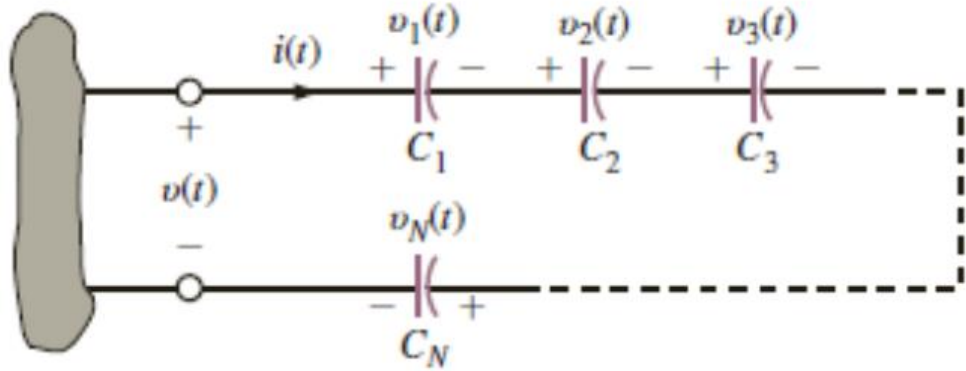

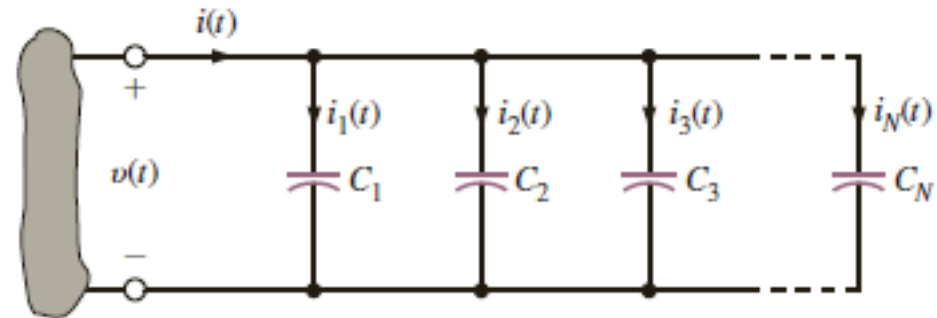
$$\begin{aligned}
 v(t) &= v_1(t) + v_2(t) + \dots + v_N(t) \\
 &= \frac{1}{C_1} i(t) dt + \frac{1}{C_2} i(t) dt + \dots + \frac{1}{C_N} i(t) dt \\
 &= \left[\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right] i(t) dt
 \end{aligned}$$




$$\begin{aligned}
 i(t) &= i_1(t) + i_2(t) + \dots + i_N(t) \\
 &= C_1 \frac{dv(t)}{dt} + C_2 \frac{dv(t)}{dt} + \dots + C_N \frac{dv(t)}{dt} \\
 &= [C_1 + C_2 + \dots + C_N] \frac{dv(t)}{dt}
 \end{aligned}$$


Series \ Parallel Capacitors

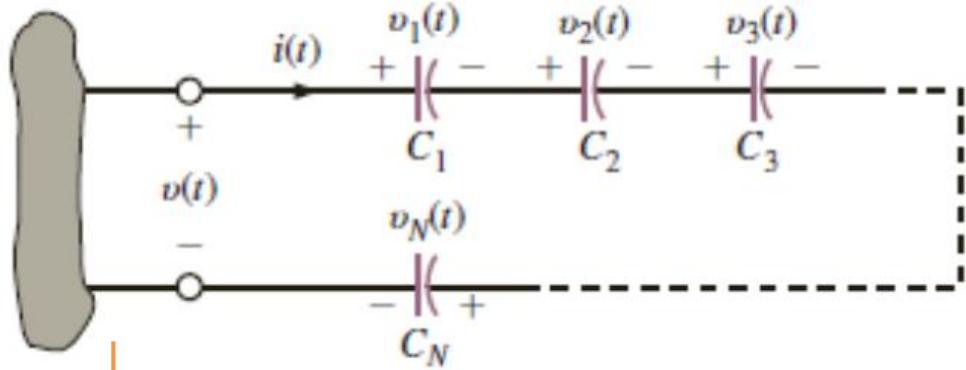

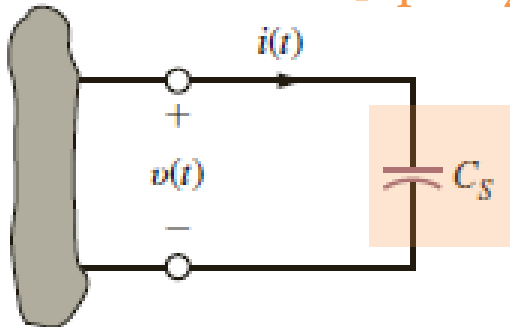
$$\begin{aligned} v(t) &= v_1(t) + v_2(t) + \dots + v_N(t) \\ &= \frac{1}{C_1} i(t) dt + \frac{1}{C_2} i(t) dt + \dots + \frac{1}{C_N} i(t) dt \\ &= \left[\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right] i(t) dt \end{aligned}$$


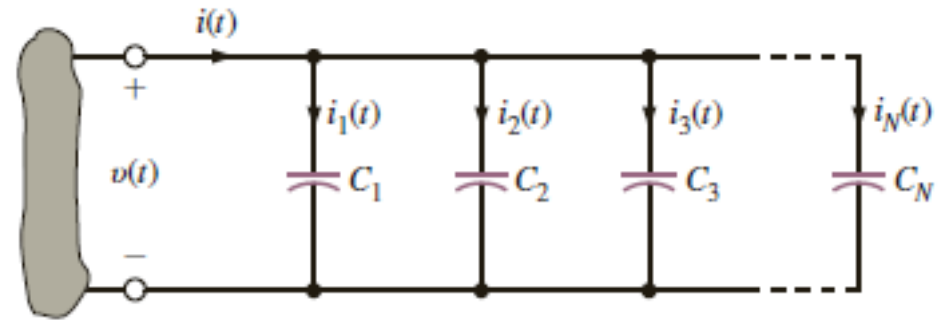
$$\frac{1}{C_S} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$



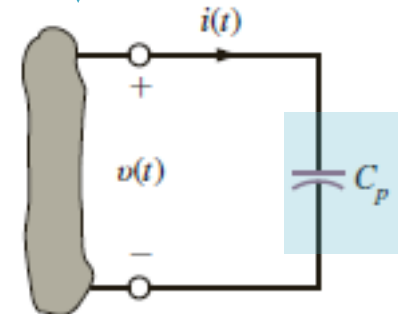
$$\begin{aligned} i(t) &= i_1(t) + i_2(t) + \dots + i_N(t) \\ &= C_1 \frac{dv(t)}{dt} + C_2 \frac{dv(t)}{dt} + \dots + C_N \frac{dv(t)}{dt} \\ &= [C_1 + C_2 + \dots + C_N] \frac{dv(t)}{dt} \end{aligned}$$



$$C_P = C_1 + C_2 + \dots + C_N$$

Learning Assessment E6.12

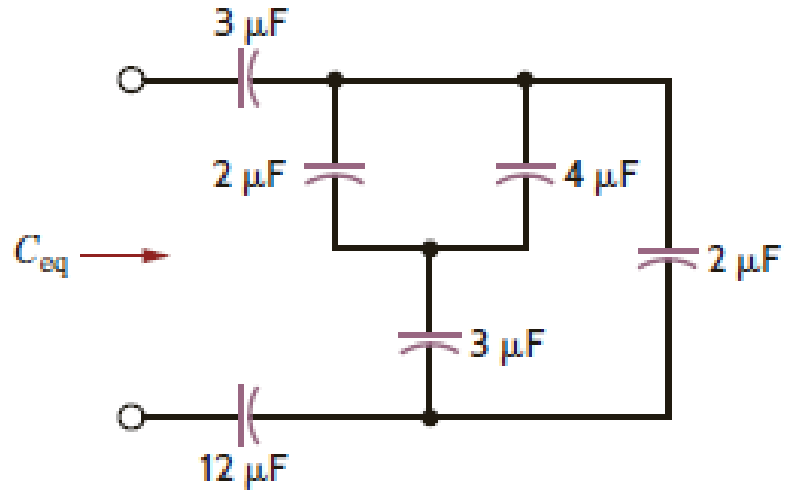Compute the equivalent capacitance of the network provided.



Learning Assessment E6.15

Find L_T in the network provided.

