

Exam #4 → Thursday, March 28

Concepts Chapter #4 & #6:

1) Op-Amp

- Model
- Circuit Analysis
 - Ideal behavior
 - Non-ideal behavior


2) Capacitor / Inductor

- Model / Behavior
- DC Analysis
- Series / Parallel Combination

*** “Bate”: bring your own set of equations (no problems, photocopies, solutions, etc)... subject to approval by the professor

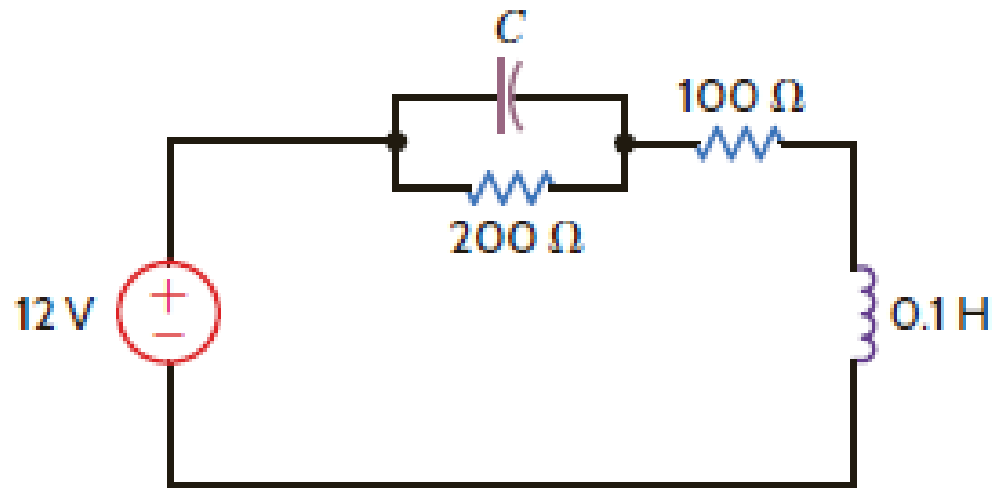
Problem 6.38

Find the value of C if the energy stored in the capacitor equals the energy stored in the inductor.




Learning Assessment E6.11

Two initially uncharged capacitors are connected as shown in the circuit below. After a period of time, the voltage reaches the value shown. Determine the value of C_1 .

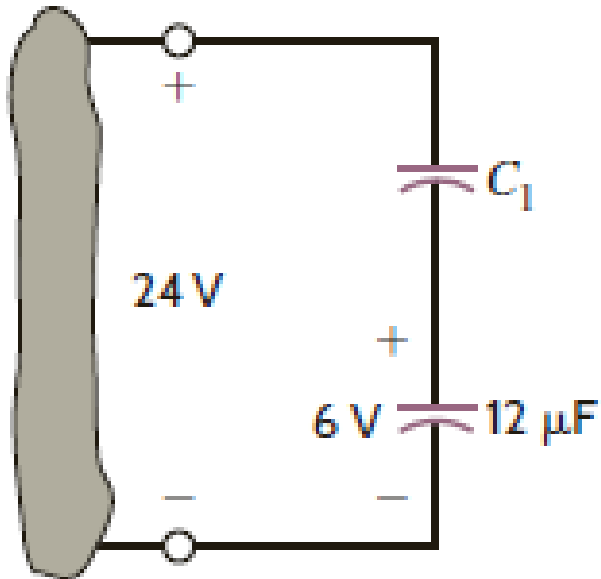


Problem 6.57

If the total capacitance of the provided network is $10\mu\text{F}$, find the value of C .

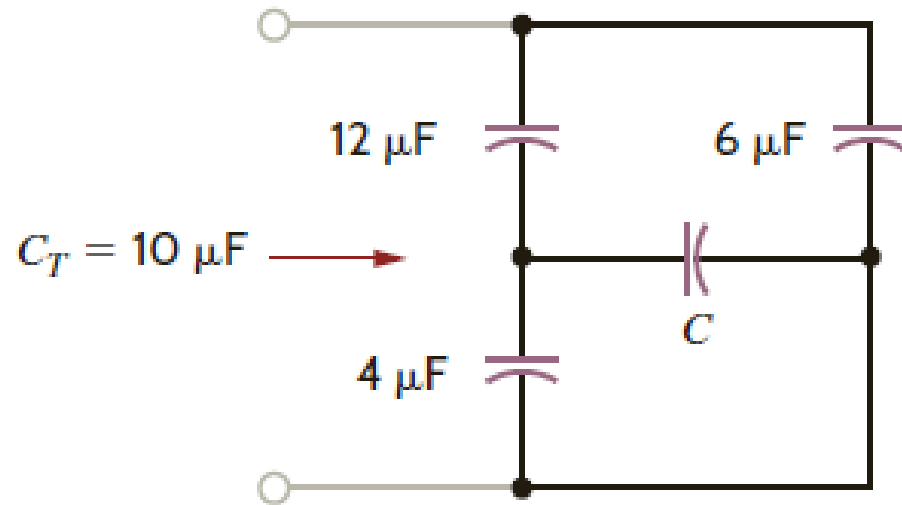

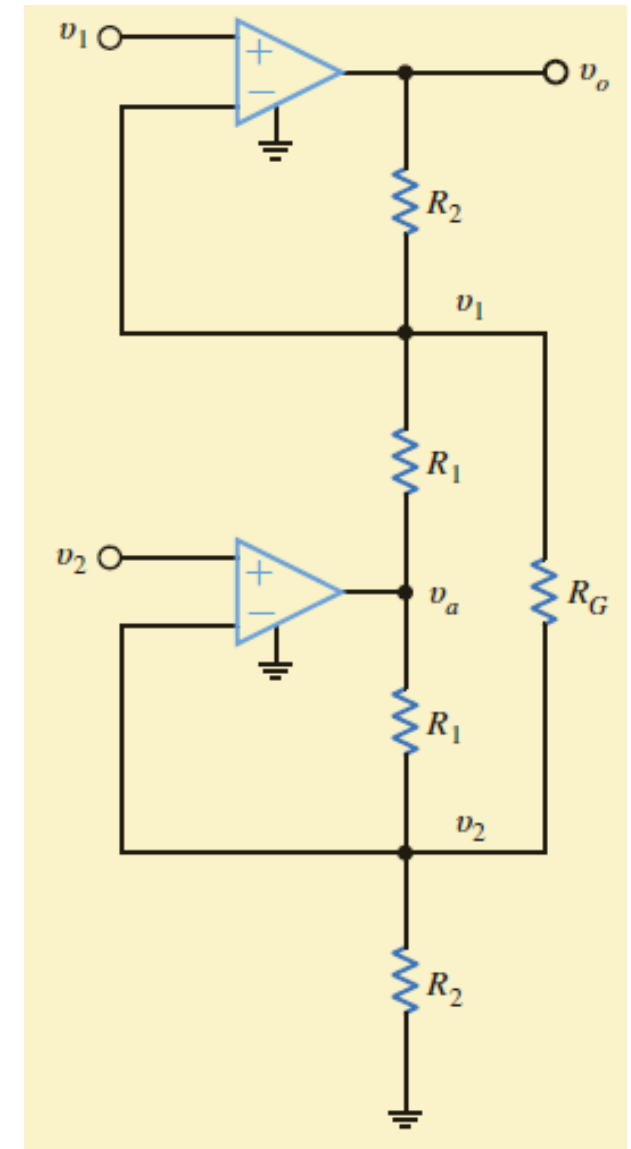
Example 4.5

The circuit shown is a precision differential voltage-gain device. It is used to provide a single-ended input for an analog-to-digital converter. Derive an expression for the output of the circuit in terms of the two inputs.



Learning Assessment – E4.5

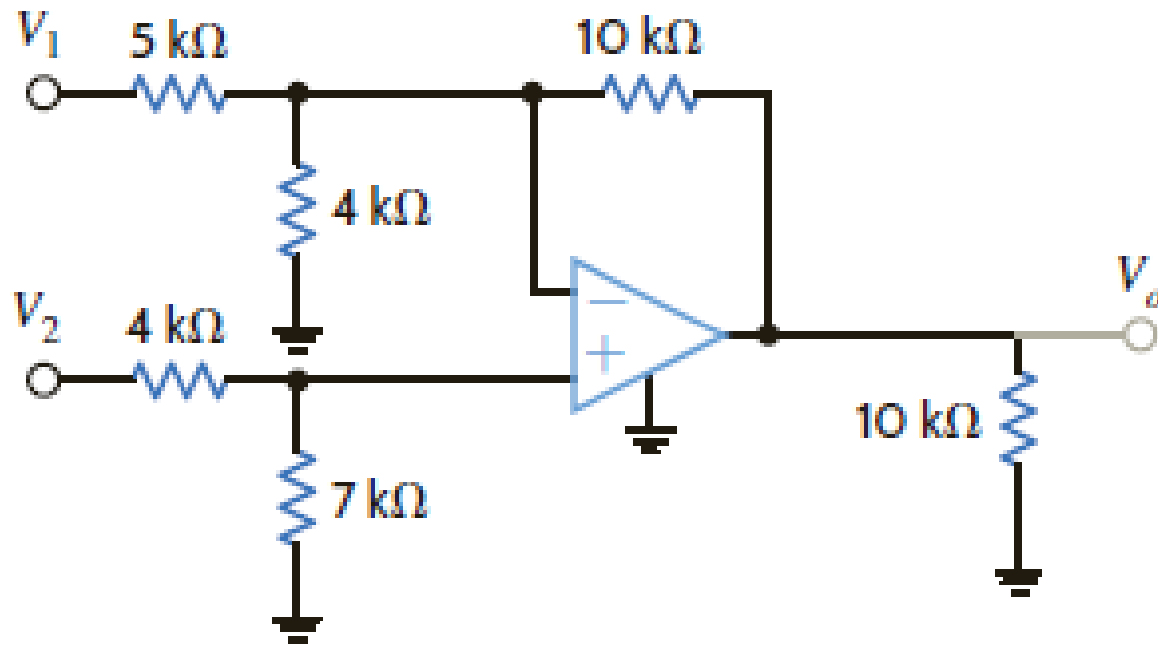
Assuming ideal op-amp behavior find V_o in terms of V_1 and V_2 . If $V_1=V_2=4$ find V_o . If the op-amp power supplies are $\pm 15V$ and $V_2=2V$, what is the allowable range of V_1 ?



Learning Assessment – E4.5

Assuming ideal op-amp behavior find V_o in terms of V_1 and V_2 . If $V_1=V_2=4$ find V_o . If the op-amp power supplies are $\pm 15V$ and $V_2=2V$, what is the allowable range of V_1 ?

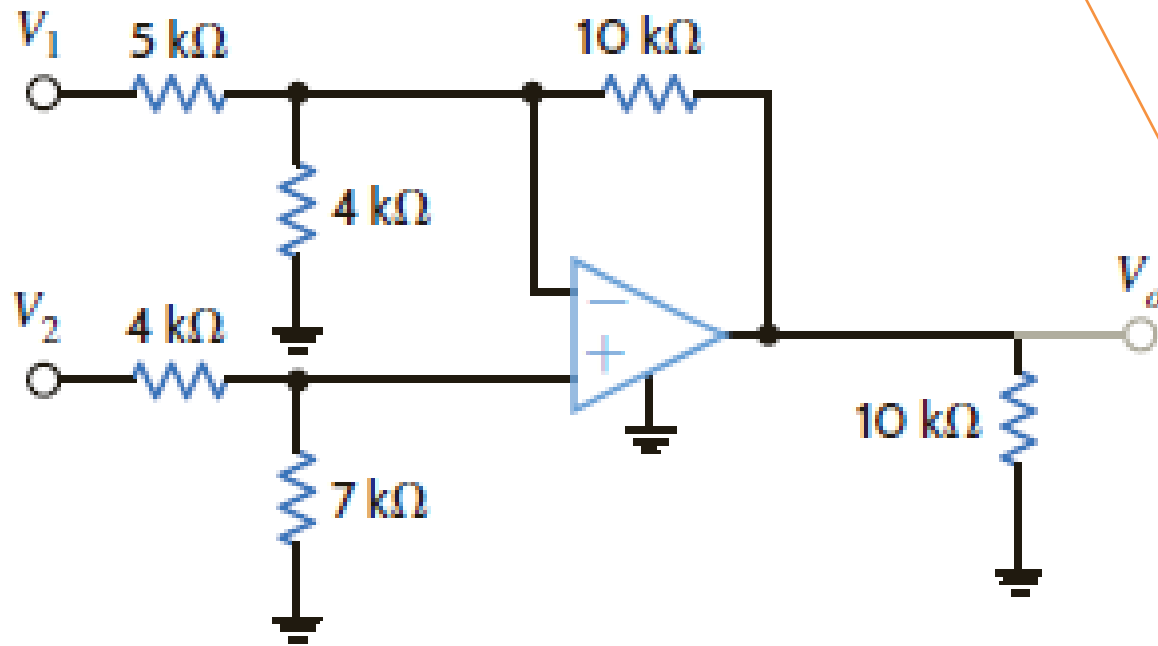→ Superposition: Inverting Amp. / Non-Inverting Amp.



$$V_o' = -V_1 \left[\frac{10k}{5k} \right] = -2 \cdot V_1$$

$$V_o'' = V_2 \left[\frac{7k}{11k} \right] \left[1 + \frac{10k}{4k // 5k} \right] = 3.5 \cdot V_2$$

$$\therefore V_o = -2 \cdot V_1 + 3.5 \cdot V_2$$


$$-15V \leq V_o \leq 15V$$

$$\therefore V_o = -2 \cdot V_1 + 3.5 \cdot V_2 \leq 15$$

$$\therefore V_o = -2 \cdot V_1 + 3.5 \cdot V_2 \geq -15$$


Learning Assessment E6.10

For the provided circuit find the energy stored in the capacitor and the inductor.

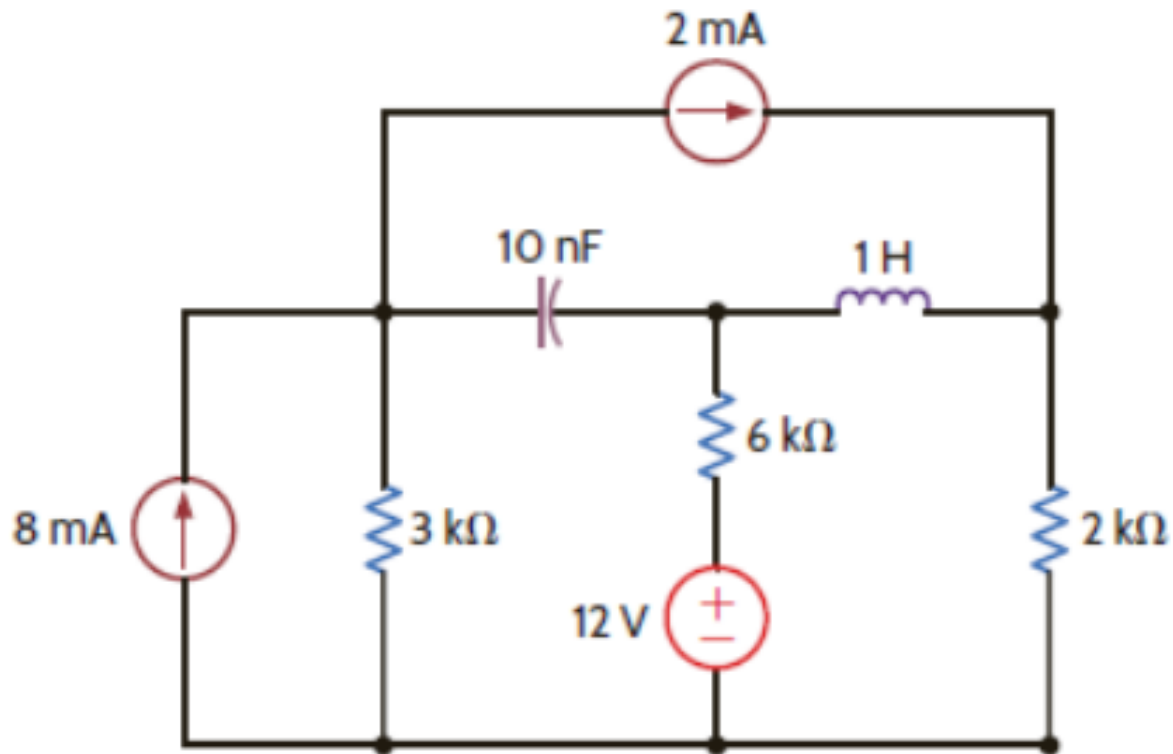

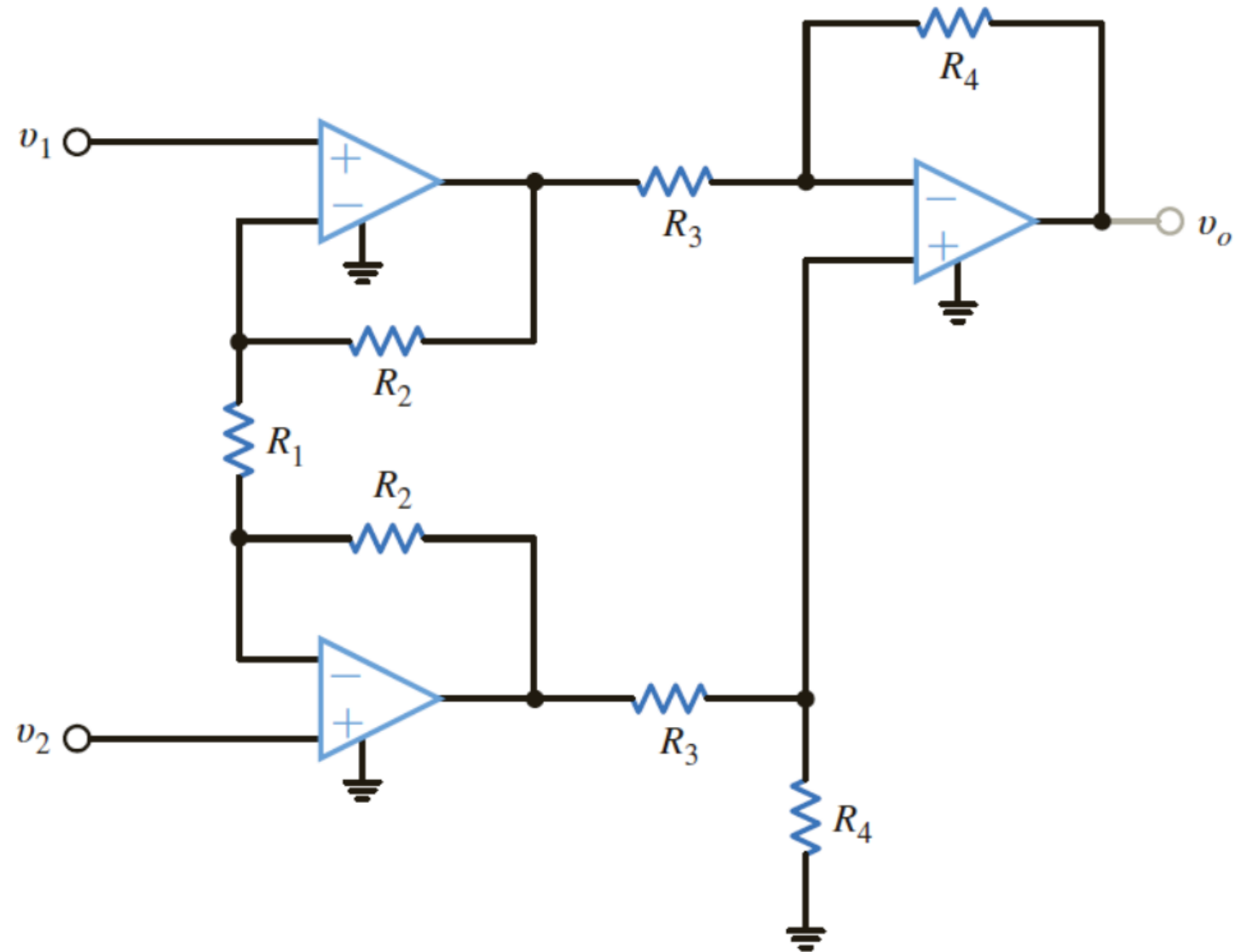
Problem 4.43

Assuming ideal op-amp behavior, find the expression for v_o in terms of $(v_2 - v_1)$.



Learning Assessment – E4.6

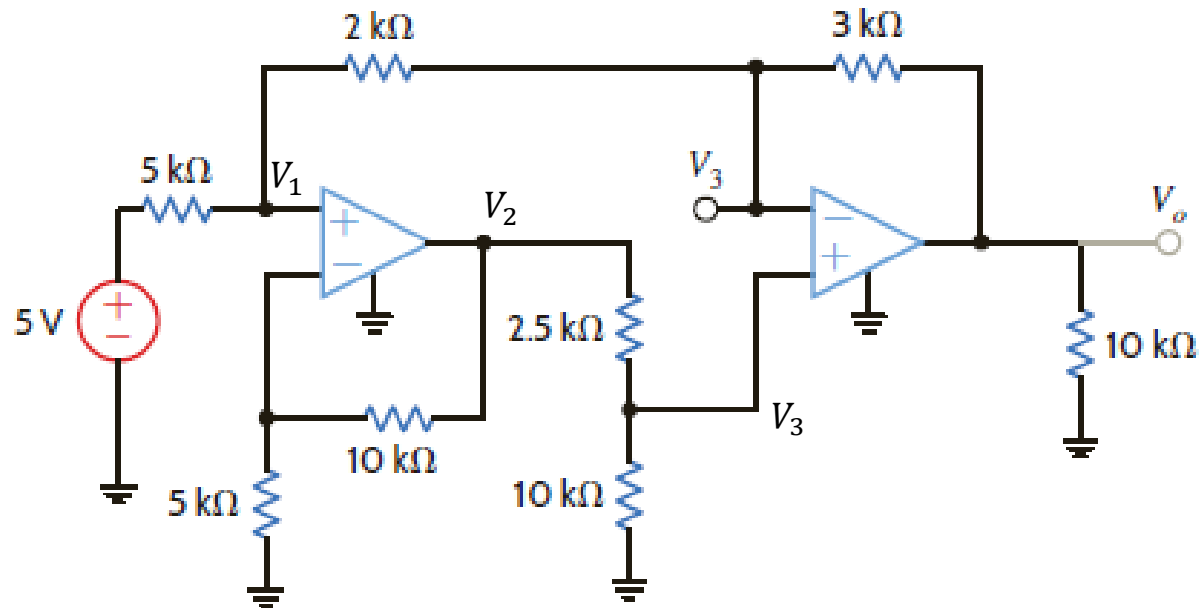
Assuming ideal op-amp behavior find V_0 and V_3 in the provided circuit.



Learning Assessment – E4.6

Assuming ideal op-amp behavior find V_0 and V_3 in the provided circuit.

Superposition:
Voltage Divider

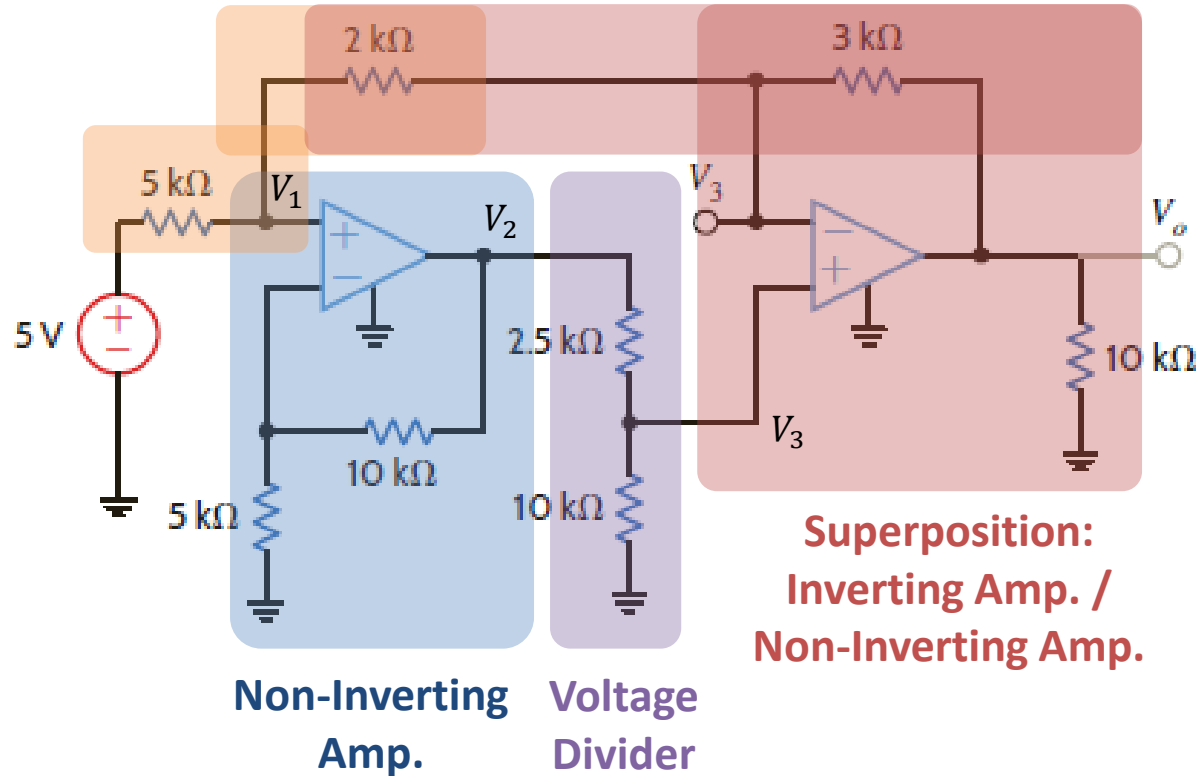

$$V_2 = \left[1 + \frac{10k}{5k} \right] V_1 = 3 \cdot V_1$$

$$V_3 = \left[\frac{10k}{10k + 2.5k} \right] V_2 = \frac{4}{5} \cdot V_2 = \frac{12}{5} \cdot V_1$$

$$\begin{aligned} V_0 &= \left[1 + \frac{3k}{2k} \right] V_3 - \left[\frac{3k}{2k} \right] V_1 \\ &= \frac{5}{2} \cdot V_3 - \frac{3}{2} \cdot V_1 = 6 \cdot V_1 - \frac{3}{2} \cdot V_1 = \frac{9}{2} \cdot V_1 \end{aligned}$$

$$V_1 = \left[\frac{2k}{7k} \right] 5 + \left[\frac{5k}{7k} \right] V_3 = \frac{10}{7} + \frac{12}{7} \cdot V_1$$

$$\therefore V_1 = -2V$$

$$\therefore V_0 = -9V$$

$$\therefore V_3 = -4.8V$$