


# Last Lecture → Sinusoids

$$x(t) = X_M \cdot \sin(\omega t + \theta)$$

- $X_m \rightarrow$  amplitude / maximum value
- $\omega \rightarrow$  radian / angular frequency
- $\theta \rightarrow$  phase angle

- $T \rightarrow$  period
- $f = \frac{1}{T} \rightarrow$  # cycles per second

$$\omega = \frac{2\pi}{T} = 2\pi f$$

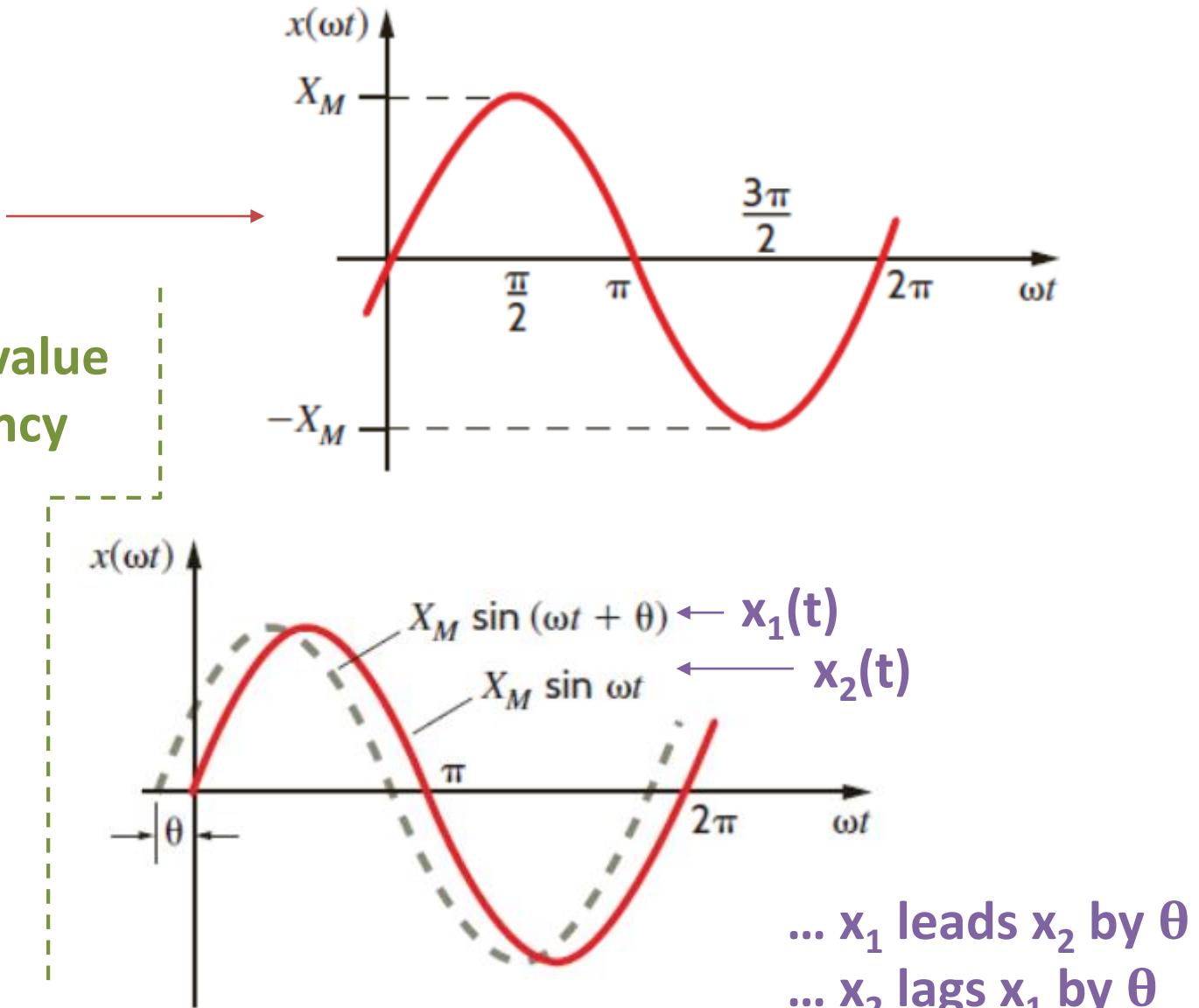

# Last Lecture → Solving Circuits in Time Domain

Derive the expression for the current  $i(t)$  using the forcing function  $v(t) = V_M e^{j\omega t}$  instead.

*response*

$$i(t) = I_M e^{j(\omega t + \varphi)}$$


*KVL*

$$v(t) = R \cdot i(t) + L \frac{di(t)}{dt}$$

*Differential Equation*


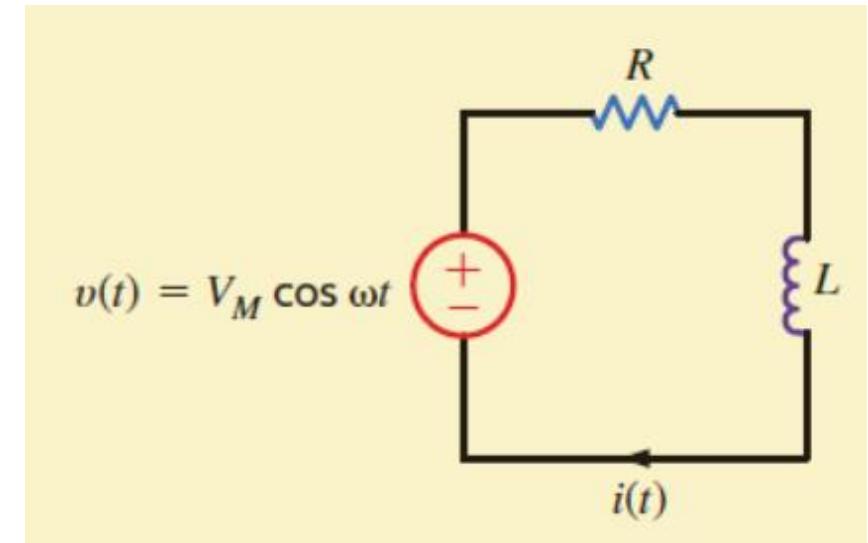
$$V_M e^{j\omega t} = R I_M e^{j(\omega t + \varphi)} + L \frac{d}{dt} (I_M e^{j(\omega t + \varphi)})$$



*Solution*

$$\therefore I_M = \frac{V_M}{\sqrt{R^2 + \omega^2 L^2}} \quad \therefore \varphi = -\tan^{-1} \left( \frac{\omega L}{R} \right)$$



$$i(t) = \frac{V_M}{\sqrt{R^2 + \omega^2 L^2}} \cos \left( \omega t - \tan^{-1} \left( \frac{\omega L}{R} \right) \right)$$

# Last Lecture → Phasors

Representation of a complex number with just the magnitude and the phase angle.

- **Forcing Function**

$$v(t) = V_M e^{j(\omega t + \theta)}$$



- **Steady State Response**

$$i(t) = I_M e^{j(\omega t + \varphi)}$$

$e^{j(\omega t)}$   
common to  
every term


$$v(t) = V_M \cos(\omega t + \theta) = \operatorname{Re}[V_M e^{j(\omega t + \theta)}]$$

$$V = \operatorname{Re}[V_M \langle \theta | e^{j\omega t}] = V_M \langle \theta$$

phasor

# Phasor Relationships → Resistor

- *Time Domain*

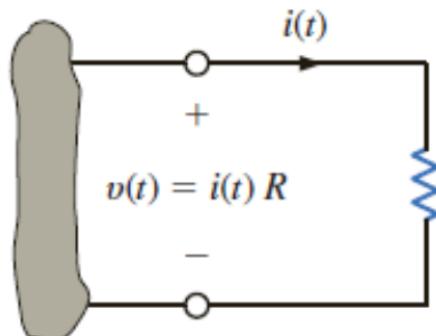


$$v(t) = R \cdot i(t)$$



$$V_M e^{j(\omega t + \theta_v)} = R \cdot I_M e^{j(\omega t + \theta_i)}$$

- *Frequency Domain*

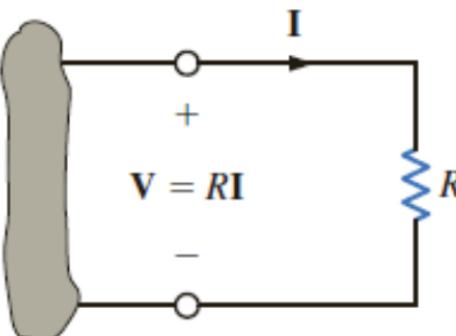

$$V = RI$$

$$\therefore V_M e^{j\theta_v} = R \cdot I_M e^{j\theta_i}$$

$$\hookrightarrow V_M \langle \theta_v \rangle = R \cdot I_M \langle \theta_i \rangle$$

- $v(t) = V_M e^{j(\omega t + \theta_v)}$

- $i(t) = I_M e^{j(\omega t + \theta_i)}$


$$\frac{V_M \langle \theta_v \rangle}{I_M \langle \theta_i \rangle} = R$$

$$\therefore \theta_v = \theta_i$$

→  $v(t)$  and  $i(t)$  are in phase


# Phasor Relationships → Inductor

- *Time Domain*

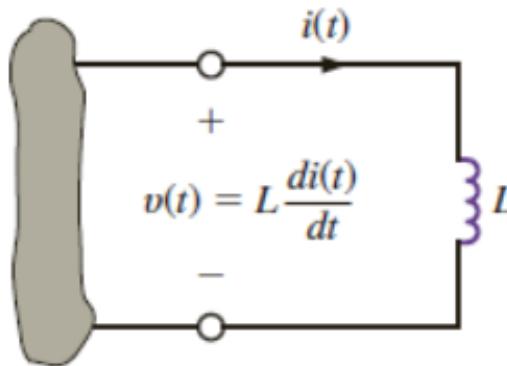

$$v(t) = L \cdot \frac{di(t)}{dt}$$

- *Frequency Domain*

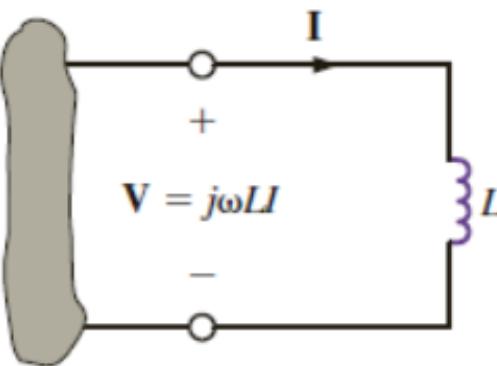

$$\therefore V_M e^{j\theta_v} = j\omega L \cdot I_M e^{j\theta_i}$$

$$\hookrightarrow V_M \langle \theta_v = j\omega L \cdot I_M \langle \theta_i$$

- $v(t) = V_M e^{j(\omega t + \theta_v)}$

- $i(t) = I_M e^{j(\omega t + \theta_i)}$


$$\frac{V_M \langle \theta_v}{I_M \langle \theta_i} = j\omega L$$

$$\therefore \theta_v = \theta_i + 90^\circ$$

→  $v(t)$  leads  $i(t)$  by  $90^\circ$

# Phasor Relationships → Capacitance


- *Time Domain*

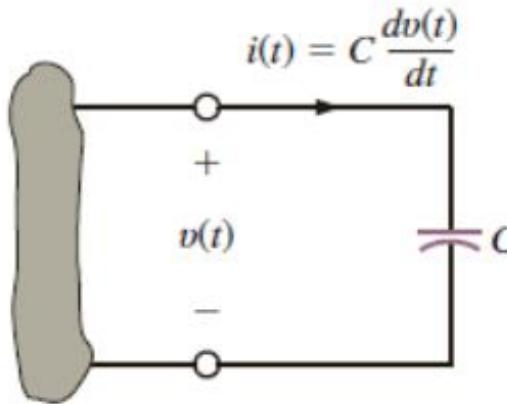

$$i(t) = C \cdot \frac{dv(t)}{dt}$$

$$I_M e^{j(\omega t + \theta_i)} = C \cdot \frac{d}{dt} V_M e^{j(\omega t + \theta_v)}$$

- *Frequency Domain*

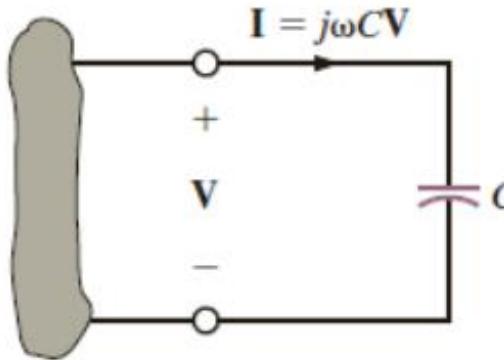

$$\therefore I_M e^{j\theta_i} = j\omega C \cdot V_M e^{j\theta_v}$$

$$\hookrightarrow I_M \langle \theta_i = j\omega C \cdot V_M \langle \theta_v$$

- $v(t) = V_M e^{j(\omega t + \theta_v)}$

- $i(t) = I_M e^{j(\omega t + \theta_i)}$

$$\frac{V_M \langle \theta_v}{I_M \langle \theta_i} = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

$$\therefore \theta_v = \theta_i - 90^\circ$$


$\rightarrow v(t)$  lags  $i(t)$  by  $90^\circ$

# Impedance

The ratio of the phasor voltage  $V$  to the phasor current  $I$ .

$$Z = \frac{V}{I} \text{ [Ohms]}$$
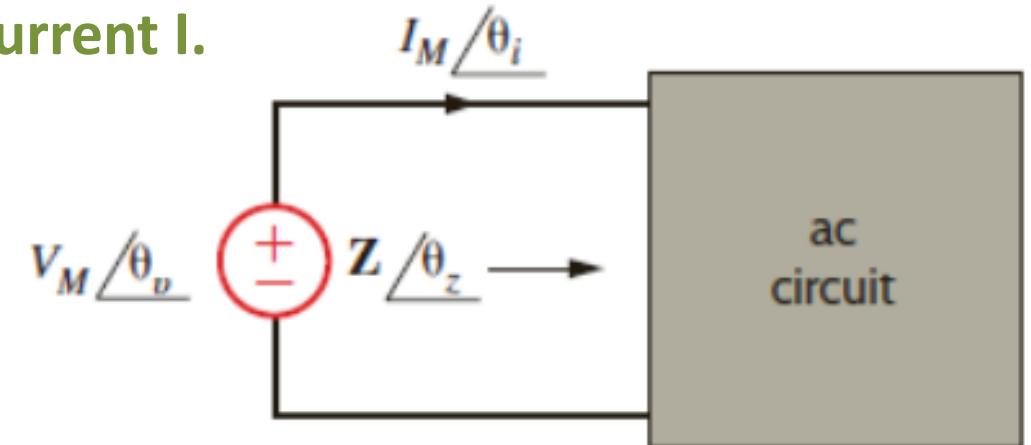
$$= \frac{V_M \langle \theta_v \rangle}{I_M \langle \theta_i \rangle} = \frac{V_M}{I_M} \langle (\theta_v - \theta_i) \rangle = Z \langle \theta_z \rangle$$



$$Z \langle \theta_z \rangle = R + jX$$

↓      ↓

*Resistance      Reactance*

*Polar Coordinates*

$$Z = \sqrt{R^2 + X^2}$$

$$\langle \theta_z \rangle = \tan^{-1} \left( \frac{X}{R} \right)$$

*Rectangular Coordinates*

$$\begin{array}{l} R = Z \cos \theta_z \\ X = Z \sin \theta_z \end{array}$$

# Impedance


The ratio of the phasor voltage  $V$  to the phasor current  $I$ .

Series → Equivalent Impedance

$$Z_s = Z_1 + Z_2 + \dots + Z_n$$

Parallel → Equivalent Impedance

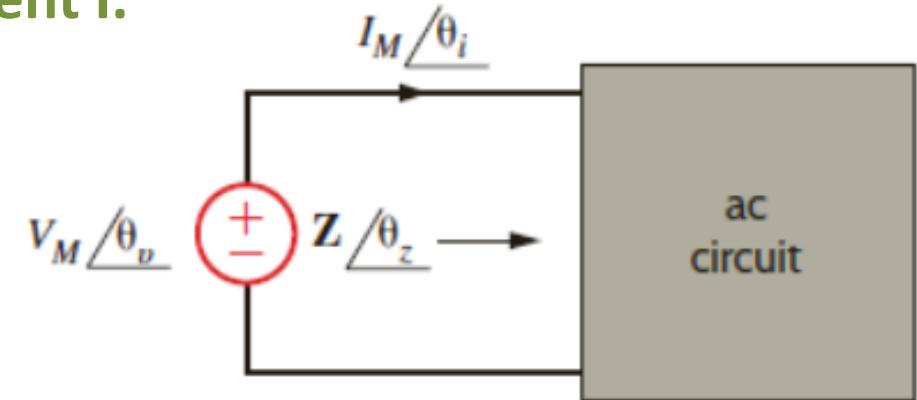
$$\frac{1}{Z_p} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}$$



KVL & KCL are valid in the frequency domain!
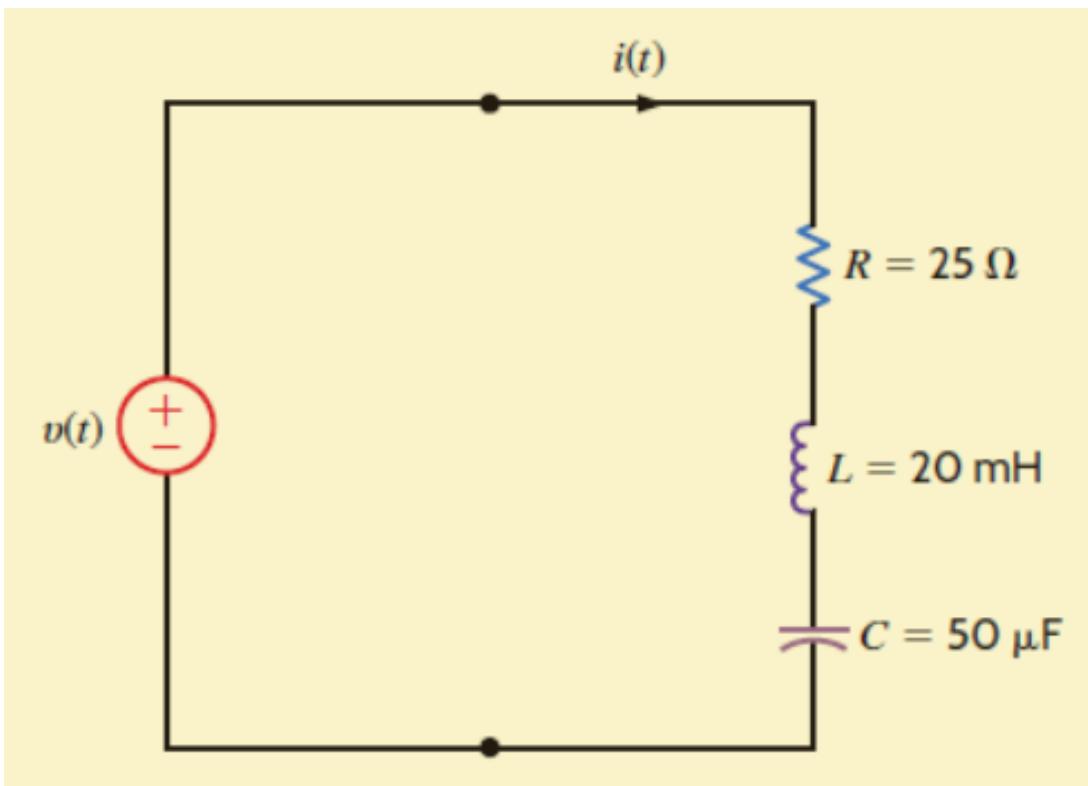
## Example 8.9

Determine the equivalent impedance of the network provided if the frequency is  $f=60\text{Hz}$ . Then compute the current  $i(t)$  if the voltage source is  $v(t) = 50 \cos(\omega t + 30^\circ) \text{ V}$



# Admittance

The ratio of the phasor current  $I$  to the phasor voltage  $V$ .

$$Y = \frac{I}{V} = \frac{1}{Z} \text{ [Siemens]}$$

$$Y \langle \theta_y = G + jB$$

↑      ↑  
*Conductance*    *Susceptance*

Parallel → Equivalent Admittance


$$Y_p = Y_1 + Y_2 + \dots + Y_n$$

Series → Equivalent Admittance

$$\frac{1}{Y_s} = \frac{1}{Y_1} + \frac{1}{Y_2} + \dots + \frac{1}{Y_n}$$

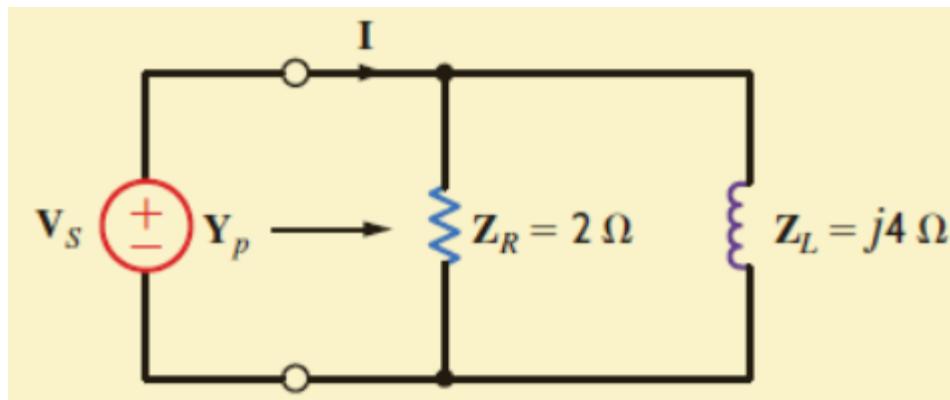
## Example 8.10

Calculate the equivalent admittance  $Y_p$  for the network provided and use it to determine the current  $I$  if  $V_s = 60\langle 45^\circ \rangle$ .




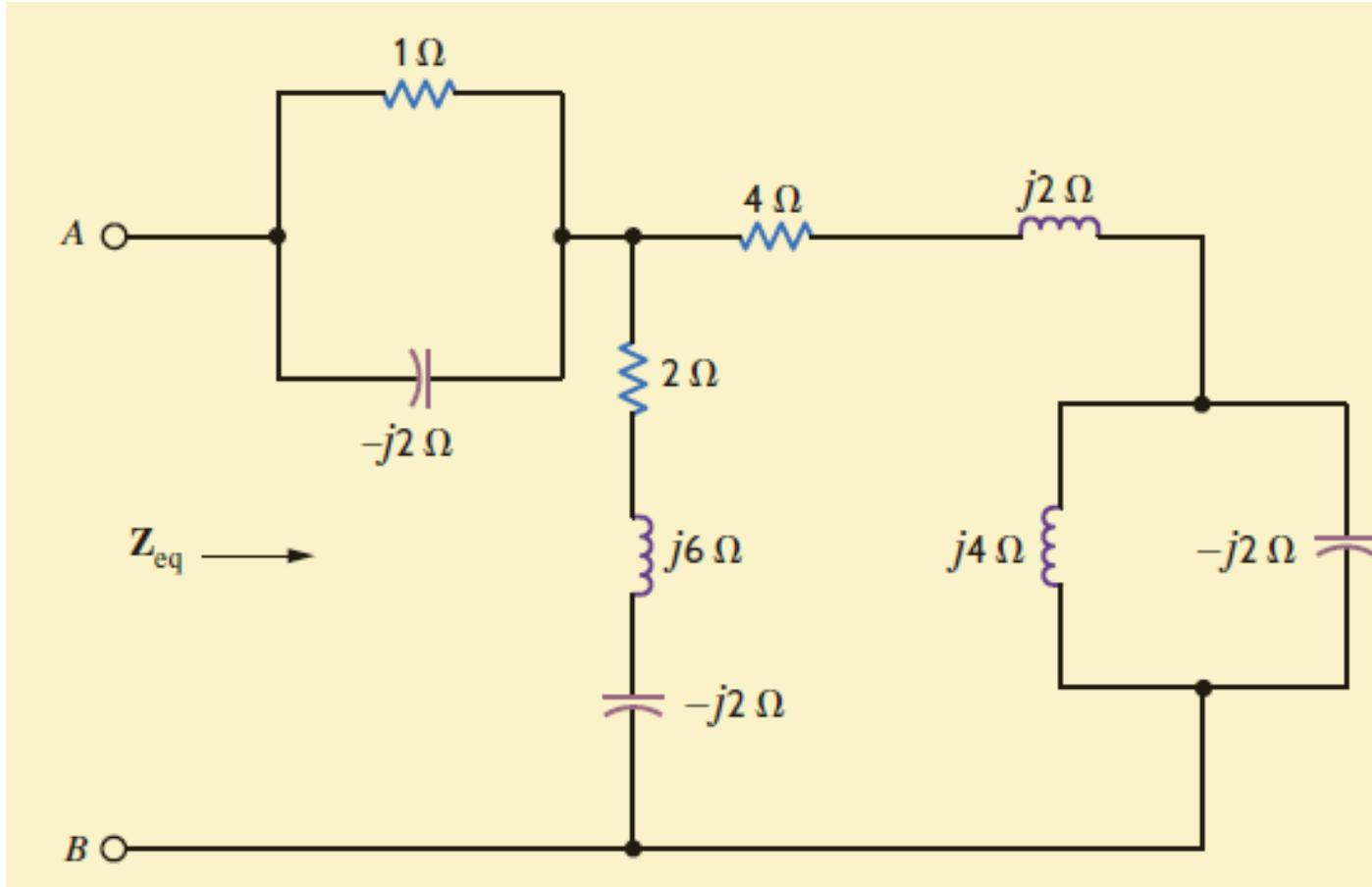
## Example 8.11

For the given circuit calculate the equivalent impedance  $Z_{eq}$  at terminals A-B.


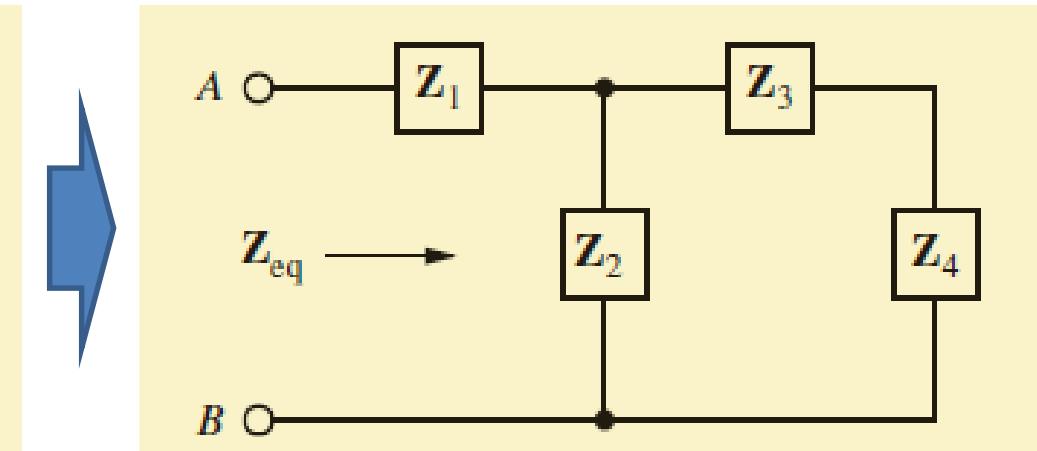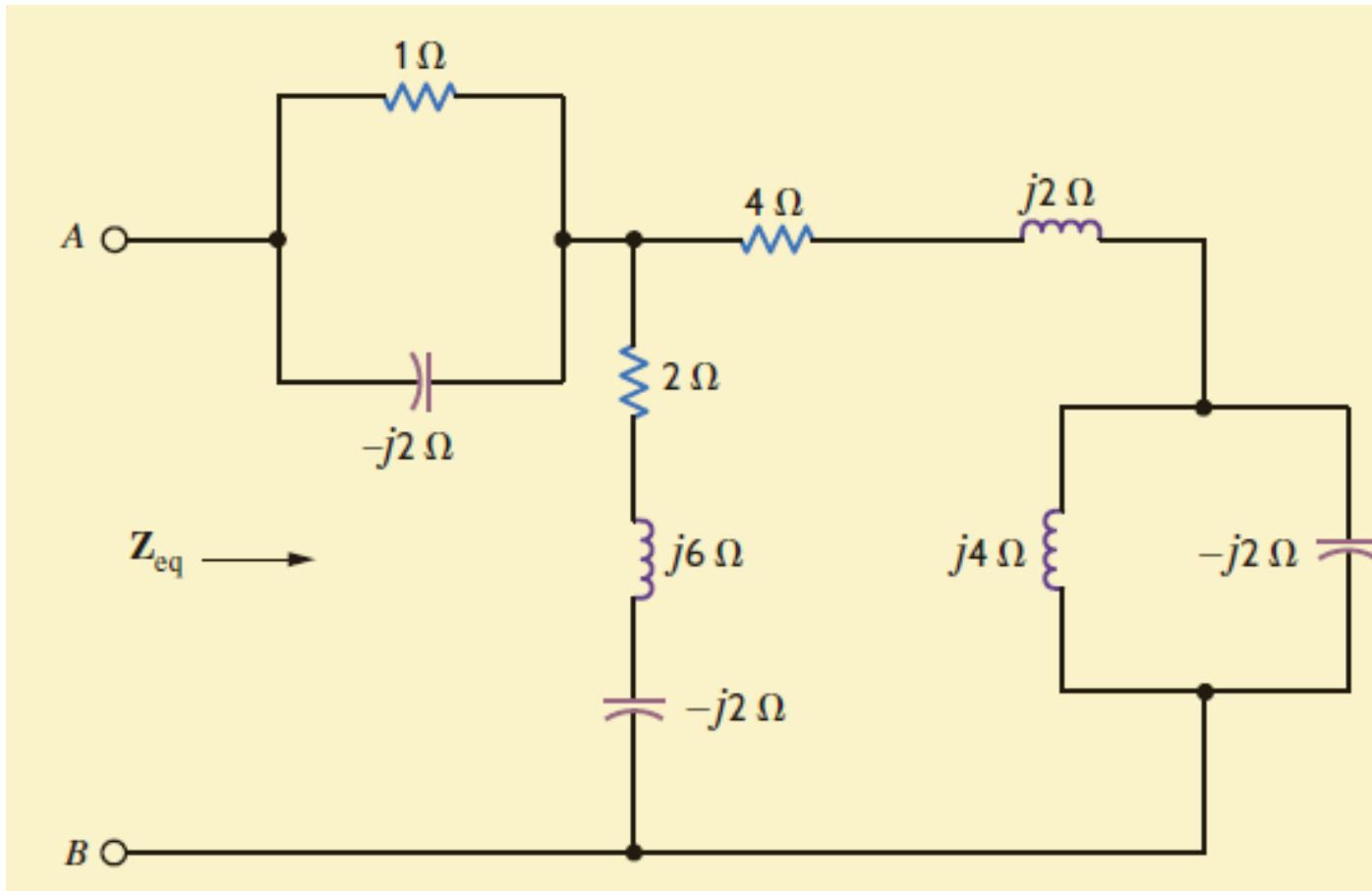
## Example 8.11

For the given circuit calculate the equivalent impedance  $Z_{eq}$  at terminals A-B.




Technique for taking the reciprocal...

$$\frac{1}{R + jX} = \frac{R - jX}{R^2 + X^2}$$


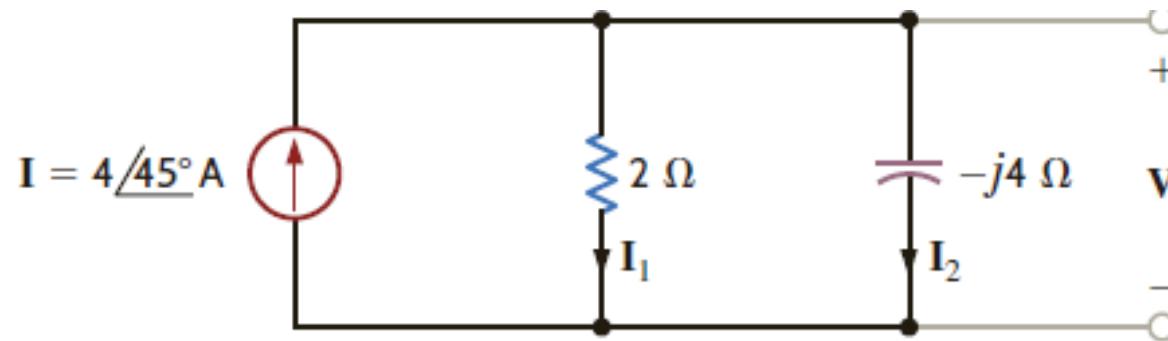
# Learning Assessment E8.12

Draw the phasor diagram to illustrate all currents and voltages for the network provided.


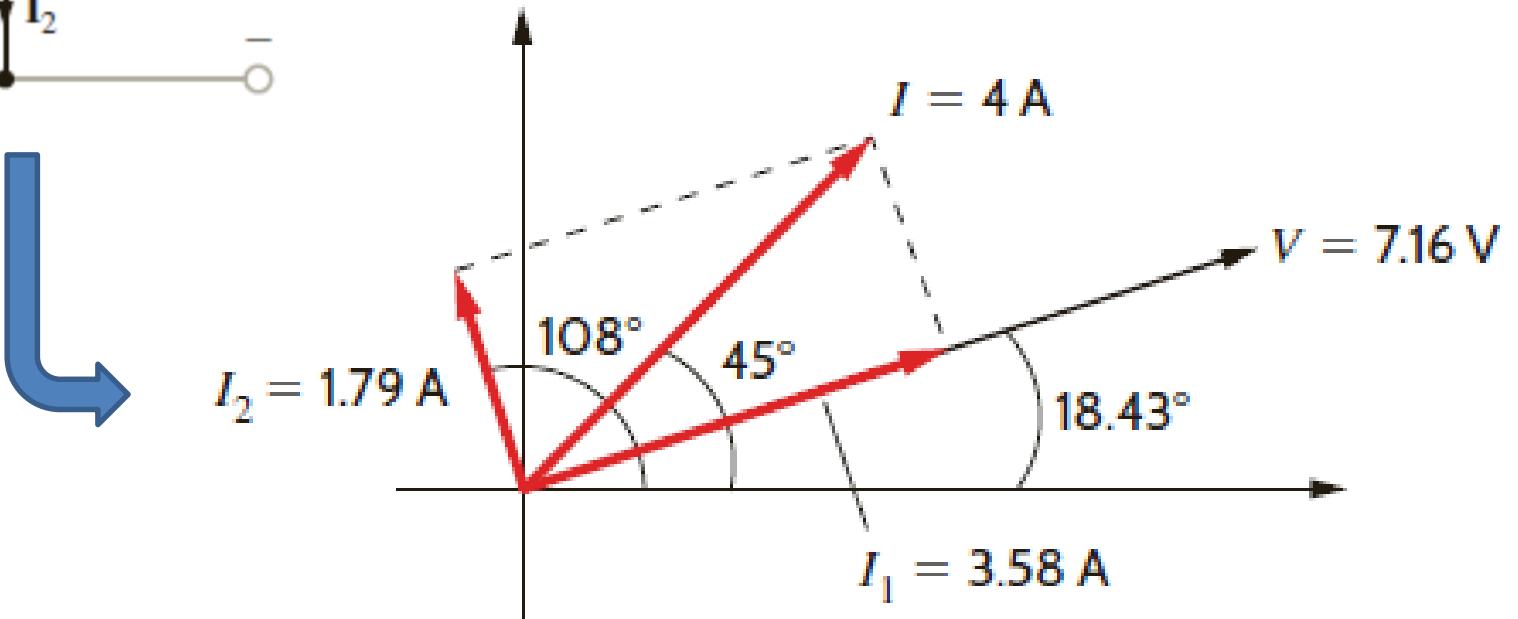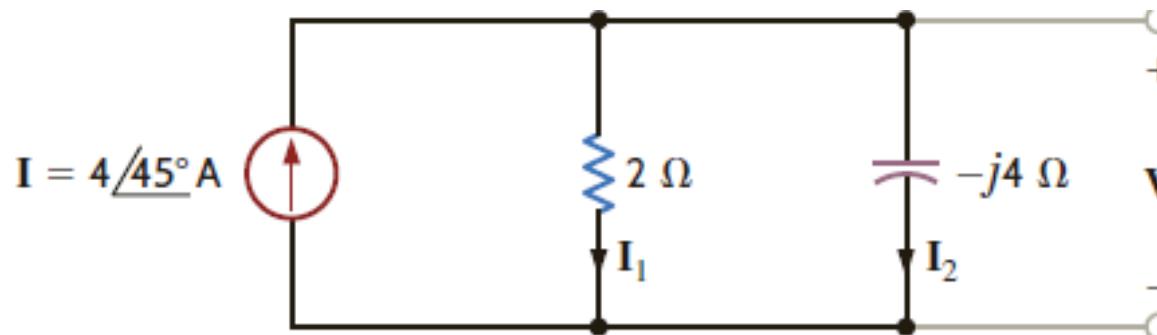
# Learning Assessment E8.12

Draw the phasor diagram to illustrate all currents and voltages for the network provided.



## Example 8.15

For the given network determine  $I_o$  using nodal analysis.

