

Last Lecture → Impedance

The ratio of the phasor voltage V to the phasor current I .

$$Z = \frac{V}{I} \text{ [Ohms]}$$

$$= \frac{V_M \angle \theta_v}{I_M \angle \theta_i} = \frac{V_M}{I_M} \angle (\theta_v - \theta_i) = Z \angle \theta_z$$

Resistance

Reactance

$$Z \angle \theta_z = R + jX$$

KVL & KCL are valid in the frequency domain!

PASSIVE ELEMENT	IMPEDANCE
R	$Z = R$
L	$Z = j\omega L = jX_L, X_L = \omega L$
C	$Z = \frac{1}{j\omega C} = -\frac{j}{\omega C} = -jX_C, X_C = \frac{1}{\omega C}$

Series → Equivalent Impedance

$$Z_s = Z_1 + Z_2 + \cdots + Z_n$$

Parallel → Equivalent Impedance

$$\frac{1}{Z_p} = \frac{1}{Z_1} + \frac{1}{Z_2} + \cdots + \frac{1}{Z_n}$$

Last Lecture → Admittance

The ratio of the phasor current I to the phasor voltage V .

$$Y = \frac{I}{V} = \frac{1}{Z} \text{ [Siemens]}$$

Conductance

$$Y \angle \theta_y = G + jB$$

Susceptance

KVL & KCL are valid in the frequency domain!

PASSIVE ELEMENT

IMPEDANCE

R

$$Z = R$$

L

$$Z = j\omega L = jX_L, X_L = \omega L$$

C

$$Z = \frac{1}{j\omega C} = -\frac{j}{\omega C} = -jX_C, X_C = \frac{1}{\omega C}$$

Parallel → Equivalent Admittance


$$Y_p = Y_1 + Y_2 + \cdots + Y_n$$

Series → Equivalent Admittance

$$\frac{1}{Y_s} = \frac{1}{Y_1} + \frac{1}{Y_2} + \cdots + \frac{1}{Y_n}$$


Problem 8.25

The admittance of the box in the figure provided is $0.1 + j0.2 \text{ S}$ at 500 rad/s. What is the impedance at 300 rad/s?

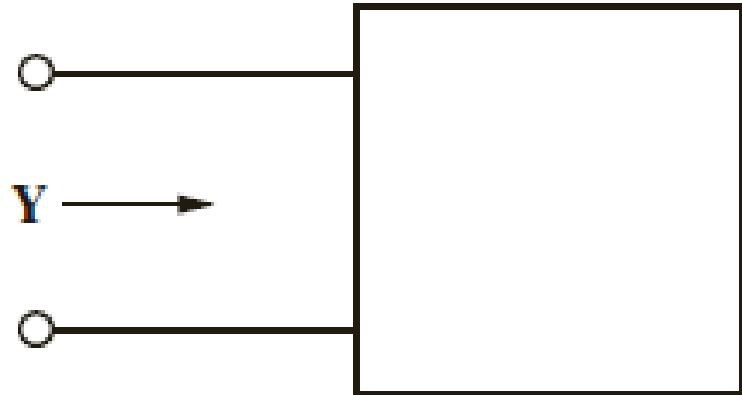

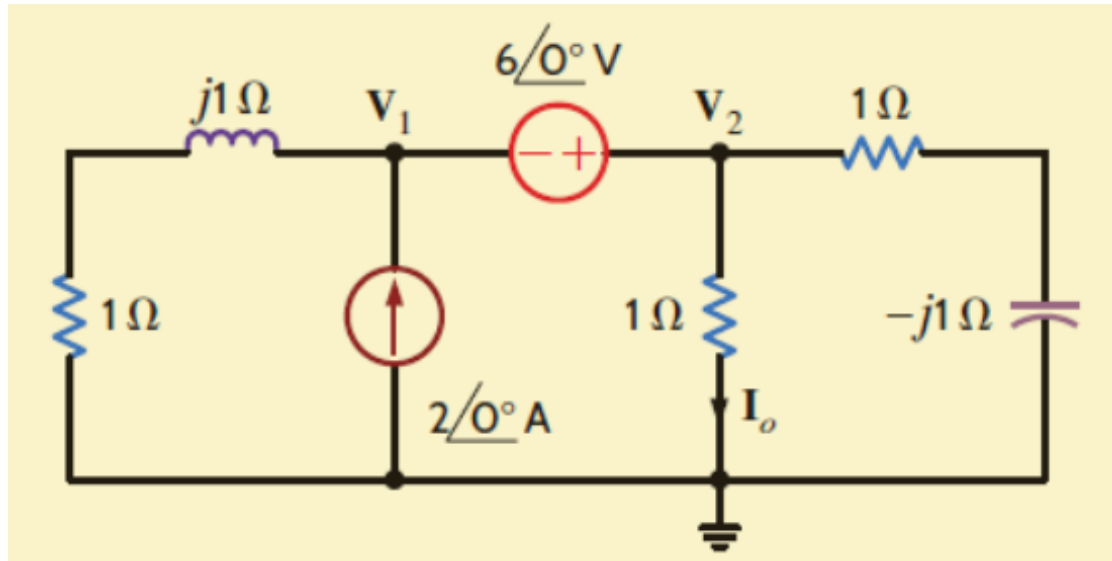
Example 8.15

For the given network determine I_o using nodal analysis.



Learning Assessment E8.20

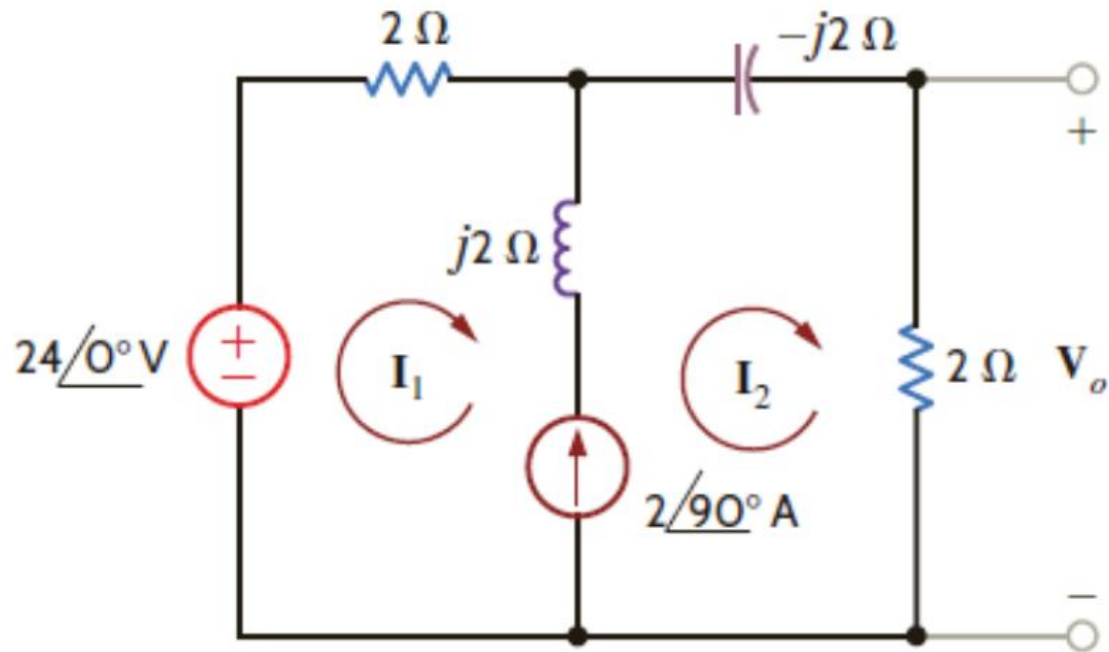For the given network use (a) mesh equations and (b) Thevenin's theorem to find V_o .



Learning Assessment E8.23

For the given network use (a) superposition and (b) source transformation to find V_o .

