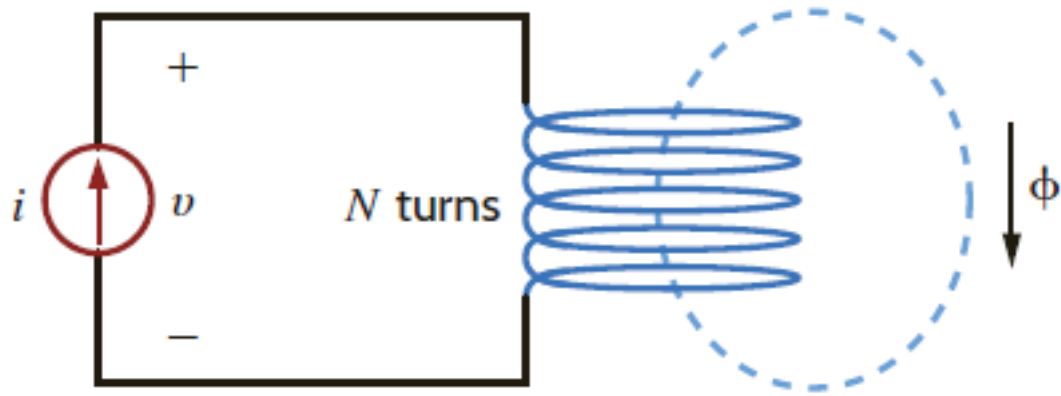


Magnetically Coupled Networks → Chapter #10

- **Mutual Inductance / Coefficient of Coupling / Turns Ratio**
- **Circuit Analysis with Mutual Inductance**
- **Circuit Analysis with Ideal Transformers**

Single Coil Behavior



Flux Linkage $\rightarrow \lambda$

$$\lambda = N \cdot \phi$$


coil turns

magnetic flux

$$\lambda = L \cdot i$$

$$\hookrightarrow \phi = \frac{L}{N} i$$

Single Coil Behavior

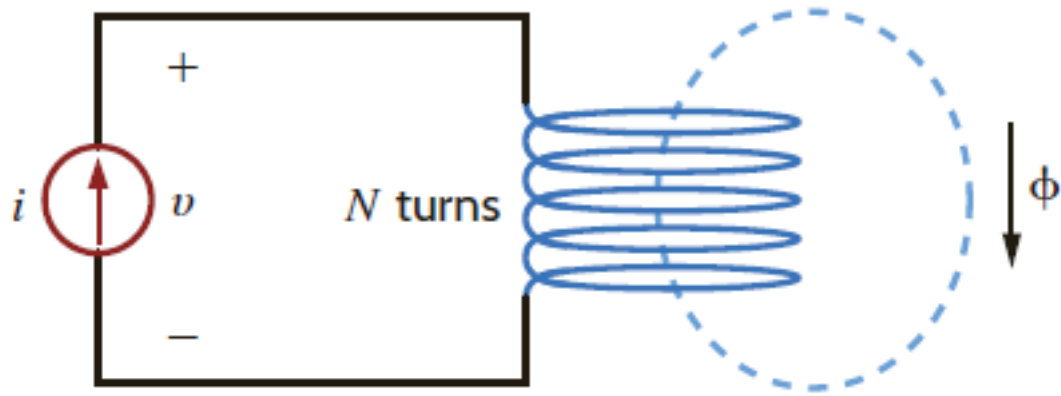

Flux Linkage $\rightarrow \lambda$

coil turns \rightarrow N

magnetic flux \rightarrow ϕ

$$\lambda = N \cdot \phi$$


$$\lambda = L \cdot i$$

$\hookrightarrow \phi = \frac{L}{N} i$


Faraday's Law $\rightarrow v = f(\lambda)$

$$v = \frac{d\lambda}{dt}$$

$$= L \frac{di}{dt} + i \frac{dL}{dt}$$

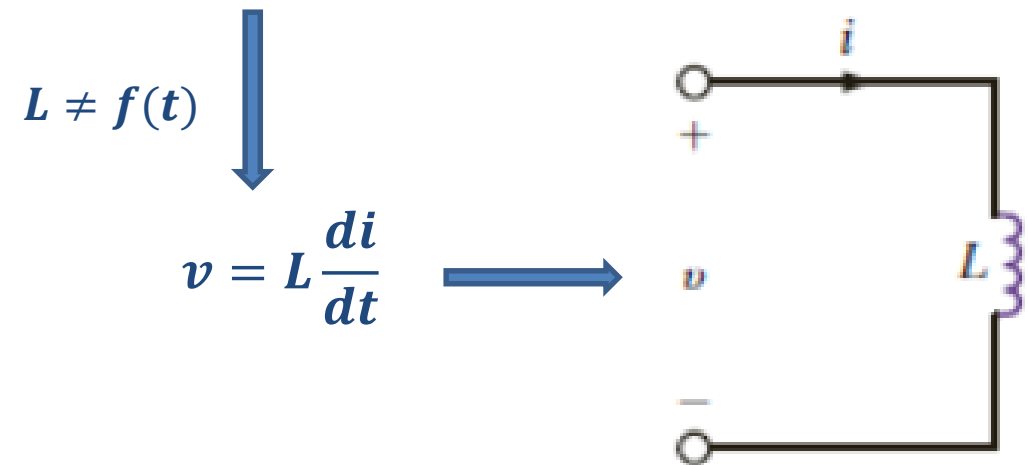

Two Coils → Magnetically Coupled

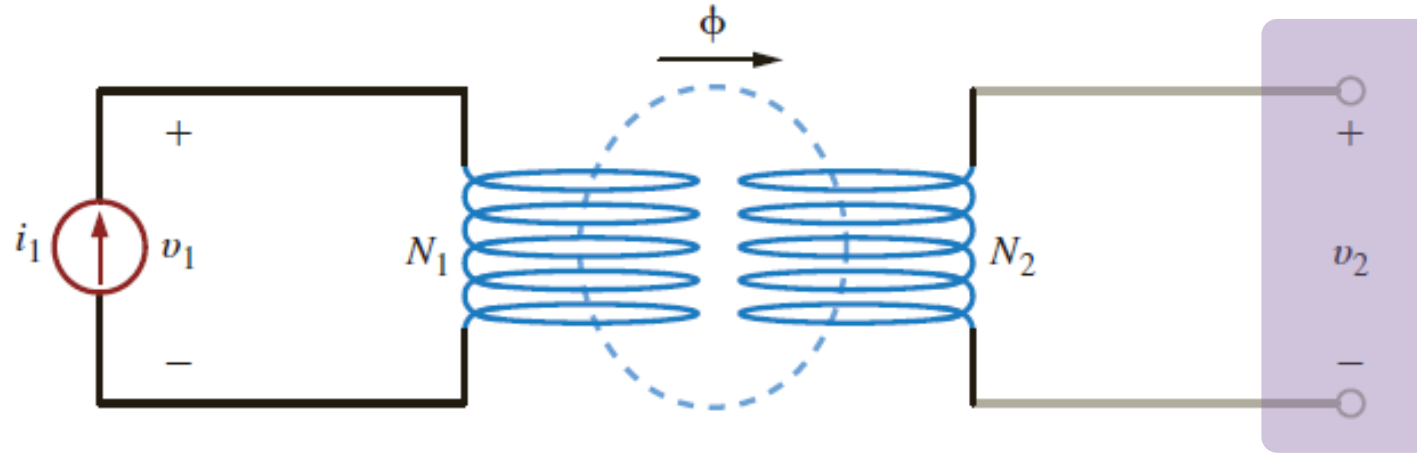

No Load!
→ $i_2 = 0$


$$\lambda_1 = N_1 \cdot \phi = L_1 \cdot i_1$$

$$v_1 = \frac{d\lambda_1}{dt}$$

$$\lambda_2 = N_2 \cdot \phi$$

$$v_2 = \frac{d\lambda_2}{dt}$$

Two Coils → Magnetically Coupled

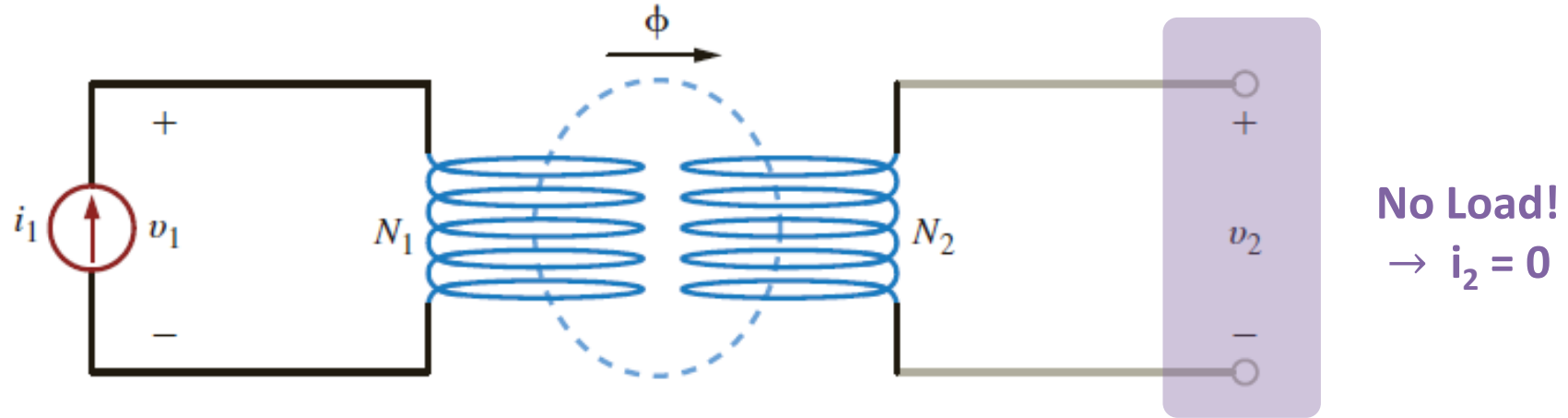

$$\lambda_1 = N_1 \cdot \phi = L_1 \cdot i_1$$

$$v_1 = \frac{d\lambda_1}{dt}$$

$$\lambda_2 = N_2 \cdot \phi$$


$$v_2 = \frac{d\lambda_2}{dt}$$

L_{21} → Mutual Inductance

$$v_2 = \frac{d\lambda_2}{dt} = \frac{d}{dt}(N_2 \cdot \phi) = \frac{d}{dt}\left(\frac{N_2}{N_1} \cdot \lambda_1\right) = \frac{d}{dt}\left(\frac{N_2}{N_1} \cdot L_1 \cdot i_1\right) = \frac{N_2}{N_1} L_1 \frac{di_1}{dt}$$

Magnetically Coupled Coils


Using Superposition

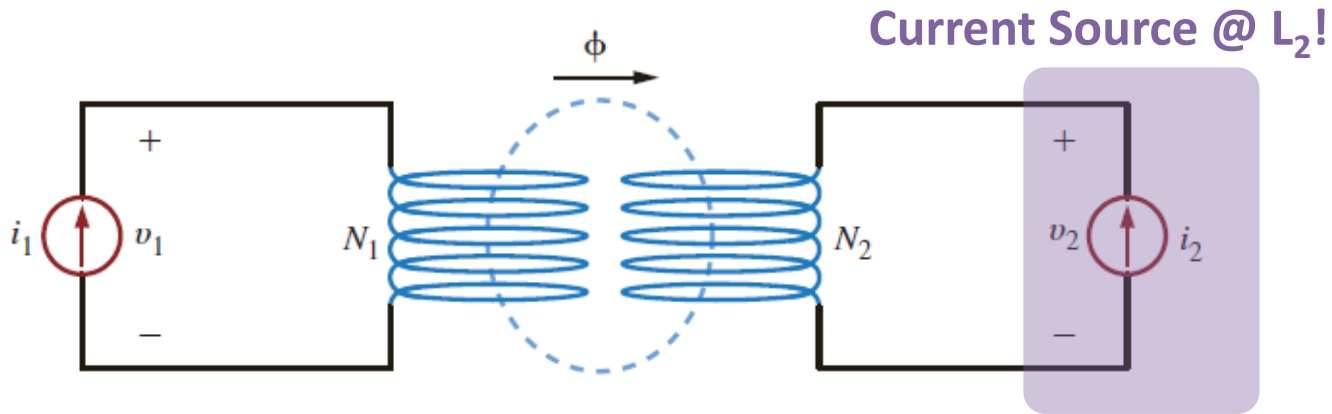

$$v_1 = L_1 \frac{di_1}{dt} + L_{12} \frac{di_2}{dt}$$

$$v_2 = L_2 \frac{di_2}{dt} + L_{21} \frac{di_1}{dt}$$

Magnetically Coupled Coils

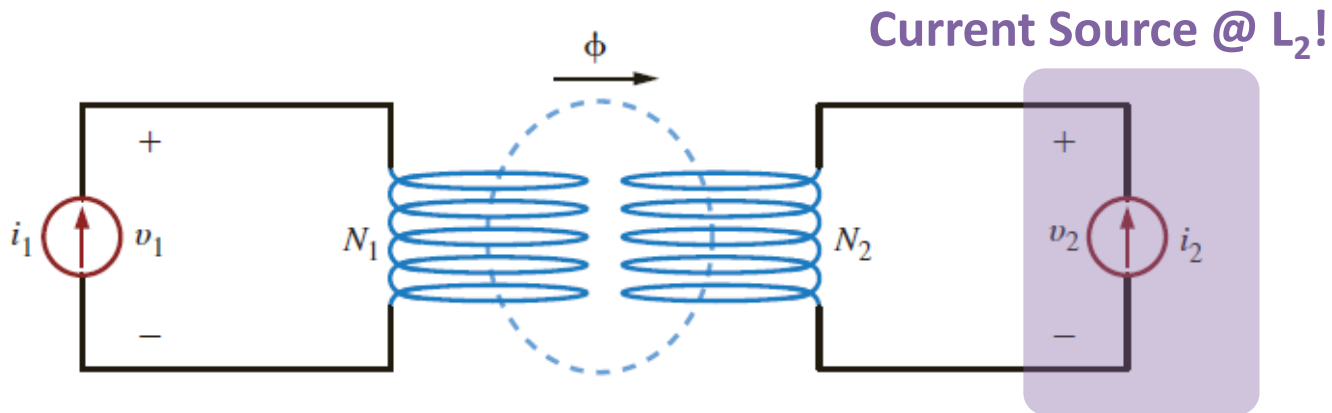

Using Superposition

$$v_1 = L_1 \frac{di_1}{dt} + L_{12} \frac{di_2}{dt}$$

$$v_2 = L_2 \frac{di_2}{dt} + L_{21} \frac{di_1}{dt}$$


Self Term
Mutual Term

$$L_{12} = L_{21} = M$$

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

Magnetically Coupled Coils

Using Superposition

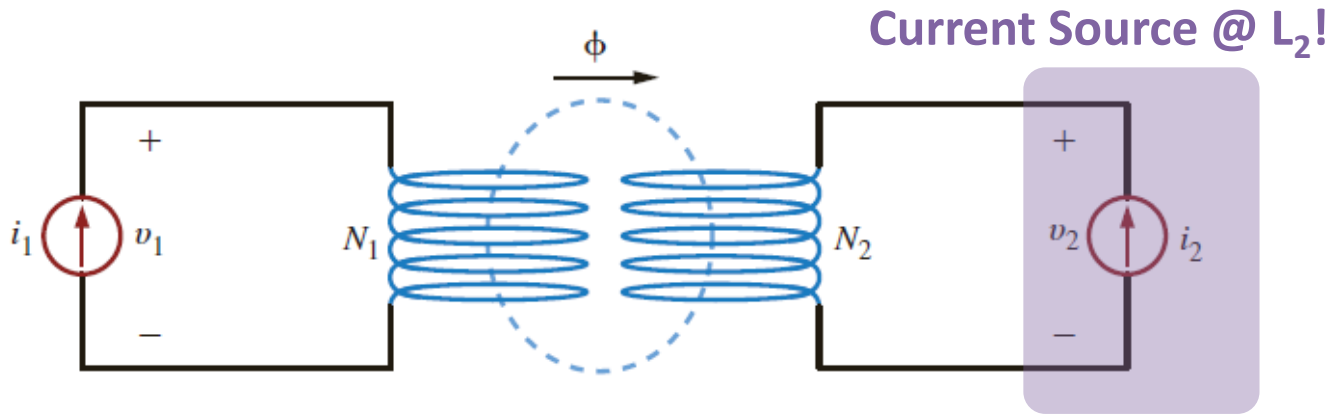


$$v_1 = L_1 \frac{di_1}{dt} + L_{12} \frac{di_2}{dt}$$

$$v_2 = L_2 \frac{di_2}{dt} + L_{21} \frac{di_1}{dt}$$

Self Term
Mutual Term


$L_{12} = L_{21} = M$
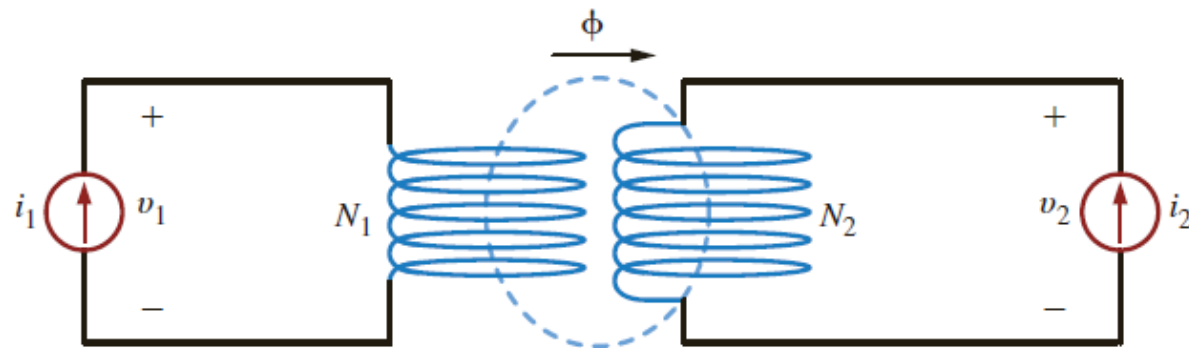
$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$




$$v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} \quad v_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

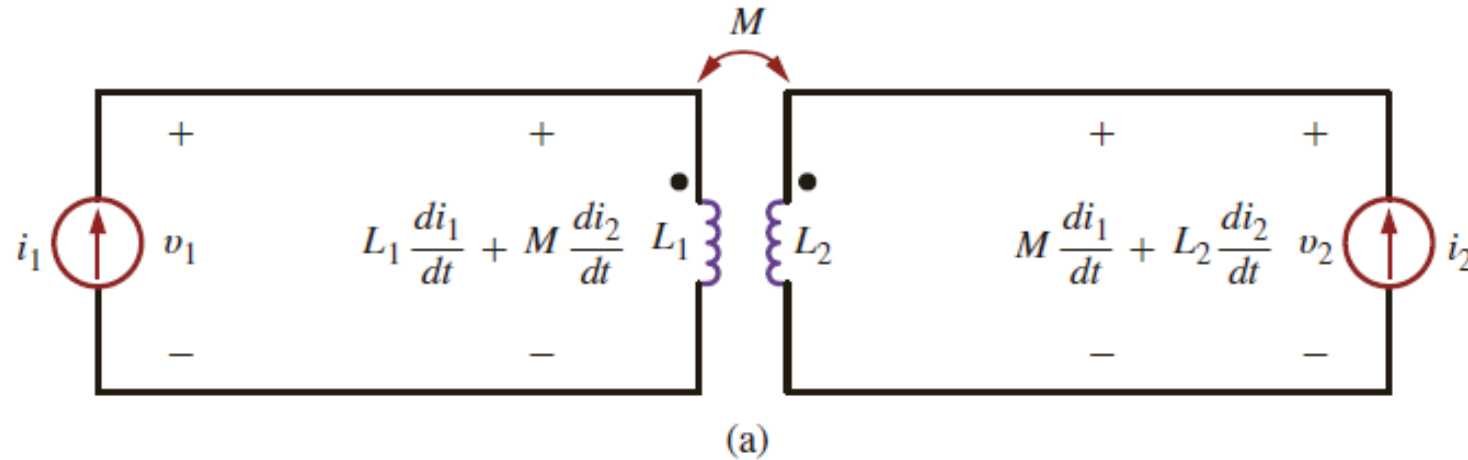Magnetically Coupled Coils → Circuit Diagram



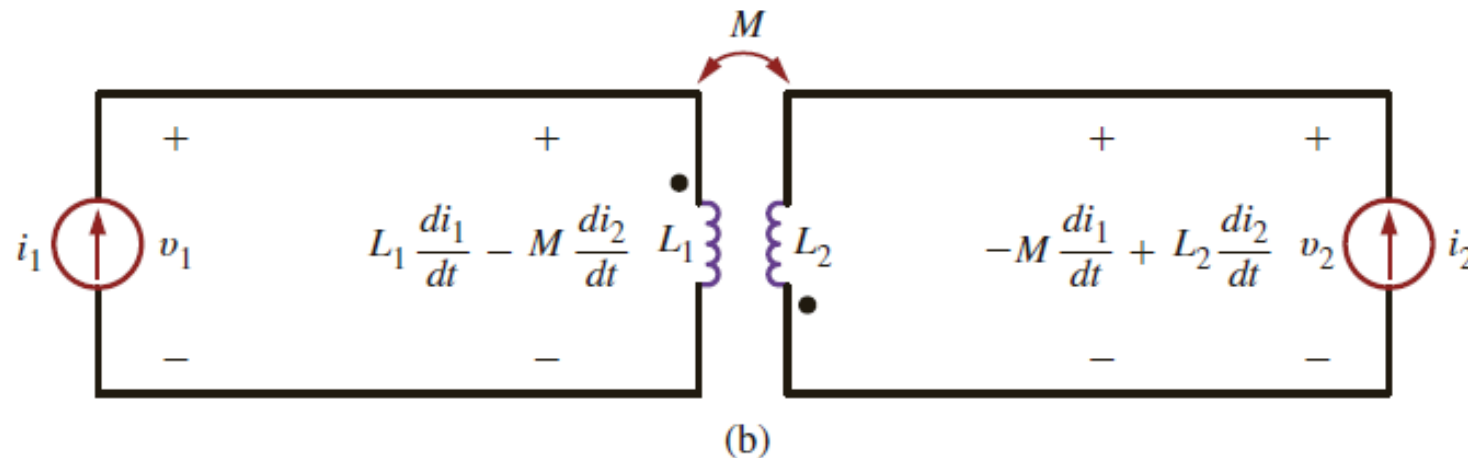
- Current enters the dotted terminal → voltage at coupled coil is positive at the dotted terminal



- Current enters the undotted terminal → voltage at coupled coil is positive at the undotted terminal


Example 10.4

Determine V_o for the given circuit.

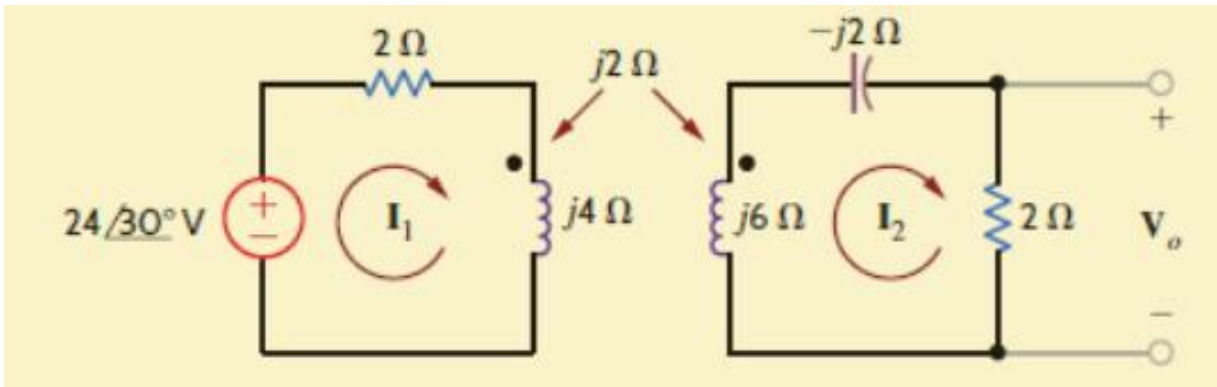

Example 10.4

Determine V_o for the given circuit.

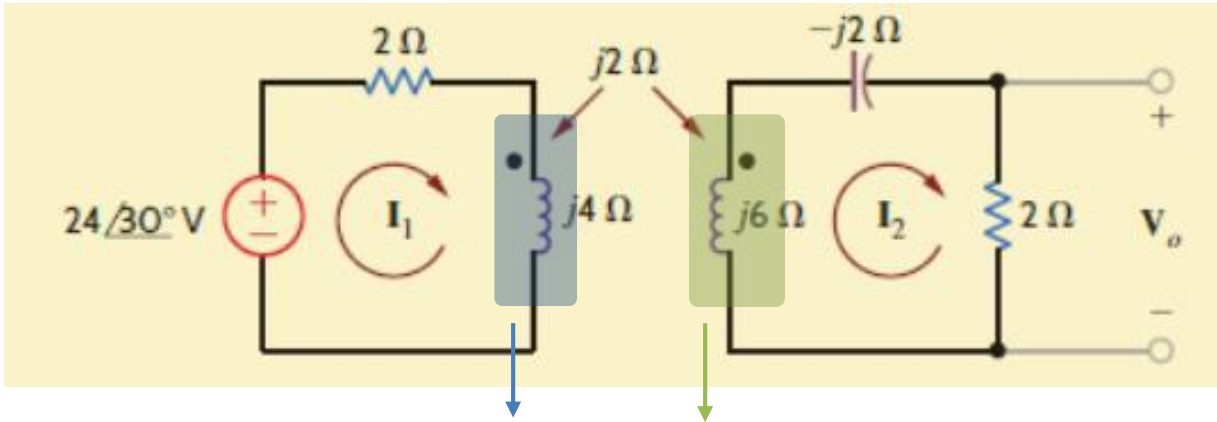


$$V_1 = jX_{L1}I_1 - jX_{LM}I_2$$


$$V_2 = jX_{L2}I_2 - jX_{LM}I_1$$

Learning Extension E10.7

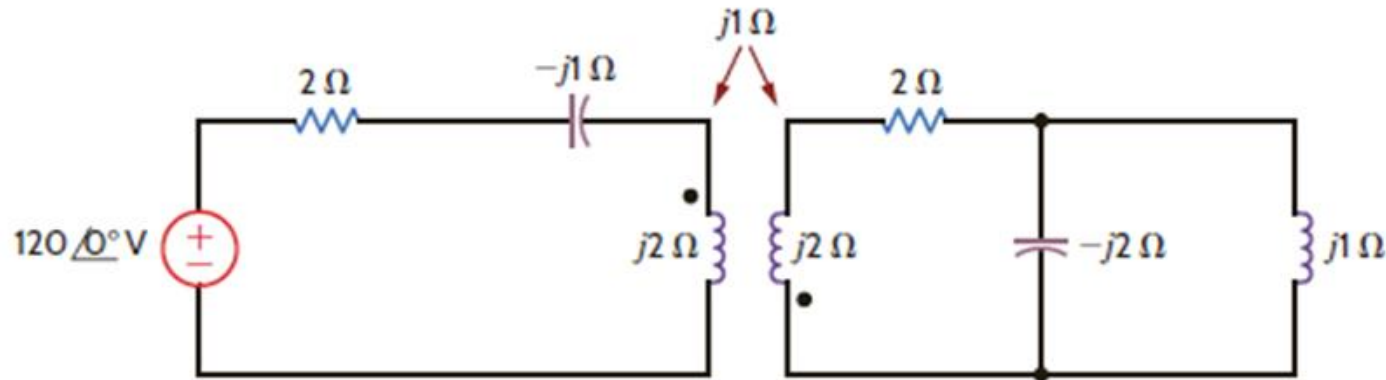Find the impedance seen by the source in the circuit below.



Magnetically Coupled Coils → Energy

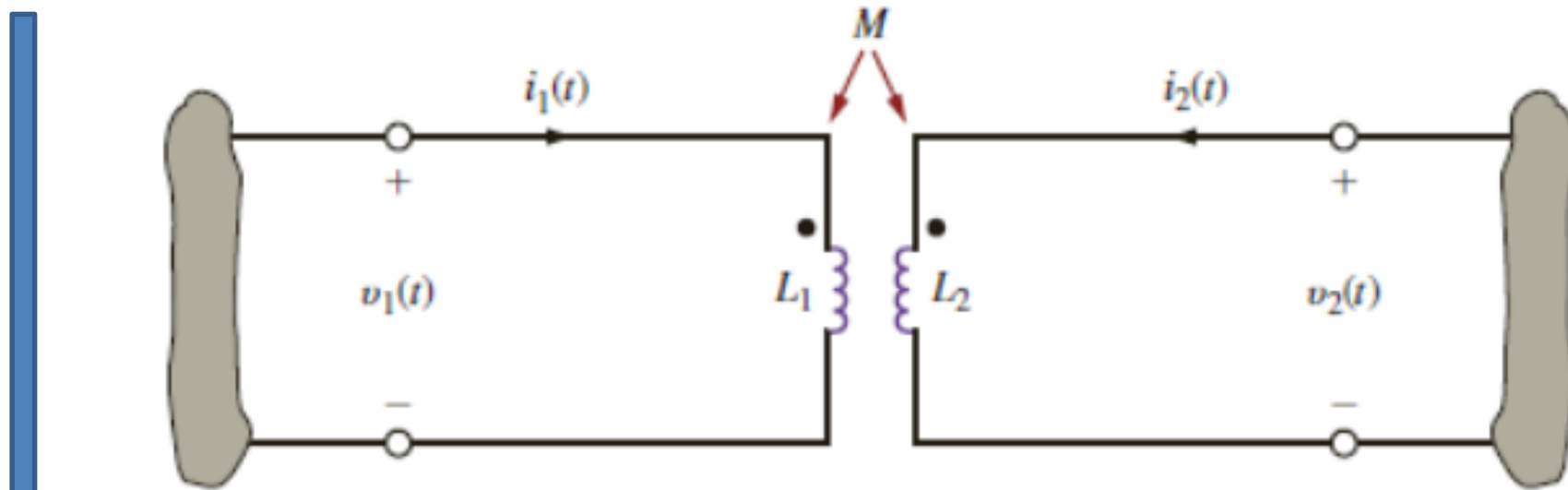


$$w(t) = \frac{1}{2} L_1 [i_1(t)]^2 + \frac{1}{2} L_2 [i_2(t)]^2 \pm M i_1(t) i_2(t)$$

Coefficient of Coupling $k = \frac{M}{\sqrt{L_1 L_2}} \quad 0 \leq k \leq 1$


Learning Assessment → E10.8

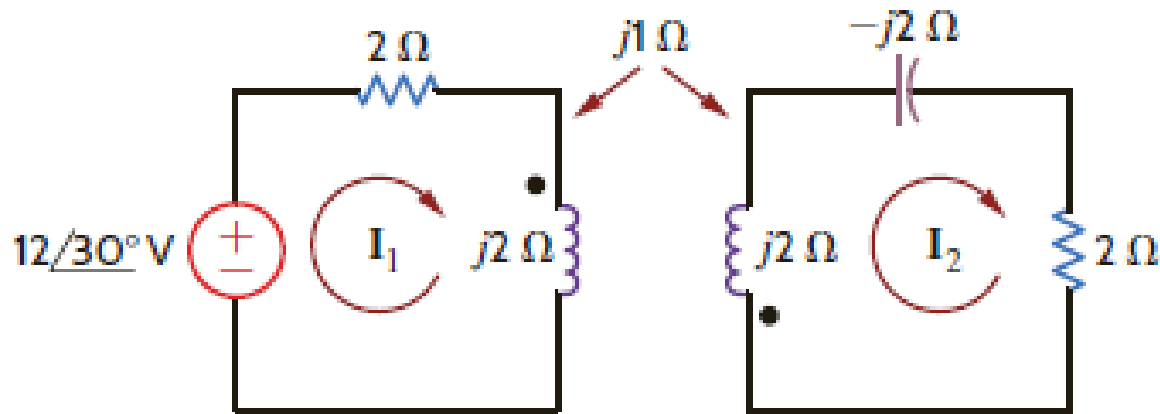Assuming the network operates at 60Hz, compute the energy stored in the mutually coupled inductors at time $t=10\text{ms}$.



Learning Assessment → E10.8

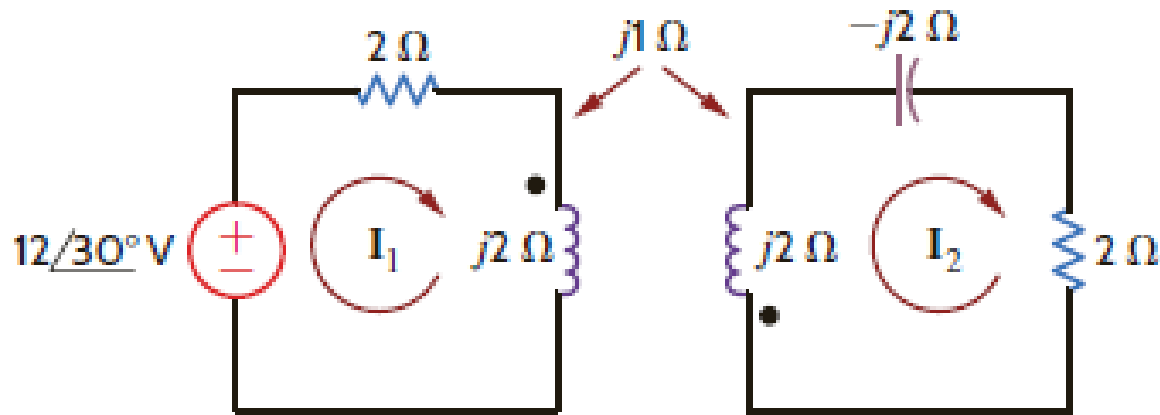Assuming the network operates at 60Hz, compute the energy stored in the mutually coupled inductors at time $t=10\text{ms}$.



$$\begin{aligned}
 I_1, I_2 &\rightarrow i_1(t), i_2(t) \\
 &\rightarrow i_1(t = 10\text{ms}), i_2(t = 10\text{ms}) \\
 &\rightarrow w(t = 10\text{ms})
 \end{aligned}$$

Problem → 10.41

Given the network shown below, determine the value of the capacitor C that will cause the impedance seen by the $24\angle 0^\circ$ V voltage source to be purely resistive, $f=60\text{Hz}$.

