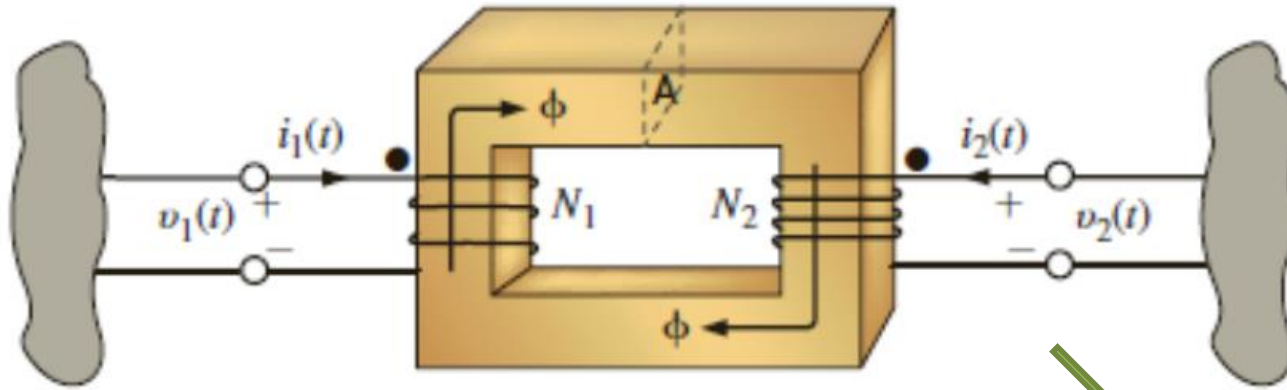


# Last Lecture → Ideal Transformer



Assuming an ideal magnetic core with infinite permeability...

$$\left. \begin{aligned} P_1 + P_2 &= 0 \\ v_1 \cdot i_1 + v_1 \cdot \frac{N_2}{N_1} \cdot i_2 &= 0 \end{aligned} \right\} \therefore \frac{i_2}{i_1} = -\frac{N_1}{N_2}$$


$$\lambda_1 = N_1 \cdot \phi$$

$$\lambda_2 = N_2 \cdot \phi$$

$$v_1 = \frac{d\lambda_1}{dt} = N_1 \frac{d\phi}{dt}$$

$$v_2 = \frac{d\lambda_2}{dt} = N_2 \frac{d\phi}{dt}$$

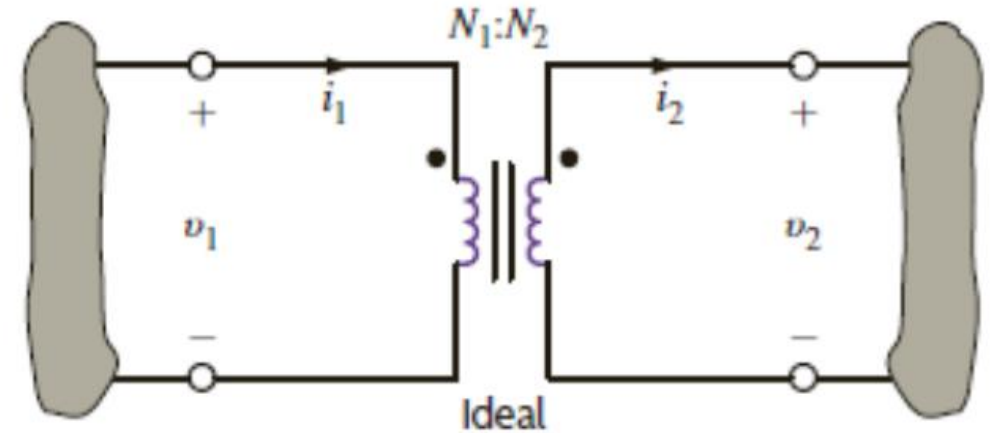
$$\therefore \frac{v_2}{v_1} = \frac{N_2}{N_1}$$



$$\frac{v_2}{v_1} = \frac{N_2}{N_1}$$

$$\frac{i_2}{i_1} = \frac{N_1}{N_2}$$

## Last Lecture → Ideal Transformer

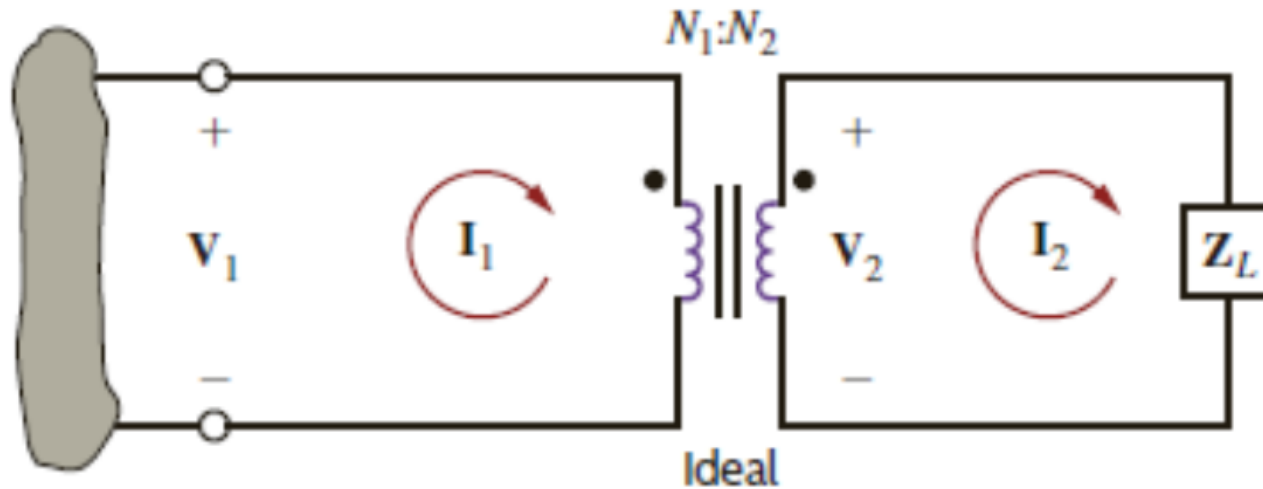

$$\frac{N_2}{N_1} = n \rightarrow V_2 = \frac{N_2}{N_1} V_1 = n \cdot V_1$$

$$I_2 = \frac{N_1}{N_2} I_1 = \frac{1}{n} \cdot I_1$$

$$Z_L = \frac{V_2}{I_2}$$


$$Z_1 = \frac{V_1}{I_1} = \frac{1}{n^2} Z_L$$

- *If both voltages are referenced positive at the dotted terminals or un-dotted terminals, then  $V_2/V_1 = N_2/N_1$ . If this is not true, then  $V_2/V_1 = -N_2/N_1$ .*
- *If both currents are defined as entering at dotted terminals or un-dotted terminals, then  $I_2/I_1 = -N_1/N_2$ . If this is not true, then  $I_2/I_1 = N_1/N_2$ .*
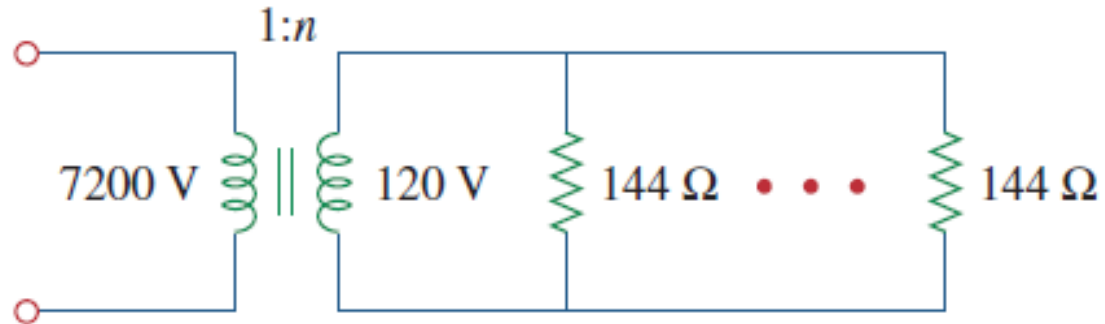
# Problem


Ten bulbs in parallel are supplied by a 7,200/120 V transformer as shown, where the bulbs are modeled by the  $144\ \Omega$  resistors. Find:

- the turns ratio  $n$ ,
- the current through the primary winding.


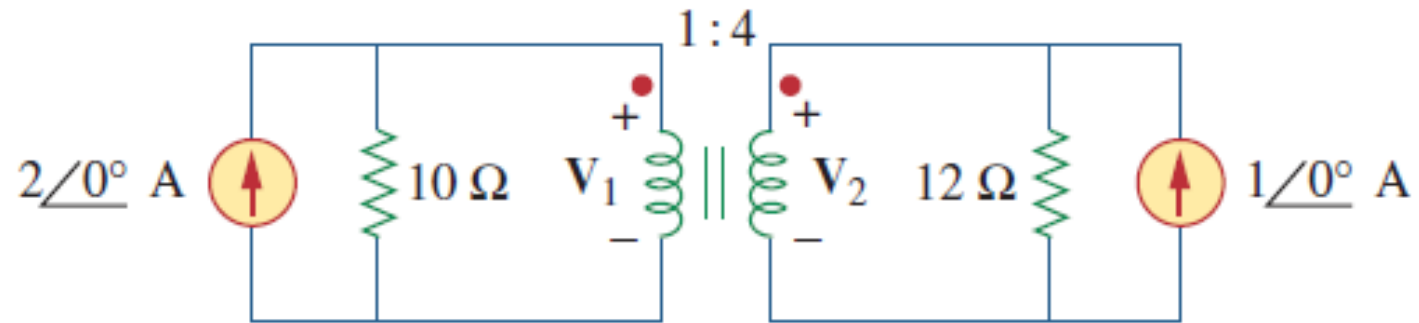
# Problem


Obtain  $V_1$  and  $V_2$  in the ideal transformer circuit provided.


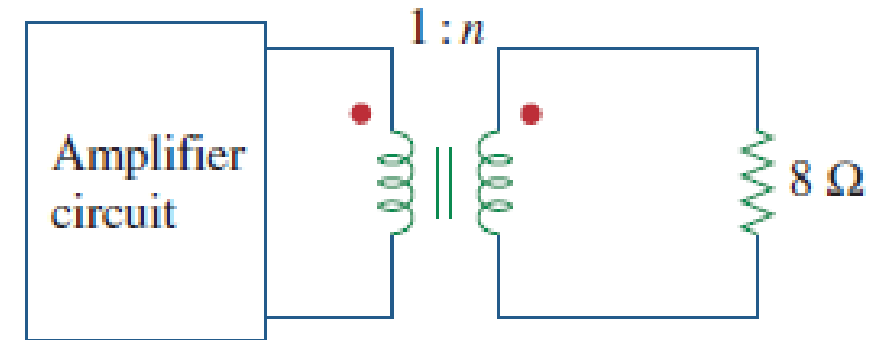
# Problem

A transformer is used to match an amplifier with an  $8\Omega$  load as shown in the figure provided. The Thevenin equivalent of the amplifier is:  $V_{th} = 10V$ ,  $Z_{th} = 128\Omega$ .

- Find the required turns ratio  $n$  for maximum energy power transfer
- Determine the primary and secondary currents
- Determine the primary and secondary voltages



# Problem

Find the Thevenin equivalent for the circuit provided at terminals a-b.

