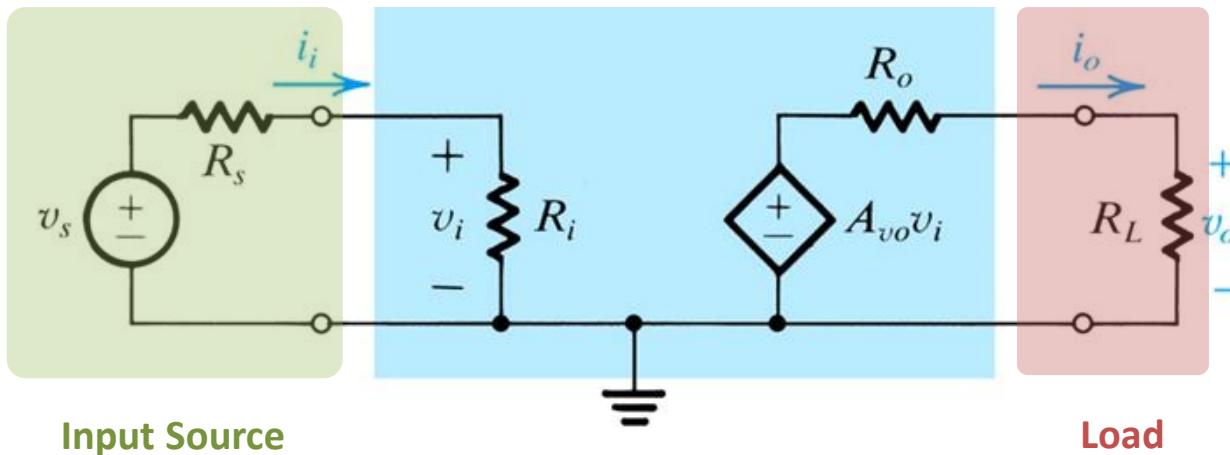


Last Lecture → Amplifier Circuit Model

8/16/2019

... is the description of the amplifier's terminal behavior, neglecting internal operation / transistor design

Amplifier Circuit Model




$$v_o = A_{vo} v_s \underbrace{\frac{R_i}{R_i + R_s} \frac{R_L}{R_L + R_o}}_{\text{non-ideal model}} = \underbrace{A_{vo} v_s}_{\text{ideal model}}$$

Amp. Loading Loading

Ideal Assumptions...

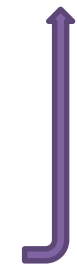- $R_i = \infty$ or $R_i \gg R_s$
- $R_o = 0$ or $R_o \ll R_L$



Last Lecture → Types of Amplifiers


8/16/2019

Voltage Amplifier

Gain → A_v [V/V]

$R_i = \infty$

$R_o = 0$

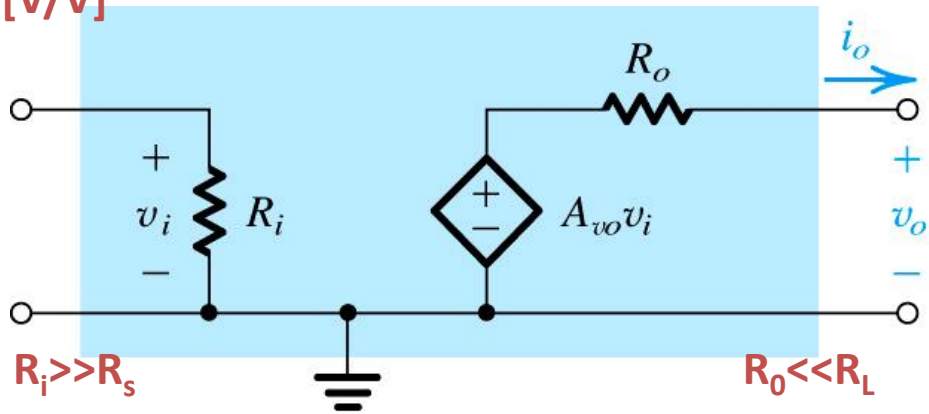


Current Amplifier

Gain → A_i [A/A]

$R_i = 0$

$R_o = \infty$

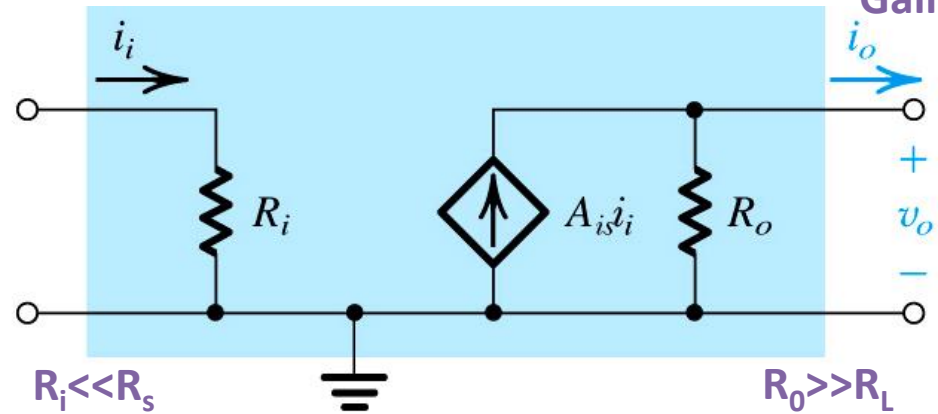


Trans-conductance Amplifier

Gain → A_v [A/V]

$R_i = \infty$

$R_o = \infty$

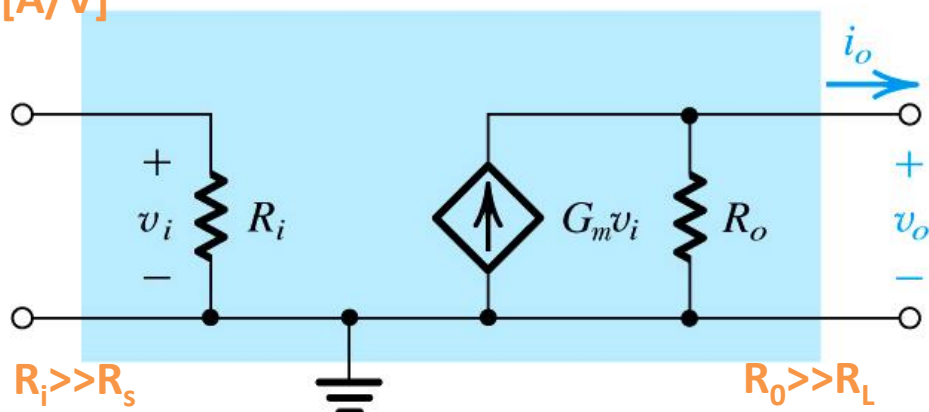


Trans-resistance Amplifier

Gain → A_v [V/A]

$R_i = 0$



$R_o = 0$

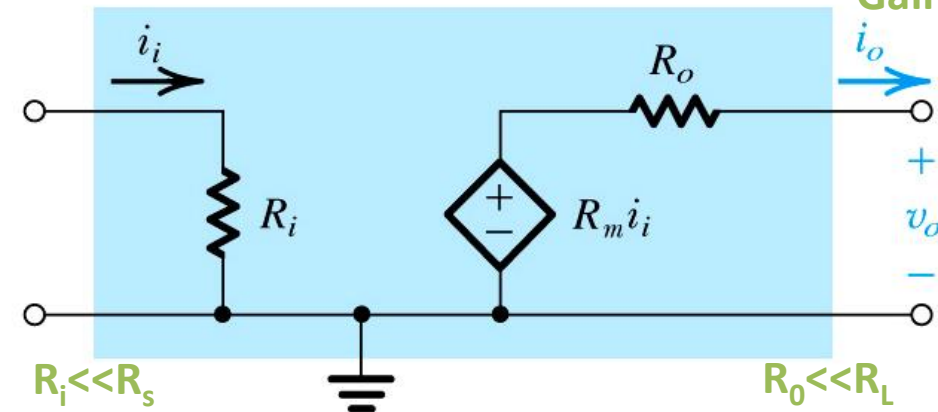

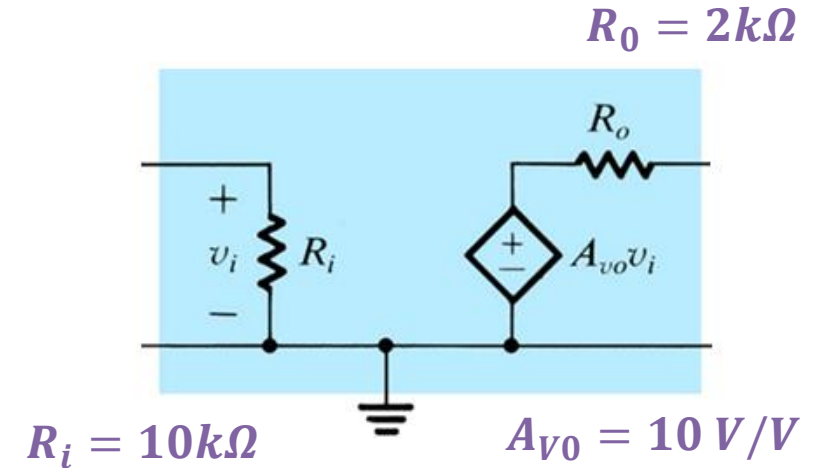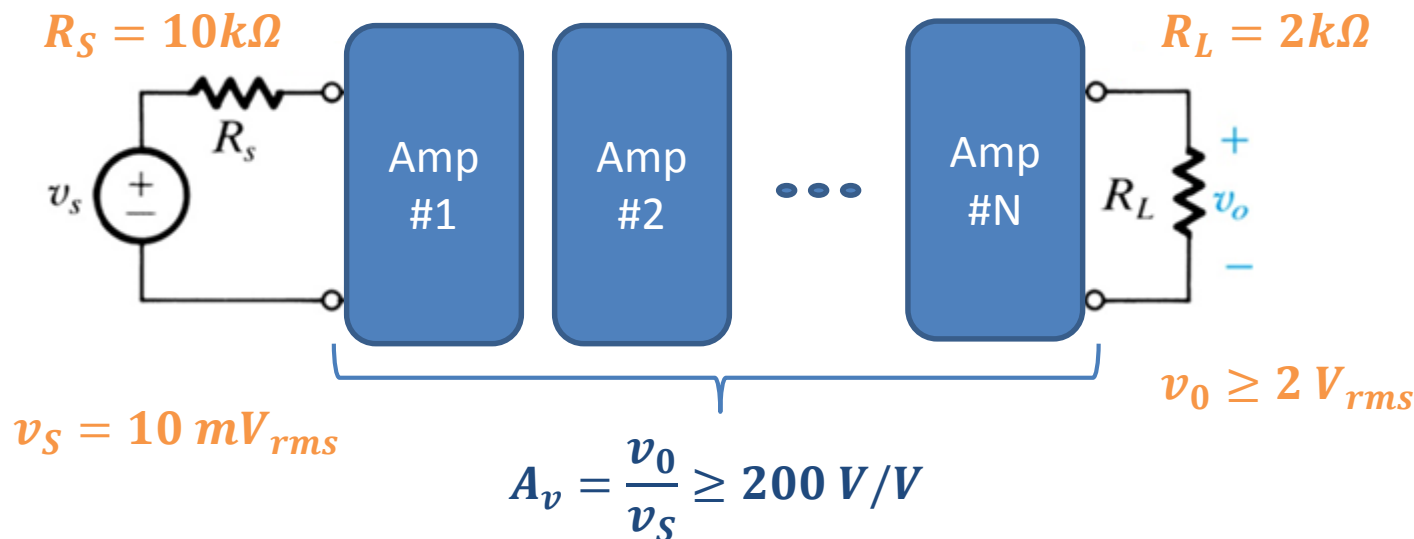Problem D1.49

8/16/2019

A designer has available voltage amplifiers with an input resistance of $10\text{k}\Omega$, an output resistance of $2\text{k}\Omega$, and an open-circuit voltage gain of 10V/V . The signal source has a $10\text{k}\Omega$ resistance and provides a $10\text{-mV}_{\text{rms}}$ signal, and it is required to provide a signal of at least 2V_{rms} to a $2\text{k}\Omega$ load. How many amplifier stages are required? What is the output voltage actually obtained?



- $N = 3$

$$A_v = \left[\frac{R_i}{R_i + R_S} \right] \left[A_{V0} \frac{R_i}{R_i + R_0} \right]^2 \left[A_{V0} \frac{R_L}{R_L + R_0} \right]$$

$$A_v = 172\text{ V/V}$$


- $N = 4$

$$A_v = \left[\frac{R_i}{R_i + R_S} \right] \left[A_{V0} \frac{R_i}{R_i + R_0} \right]^3 \left[A_{V0} \frac{R_L}{R_L + R_0} \right]$$

$$A_v = 1430\text{ V/V}$$

Input / Output Impedance

8/16/2019

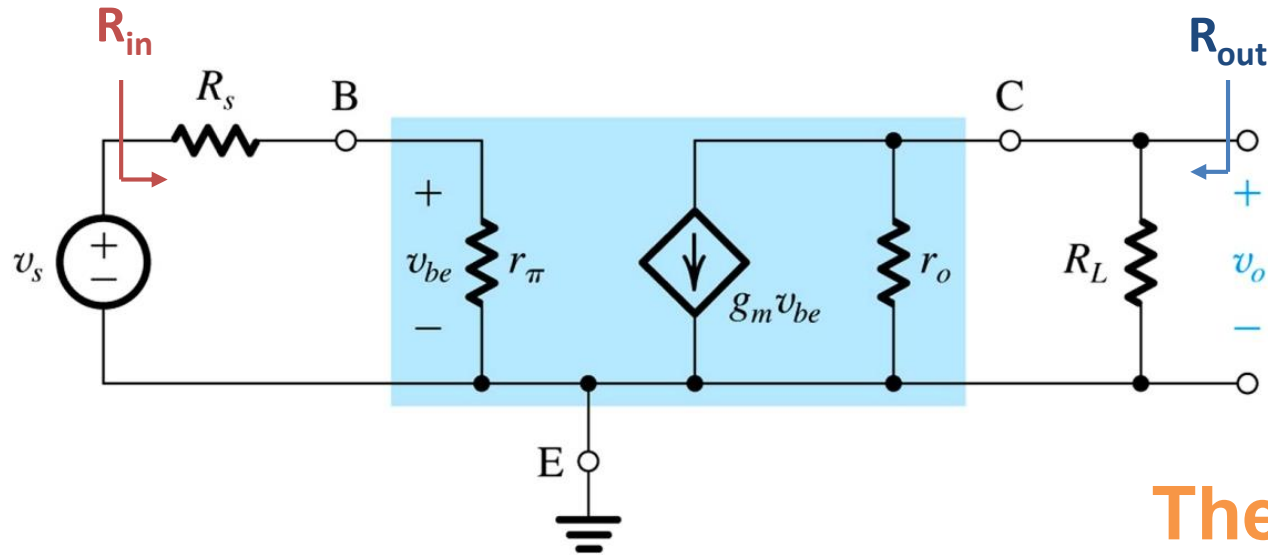

R_{in} → input impedance

R_{out} → output impedance

Thevenin's Resistance


- No dependent Source
 R_{th} → series / parallel combination
- Dependent Source
Place test source $V_x=1V$ at terminals

$$R_{th} = \frac{V_x}{I_x} = \frac{1}{I_x}$$
- For R_{out} turn "off" input source!

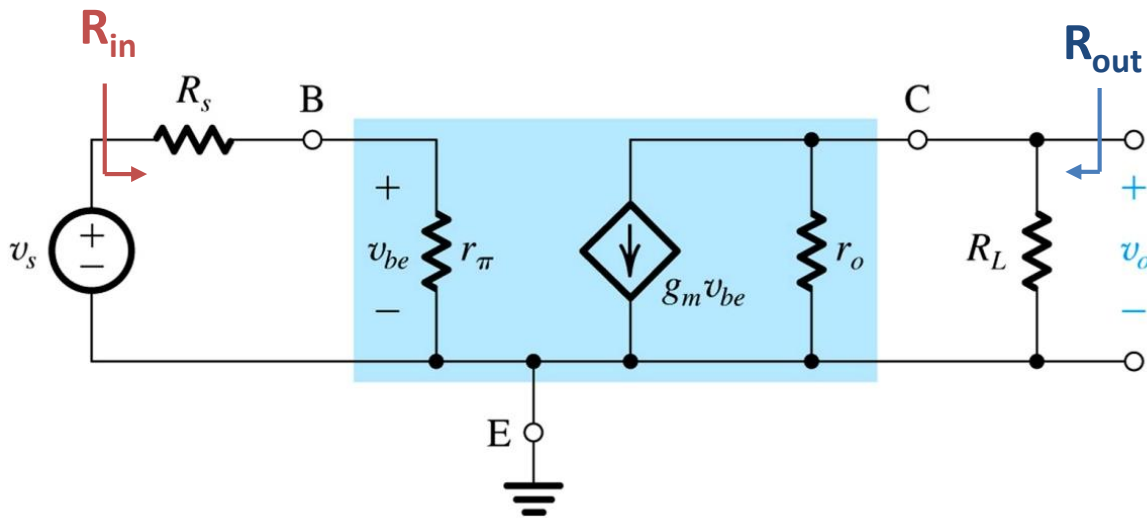Example 1.4

8/16/2019

For the following circuit derive an expression for the voltage gain v_o/v_s , and evaluate its magnitude for the case $R_s=5\text{k}\Omega$, $r_\pi=2.5\text{k}\Omega$, $g_m=40\text{mA/V}$, $r_o=100\text{k}\Omega$, and $R_L=5\text{k}\Omega$. What would be the gain value if the effect of r_o were neglected? Calculate the value for the impedance seen by the source and at the output terminals.



$$A_v = \frac{v_o}{v_s} = \left[\frac{v_o}{v_{be}} \right] \left[\frac{v_{be}}{v_s} \right] = \left[\frac{r_\pi}{r_\pi + R_s} \right] [-g_m r_o \parallel R_L]$$

$$= [0.33][190] = -63 \text{ V/V}$$

for $r_o \gg R_L \rightarrow$

$$A_v = [0.33][200] = -66 \text{ V/V}$$


$$R_{in} = R_s + r_\pi = 7.5 \text{ k}\Omega$$

$$R_{out} = r_o \parallel R_L = 4.76 \text{ k}\Omega$$

Input / Output Impedance

8/16/2019

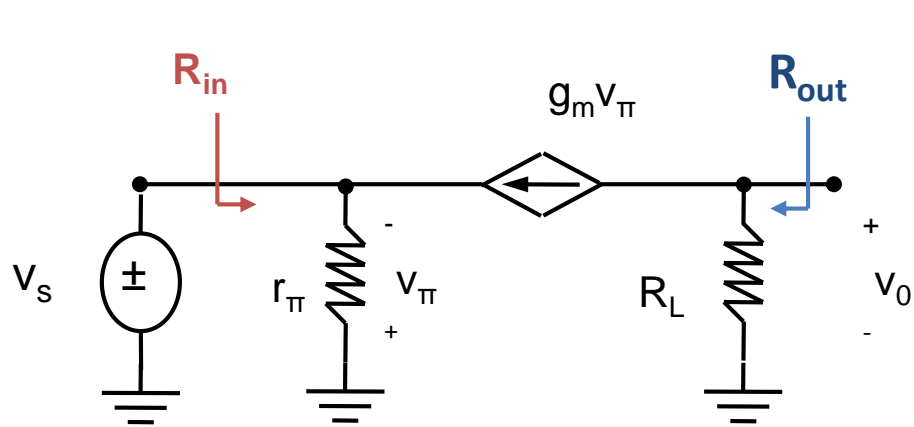For the circuit provided find the expression for the input and output resistances, R_{in} and R_{out} respectively.



$$R_{out} = \frac{1}{I_y} = R_L$$

$$R_{in} = \frac{1}{I_x} = \frac{1}{g_m} \left[\frac{1}{1 + \frac{1}{g_m r_{\pi}}} \right]$$

$$\text{for } g_m r_{\pi} \gg 1 \rightarrow R_{in} \approx \frac{1}{g_m}$$