

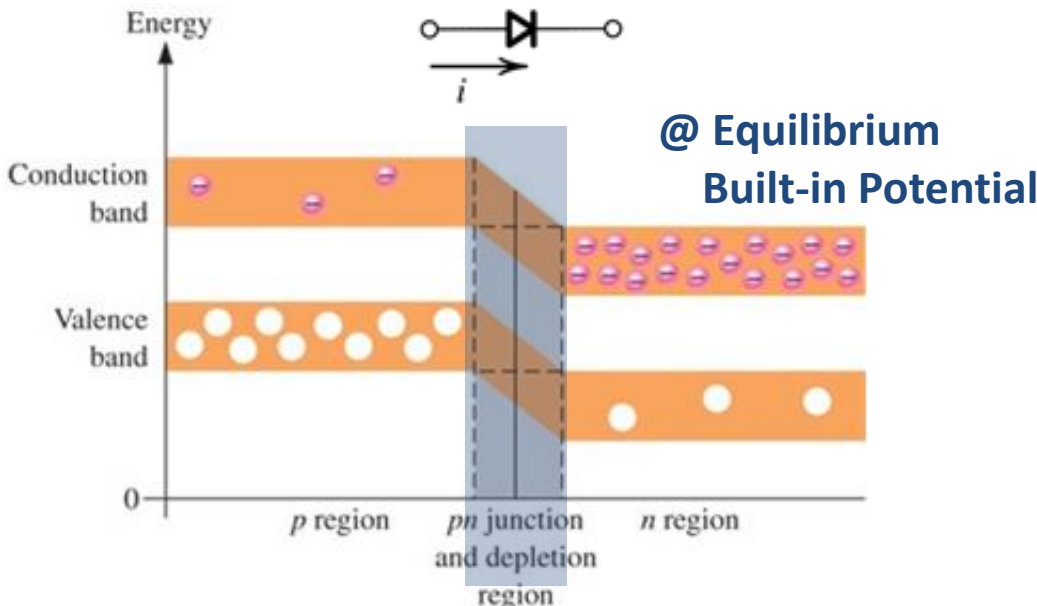
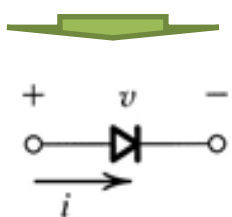


Last Lecture → PN Junction


8/23/2019

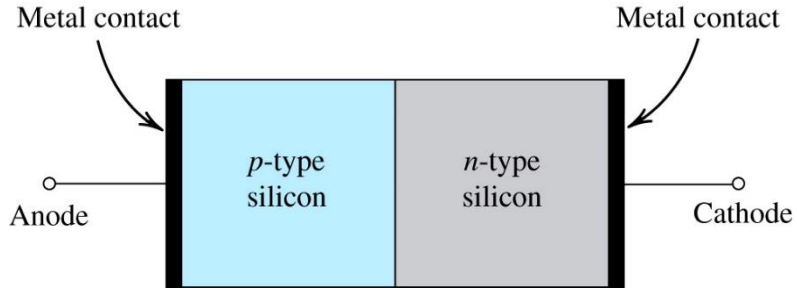

- **Reversed Biased** → $V_d < 0$

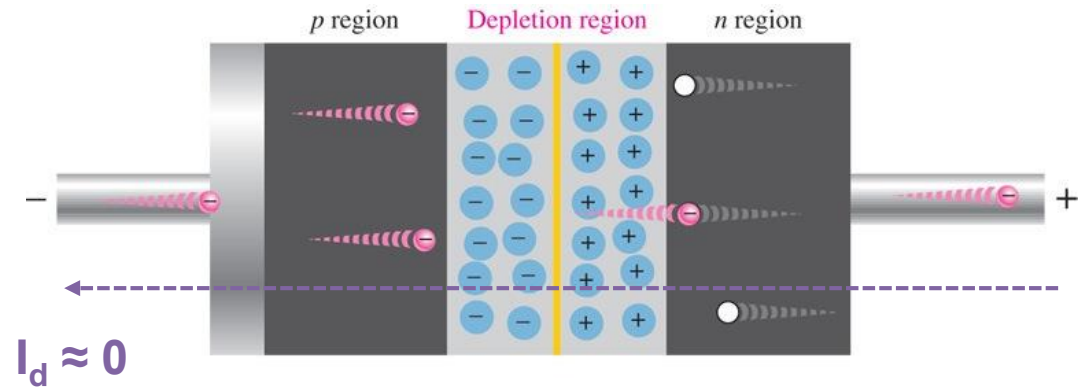


- **Forward Biased** → $V_d > V_0$

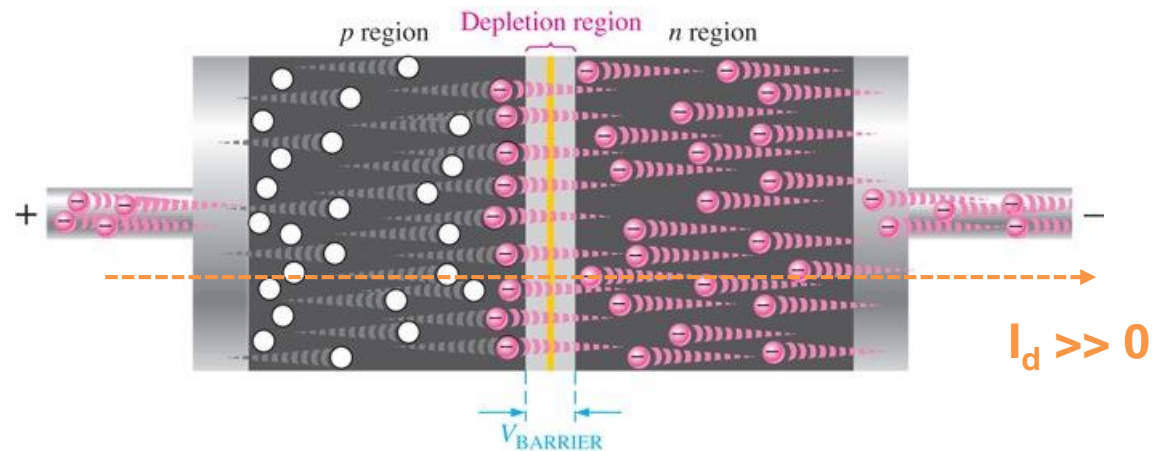

Last Lecture → Diode Behavior



8/23/2019

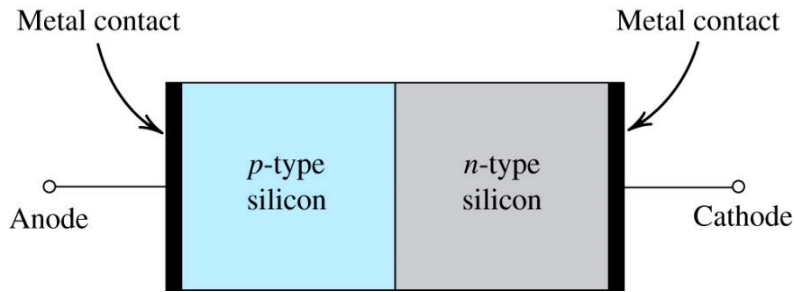

Characteristic Regions

- **Forward Bias:** $v > 0$
- **On** $v \geq 0.5V$
- **Reverse Bias:** $v < 0$
- **Breakdown:** $v \ll 0$

Zener-Knee Voltage (V_{ZK})

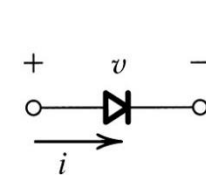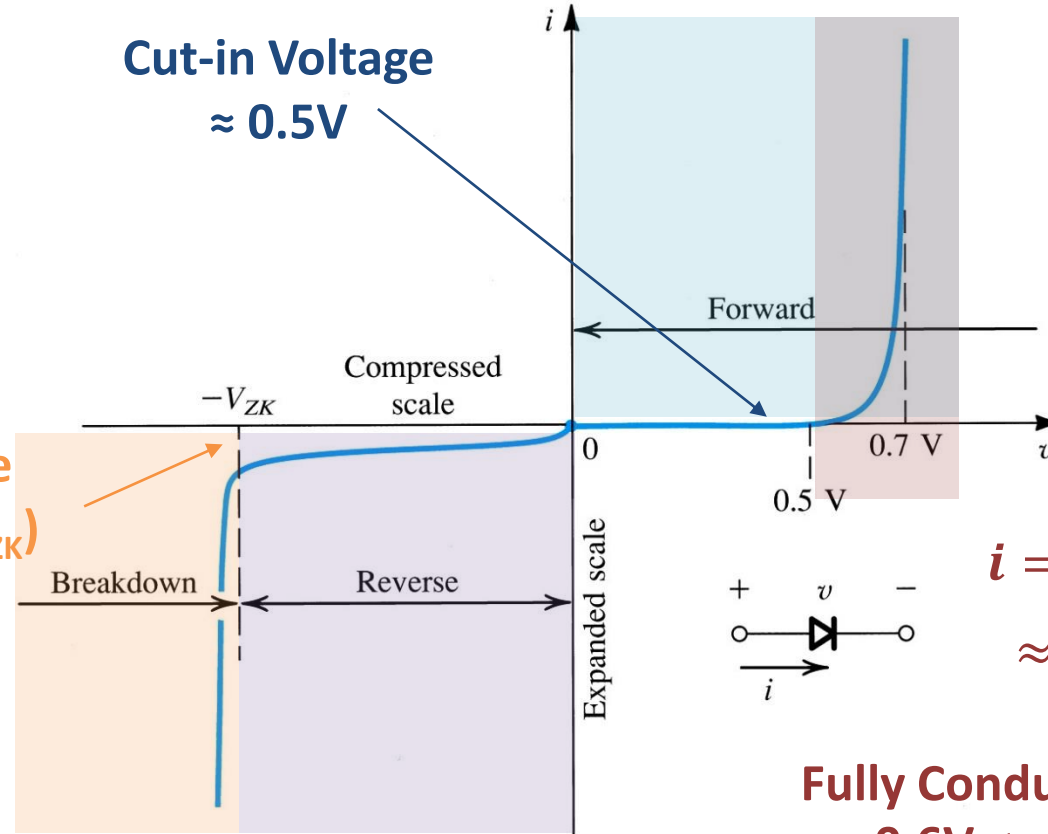

$$i = I_S(e^{v/V_T} - 1)$$

$$\approx I_S e^{v/V_T}$$

Fully Conducting Region
 $0.6V < v < 0.8V$

$$i = -I_S e^{-|v|/V_T}$$

$$i \approx -I_S$$


- $I_S \rightarrow$ saturation current
- $V_T \rightarrow$ thermal voltage

Last Lecture → Exponential Model

8/23/2019

- DC Analysis
 - Ideal Model
 - Constant-Voltage-Drop Model
 - Exponential Model
 - Graphical Analysis
 - Numerical Analysis
- AC Analysis
 - Small Signal Model

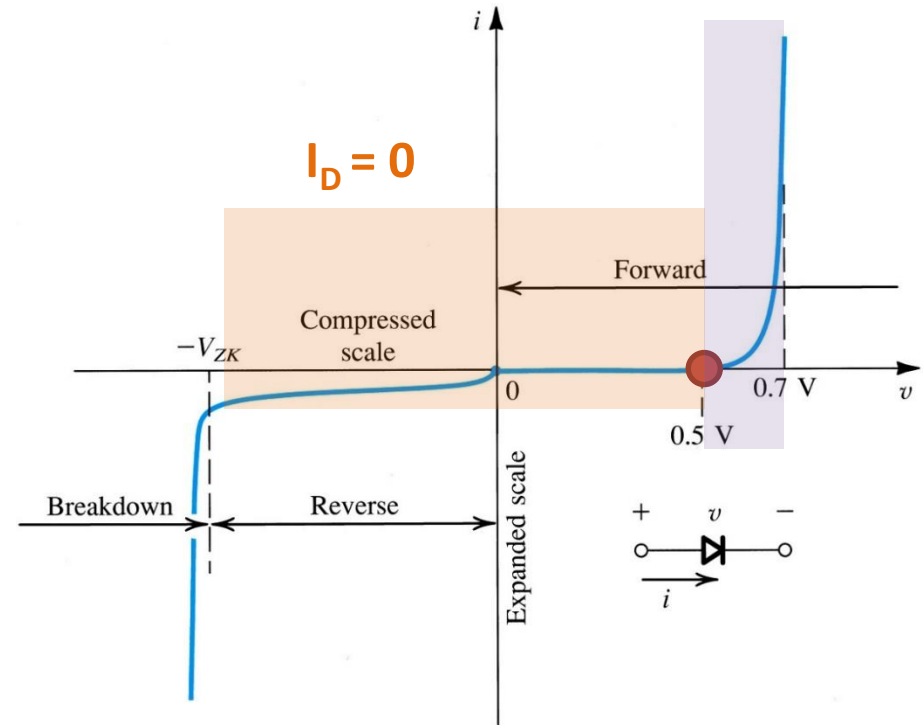Your simulation results are as good as your model!!!!



Exponential Model

for $v < 0.5$ → $I_D \approx 0$


for $v \geq 0.5$ → $I_D \approx I_S e^{v_D/V_T}$

Problem

8/23/2019

Assuming that the diodes available have 0.7V drop at 1mA,


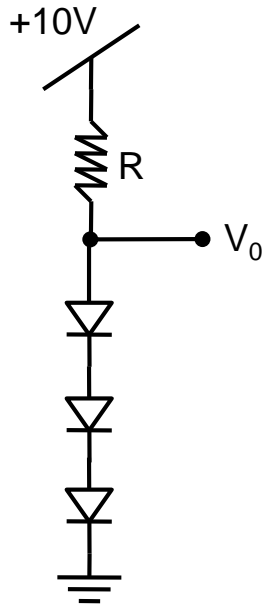
- design the given circuit to provide an output voltage of 2.4V
- find the output voltage for $R = 642\Omega$



Diode Models


8/23/2019

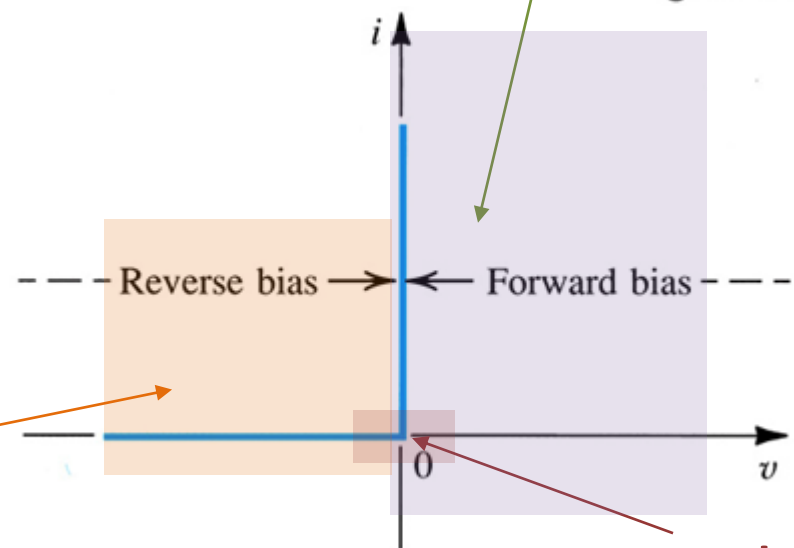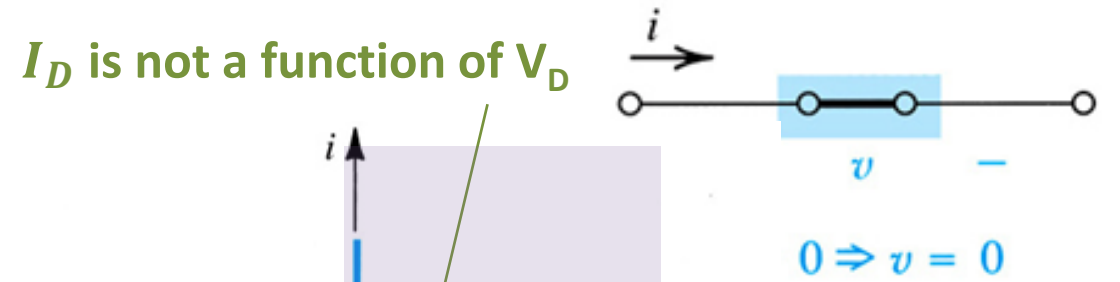- DC Analysis
 - ✓ Ideal Model
 - Constant-Voltage-Drop Model
 - ✓ Exponential Model
 - Graphical Analysis
 - ✓ Numerical Analysis
- AC Analysis
 - Small Signal Model



No reverse current

No voltage drop when conducting current

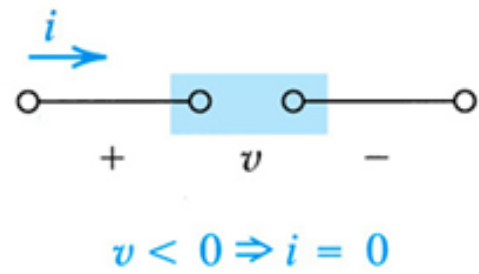


Ideal Model

for $v < 0 \rightarrow I_D = 0$
 for $I_D > 0 \rightarrow v = 0$


Solving Circuits with Diodes

8/23/2019

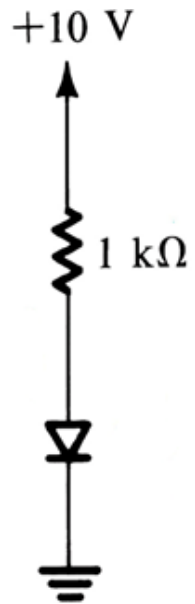1. Choose a model for the diode
2. Make an educated guess of the region of operation of the diode
3. Solve the circuit via mesh / nodal analysis
4. Verify if the condition of the region of operation are satisfied!



(a)

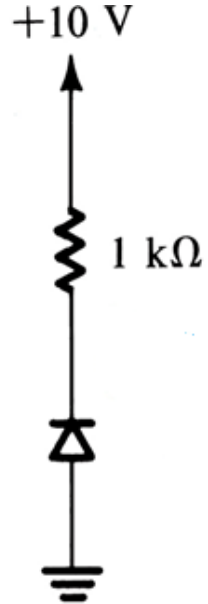

(b)


For the given circuits, determine the current flowing through the resistor.

Solving Circuits with Diodes

8/23/2019

1. Choose a model for the diode
2. Make an educated guess of the region of operation of the diode
3. Solve the circuit via mesh / nodal analysis
4. Verify if the condition of the region of operation are satisfied!

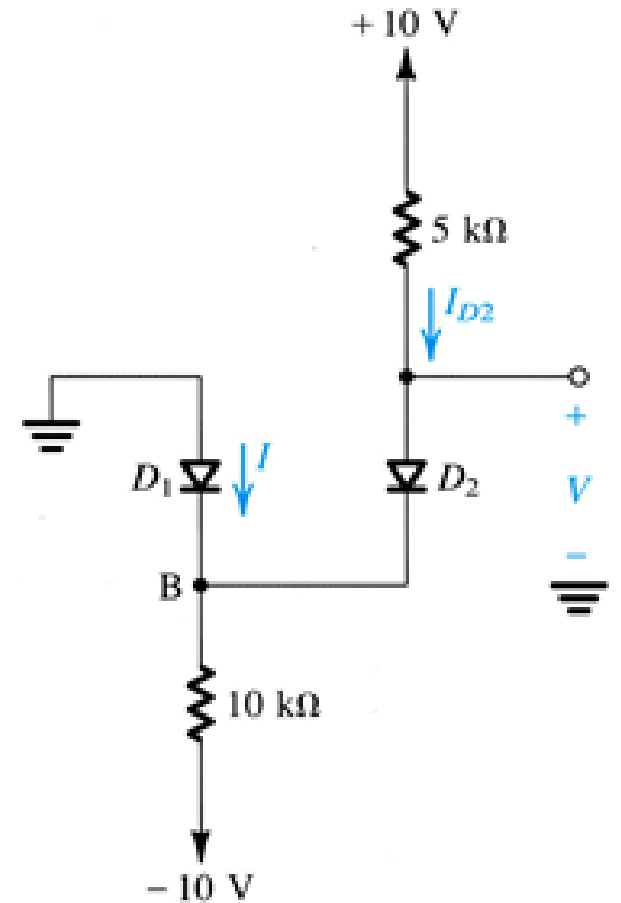Example 4.2 - Assuming the diodes to be ideal, find the values of I and V in the given circuits ...



(b)