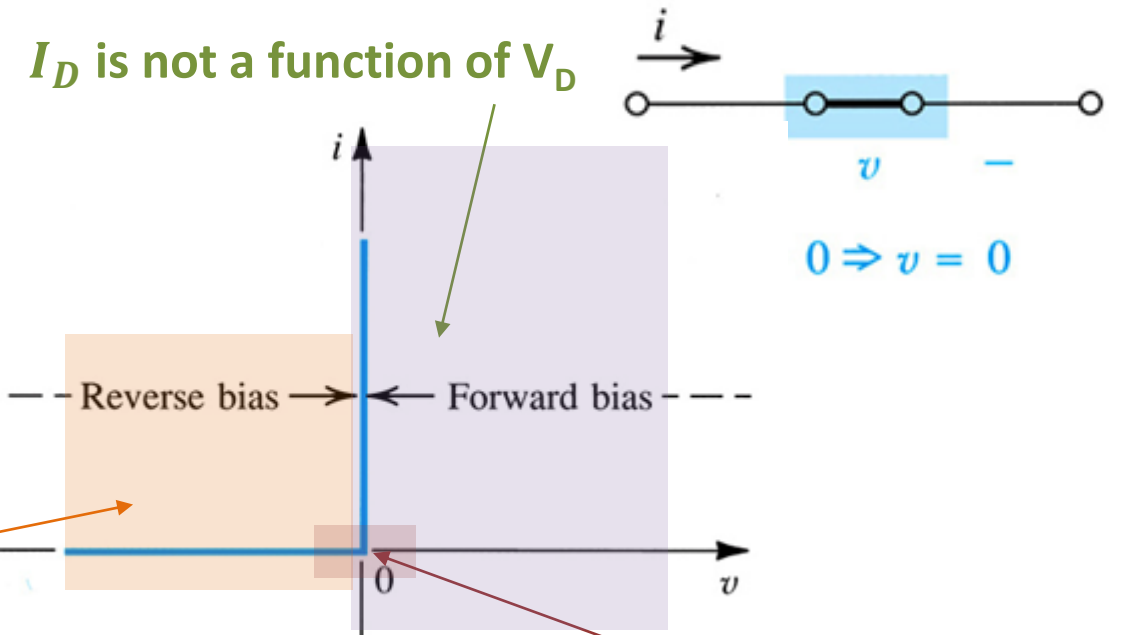



Last Lecture → Ideal Model

8/26/2019

- DC Analysis
 - ✓ Ideal Model
 - Constant-Voltage-Drop Model
 - ✓ Exponential Model
 - Graphical Analysis
 - ✓ Numerical Analysis
- AC Analysis
 - Small Signal Model



No reverse current

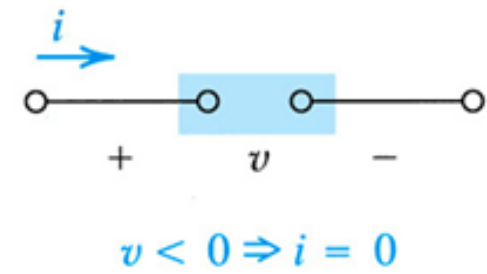

No voltage drop when conducting current

Ideal Model

for $v < 0 \rightarrow I_D = 0$


for $I_D > 0 \rightarrow v = 0$

Solving Circuits with Diodes

8/26/2019


1. Choose a model for the diode
2. Make an educated guess of the region of operation of the diode
3. Solve the circuit via mesh / nodal analysis
4. Verify if the condition of the region of operation are satisfied!

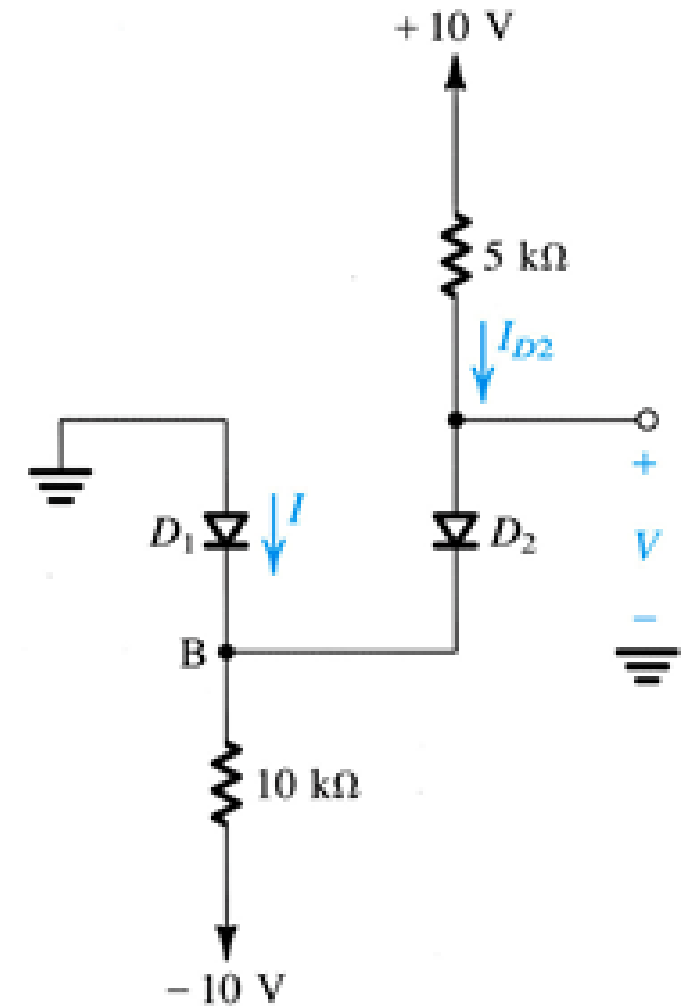Example 4.2 - Assuming the diodes to be ideal, find the values of I and V in the given circuits ...




Diode Logic Gates

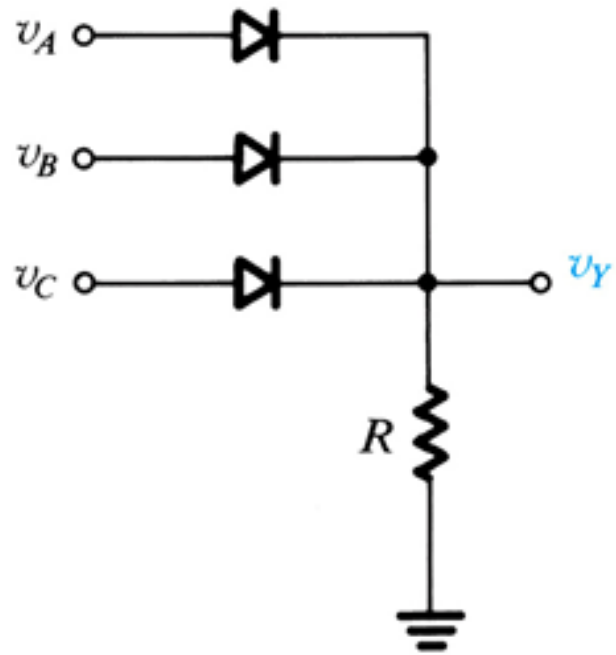Diodes together with resistors can be used to implement logic functions...




(a)

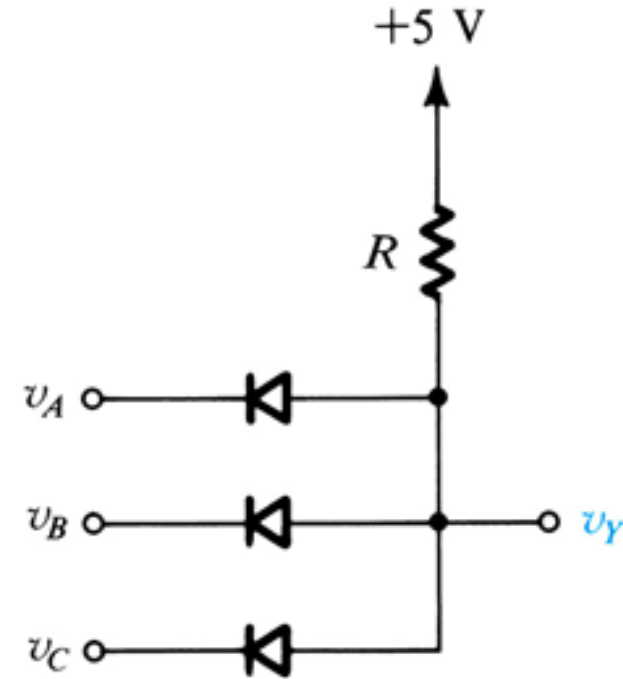

(b)

Constant-Voltage-Drop Model

8/26/2019

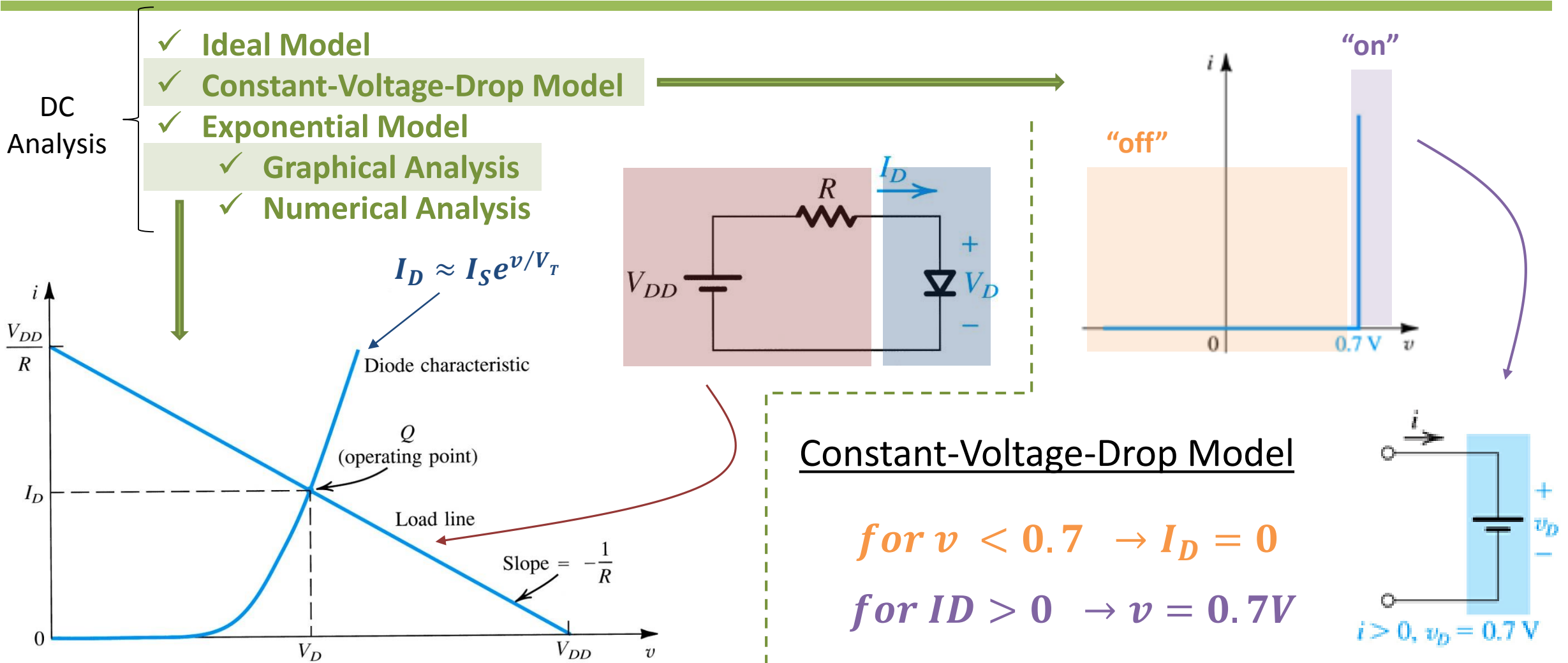

Diode Models → Comparison


8/26/2019

For the given circuit determine I_d using all three models of the diodes. Assume

- $V_{DD} = 5V$
- $R = 1k\Omega$

Assume

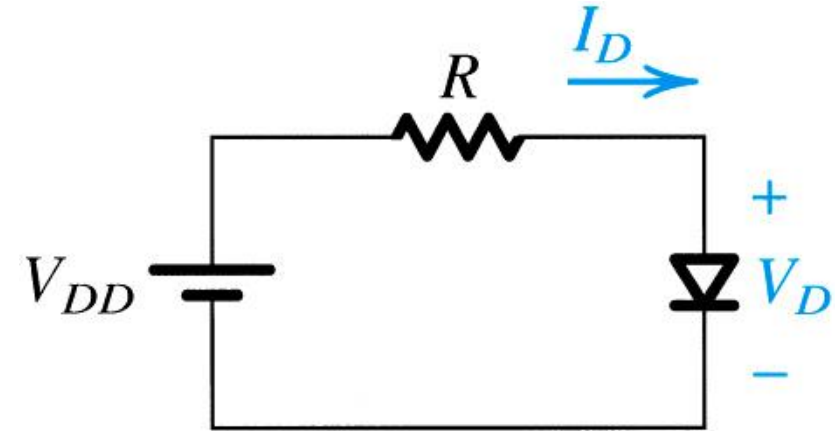- $V_D = 0.7V$ (constant voltage model)
- $I_{DQ} = 1mA$ @ $0.7V$ (exponential model)



Model	I_d (mA)
Ideal	5.00
Constant Voltage Drop	4.30
Exponential	4.26

Linear model pretty close to the actual value!

Diode Application → Rectifier

8/26/2019

For the given circuit:

- 1) Plot v_o vs v_i
- 2) Plot $v_o(t)$
- 3) Plot $v_d(t)$

