
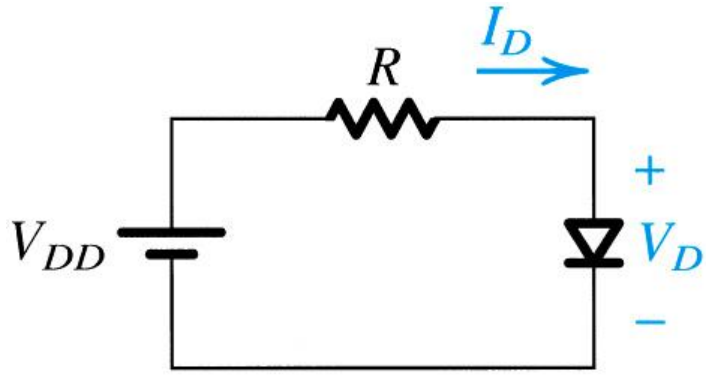


Last Lecture

8/26/2019

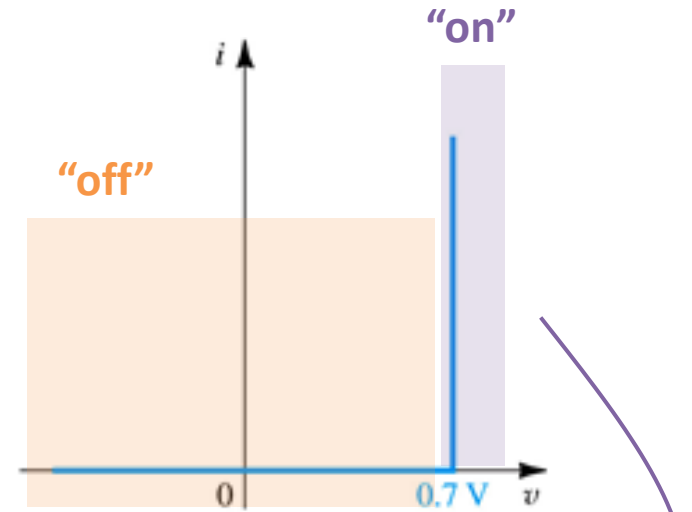
- DC Analysis
- ✓ Ideal Model
 - ✓ Constant-Voltage-Drop Model
 - ✓ Exponential Model
 - ✓ Graphical Analysis
 - ✓ Numerical Analysis



Constant-Voltage-Drop Model

for $v < 0.7 \rightarrow I_D = 0$

for $I_D > 0 \rightarrow v = 0.7V$

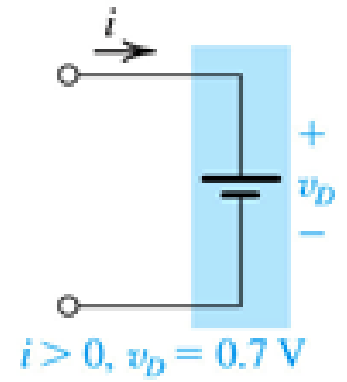


Diode Application → Rectifier

8/26/2019

For the given circuit, assuming ideal diode behavior plot:

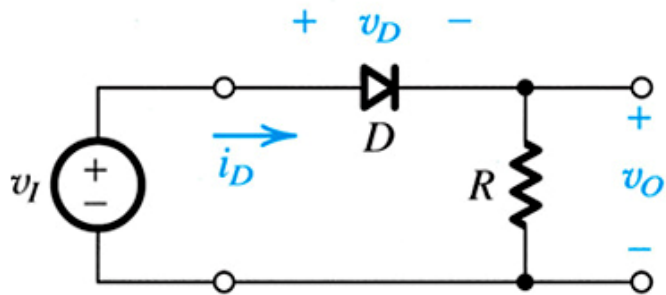- 1) v_o vs v_i
- 2) $v_o(t)$
- 3) $v_d(t)$



$D = \text{on} \rightarrow v_i > 0$

$$v_o = v_i$$


$$v_D = 0$$

$$I_D = \frac{v_i}{R}$$

$D = \text{off} \rightarrow v_i < 0$

$$v_o = 0$$

$$v_D = v_i$$


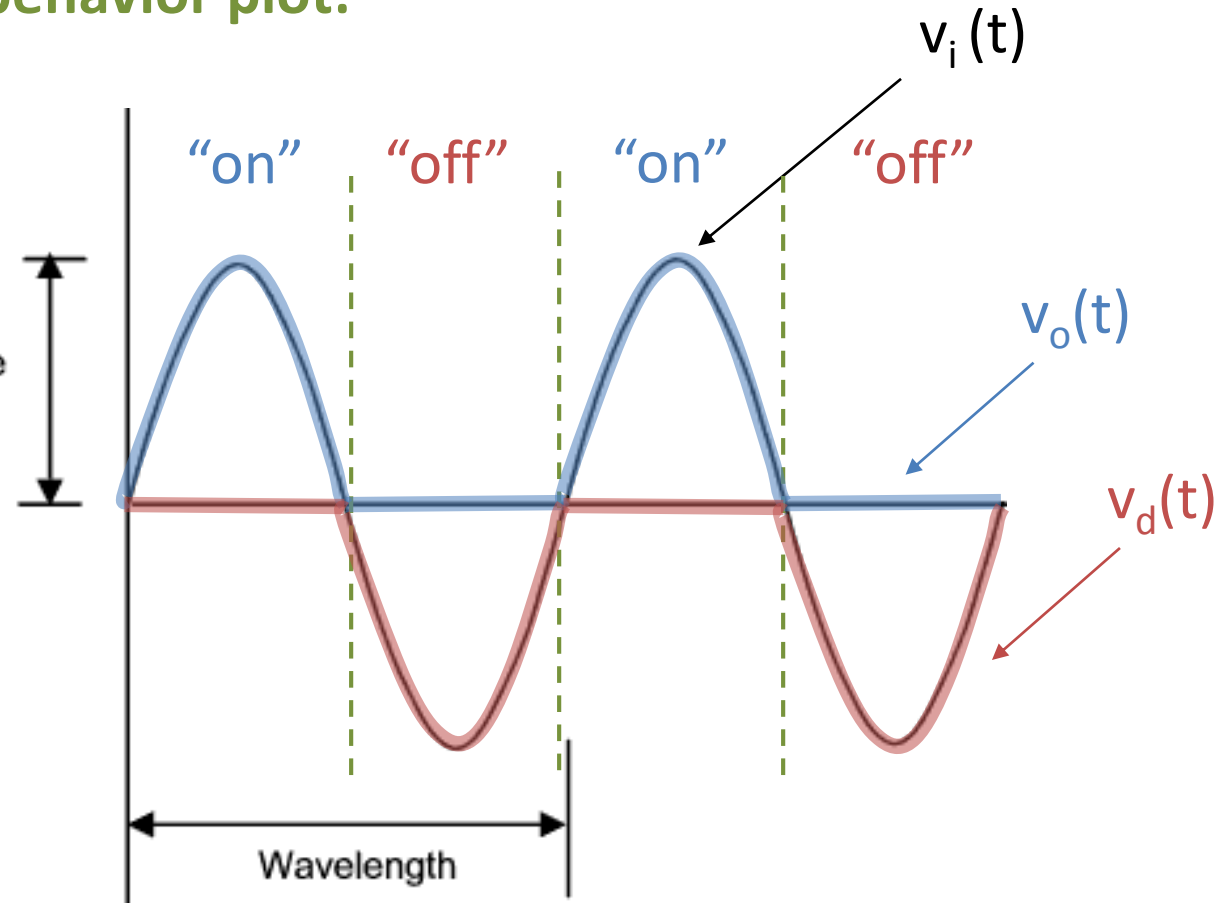


Example 4.1

8/26/2019


For the following circuit, assuming v_s is a sinusoid with 24-V peak amplitude and a CVD diode model find

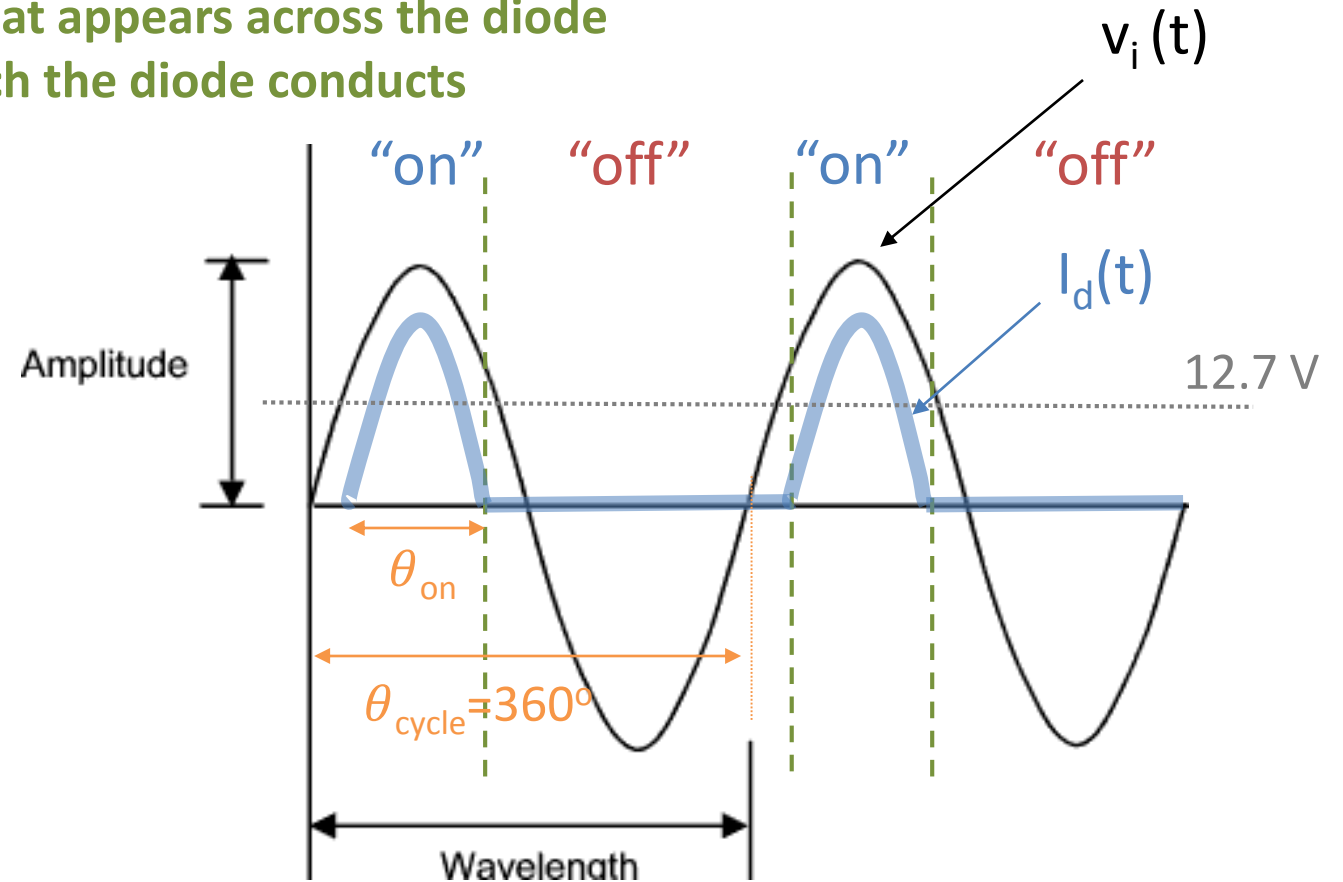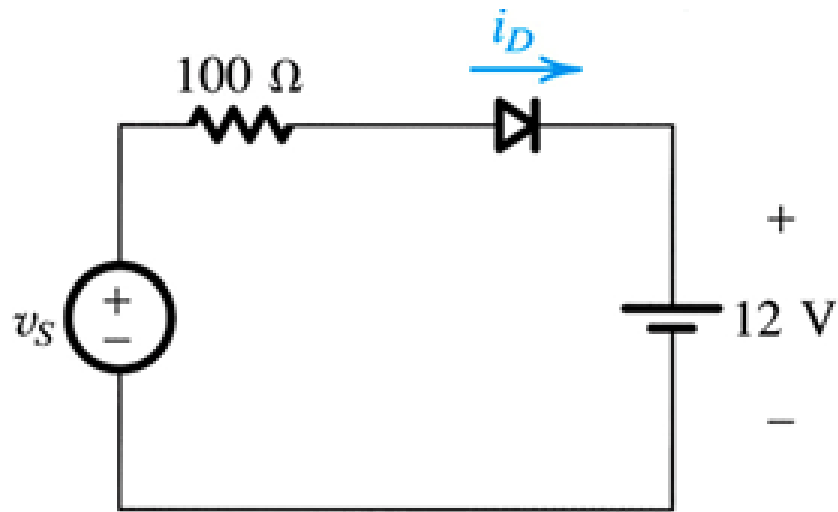- the peak value of the diode current
- the maximum reverse-bias voltage that appears across the diode
- the fraction of each cycle during which the diode conducts



Small-Signal Model

8/26/2019

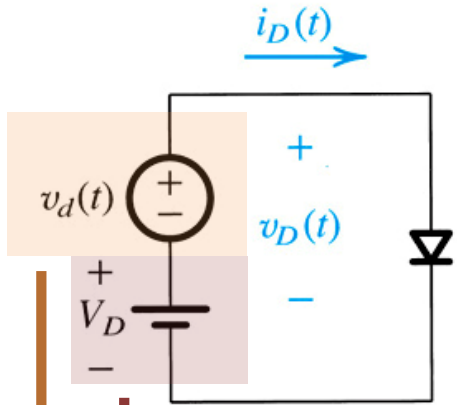


$$i_D = I_S e^{v_D/V_T}$$

∴ DC and AC Analysis can be performed separately...
superposition!

$$\begin{aligned} i_D(t) &= I_S e^{v_D(t)/V_T} \\ &= I_S e^{(V_D + v_d(t))/V_T} \\ &= I_{bias} e^{v_d(t)/V_T} \end{aligned}$$
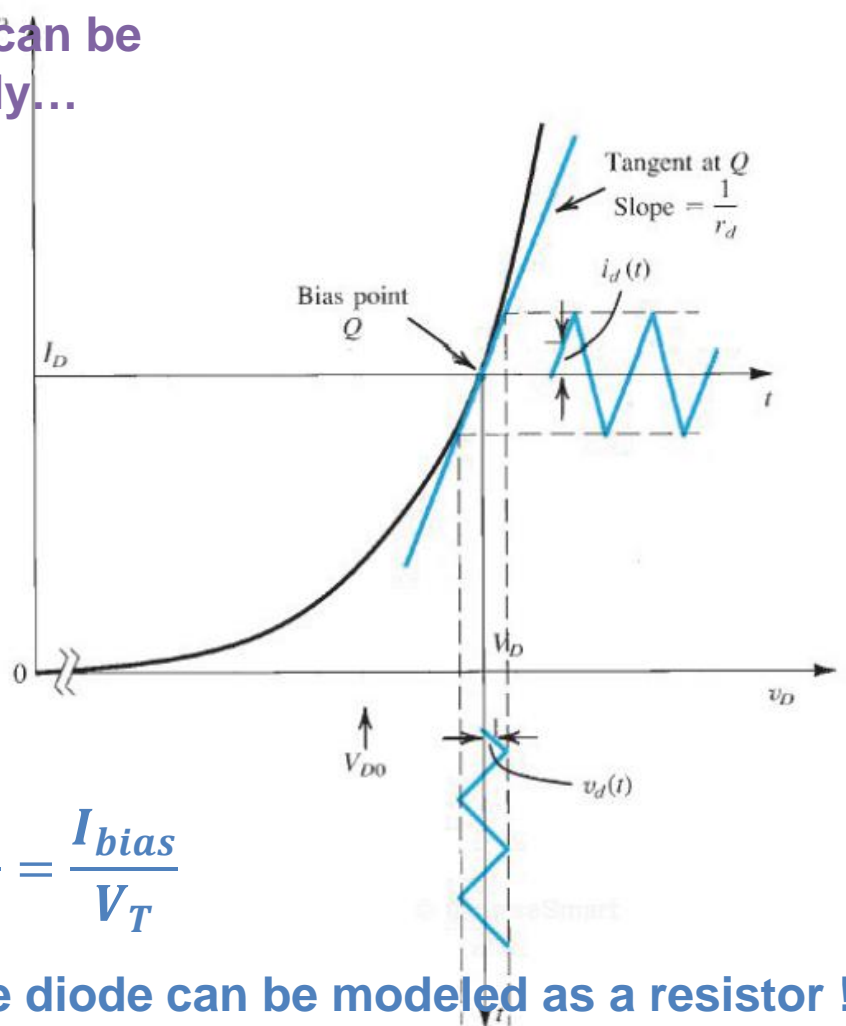
$$i_D(t) \approx \underbrace{I_{bias}}_{\text{DC}} + \underbrace{\frac{I_{bias}}{V_T} v_d(t)}_{\text{AC}}$$



DC Signal

→ establishes the bias point

AC Signal

→ small changes at the bias point


$$\frac{1}{r_d} = \frac{\Delta i_D}{\Delta v_D} = \frac{i_d}{v_d} = \frac{I_{bias}}{V_T}$$

∴ The AC behavior of the diode can be modeled as a resistor !

Small-Signal Model


8/26/2019

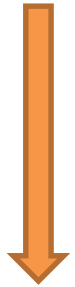- Diode y modeled as a variable resistor
- Its value is defined via linearization of exponential model
- Around bias point defined by constant voltage drop model




The total instantaneous circuit is divided into steady-state and time varying components, which may be analyzed separately and solved via algebra.

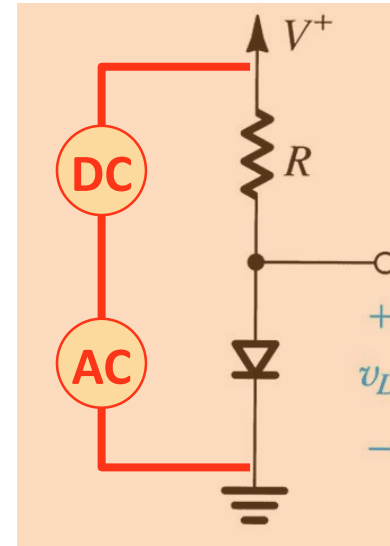
- 1) In steady-state, diode represented as CVDM.
- 2) In time-varying, diode represented as resistor.



(a)

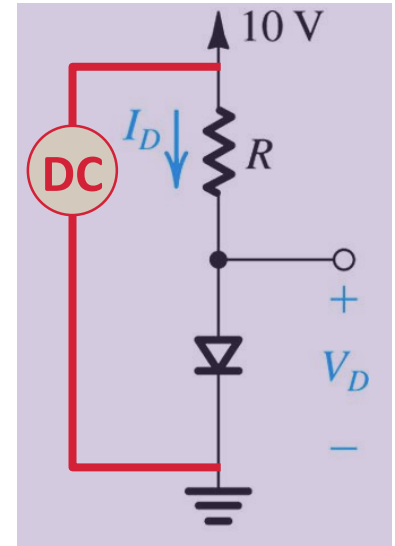

(b)

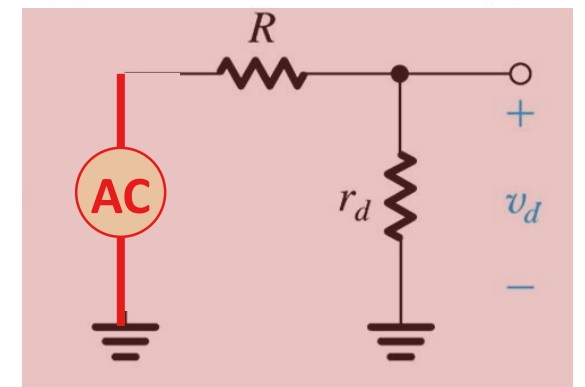

(c)

Problem D 4.56


8/26/2019

$$I_S = 69 \times 10^{-16} \text{ A}$$

A particular design of a voltage regulator is shown below. Diodes D_1 and D_2 are 10-mA units; that is, each has a voltage drop of 0.7V at a current of 10mA. Use the diode exponential model and iterative analysis to answer the following questions:

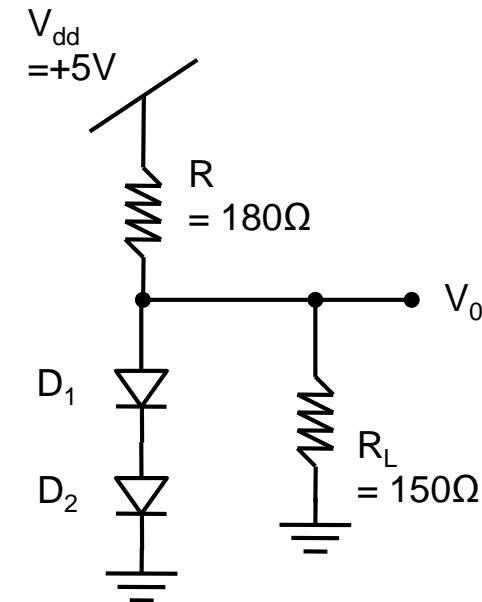- a) What is the regulator output voltage V_0 with the 150Ω load connected?
- b) With the load connected, calculate the output voltage change when the supply decreases 1V / 0.1V / 0.01V of its nominal value?

** for part b) use both the large signal model (exponential) and the small signal



$$I_D = 10.63 \text{ mA}$$

$$V_0 = 1.403 \text{ V}$$

ΔV_{DD}	I_D large signal model	v_0 large signal model	Δv_0 large signal model	Δv_0 small signal model
1.0V				
0.1V				
0.01V				