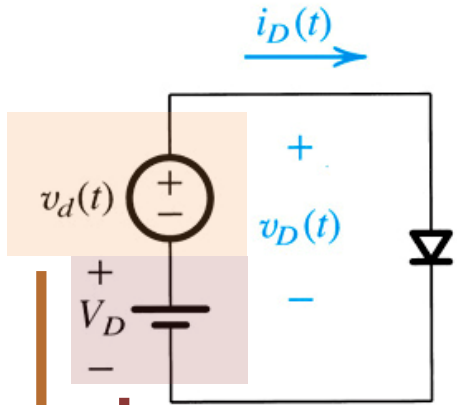


Last Lecture → Small Signal Model

9/3/2019




$$i_D = I_S e^{v_D/V_T}$$

∴ DC and AC Analysis can be performed separately...
superposition!

$$\begin{aligned} i_D(t) &= I_S e^{v_D(t)/V_T} \\ &= I_S e^{(V_D + v_d(t))/V_T} \\ &= I_{bias} e^{v_d(t)/V_T} \end{aligned}$$
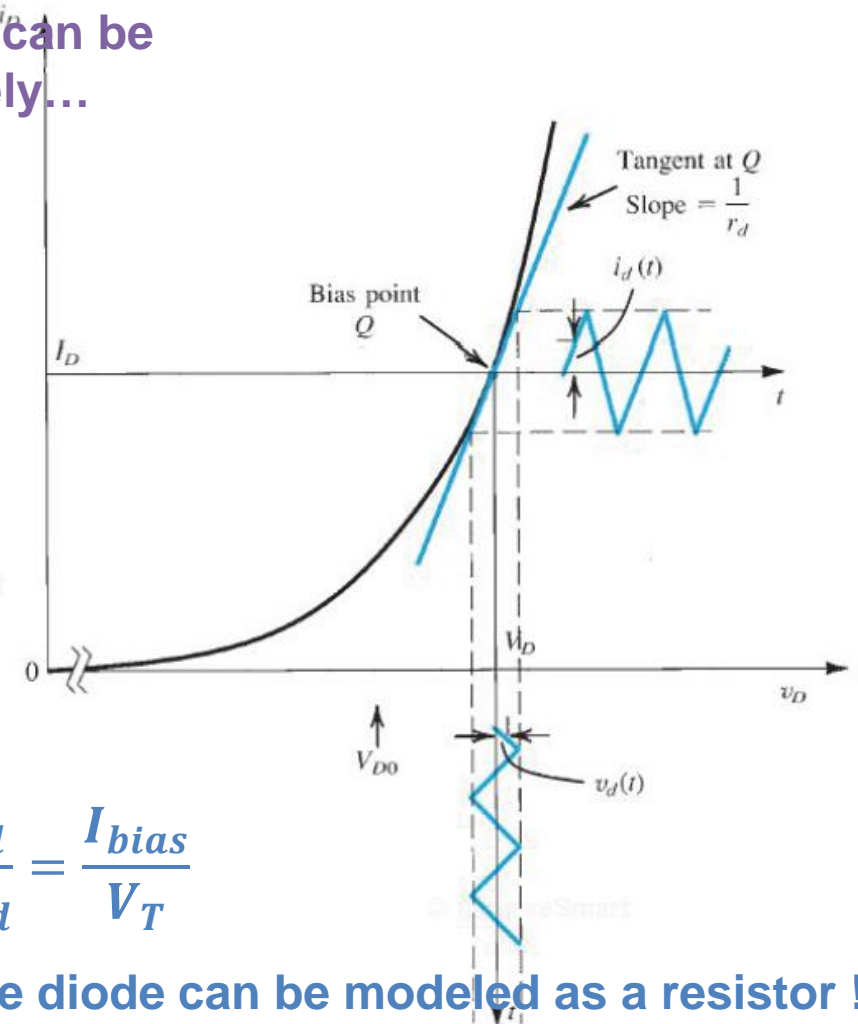
$$i_D(t) \approx \underbrace{I_{bias}}_{\text{DC}} + \underbrace{\frac{I_{bias}}{V_T} v_d(t)}_{\text{AC}}$$



$$\frac{1}{r_d} = \frac{\Delta i_D}{\Delta v_D} = \frac{i_d}{v_d} = \frac{I_{bias}}{V_T}$$

∴ The AC behavior of the diode can be modeled as a resistor !

DC Signal

→ establishes the bias point


AC Signal

→ small changes at the bias point

Last Lecture → Small Signal Model


9/3/2019

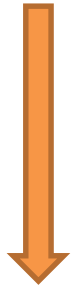- Diode modeled as a variable resistor
- Its value is defined via linearization of exponential model
- Around bias point defined by constant voltage drop model




The total instantaneous circuit is divided into steady-state and time varying components, which may be analyzed separately and solved via algebra.

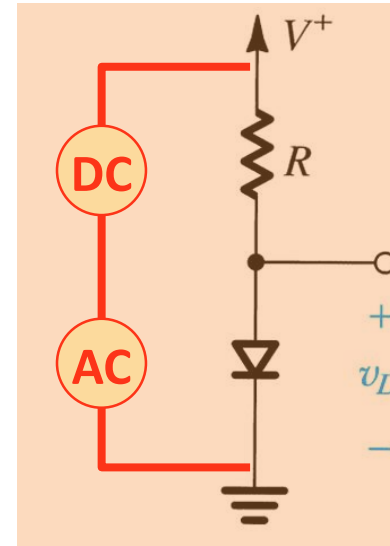
- 1) In steady-state, diode represented as CVDM.
- 2) In time-varying, diode represented as resistor.



(a)

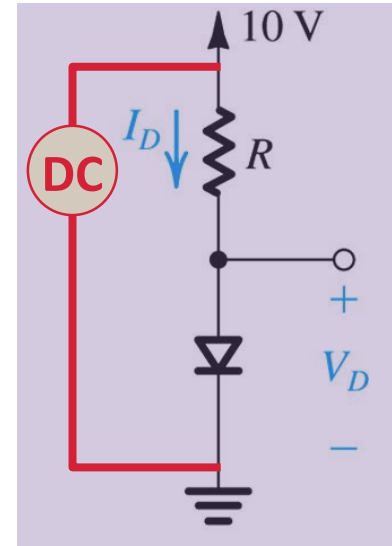

(b)

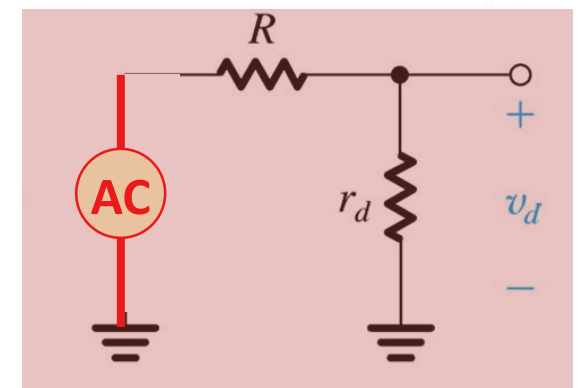

(c)

Problem D 4.56

9/3/2019


$$I_S = 69 \times 10^{-16} \text{ A}$$

A particular design of a voltage regulator is shown below. Diodes D_1 and D_2 are 10-mA units; that is, each has a voltage drop of 0.7V at a current of 10mA. Use the diode exponential model and iterative analysis to answer the following questions:

- a) What is the regulator output voltage V_0 with the 150Ω load connected?
- b) With the load connected, calculate the output voltage change when the supply decreases 1V / 0.1V / 0.01V of its nominal value?

** for part b) use both the large signal model (exponential) and the small signal

ΔV_{DD}	I_D large signal model	v_0 large signal model	Δv_0 large signal model	Δv_0 small signal model
1.0V				
0.1V				
0.01V				

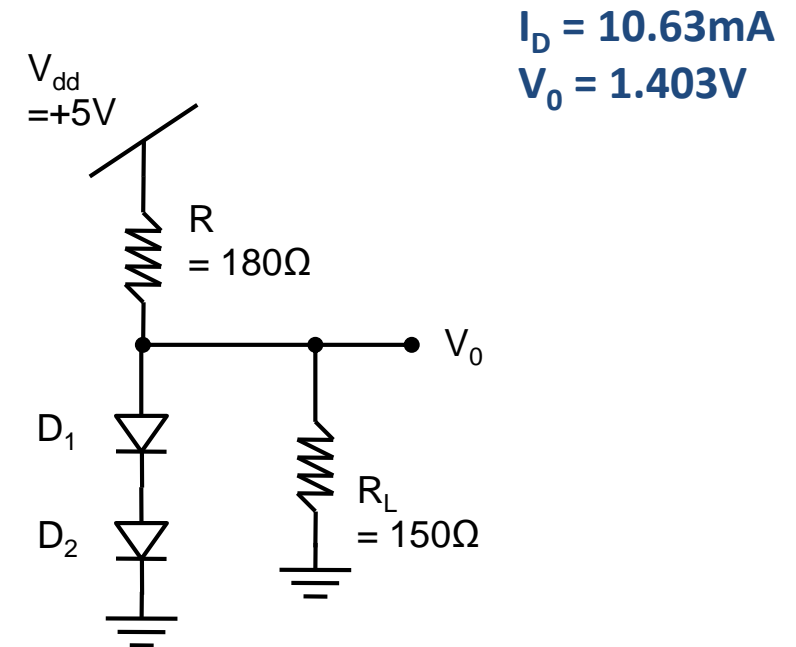

Problem D 4.56

9/3/2019

$$I_S = 69 \times 10^{-16} \text{ A}$$


A particular design of a voltage regulator is shown below. Diodes D_1 and D_2 are 10-mA units; that is, each has a voltage drop of 0.7V at a current of 10mA. Use the diode exponential model and iterative analysis to answer the following questions:

- a) What is the regulator output voltage V_0 with the 150Ω load connected?
- b) With the load connected, calculate the output voltage change when the supply decreases 1V / 0.1V / 0.01V of its nominal value?

** for part b) use both the large signal model (exponential) and the small signal

ΔV_{DD}	I_D large signal model	v_0 large signal model	Δv_0 large signal model	Δv_0 small signal model
1.0V	5.48mA	1.370	-33mV	-24mV
0.1V	10.10mA	1.400	-3mV	-2.4mV
0.01V	10.57mA	1.4028	-0.2mV	-0.2mV

Small Signal Behavior!

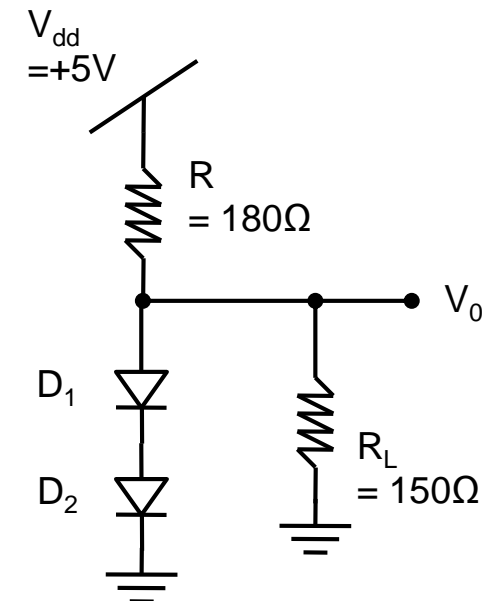


$$I_D = 10.63 \text{ mA}$$

$$V_0 = 1.403 \text{ V}$$

Zener Diodes → Chapter 4.4

9/3/2019

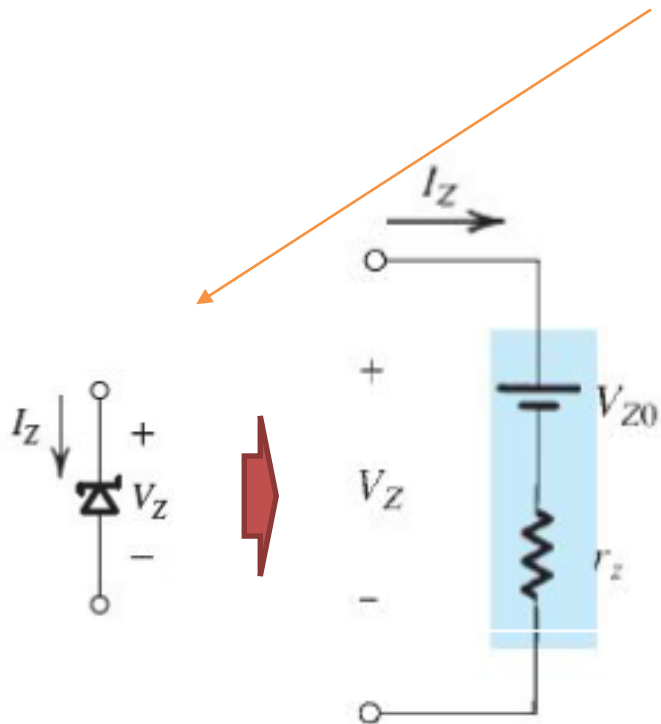
- Under certain circumstances, diodes may be intentionally used in the reverse breakdown region.
- These are referred to as **Zener Diodes**.



$$V_Z = V_{Z0} + r_z \cdot i_z$$

= v_z → small signal behavior

*** for $V_Z \geq V_{Z0}$
 $I_Z \geq I_{ZK}$

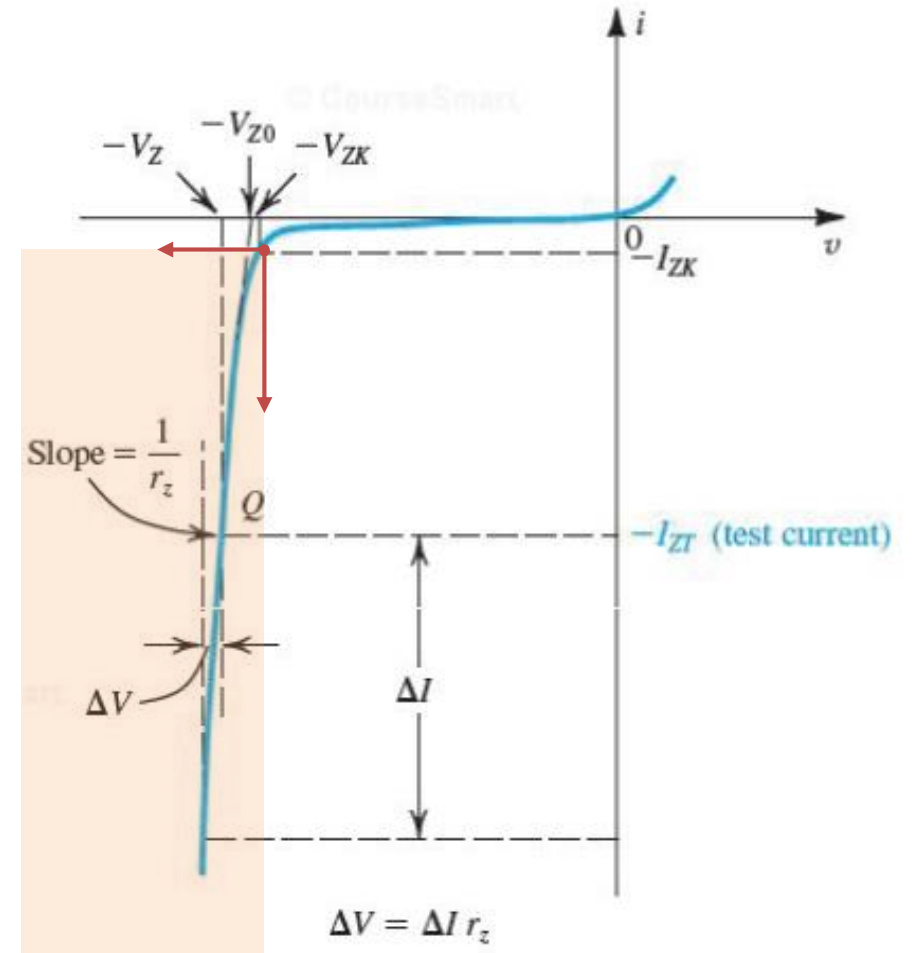

Exercise 4.17


9/3/2019

A zener diode exhibit a constant voltage of 5.6V for current greater than five times the knee current. I_{ZK} is specified to be 1mA. The zener is to be used in the design of a shunt regulator fed from a 15-V supply through a resistor R. The load current varies over the range of 0mA to 15mA. Find a suitable value for the resistor R. What is the maximum power dissipation of the zener diode?

DC Power Supply → Chapter 4.5


9/3/2019

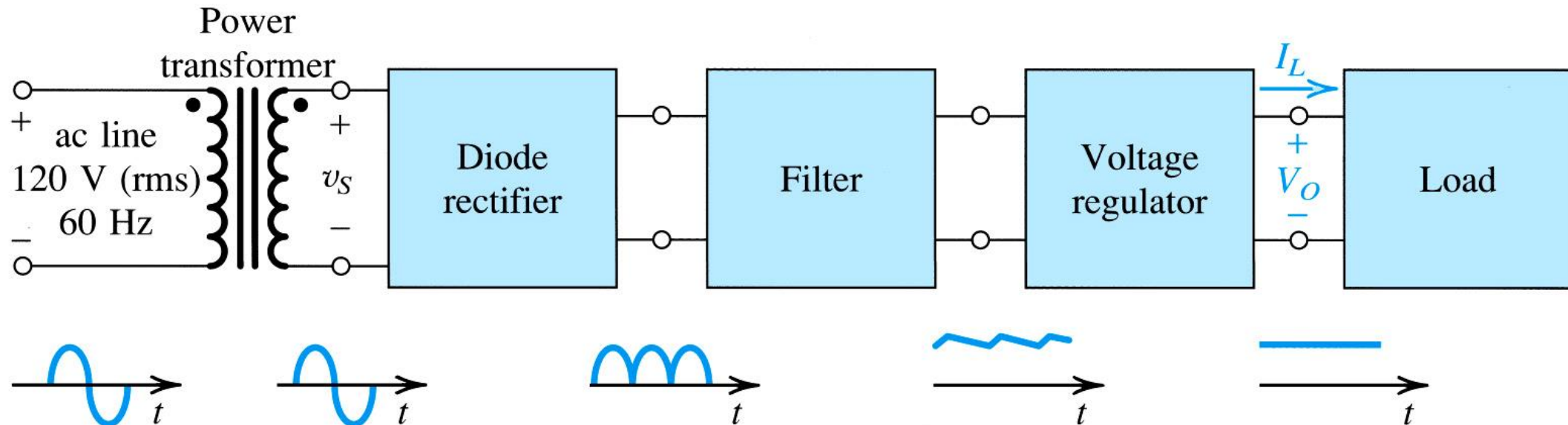- **Power Transformer** – lowers down the 120V-AC input voltage and provides electrical isolation
- **Diode rectifiers** – converts the AC signal to an unipolar output
- **Filter** – reduces the voltage fluctuations of the rectified signal
- **Voltage Regulator** - reduces the ripple and stabilizes the output voltage from variations caused by changes in the load current




The Half-Wave Rectifier


9/3/2019

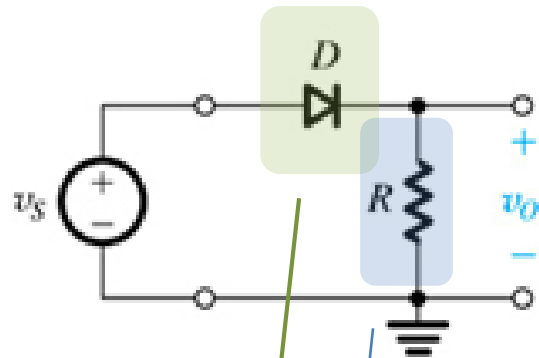

DC Response

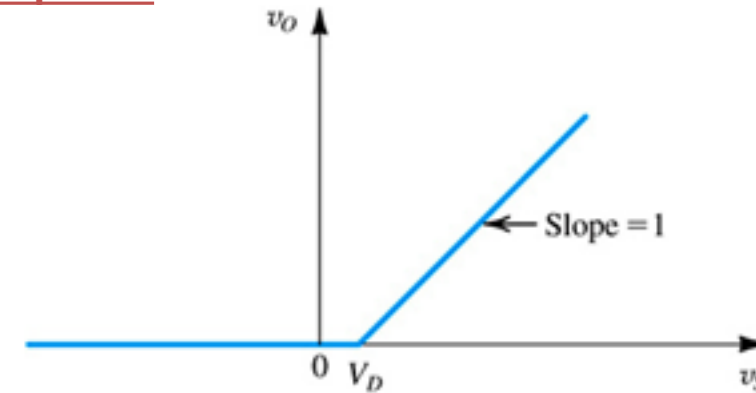

Transient Response

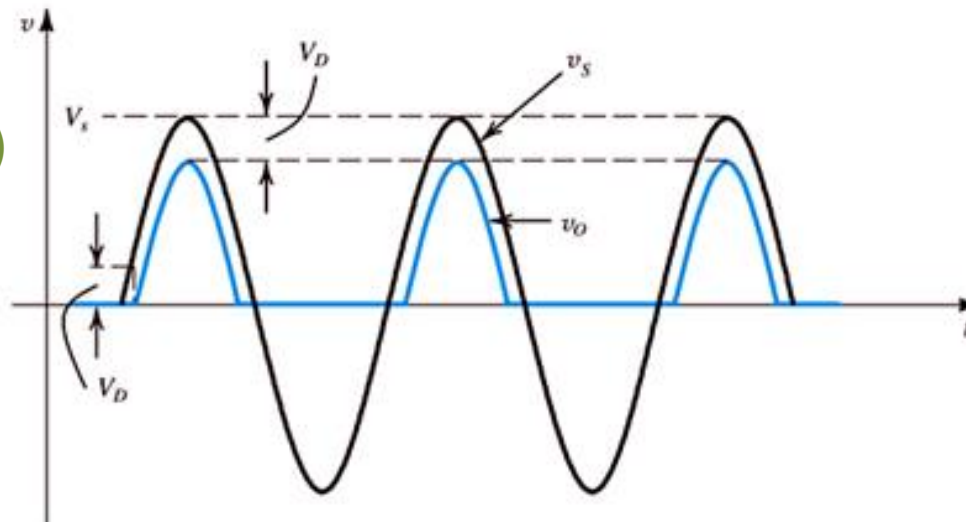

Diode Parameter Specifications:

- Current-handling capability – $I_D(max)$
- Peak inverse voltage – $PIV = V_R(max)$

Output Specifications:

- Average Voltage – $V_o(avg)$
- Average Current – $I_L(avg)$

Diode Ratings

$$I_D(max) = \frac{V_S - V_D}{R}$$

$$PIV = V_S$$

Conduction Angle

$$\theta = \sin^{-1}\left(\frac{V_D}{V_S}\right)$$

$$\Delta\theta = \pi - 2\theta$$

Average Output

$$\bar{V}_0 \approx \frac{V_S}{\pi} - \frac{V_D}{2}$$

$$\bar{I}_L \approx \frac{\bar{V}_0}{R}$$