

Examen #1 → miércoles 11 de septiembre @ S-227

9/4/2019

- Amplificadores
- Diodos / Diodos Zener
- Rectificadores

BATE:

Todo estudiante podrá traer su propio bate al examen. No obstante, dicho bate deberá circunscribirse a las siguientes características y normas establecidas:


1. Una hoja tamaño carta por ambos lados
2. No se permiten:
 - problemas resueltos
 - problemas del libro
 - fotocopias
3. Deberá ser entregado al profesor de ser solicitado

***** La falta de cumplimiento de dichas normas resultara en la reprobación del examen.**

Last Lecture → Zener Diode

9/4/2019

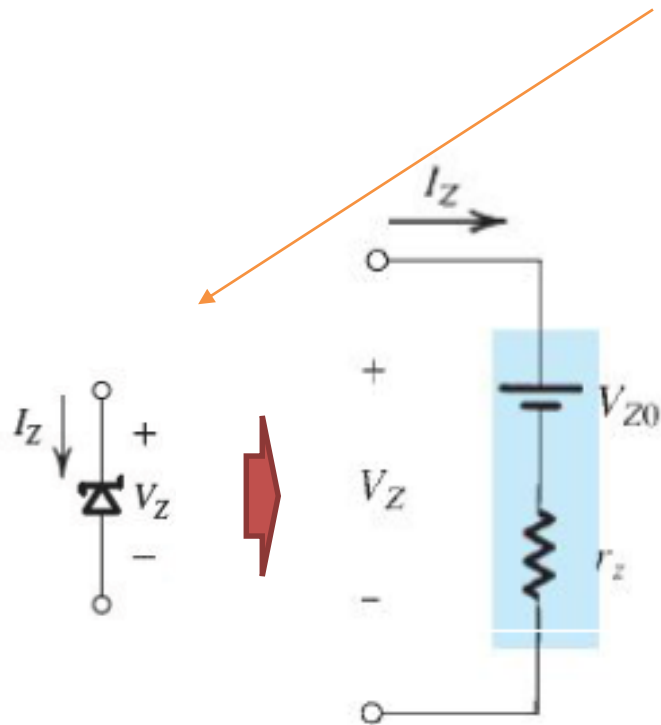
- Under certain circumstances, diodes may be intentionally used in the reverse breakdown region.
- These are referred to as **Zener Diodes**.



$$V_Z = V_{Z0} + r_z \cdot i_z$$

= v_z → small signal behavior

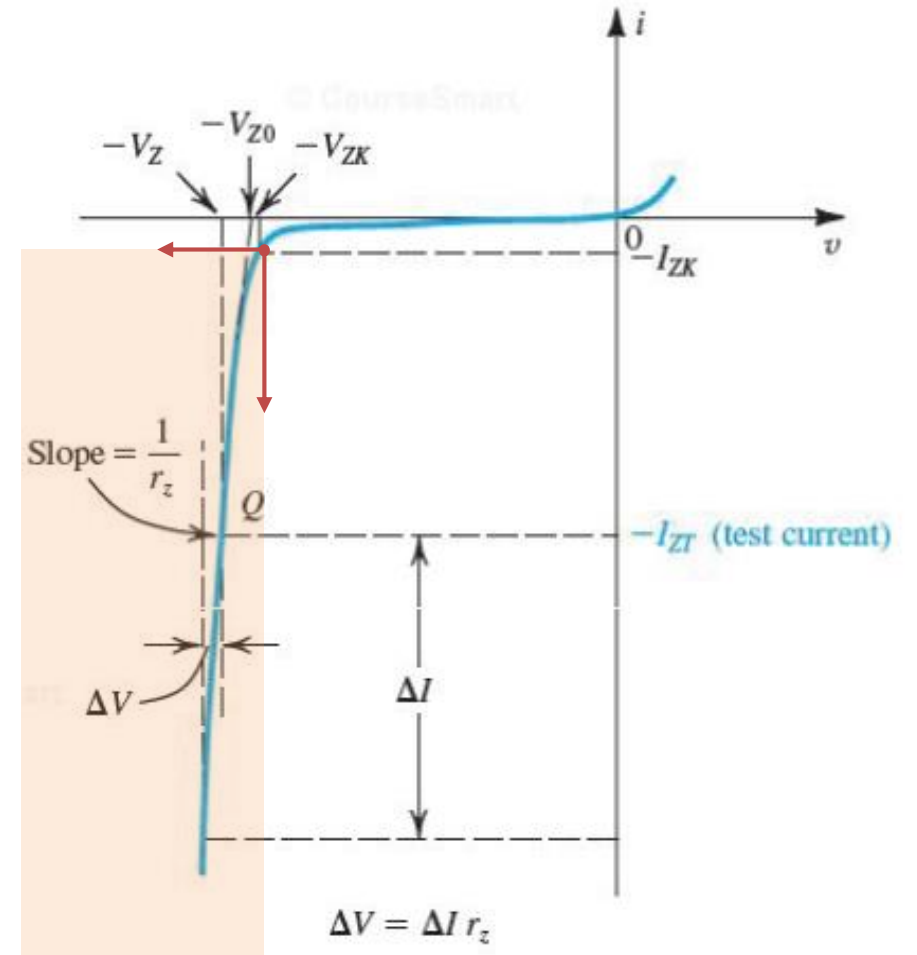
*** for $V_Z \geq V_{Z0}$
 $I_Z \geq I_{ZK}$



Last Lecture → DC Power Supply


9/4/2019

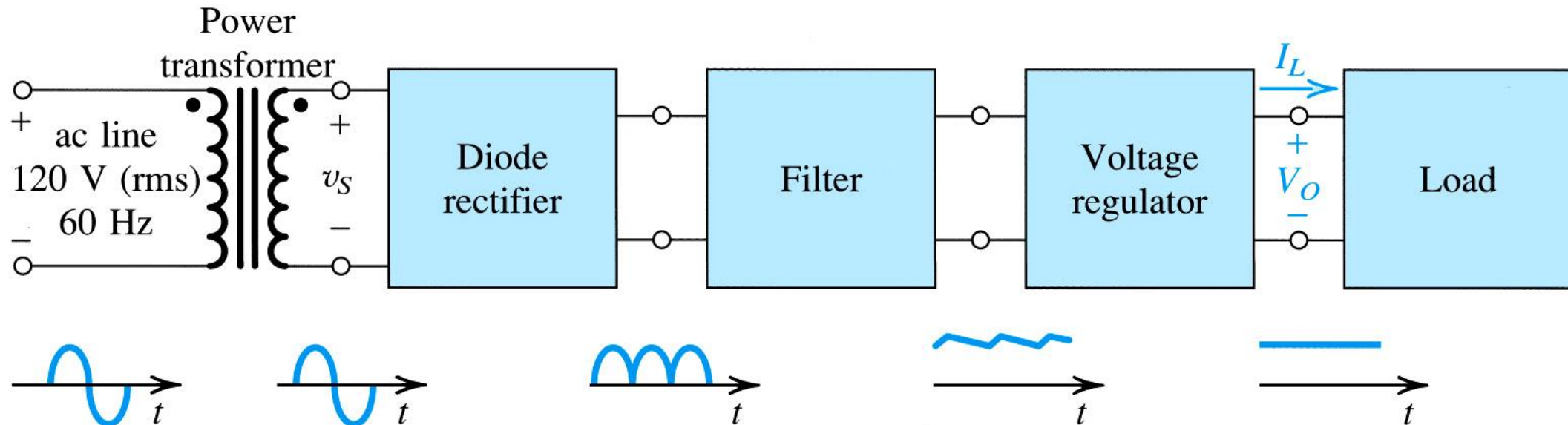- **Power Transformer** – lowers down the 120V-AC input voltage and provides electrical isolation
- **Diode rectifiers** – converts the AC signal to an unipolar output
- **Filter** – reduces the voltage fluctuations of the rectified signal
- **Voltage Regulator** - reduces the ripple and stabilizes the output voltage from variations caused by changes in the load current




Last Lecture → Half Wave Rectifier


9/4/2019

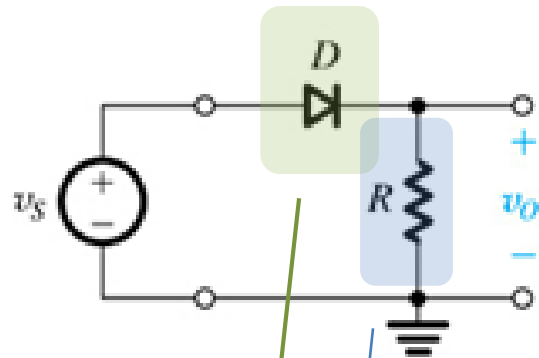

DC Response

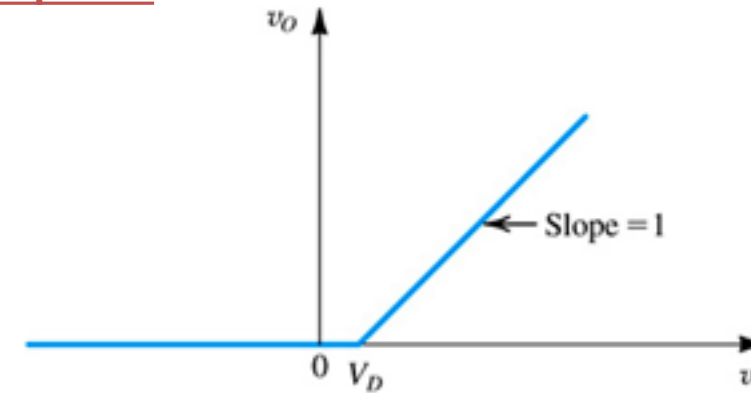

Transient Response

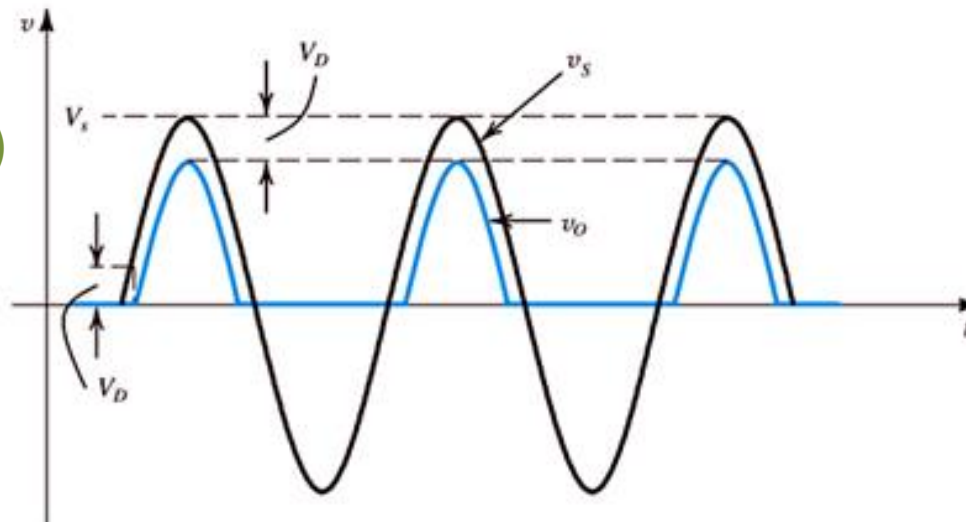

Diode Parameter Specifications:

- Current-handling capability – $I_D(max)$
- Peak inverse voltage – $PIV = V_R(max)$

Output Specifications:

- Average Voltage – $V_o(avg)$
- Average Current – $I_L(avg)$

Diode Ratings

$$I_D(max) = \frac{V_S - V_D}{R}$$

$$PIV = V_S$$

Conduction Angle

$$\theta = \sin^{-1}\left(\frac{V_D}{V_S}\right)$$

$$\Delta\theta = \pi - 2\theta$$


Average Output

$$\bar{V}_0 \approx \frac{V_S}{\pi} - \frac{V_D}{2}$$


$$\bar{I}_L \approx \frac{\bar{V}_0}{R}$$

The Full-Wave Rectifier


9/4/2019

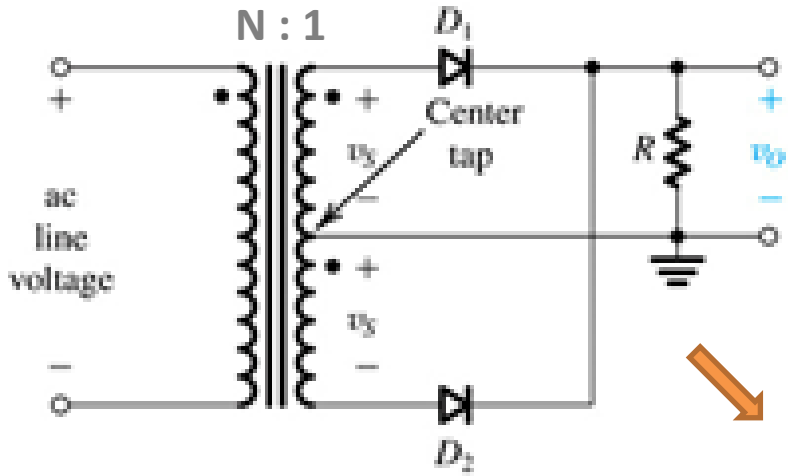

DC Response

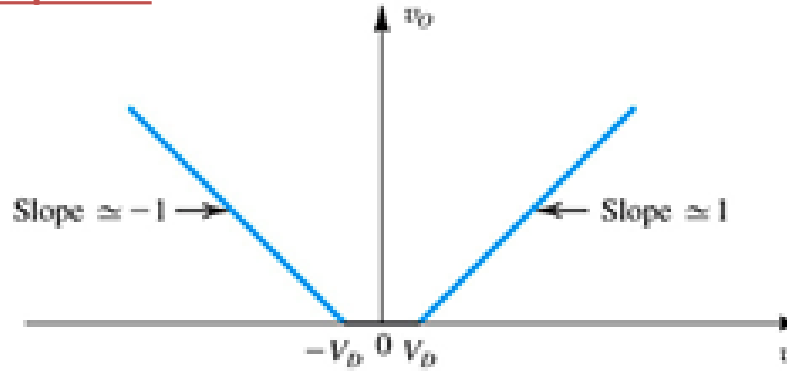

Transient Response

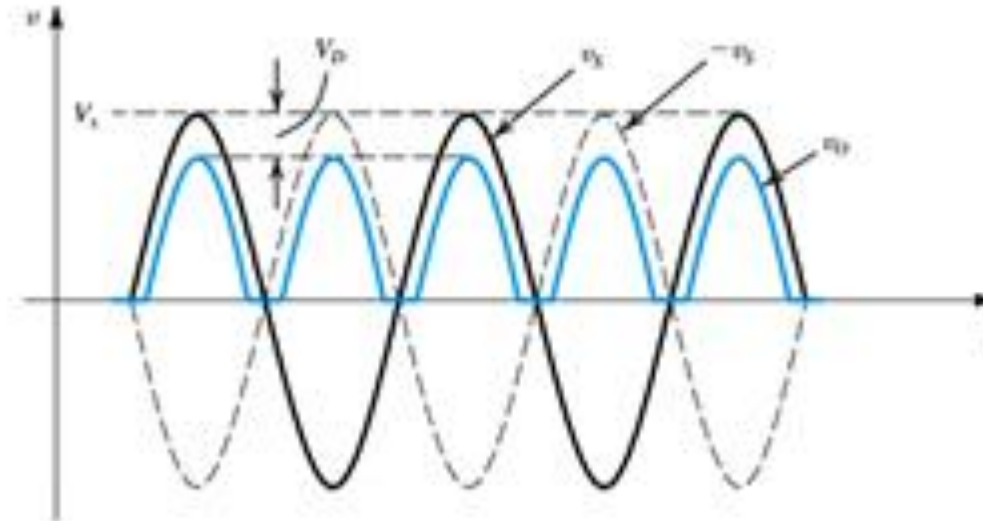

Diode Parameter Specifications:

- **Current-handling capability** – $I_D(\text{max})$
- **Peak inverse voltage** – $\text{PIV} = V_R(\text{max})$

Output Specifications:

- **Average Voltage** – $V_0(\text{avg})$
- **Average Current** – $I_L(\text{avg})$

Diode Ratings

$$I_{\text{max}} = \frac{V_S - V_D}{R}$$

$$\text{PIV} = 2V_S - V_D$$

Conduction Angle

$$\theta = \sin^{-1} \left(\frac{V_D}{V_S} \right)$$

$$\Delta\theta = \pi - 2\theta$$


Average Output

$$\bar{V}_0 \approx \frac{2V_S}{\pi} - V_D$$


$$\bar{I}_L \approx \frac{\bar{V}_0}{R}$$

The Bridge Rectifier

9/4/2019

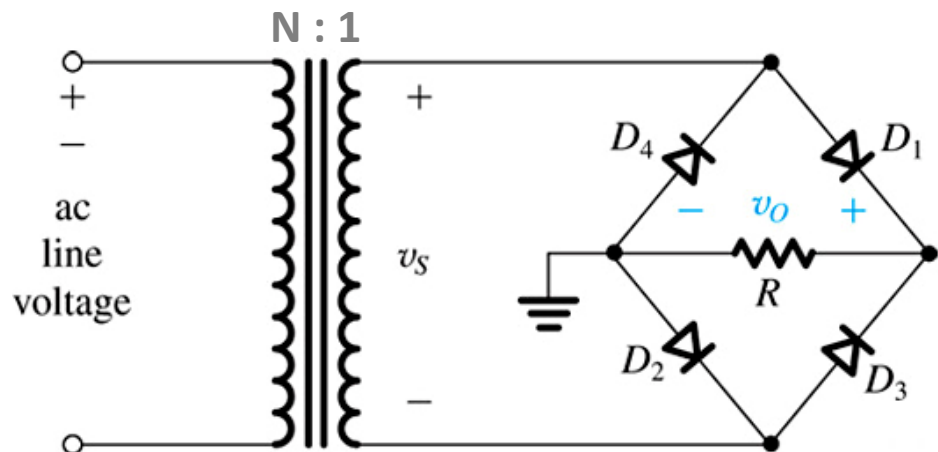

Transient Response

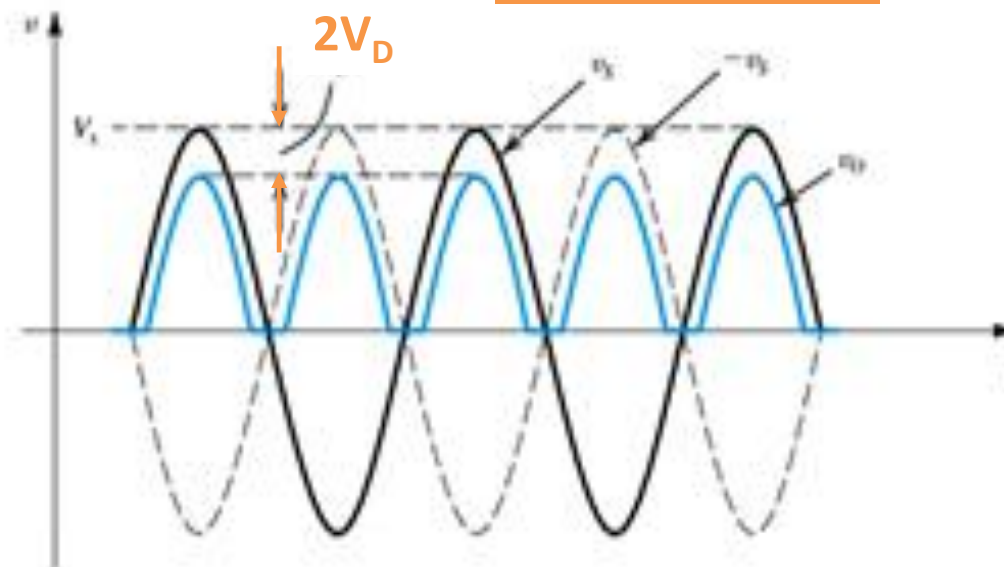

Diode Parameter Specifications:

- **Current-handling capability** – $I_D(\max)$
- **Peak inverse voltage** – $PIV = V_R(\max)$

Output Specifications:

- **Average Voltage** – $V_0(\text{avg})$
- **Average Current** – $I_L(\text{avg})$

Diode Ratings

$$I_{max} = \frac{V_S - 2V_D}{R}$$

$$PIV = V_S - V_D$$

Conduction Angle

$$\theta = \sin^{-1} \left(\frac{2V_D}{V_S} \right)$$

$$\Delta\theta = \pi - 2\theta$$

Average Output

$$\bar{V}_0 = \frac{2V_S}{\pi} - 2V_D$$

$$\bar{I}_L = \frac{\bar{V}_0}{R}$$

Rectifiers

9/4/2019

Half Wave

- Diode Ratings

$$I_{max} = \frac{V_S - V_D}{R}$$

$$PIV = V_S$$

- Average Output

$$\bar{V}_0 \approx \frac{V_S}{\pi} - \frac{V_D}{2}$$

$$\bar{I}_L \approx \frac{\bar{V}_0}{R}$$

Full Wave

Center-Tap

- Diode Ratings

$$I_{max} = \frac{V_S - V_D}{R}$$

$$PIV = 2V_S - V_D$$

- Average Output

$$\bar{V}_0 = \frac{2V_S}{\pi} - V_D$$

$$\bar{I}_L = \frac{\bar{V}_0}{R}$$

Bridge

- Diode Ratings

$$I_{max} = \frac{V_S - 2V_D}{R}$$

$$PIV = V_S - V_D$$

- Average Output

$$\bar{V}_0 = \frac{2V_S}{\pi} - 2V_D$$

$$\bar{I}_L = \frac{\bar{V}_0}{R}$$

Problem 4.71

9/4/2019

It is required to design a full-wave rectifier circuit using a center-tap transformer to provide an average output voltage of a) 10V and b) 100V. In each case find the required turn ratio of the transformer. Assume that a conducting diode has a voltage drop of 0.7V. The ac line is $120 V_{\text{rms}}$.

