

# Examen #1 → miércoles 11 de septiembre @ S-227

9/4/2019

- Amplificadores
- Diodos / Diodos Zener
- Rectificadores

## BATE:

Todo estudiante podrá traer su propio bate al examen. No obstante, dicho bate deberá circunscribirse a las siguientes características y normas establecidas:

1. Una hoja tamaño carta por ambos lados
2. No se permiten:
  - problemas resueltos
  - problemas del libro
  - fotocopias
3. Deberá ser entregado al profesor de ser solicitado

**\*\*\* La falta de cumplimiento de dichas normas resultara en la reprobación del examen.**

# Last Lecture → Rectifiers

9/4/2019

## Half Wave

- Diode Ratings

$$I_{max} = \frac{V_S - V_D}{R}$$

$$PIV = V_S$$

- Average Output

$$\bar{V}_0 \approx \frac{V_S}{\pi} - \frac{V_D}{2}$$

$$\bar{I}_L \approx \frac{\bar{V}_0}{R}$$

## Full Wave

### Center-Tap

- Diode Ratings

$$I_{max} = \frac{V_S - V_D}{R}$$

$$PIV = 2V_S - V_D$$

- Average Output

$$\bar{V}_0 = \frac{2V_S}{\pi} - V_D$$

$$\bar{I}_L = \frac{\bar{V}_0}{R}$$

### Bridge

- Diode Ratings

$$I_{max} = \frac{V_S - 2V_D}{R}$$

$$PIV = V_S - V_D$$


- Average Output

$$\bar{V}_0 = \frac{2V_S}{\pi} - 2V_D$$

$$\bar{I}_L = \frac{\bar{V}_0}{R}$$

# The Rectifier with a Filter Capacitor


9/4/2019

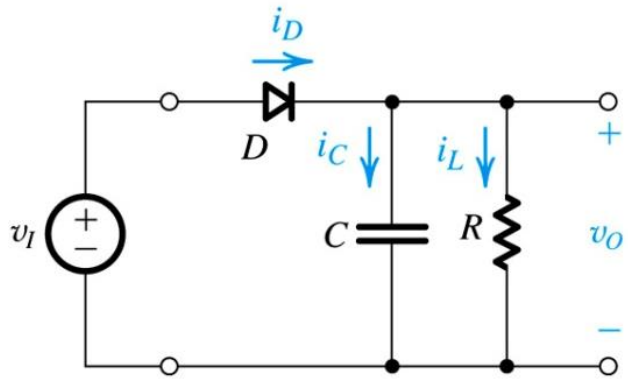

$$v_0(t) = V_s e^{-t/CR}$$

assume  $CR \gg T$

Assuming Ideal Diode!

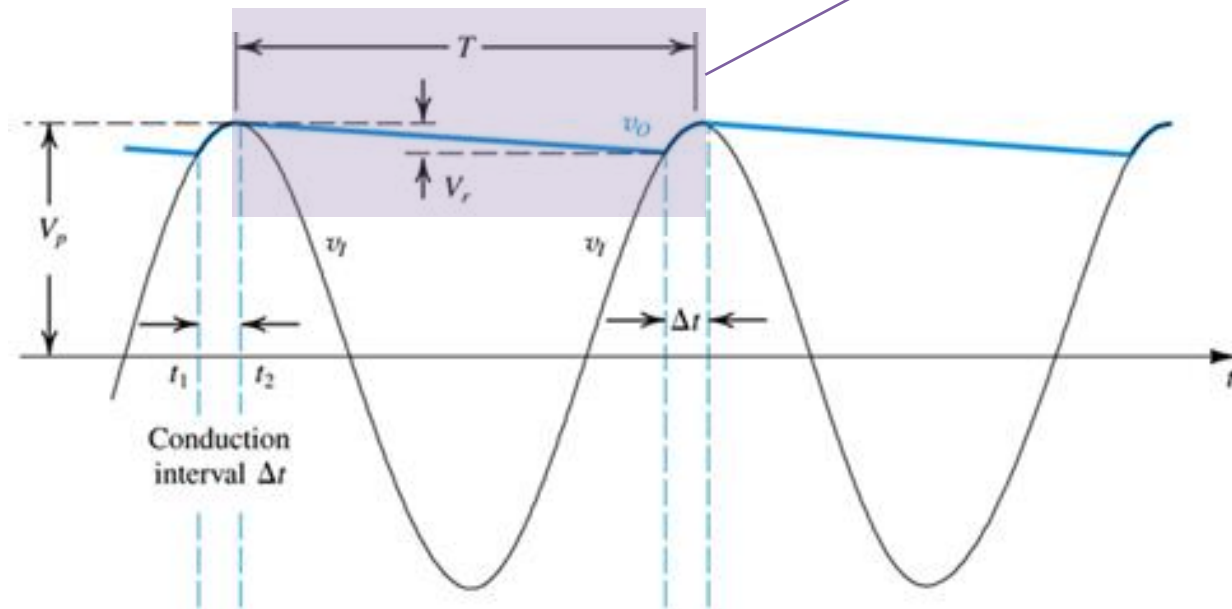

• Half-Wave

$$\bar{V}_0 = V_s - \frac{V_r}{2}$$

$$\bar{I}_L = \frac{\bar{V}_0}{R}$$

$$V_r = \frac{V_s}{fCR} \approx \frac{I_L}{fC}$$

$$\Delta\theta \approx \sqrt{2V_r/V_s}$$

$$i_{Davg} = I_L \left( 1 + \pi\sqrt{2V_s/V_r} \right)$$

$$i_{Dmax} = I_L \left( 1 + 2\pi\sqrt{2V_s/V_r} \right)$$

$$\bar{V}_0 = V_s - \frac{V_r}{2}$$

$$\bar{I}_L = \frac{\bar{V}_0}{R}$$

$$V_r = \frac{V_s}{2fCR} \approx \frac{I_L}{2fC}$$

$$\Delta\theta \approx \sqrt{2V_r/V_s}$$

$$i_{Davg} = I_L \left( 1 + \pi\sqrt{V_s/2V_r} \right)$$

$$i_{Dmax} = I_L \left( 1 + 2\pi\sqrt{V_s/2V_r} \right)$$

• Full-Wave

# Problem D 4.78

9/4/2019

It is required to use a peak rectifier to design a dc power supply that provides an average dc output voltage of 15V on which a maximum of  $\pm 1$ -V ripple is allowed. The rectifier feeds a load of  $150\Omega$ . The rectifier is fed from the line voltage ( $120V_{\text{rms}}$ , 60Hz) through a transformer. The diodes available have a 0.7-V drop when conducting. If the designer opts for the half-wave rectifier circuit:

- a) Specify the rms voltage that must appear across the transformer secondary.
- b) Find the required value of the filter capacitor and the voltage rating.
- c) Find the maximum reverse voltage that will appear across the diode, and specify the PIV rating of the diode.
- d) Calculate the average current rating through the diode during conduction.
- e) Calculate the peak diode current.

# Problem P 1.62

9/4/2019


---

An amplifier with an input resistance of  $10\text{k}\Omega$ , when driven by a current source of  $1\mu\text{A}$  and a source resistance of  $100\text{k}\Omega$ , has a short-circuit output current of  $10\text{mA}$  and an open-circuit output voltage of  $10\text{V}$ . The device is driving a  $4\text{k}\Omega$  load. Give the values of the voltage gain, current gain, and power gain. Determine the type of amplifier.
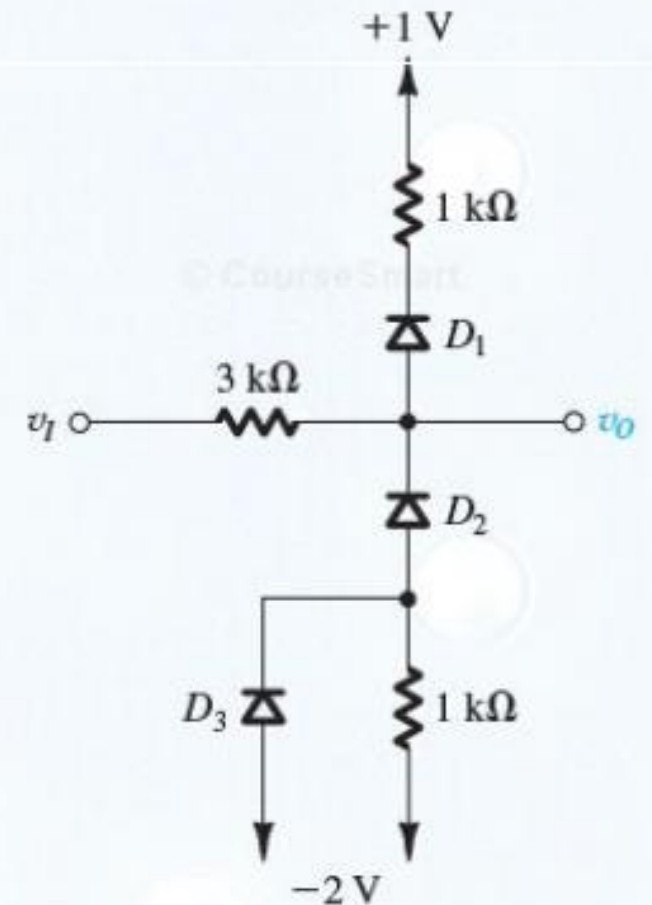
# Problem P 4.93

9/4/2019

Sketch and label the voltage transfer characteristic  $v_o$  versus  $v_i$  of the circuit provided over a  $\pm 10\text{-V}$  range of input signals. Assume that the diodes can be represented by the constant-voltage-drop model with  $V_D = 0.7\text{V}$ . What are the slopes of the characteristic at the extreme  $\pm 10\text{-V}$  levels.



# Problem 4.74

9/4/2019

The circuit provided below implements a complementary-output rectifier. Sketch and clearly label the waveforms of  $V_o^+$  and  $V_o^-$ . Assume a 0.7-V drop across each conducting diode. If the magnitude of the average of each output is to be 15V, find the required amplitude of the sine wave across the entire secondary winding. What is the PIV of each diode?

