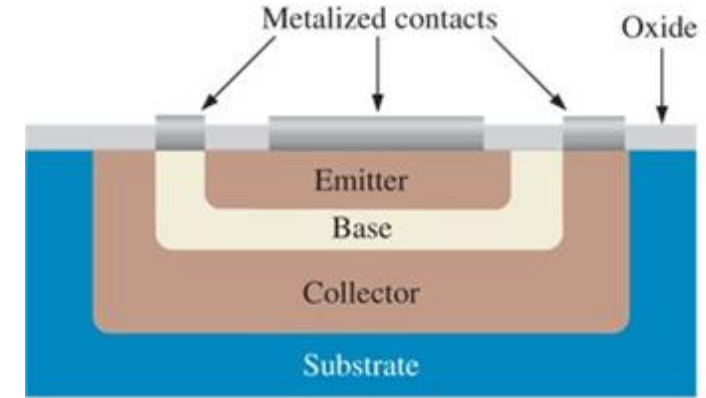


Bipolar Junction Transistors → Chapter 6


9/16/2019

- A three terminal device
- Invented in 1948 at Bell Telephone Laboratories
- Ushered in a new era of solid-state circuits
- Replaced by MOSFET as predominant transistors


cross section →



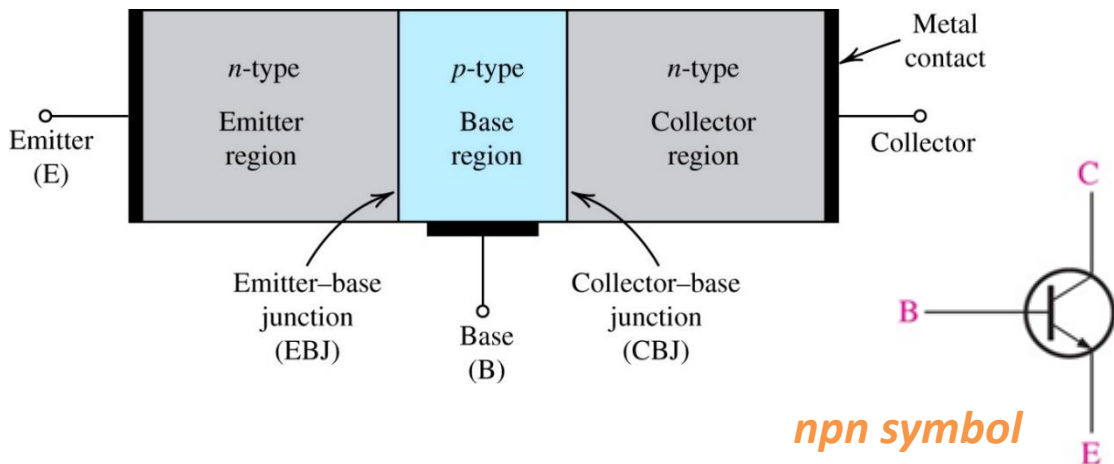Simplified structure of the *npn* transistor



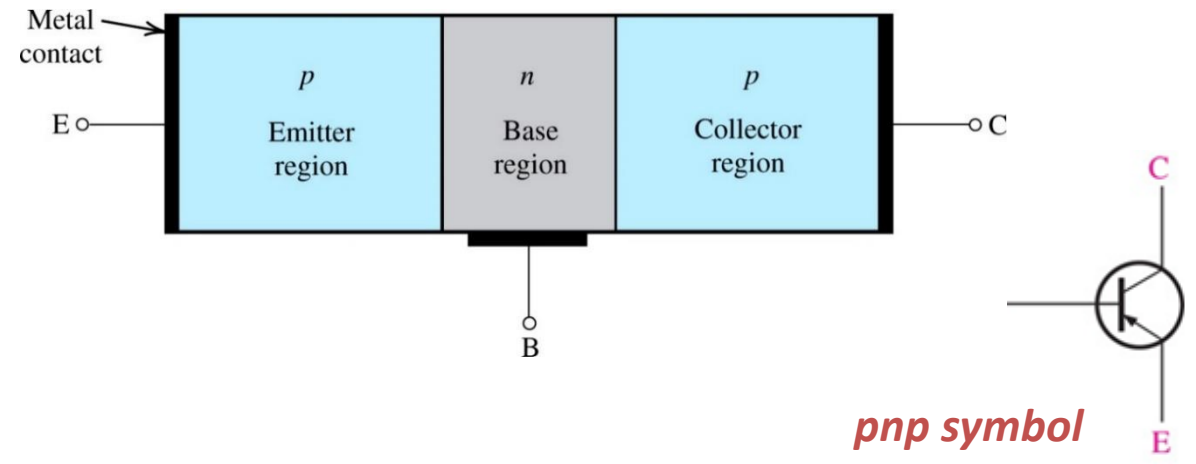Simplified structure of the *pnp* transistor



BJT → npn


9/16/2019

Voltages are measured with respect to the emitter (lowest potential)

- V_{BE} – base to emitter voltage
- V_{CE} – collector to emitter voltage

Electrons flow from the emitter to the collector terminal

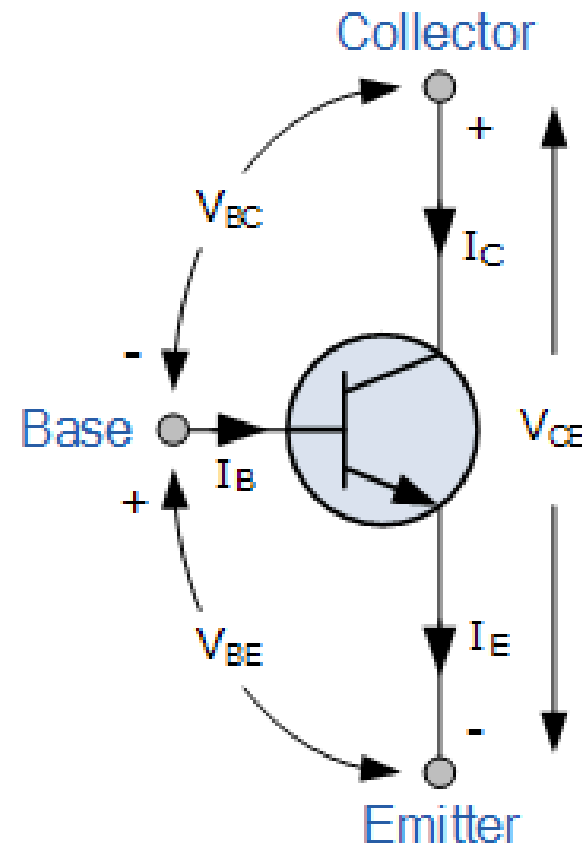- I_B – base current (in)
- I_E – emitter current
- I_C – collector current



BJT → pnp


9/16/2019

Voltages are measured with respect to the emitter (highest potential)

- V_{EB} – base to emitter voltage
- V_{EC} – collector to emitter voltage

Holes flow from the emitter to the collector terminal

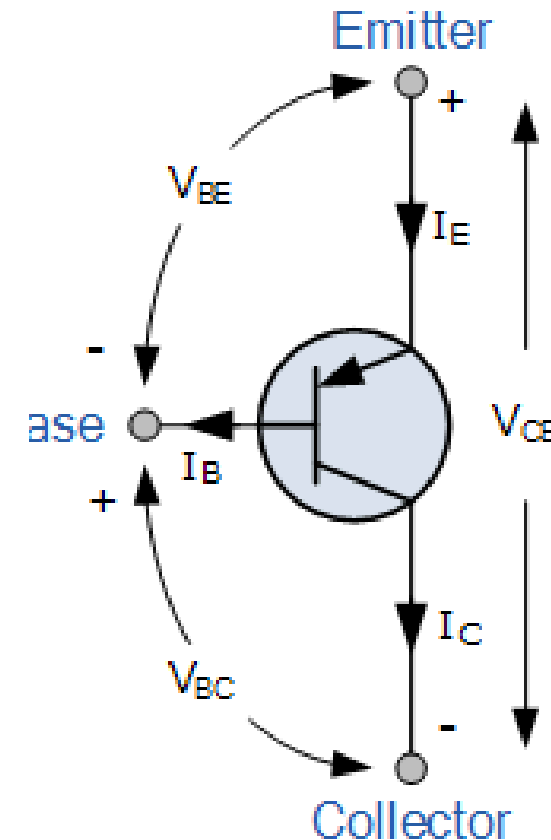- I_B – base current (out)
- I_E – emitter current
- I_C – collector current





BJT Operation

- Two external voltage sources are required for biasing
- Three operation modes:

used for
switching!

- 1) Cut-Off
- 2) Saturation
- 3) Active

used for amplification!

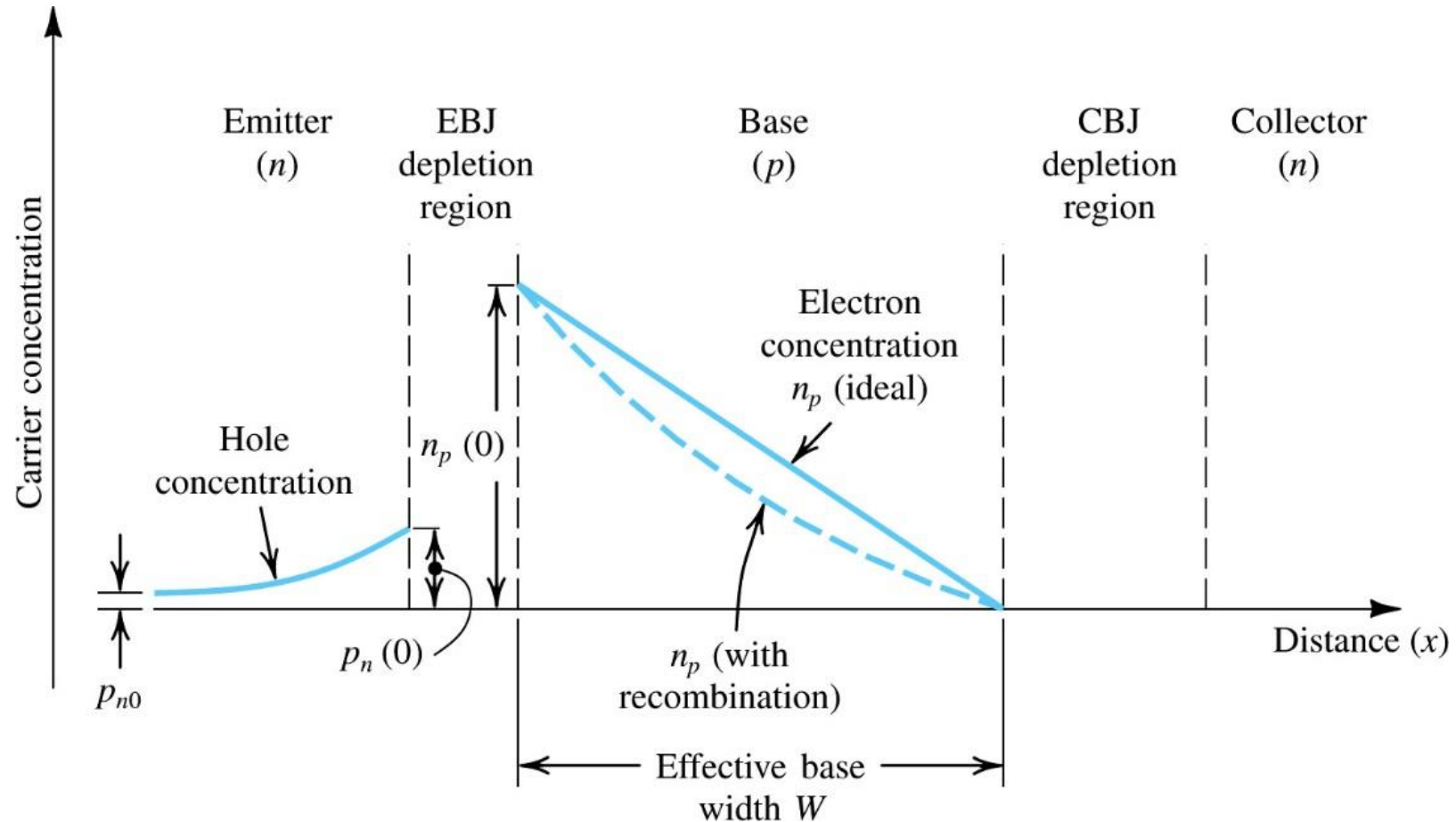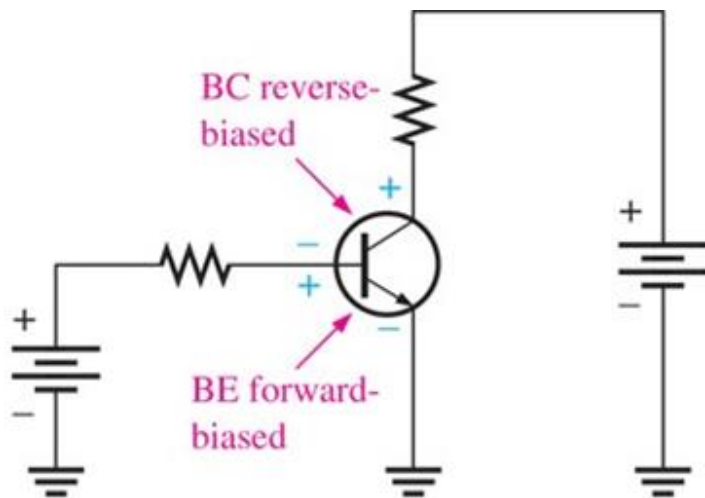



BJT Operation

- Two external voltage sources are required for biasing
- Three operation modes:

used for switching!

- 1) Cut-Off
- 2) Saturation
- 3) Active


used for amplification!

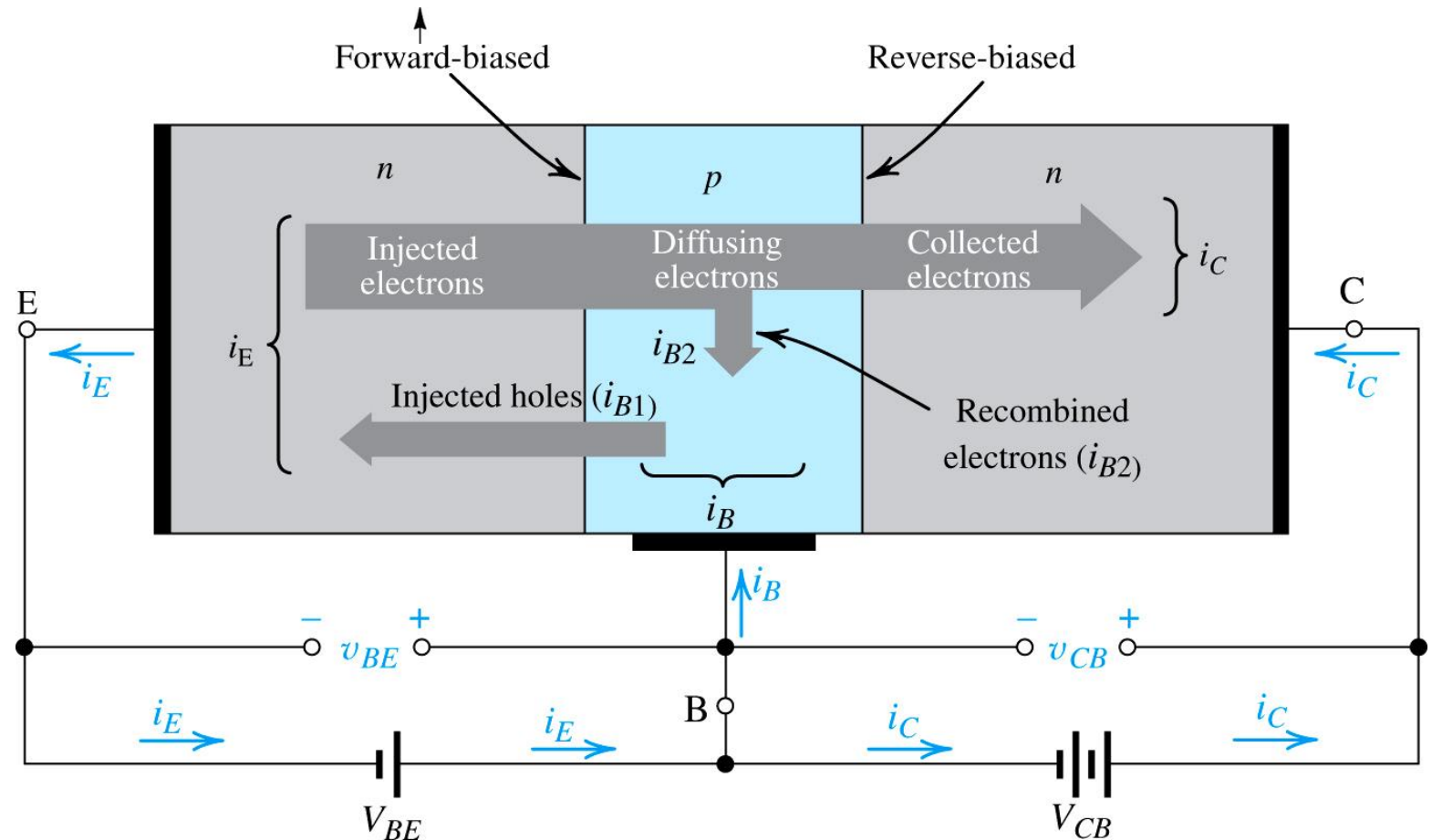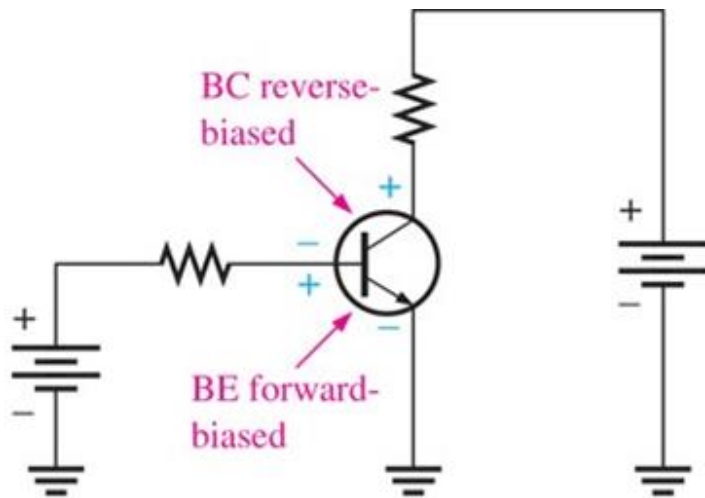

BJT Mathematical Model → Active


9/16/2019

• $i_C = f(v_{BE})$

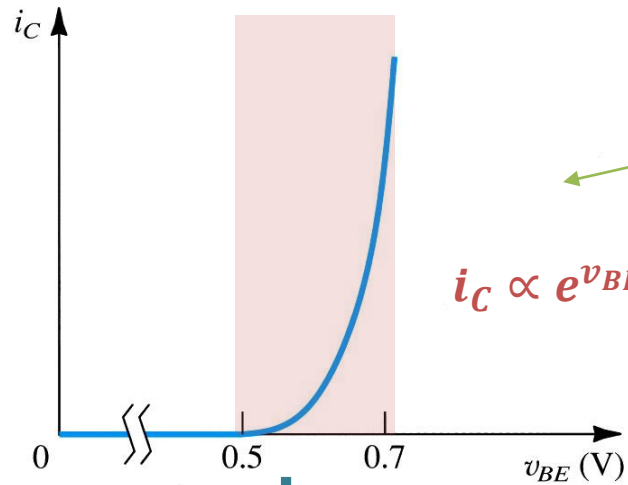


$i_C \propto e^{v_{BE}/V_T}$

• $i_C = f(v_{CE})$

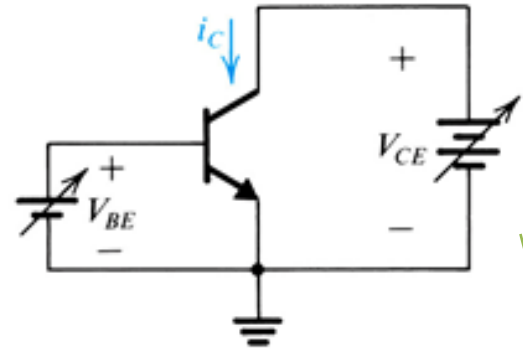

$i_C \propto \frac{v_{CE}}{V_A}$

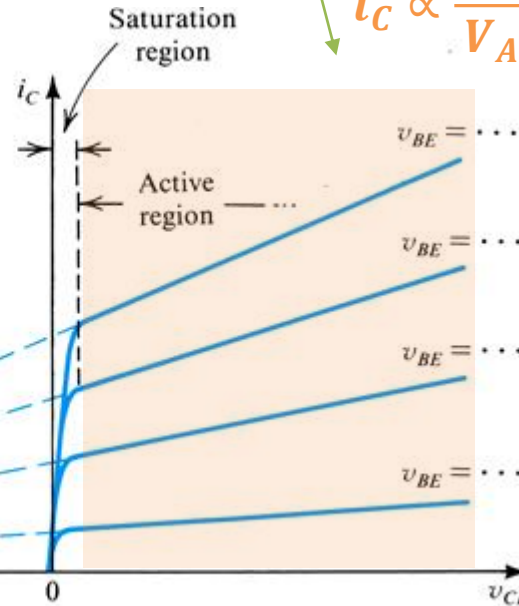

Collector Current

$$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A} \right)$$

$$\approx I_S e^{v_{BE}/V_T}$$

Current & Parameters

$$i_B = \frac{i_C}{\beta}$$

$$i_E = i_B + i_C = \frac{\beta + 1}{\beta} i_C = \frac{i_C}{\alpha}$$

I_S - Saturation Current [$10^{-12} - 10^{-18}$] A

$$I_S = \frac{A_E q D_n n_i}{N_A W}$$

β - Current Gain [50 - 200] A/A

$$\beta_{forced} = \frac{i_C}{i_B} |_{sat} \leq \beta$$

α - Constant

$$\alpha = \frac{\beta}{\beta + 1}$$


V_A - Early Voltage [10 - 100] V

Large Signal Model → npn

9/16/2019

Active Mode

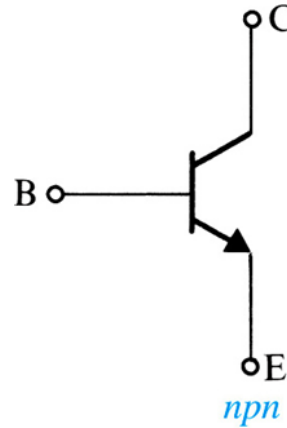- $v_{BE} \rightarrow$ forward bias
- $v_{BC} \rightarrow$ reverse bias
- $v_{CE} > 0.3V$
- $i_C = f(v_{BE})$




Saturation Mode

- $v_{BE} \rightarrow$ forward bias
- $v_{BC} \rightarrow$ forward bias
- $i_C \neq f(v_{BE})$
- $i_C / i_B = \beta_{forced} < \beta$

active circuit model

saturation circuit model

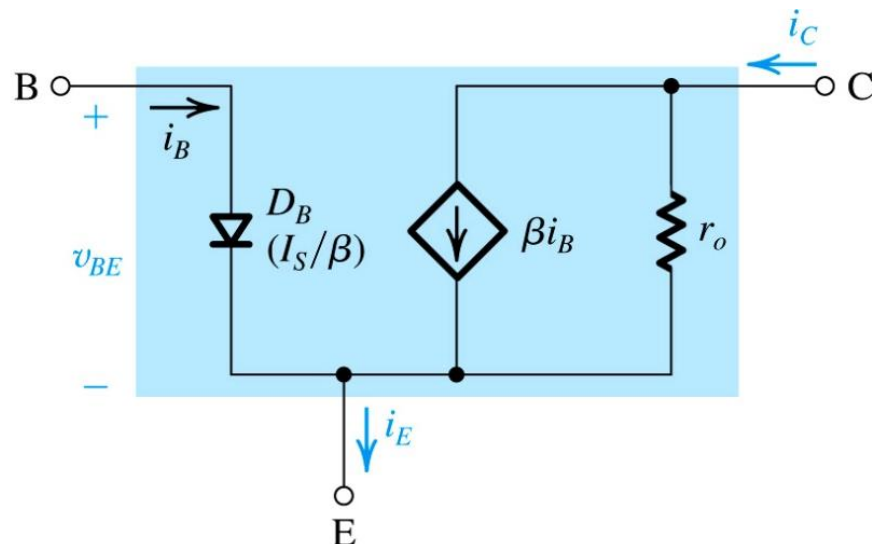



Large Signal Model → pnp

9/16/2019

Active Mode

- $v_{EB} \rightarrow$ forward bias
- $v_{CB} \rightarrow$ reverse bias
- $v_{EC} > 0.3V$
- $i_C = f(v_{EB})$

active circuit model

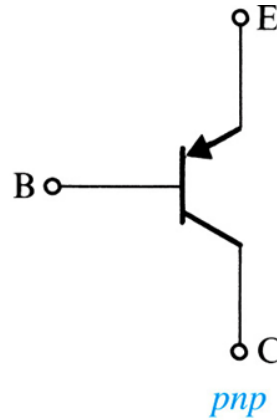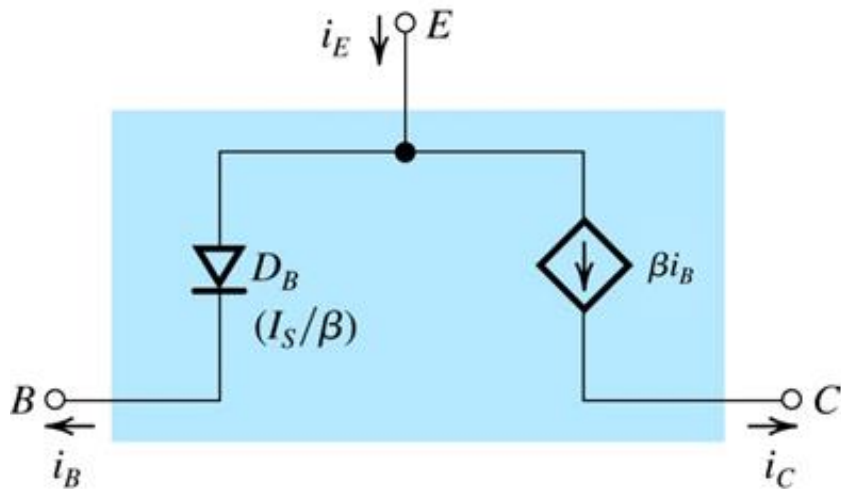

saturation circuit model

Saturation Mode

- $v_{EB} \rightarrow$ forward bias
- $v_{CB} \rightarrow$ forward bias
- $i_C \neq f(v_{EB})$
- $i_C / i_B = \beta_{forced} < \beta$