

Last Lecture → BJTs

9/16/2019

- Two external voltage sources are required for biasing
- Three operation modes:


1) Cut-Off

used for switching (digital)


2) Saturation

3) Active


used for amplification (analog)

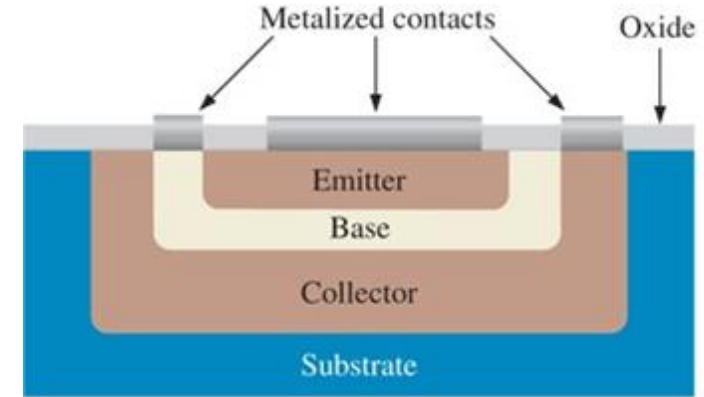

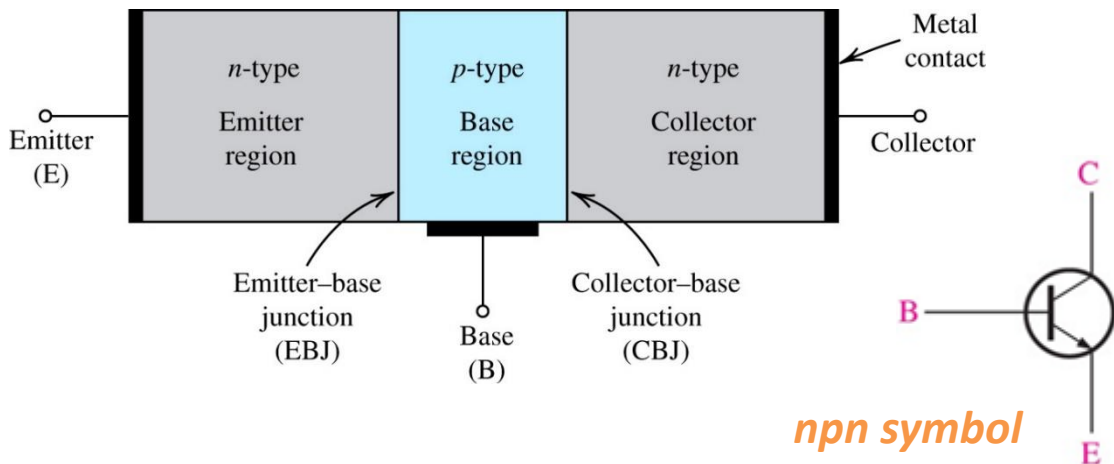- Simplified structure of the *npn* transistor



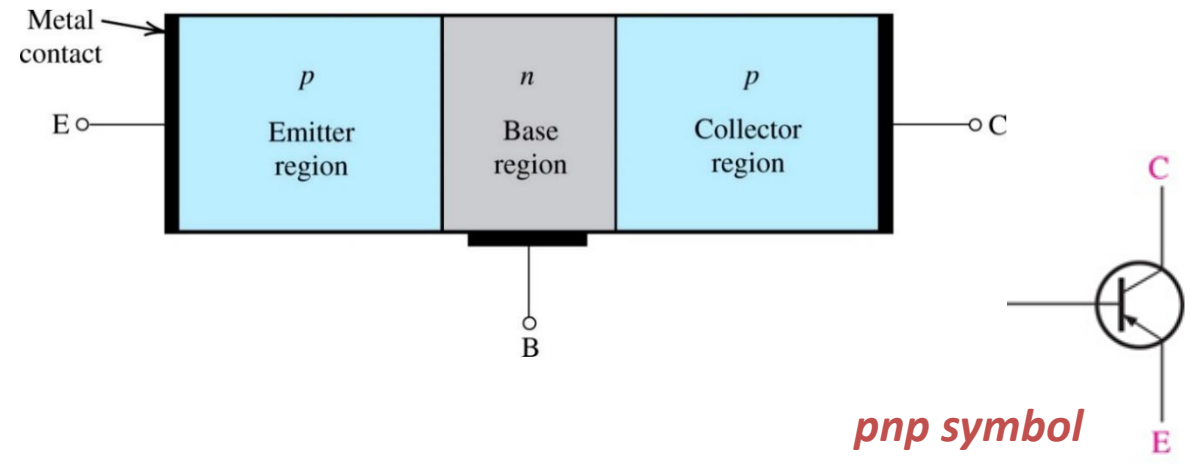- Simplified structure of the *npn* transistor




Last Lecture → BJTs

9/16/2019

- **npn**

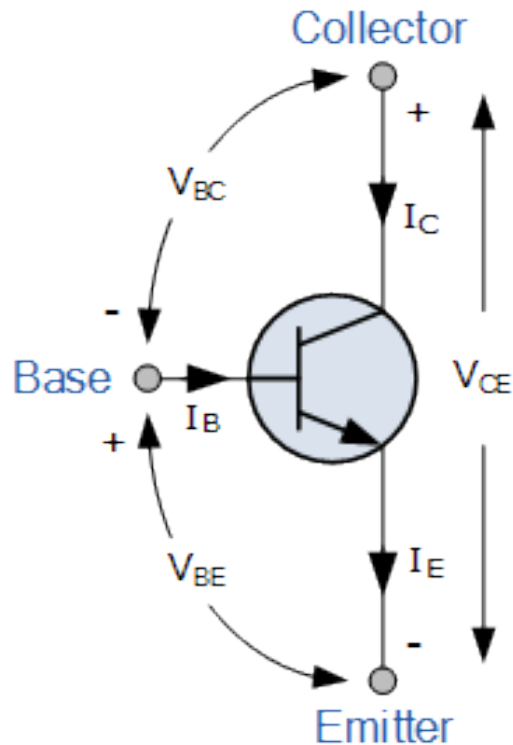
Voltages are measured with respect to the emitter (lowest potential)



- I_B – base current
- I_E – emitter current
- I_C – collector current

- **pnp**

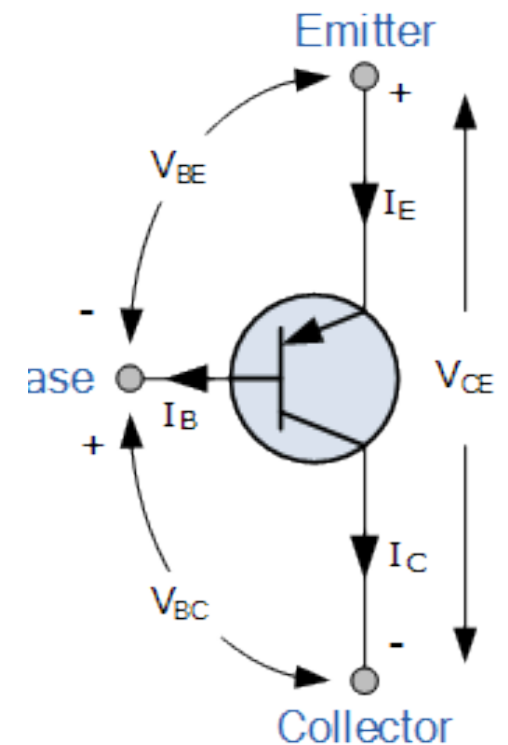
Voltages are measured with respect to the emitter (highest potential)



Last Lecture → Active Model

9/16/2019


• $i_C = f(v_{BE})$

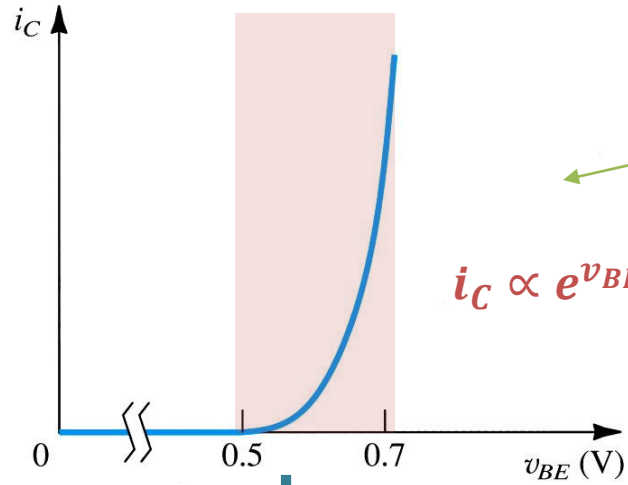

$i_C \propto e^{v_{BE}/V_T}$

• $i_C = f(v_{CE})$


$i_C \propto \frac{v_{CE}}{V_A}$

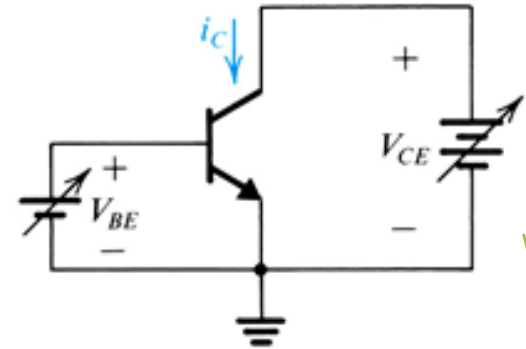


Collector Current

$$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A} \right)$$

$$\approx I_S e^{v_{BE}/V_T}$$

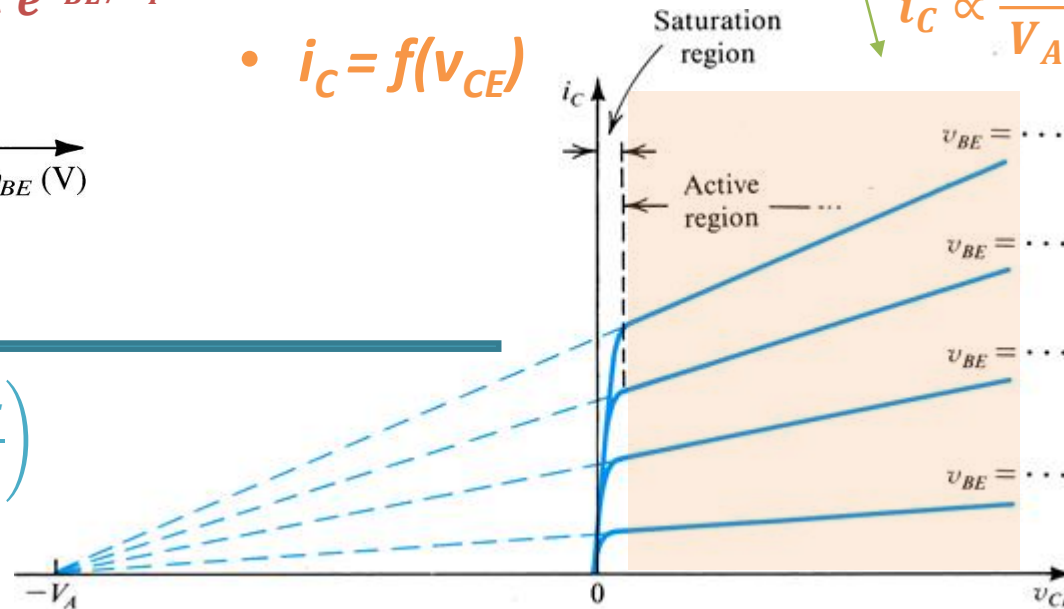

Large Signal Model

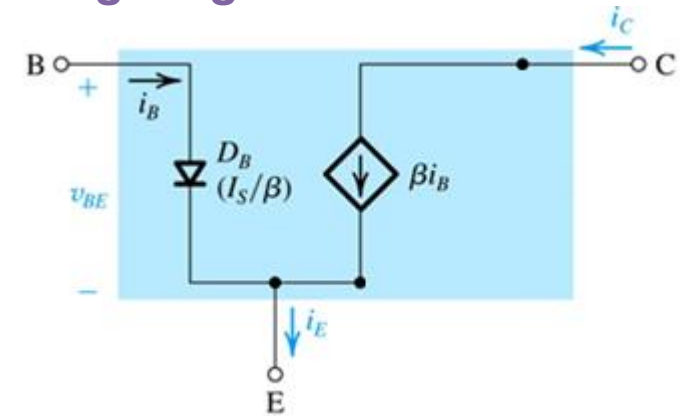



Base / Emitter Currents

$$i_B = \frac{i_C}{\beta}$$



$$i_E = i_B + i_C = \frac{\beta + 1}{\beta} i_C = \frac{i_C}{\alpha}$$

BJTs: Conditions & Models

9/16/2019

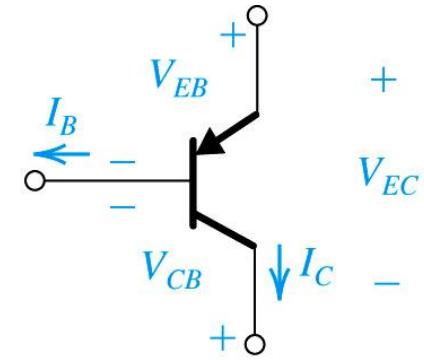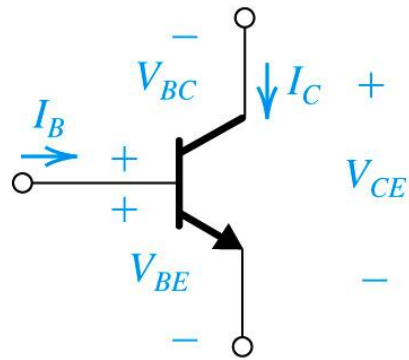



- **Cut-OFF**

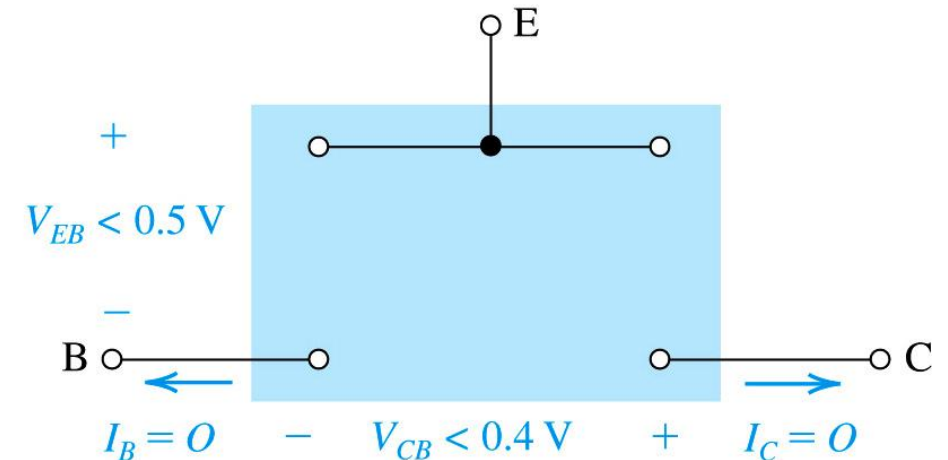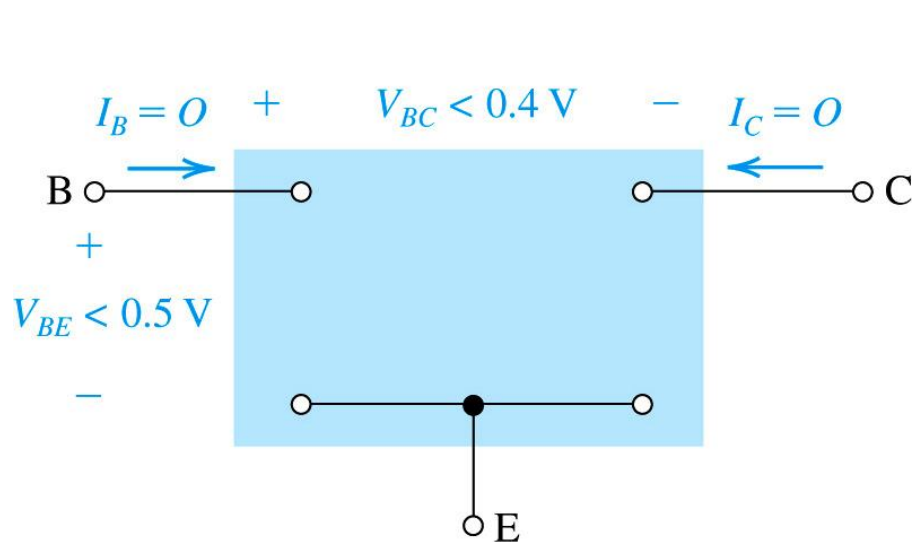



BJTs: Conditions & Models

9/16/2019

- **Active**

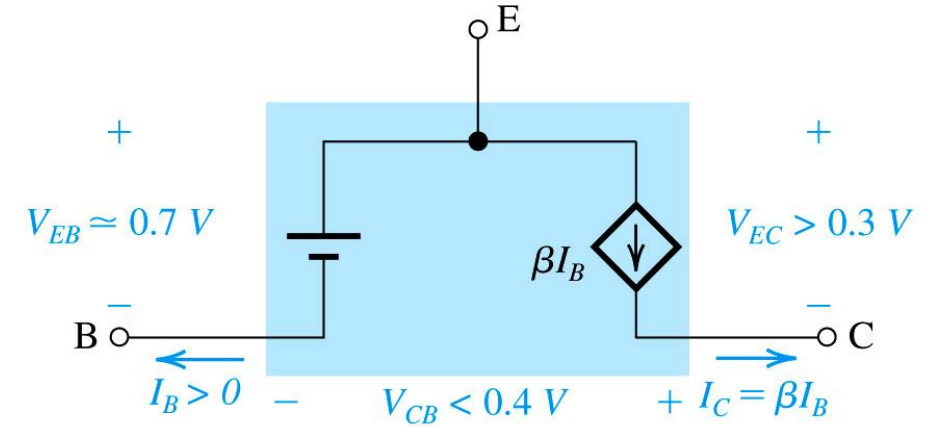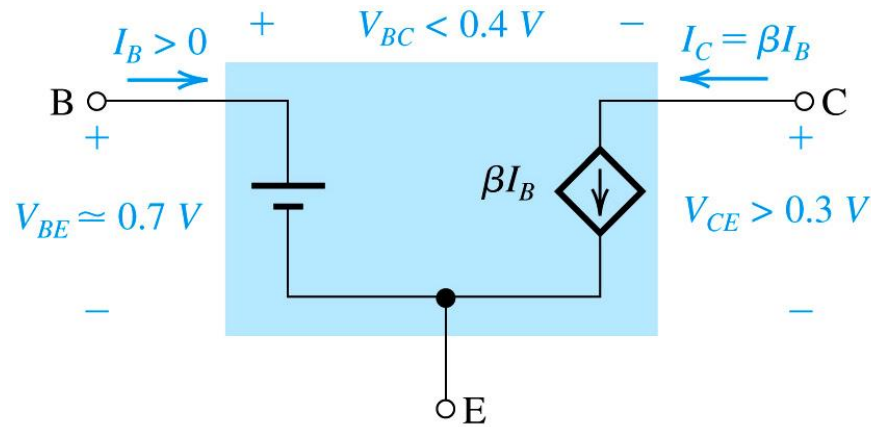

- **Saturation**

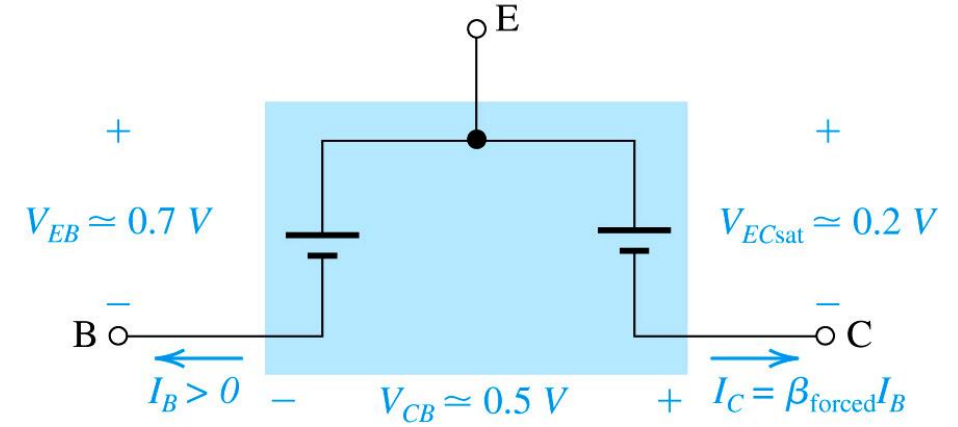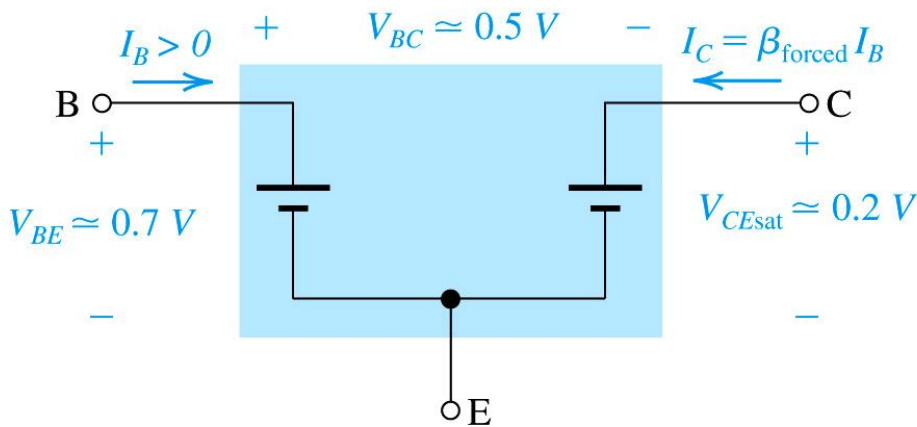

BJTs: Large Signal Analysis


9/16/2019

- 1) When applicable, simplify the circuit
- 2) Determine if BE/EB junction is forward (transistor = “on”)
 - If reverse, transistor \rightarrow cut off
 - If forward, transistor \rightarrow active / saturation
 - \therefore Make an educated guess of the region of operation
- 3) Substitute the appropriate model and or assumptions
- 4) Solve for the transistor operating point (I_C & V_{CE})
- 5) Verify proper operation @ the assumed region
 - If cut off $\rightarrow V_{BE} < 0.5V$
 - If active $\rightarrow V_{BE} \geq 0.5V, V_{CE} \geq 0.3V$
 - If saturation $\rightarrow V_{BE} \geq 0.5V, I_C / I_B < \beta$

Example 6.1

9/16/2019

An npn transistor having $I_s = 10^{-15}\text{A}$, $\beta = 100$, and $V_A = \infty$ is connected as follows: the emitter is grounded, the base is fed with a constant-current source supplying a dc current of $10\mu\text{A}$, and the collector is connected to a 5-V dc supply via a resistance R_C of $3\text{k}\Omega$. Assuming that the transistor is operating in the active mode, find V_{BE} and V_{CE} . Use these values to verify active-mode operation. Replace the current source with a resistance connected from the base to the 5-V dc supply. What resistance value is needed to result in the same operating conditions?

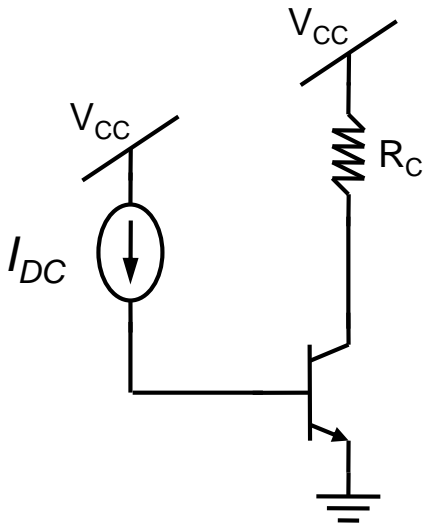

Example 6.3

9/16/2019

For the given circuit ($R_B=10\text{k}\Omega$, $R_C=1\text{k}\Omega$, $V_{CC}=10\text{V}$) assuming V_{BE} remains constant at 0.7V and transistor β is specified to be 50, it is required to determine the value of the voltage V_{BB} that results in the transistor operating

- in the active mode with $V_{CE}=5\text{V}$
- at the edge of saturation ($V_{CEsat} = 0.3\text{V}$)
- deep in saturation ($V_{CEsat} = 0.2\text{V}$) with $\beta_{\text{forced}}=10$.

